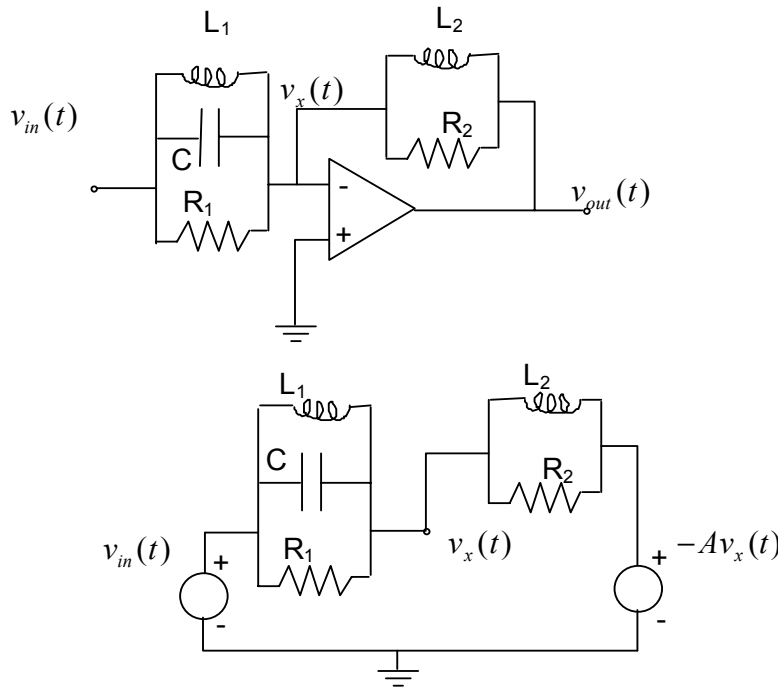


Sample Final Exam (finals01)
Covering Chapters 1-9 of *Fundamentals of Signals & Systems*

Problem 1 (20 marks)


Consider the causal op-amp circuit initially at rest depicted below. Its LTI circuit model with a voltage-controlled source is also given below.

(a) [8 marks] Transform the circuit using the Laplace transform, and find the transfer function $H_A(s) = V_{out}(s)/V_{in}(s)$. Then, let the op-amp gain $A \rightarrow +\infty$ to obtain the ideal transfer function $H(s) = \lim_{A \rightarrow +\infty} H_A(s)$.



Answer:

The transformed circuit is

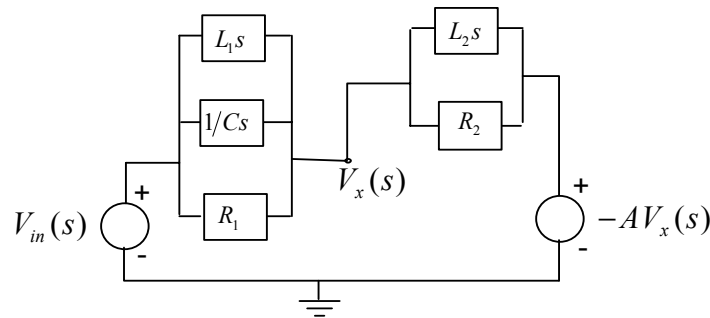

There are two supernodes for which the nodal voltages are given by the source voltages. The remaining nodal equation is

$$\frac{V_{in}(s) - V_x(s)}{R_1 \parallel \frac{1}{Cs} \parallel L_1 s} + \frac{-AV_x(s) - V_x(s)}{R_2 \parallel L_2 s} = 0$$

where $R_1 \parallel \frac{1}{Cs} \parallel L_1 s = \frac{1}{Cs + \frac{1}{R_1} + \frac{1}{L_1 s}} = \frac{R_1 L_1 s}{R_1 L_1 C s^2 + L_1 s + R_1}$ and $R_2 \parallel L_2 s = \frac{R_2 L_2 s}{R_2 + L_2 s}$. Simplifying the above equation, we get:

$$\frac{R_1 L_1 C s^2 + L_1 s + R_1}{R_1 L_1 s} V_{in}(s) - \left[\frac{(A+1)(R_2 + L_2 s)}{R_2 L_2 s} + \frac{R_1 L_1 C s^2 + L_1 s + R_1}{R_1 L_1 s} \right] V_x(s) = 0$$

Thus, the transfer function between the input voltage and the node voltage is given by

$$\begin{aligned} \frac{V_x(s)}{V_{in}(s)} &= \frac{\frac{R_1 L_1 C s^2 + L_1 s + R_1}{R_1 L_1 s}}{\frac{(A+1)(R_2 + L_2 s)}{R_2 L_2 s} + \frac{R_1 L_1 C s^2 + L_1 s + R_1}{R_1 L_1 s}} \\ &= \frac{R_2 L_2 s (R_1 L_1 C s^2 + L_1 s + R_1)}{R_1 L_1 s (A+1)(R_2 + L_2 s) + R_2 L_2 s (R_1 L_1 C s^2 + L_1 s + R_1)} \end{aligned}$$

The transfer function between the input voltage and the output voltage is


$$H_A(s) = \frac{V_{out}(s)}{V_{in}(s)} = \frac{-AV_x(s)}{V_{in}(s)} = \frac{-AR_2 L_2 s (R_1 L_1 C s^2 + L_1 s + R_1)}{R_1 L_1 s (A+1)(R_2 + L_2 s) + R_2 L_2 s (R_1 L_1 C s^2 + L_1 s + R_1)}$$

The ideal transfer function is the limit as the op-amp gain tends to infinity:

$$H(s) = \lim_{A \rightarrow \infty} H_A(s) = -\frac{R_2 L_2 (R_1 L_1 C s^2 + L_1 s + R_1)}{R_1 L_1 (R_2 + L_2 s)} = -\frac{L_2 (L_1 C s^2 + \frac{L_1}{R_1} s + 1)}{L_1 (1 + \frac{L_2}{R_2} s)}$$

(b) [5 marks] The circuit is used as a cascade equalizer for the system

$G(s) = -50 \frac{s+1}{0.01s^2 + 0.1s + 1}$, that is, $|G(j\omega)H(j\omega)| = 0dB, \forall \omega$. Let $L_1 = 10H$. Find the values of the remaining circuit components L_2, R_1, R_2, C .

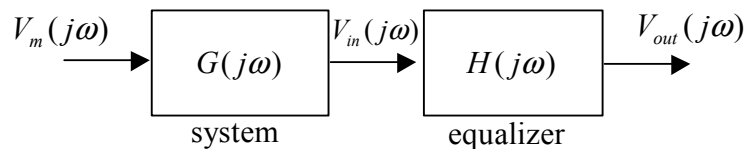

Component values are obtained by setting

$$H(s) = G^{-1}(s) = -0.02 \frac{0.01s^2 + 0.1s + 1}{s+1} = -\frac{L_2}{L_1} \frac{(L_1 C s^2 + \frac{L_1}{R_1} s + 1)}{(\frac{L_2}{R_2} s + 1)}$$


Sample Final Exam Covering Chapters 1-9 (finals01)

which yields $\Leftrightarrow L_2 = 0.2H, R_1 = 100\Omega, R_2 = 0.2\Omega, C = 0.001F$

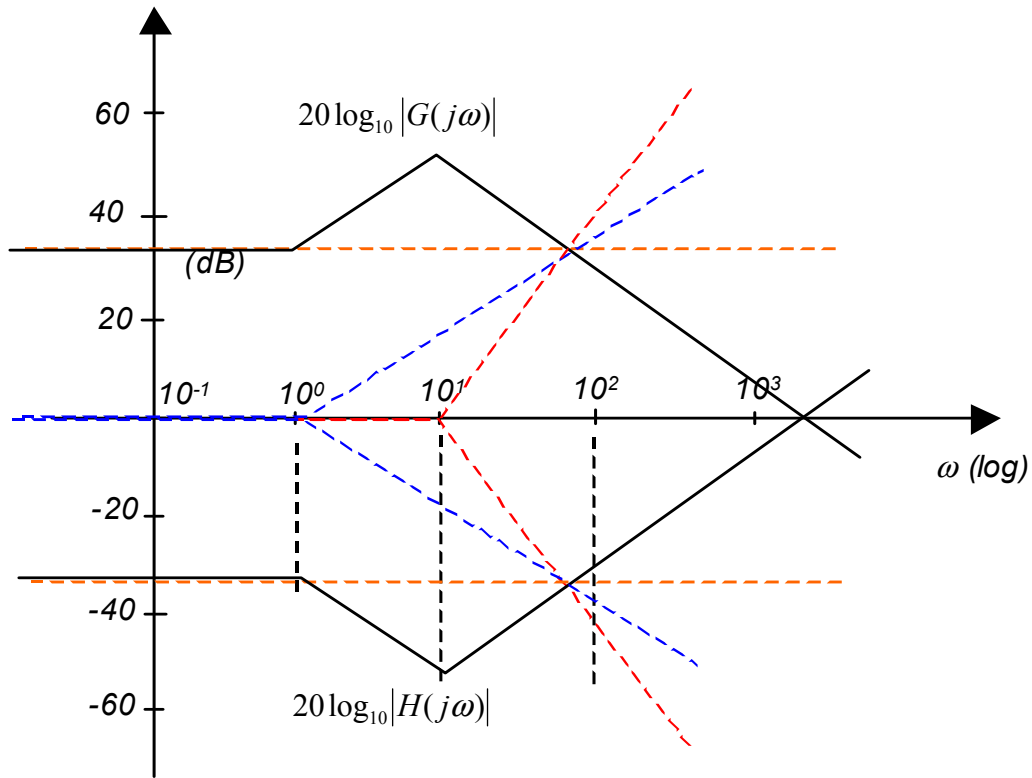(c) [7 marks] Sketch the Bode plot of $H(s)$ and $G(s)$ (magnitude only, both on the same plot).


Magnitude Bode plot of $G(j\omega) = -50 \frac{j\omega + 1}{0.01(j\omega)^2 + 0.1(j\omega) + 1}$ and desired

$$H(j\omega) = -0.02 \frac{0.01(j\omega)^2 + 0.1(j\omega) + 1}{j\omega + 1}.$$



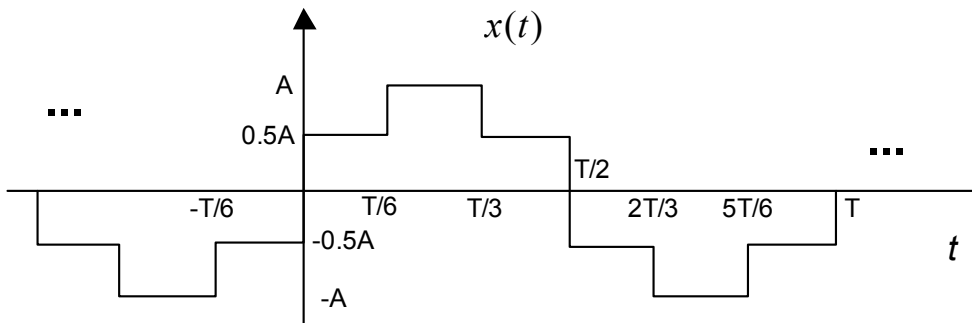Problem 2 (20 marks) Digital Signal Generator

A programmable digital signal generator generates a sinusoidal waveform by LTI filtering of a staircase approximation to a sine wave $x(t)$.



Sample Final Exam Covering Chapters 1-9 (finals01)

(a) [9 marks] Find the Fourier series coefficients a_k of the periodic signal $x(t)$. Show that the even harmonics vanish. Express $x(t)$ as a Fourier series.

Answer:

First of all, the average over one period is 0, so $a_0 = 0$. For $k \neq 0$,

$$\begin{aligned}
 a_k &= \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} x(t) e^{-jk\frac{2\pi}{T}t} dt \\
 &= -\frac{A}{2T} \int_{-\frac{T}{2}}^{\frac{T}{3}} e^{-jk\frac{2\pi}{T}t} dt - \frac{A}{T} \int_{\frac{T}{3}}^{\frac{T}{6}} e^{-jk\frac{2\pi}{T}t} dt - \frac{A}{2T} \int_{\frac{T}{6}}^0 e^{-jk\frac{2\pi}{T}t} dt \\
 &\quad + \frac{A}{2T} \int_{\frac{T}{3}}^{\frac{T}{2}} e^{-jk\frac{2\pi}{T}t} dt + \frac{A}{T} \int_{\frac{T}{6}}^{\frac{T}{3}} e^{-jk\frac{2\pi}{T}t} dt + \frac{A}{2T} \int_0^{\frac{T}{6}} e^{-jk\frac{2\pi}{T}t} dt \\
 &= \frac{A}{2T} \int_0^{\frac{T}{6}} \left(e^{-jk\frac{2\pi}{T}t} - e^{jk\frac{2\pi}{T}t} \right) dt + \frac{A}{2T} \int_{\frac{T}{3}}^{\frac{T}{2}} \left(e^{-jk\frac{2\pi}{T}t} - e^{jk\frac{2\pi}{T}t} \right) dt + \frac{A}{T} \int_{\frac{T}{6}}^{\frac{T}{3}} \left(e^{-jk\frac{2\pi}{T}t} - e^{jk\frac{2\pi}{T}t} \right) dt \\
 &= \frac{-jA}{T} \int_0^{\frac{T}{6}} \sin\left(k\frac{2\pi}{T}t\right) dt - \frac{j2A}{T} \int_{\frac{T}{3}}^{\frac{T}{2}} \sin\left(k\frac{2\pi}{T}t\right) dt - \frac{jA}{T} \int_{\frac{T}{6}}^{\frac{T}{3}} \sin\left(k\frac{2\pi}{T}t\right) dt \\
 &= \frac{jA}{T} \left(\frac{T}{2\pi k} \right) \cos\left(k\frac{2\pi}{T}t\right)_0^{\frac{T}{6}} + \frac{j2A}{T} \left(\frac{T}{2\pi k} \right) \cos\left(k\frac{2\pi}{T}t\right)_{\frac{T}{6}}^{\frac{T}{2}} + \frac{jA}{T} \left(\frac{T}{2\pi k} \right) \cos\left(k\frac{2\pi}{T}t\right)_{\frac{T}{3}}^{\frac{T}{6}} \\
 &= \frac{jA}{2\pi k} \left[\cos\left(k\frac{\pi}{3}\right) - 1 + 2\cos\left(k\frac{2\pi}{3}\right) - 2\cos\left(k\frac{\pi}{3}\right) + \cos(k\pi) - \cos\left(k\frac{2\pi}{3}\right) \right] \\
 &= \frac{jA}{2\pi k} \left[-\cos\left(k\frac{\pi}{3}\right) + \cos\left(k\frac{2\pi}{3}\right) - 1 + \cos(k\pi) \right]
 \end{aligned}$$

Note that the coefficients are purely imaginary, which is consistent with our real, odd signal. The even FS coefficients are for $k = 2m$, $m = 1, 2, \dots$:

$$\begin{aligned}
 a_k = a_{2m} &= \frac{jA}{2\pi 2m} \left[-\cos\left(m \frac{2\pi}{3}\right) + \cos\left(m \frac{4\pi}{3}\right) - 1 + \cos(m2\pi) \right] \\
 &= \frac{jA}{2\pi 2m} \left[-\cos\left(-m \frac{\pi}{3} + m\pi\right) + \cos\left(m \frac{\pi}{3} + m\pi\right) \right] \\
 &= \frac{jA}{2\pi 2m} \left[-\cos\left(m \frac{\pi}{3} - m\pi\right) + \cos\left(m \frac{\pi}{3} + m\pi\right) \right] \\
 &= \frac{jA}{2\pi 2m} \left[-\cos\left(m \frac{\pi}{3} + m\pi\right) + \cos\left(m \frac{\pi}{3} + m\pi\right) \right] = 0
 \end{aligned}$$

The Fourier series representation of $x(t)$ is

$$x(t) = \sum_{k=-\infty}^{+\infty} a_k e^{jk \frac{2\pi}{T} t} = \sum_{\substack{k=-\infty \\ k \neq 0}}^{+\infty} \frac{jA}{2\pi k} \left[-\cos\left(k \frac{\pi}{3}\right) + \cos\left(k \frac{2\pi}{3}\right) - 1 + \cos(k\pi) \right] e^{jk \frac{2\pi}{T} t}$$

(b) [3 marks] Write $x(t)$ using the real form of the Fourier series.

$$x(t) = a_0 + 2 \sum_{k=1}^{+\infty} [B_k \cos(k\omega_0 t) - C_k \sin(k\omega_0 t)]$$

Answer:


Recall that the C_k coefficients are the imaginary parts of the a_k 's. Hence

$$x(t) = \sum_{k=1}^{+\infty} \frac{-A}{\pi k} \left[-\cos\left(k \frac{\pi}{3}\right) + \cos\left(k \frac{2\pi}{3}\right) - 1 + \cos(k\pi) \right] \sin(k\omega_0 t)$$

(c) [2 marks] Design an ideal lowpass filter that will produce the perfect sinusoidal waveform

$y(t) = \sin \frac{2\pi}{T} t$ at its output with $x(t)$ as its input. Sketch its frequency response and specify its gain K and cutoff frequency ω_c .

Answer:

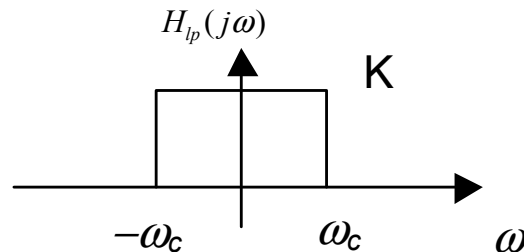

Sample Final Exam Covering Chapters 1-9 (finals01)

The cutoff should be between the fundamental and the second harmonic, say $\omega_c = \frac{3\pi}{T}$. The gain

$$\text{should be } K = \frac{-\pi}{A} \left[-\cos\left(\frac{\pi}{3}\right) + \cos\left(\frac{2\pi}{3}\right) - 1 + \cos(\pi) \right]^{-1} = \frac{-\pi}{A} \left[-\frac{1}{2} - \frac{1}{2} - 2 \right]^{-1} = \frac{\pi}{3A}.$$

(d) [6 marks] Now suppose that the first-order lowpass filter whose differential equation is given below is used to filter $x(t)$.

$$\tau \frac{d}{dt} y(t) + y(t) = Bx(t)$$

where the time constant is chosen to be $\tau = \frac{T}{2\pi}$. Give the Fourier series representation of the output

$y(t)$. Compute the total average power in the fundamental components P_{1tot} and in the third harmonic components P_{3tot} . Find the value of the dc gain B such that the output $w(t)$ produced by the fundamental harmonic of the real Fourier series of $x(t)$ has unit amplitude.

Answer:

$$H(s) = \frac{B}{\tau s + 1}$$

$$H(j\omega) = \frac{B}{\tau j\omega + 1}$$

$$y(t) = \sum_{k=-\infty}^{+\infty} a_k H(jk \frac{2\pi}{T}) e^{jk \frac{2\pi}{T} t} = \sum_{\substack{k=-\infty \\ k \neq 0}}^{+\infty} \frac{B}{jk + 1} \frac{jA}{2\pi k} \left[-\cos\left(k \frac{\pi}{3}\right) + \cos\left(k \frac{2\pi}{3}\right) - 1 + \cos(k\pi) \right] e^{jk \frac{2\pi}{T} t}$$

Power:

$$P_{1tot} = 2 \left| \frac{B}{j+1} \frac{jA}{2\pi} \left[-\cos\left(\frac{\pi}{3}\right) + \cos\left(\frac{2\pi}{3}\right) - 1 + \cos(\pi) \right] \right|^2$$

$$= 2 \left| \frac{B}{j+1} \frac{jA}{2\pi} \left[-\frac{1}{2} - \frac{1}{2} - 2 \right] \right|^2 = 2 \left| \frac{B}{j+1} \frac{j3A}{2\pi} \right|^2$$

$$= B^2 \frac{|3A|^2}{|2\pi|^2} = \frac{9A^2 B^2}{4\pi^2}$$

$$P_{3tot} = 2 \left| \frac{B}{j3+1} \frac{jA}{2\pi} \left[-\cos(\pi) + \cos(2\pi) - 1 + \cos(\pi) \right] \right|^2$$

$$= 2 \left| \frac{B}{j3+1} \frac{jA}{2\pi} [0] \right|^2 = 0$$

DC gain B :


We found that the gain at ω_0 should be

$$\frac{\pi}{3A} = |H(j\omega_0)| = \frac{B}{|\tau j\omega_0 + 1|} = \frac{B}{\sqrt{(\tau\omega_0)^2 + 1}}$$

$$\Leftrightarrow B = \frac{\pi\sqrt{(\tau\omega_0)^2 + 1}}{3A}$$

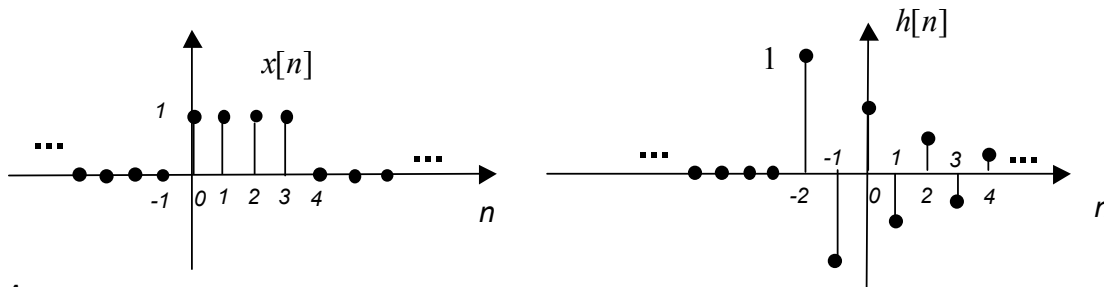Problem 3 (15 marks)

Compute the response $y[n]$ of an LTI system described by its impulse response $h[n]$ shown below and whose magnitude from a time instant to the next decays by 0.9 on its support. The input signal $x[n]$ is the rectangular pulse shown below shown below. Give a mathematical expression for $h[n]$.



Answer:

Mathematical expression for impulse response: $h[n] = (-0.9)^{(n+2)}u[n+2]$

We break down the problem into 3 intervals for n .

For $n < -2$: $h[n-k]$ is zero for $k \geq 0$, hence $g[k] = h[k]x[n-k] = 0 \forall k$ and $y[n] = 0$.

For $-2 \leq n \leq 1$: Then $g[k] = h[k]x[n-k] \neq 0$ for $k = 0, \dots, n+2$. We get

$$\begin{aligned} y[n] &= \sum_{k=0}^{n+2} g[k] = \sum_{k=0}^{n+2} (-0.9)^{n-k+2} = (-0.9)^{n+2} \sum_{k=0}^{n+2} (-0.9)^{-k} \\ &= (-0.9)^{n+2} \sum_{k=0}^{n+2} \left(-\frac{10}{9}\right)^k = (-0.9)^{n+2} \left(\frac{1 - (-0.9)^{-n-3}}{1 - (-0.9)^{-1}} \right) \\ &= \frac{(-0.9)^{n+2} - (-0.9)^{-1}}{1 - (-0.9)^{-1}} = \frac{(-0.9)^{n+3} - 1}{-1.9} \end{aligned}$$

For $n \geq 2$: Then $g[k] = h[k]x[n-k] \neq 0$ for $k = 0, \dots, 4$. We get

$$\begin{aligned} y[n] &= \sum_{k=0}^3 g[k] = \sum_{k=0}^3 (-0.9)^{n-k+2} = (-0.9)^{n+2} \sum_{k=0}^3 (-0.9)^{-k} \\ &= (-0.9)^{n+2} \left(\frac{1 - (-0.9)^{-4}}{1 - (-0.9)^{-1}} \right) \\ &= \frac{(-0.9)^{n+2} - (-0.9)^{n-2}}{1 - (-0.9)^{-1}} \end{aligned}$$

In summary, the output signal of the LTI system is

$$y[n] = \begin{cases} 0, & n < -2 \\ \frac{(-0.9)^{n+3} - 1}{-1.9}, & -2 \leq n < 1 \\ \frac{(-0.9)^{n+2} - (-0.9)^{n-2}}{1 - (-0.9)^{-1}}, & 2 \leq n \end{cases}$$

Problem 4 (10 marks)

The unit step response of an LTI system was measured to be


$$s(t) = 2e^{-\sqrt{3}t} \sin\left(t - \frac{\pi}{6}\right)u(t) + u(t) - tu(t).$$

(a) [6 marks] Find the transfer function $H(s)$ of the system. Specify its ROC. Sketch its pole-zero plot.

$$\begin{aligned}
 H(s) &= sS(s) = s\mathcal{L}\left[2e^{-\sqrt{3}t}\sin\left(t - \frac{\pi}{6}\right)u(t) + u(t) - tu(t)\right] \\
 &= s\mathcal{L}\left[2e^{-\sqrt{3}t}\left(\frac{e^{j\left(t - \frac{\pi}{6}\right)} - e^{-j\left(t - \frac{\pi}{6}\right)}}{2j}\right)u(t) + u(t) - tu(t)\right] \\
 &= s\mathcal{L}\left[2e^{-\sqrt{3}t}\left(\frac{\left(\frac{\sqrt{3}}{2} - j\frac{1}{2}\right)e^{jt} - \left(\frac{\sqrt{3}}{2} + j\frac{1}{2}\right)e^{-jt}}{2j}\right)u(t) + u(t) - tu(t)\right] \\
 &= s\mathcal{L}\left[\left(\frac{\left(\frac{\sqrt{3}}{2} - j\frac{1}{2}\right)e^{-\sqrt{3}t+jt} - \left(\frac{\sqrt{3}}{2} + j\frac{1}{2}\right)e^{-\sqrt{3}t-jt}}{j}\right)u(t) + u(t) - tu(t)\right] \\
 &= s\mathcal{L}\left[\left(\frac{\left(\frac{\sqrt{3}}{2}e^{-\sqrt{3}t+jt} - \frac{\sqrt{3}}{2}e^{-\sqrt{3}t-jt}\right) - j\frac{1}{2}e^{-\sqrt{3}t+jt} - j\frac{1}{2}e^{-\sqrt{3}t-jt}}{j}\right)u(t) + u(t) - tu(t)\right] \\
 &= s\mathcal{L}\left[\left(\sqrt{3}e^{-\sqrt{3}t}\sin t - e^{-\sqrt{3}t}\cos t\right)u(t) + u(t) - tu(t)\right] \\
 &= s\left[\frac{\sqrt{3}}{(s + \sqrt{3})^2 + 1} - \frac{s + \sqrt{3}}{(s + \sqrt{3})^2 + 1} + \frac{1}{s} - \frac{1}{s^2}\right] \\
 &= \frac{-s^3 + [(s + \sqrt{3})^2 + 1](s - 1)}{s[(s + \sqrt{3})^2 + 1]} \\
 &= \frac{-s^3 + [s^2 + 2\sqrt{3}s + 4](s - 1)}{s[(s + \sqrt{3})^2 + 1]} \\
 &= \frac{(2\sqrt{3} - 1)s^2 + (4 - 2\sqrt{3})s - 4}{s[(s + \sqrt{3})^2 + 1]} = \frac{(2\sqrt{3} - 1)\left[s^2 + \frac{(4 - 2\sqrt{3})}{(2\sqrt{3} - 1)}s - \frac{4}{(2\sqrt{3} - 1)}\right]}{s[(s + \sqrt{3})^2 + 1]}
 \end{aligned}$$

ROC: $\text{Re}\{s\} > 0$.
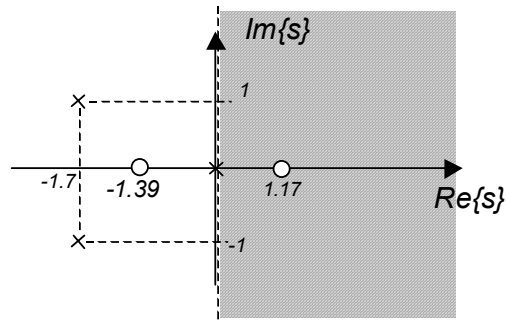
$$\begin{aligned}
 p_1 &= 0 & z_1 &= -1.3875, \\
 \text{Poles are } p_2 &= -\sqrt{3} + j, \text{ Zeros are zeros of } s^2 + 0.21748s - 1.62331: & z_2 &= 1.1700 \\
 p_3 &= -\sqrt{3} - j & z_3 &= \infty
 \end{aligned}$$



(b) [2 marks] Is the system causal? Is it stable? Justify your answers.

Answer:


System is causal: ROC is an open RHP and transfer function is rational.

This system isn't stable as ROC doesn't include the imaginary axis (or because rightmost pole 0 has a nonnegative real part.)

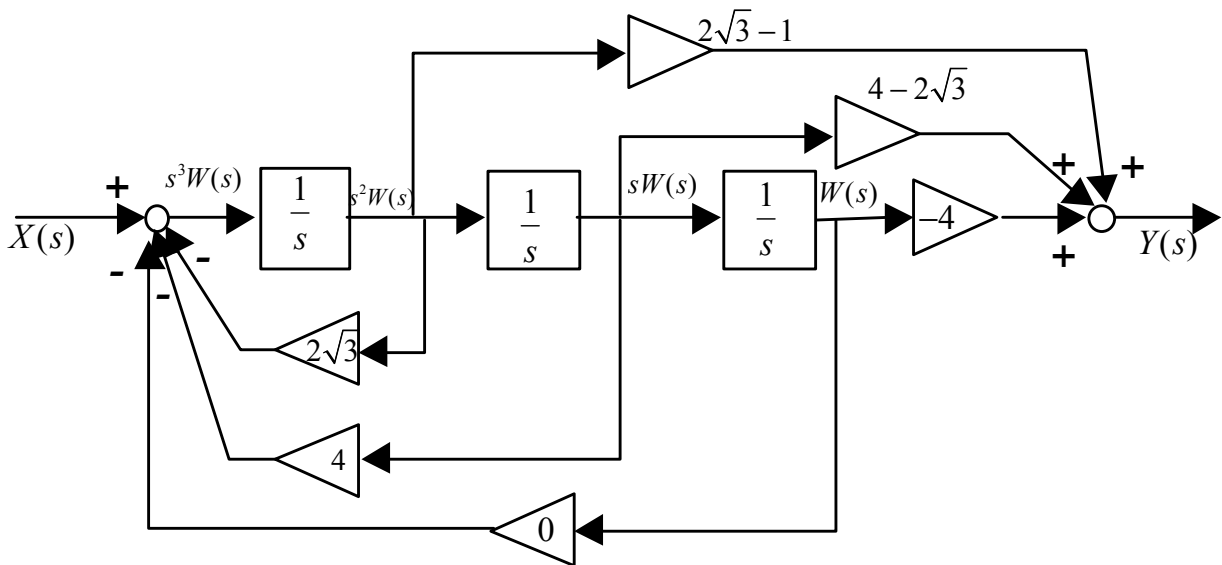(c) [2 marks] Give the direct form realization (block diagram) of $H(s)$.

Answer:

$$H(s) = \frac{(2\sqrt{3}-1)s^2 + (4-2\sqrt{3})s - 4}{s^3 + 2\sqrt{3}s^2 + 4s}$$



Problem 5 (5 marks)

True or False?

(a) The Fourier transform $Z(j\omega)$ of the convolution of a real even signal $x(t)$ and a real odd signal $y(t)$ is imaginary even.

Answer: False.

(b) The system defined by $y(t) = tx(t)$ is time-invariant.

Answer: False.

(c) The Fourier series coefficients b_k of the periodic signal $y(t) = x(10t)$ are given by $b_k = \frac{1}{10}a_k$,

where $x(t) \overset{\mathcal{F}}{\leftrightarrow} a_k$.

Answer: False.

(d) The Fourier transform $X(j\omega)$ of the product of a real signal $x(t)$ and an impulse $\delta(t)$ is real.


Answer: True.

(e) The fundamental period of the signal $x[n] = \sin(\frac{3\pi}{5}n) \cos(\frac{2\pi}{3}n)$ is 60.

Answer: False. (N=30)

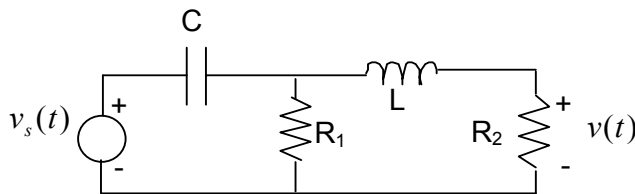
Problem 6 (15 marks)

The following circuit has initial conditions on the capacitor $v_c(0^-)$ and inductor $i_L(0^-)$.



(a) [3 marks] Transform the circuit using the unilateral Laplace transform.

Answer:

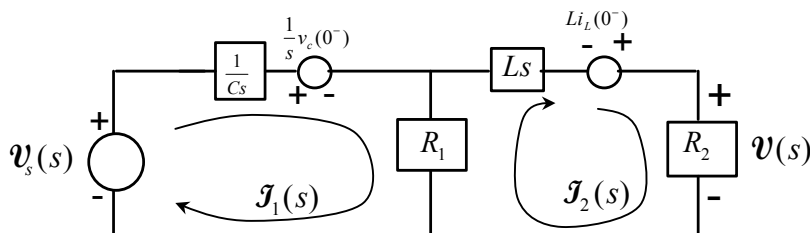

(b) [6 marks] Find the unilateral Laplace transform of $v(t)$.

Answer:

Let's use mesh analysis.

For mesh 1:

$$\begin{aligned} \mathcal{V}_s(s) - \frac{1}{Cs} \mathcal{J}_1(s) - \frac{1}{s} v_c(0^-) - R_1[\mathcal{J}_1(s) - \mathcal{J}_2(s)] &= 0 \\ \Rightarrow \mathcal{J}_2(s) &= -\frac{1}{R_1} \mathcal{V}_s(s) + \frac{1}{R_1 s} v_c(0^-) + \left(1 + \frac{1}{R_1 Cs}\right) \mathcal{J}_1(s) \end{aligned}$$

For mesh 2:

$$\begin{aligned} R_1[\mathcal{J}_1(s) - \mathcal{J}_2(s)] - (R_2 + Ls)\mathcal{J}_2(s) + Li_L(0^-) &= 0 \\ \Rightarrow \mathcal{J}_1(s) &= \frac{1}{R_1} (R_1 + R_2 + Ls)\mathcal{J}_2(s) - \frac{L}{R_1} i_L(0^-) \end{aligned}$$

Substituting, we obtain

$$\begin{aligned} \mathcal{J}_2(s) &= -\frac{1}{R_1} \mathcal{V}_s(s) + \frac{1}{R_1 s} v_c(0^-) + \left(1 + \frac{1}{R_1 Cs}\right) \left[\frac{1}{R_1} (R_1 + R_2 + Ls)\mathcal{J}_2(s) - \frac{L}{R_1} i_L(0^-) \right] \\ [R_1^2 Cs - (1 + R_1 Cs)(R_1 + R_2 + Ls)]\mathcal{J}_2(s) &= -R_1 Cs \mathcal{V}_s(s) + R_1 C v_c(0^-) - (1 + R_1 Cs) Li_L(0^-) \\ -[LR_1 Cs^2 + (L + R_1 R_2 C)s + R_1 + R_2]\mathcal{J}_2(s) &= -R_1 Cs \mathcal{V}_s(s) + R_1 C v_c(0^-) - (1 + R_1 Cs) Li_L(0^-) \end{aligned}$$

Solving for $\mathcal{J}_2(s)$, we get

$$\mathcal{J}_2(s) = \frac{R_1 Cs \mathcal{V}_s(s)}{LR_1 Cs^2 + (L + R_1 R_2 C)s + R_1 + R_2} + \frac{(1 + R_1 Cs) Li_L(0^-) - R_1 C v_c(0^-)}{LR_1 Cs^2 + (L + R_1 R_2 C)s + R_1 + R_2}$$

And finally the output voltage is

$$\mathcal{V}(s) = R_2 \mathcal{J}_2(s) = \frac{R_1 R_2 Cs \mathcal{V}_s(s)}{LR_1 Cs^2 + (L + R_1 R_2 C)s + R_1 + R_2} + \frac{R_2 (1 + R_1 Cs) Li_L(0^-) - R_1 R_2 C v_c(0^-)}{LR_1 Cs^2 + (L + R_1 R_2 C)s + R_1 + R_2}$$

(c) [6 marks] Draw the Bode plot (magnitude and phase) of the frequency response from the input voltage $\mathcal{V}_s(j\omega)$ to the output voltage $\mathcal{V}(j\omega)$. Assume that the initial conditions on the capacitor and

the inductor are 0. Use the numerical values: $R_1 = 1 \Omega$, $R_2 = \frac{109}{891} \Omega$, $L = \frac{1}{891} \text{ H}$, $C = 1 \text{ F}$.


Answer:


For the values given, the transfer function from the source voltage to the output voltage is

Sample Final Exam Covering Chapters 1-9 (finals01)

$$\begin{aligned}
 \mathcal{H}(s) &:= \frac{\mathcal{V}(s)}{\mathcal{V}_s(s)} = \frac{\frac{R_2}{L}s}{s^2 + \frac{L + R_1 R_2 C}{LR_1 C}s + \frac{R_1 + R_2}{LR_1 C}} \\
 &= \frac{109s}{s^2 + \frac{\frac{1}{891} + \frac{109}{891}}{\frac{1}{891}}s + \frac{1 + \frac{109}{891}}{\frac{1}{891}}} \\
 &= \frac{109s}{s^2 + 110s + 1000} \\
 &= \frac{109s}{(s + 10)(s + 100)} \\
 &= 0.109 \frac{s}{(\frac{1}{10}s + 1)(\frac{1}{100}s + 1)}
 \end{aligned}$$


Bode Plot:

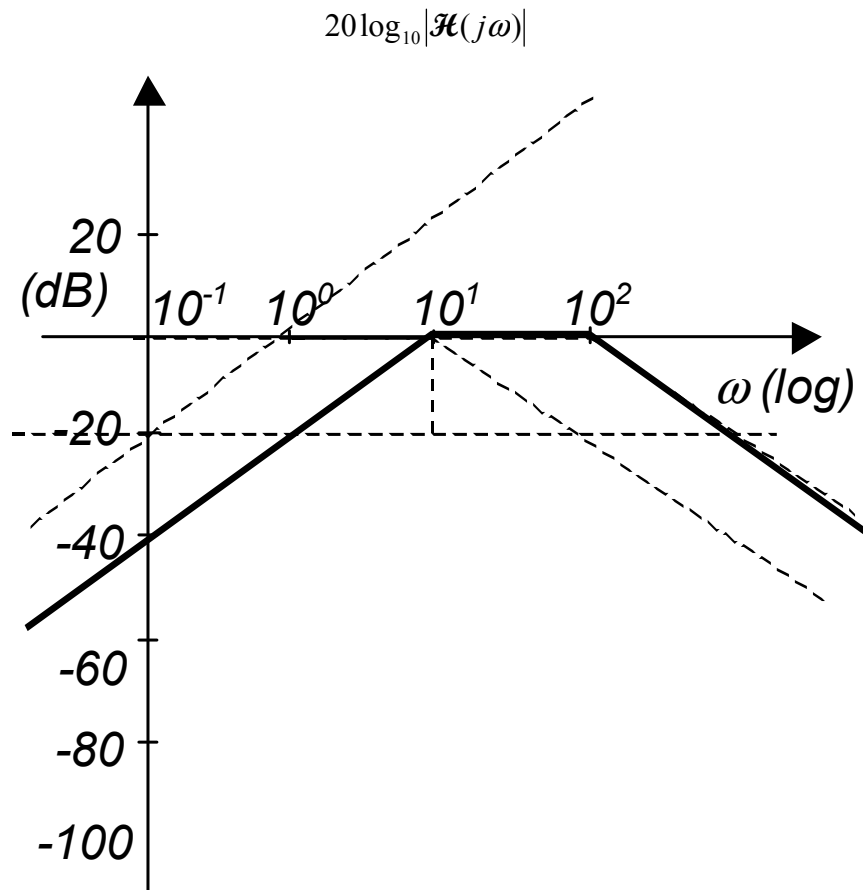

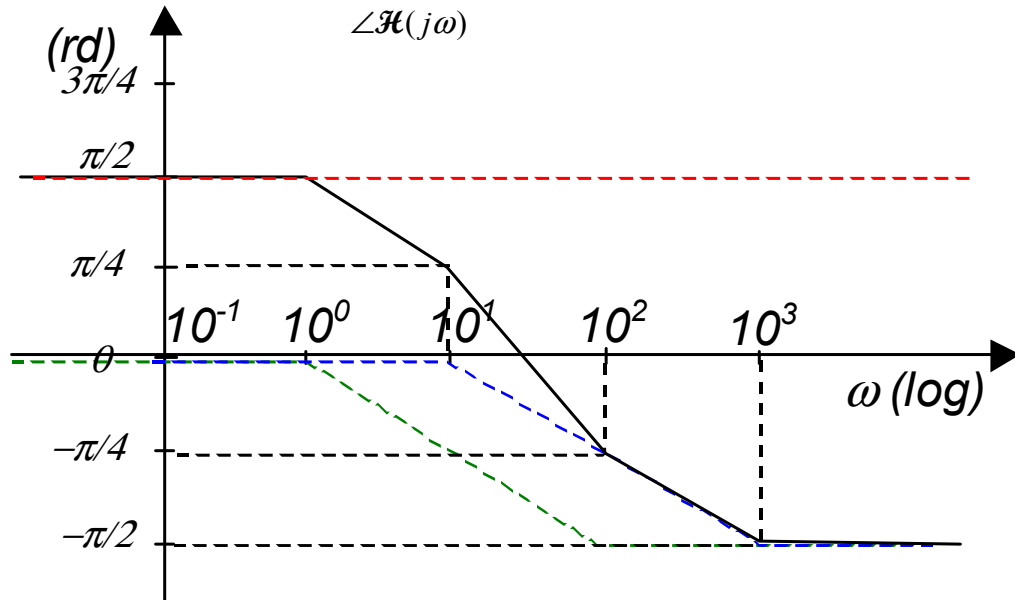

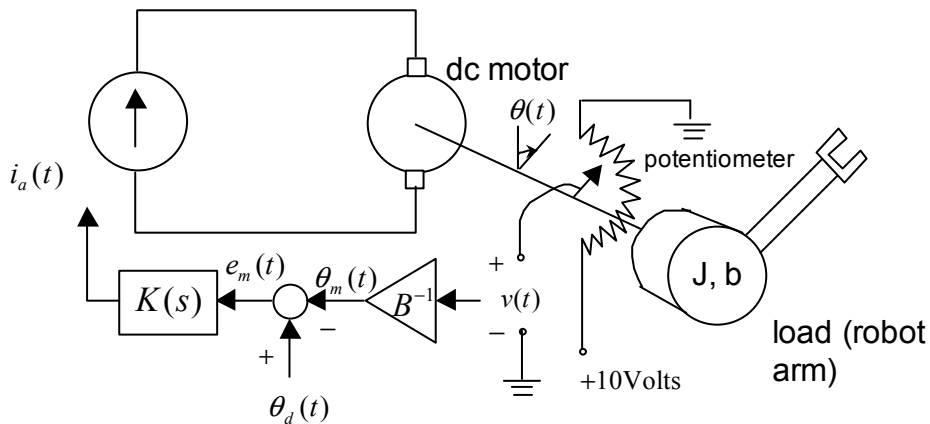Problem 7 (15 marks)

A classical technique to control the position of an inertial load (e.g., a robot arm) driven by a permanent-magnet DC motor is to vary the armature current based on a potentiometer measurement of the robot's joint angle $\theta(t)$, as shown in the diagram below.



Before closing the feedback loop, we first look at the open-loop dynamics of this system in (a) and (b). The torque $\tau(t)$ in Newton-metres applied to the load by the motor is proportional to the armature current in Amps:

$$\tau(t) = A i_a(t).$$

Sample Final Exam Covering Chapters 1-9 (finals01)

The robot arm is modeled as an inertia J with viscous friction represented by the coefficient b . The equation of movement for the load is

$$J \frac{d^2 \theta(t)}{dt^2} + b \frac{d\theta(t)}{dt} = \tau(t).$$

(a) [2 marks] Assume that the system is initially at rest. Find the open-loop transfer function

$G(s) := \Theta(s)/I_a(s)$ relating the joint angle $\Theta(s)$ to the motor's armature current input $I_a(s)$.

Answer:

$$G(s) = \frac{\Theta(s)}{I_a(s)} = \frac{A}{s(Js + b)}$$

(b) [6 marks] Assume that $A = 1 \text{ Nm/A}$, $J = 1 \text{ Nm/rad/s}^2$ and $b = 1 \text{ Nm/rad/s}$. Compute the open-loop

unit step response $s_\omega(t)$ of the load's *angular velocity* $\omega(t) = \frac{d\theta(t)}{dt}$ for a unit step in armature current. What is the $\pm 5\%$ settling time t_s (an approximation is OK)?

Answer:

$$G_\omega(s) = \frac{s\Theta(s)}{I_a(s)} = \frac{1}{s+1}$$

The unit step response $s_\omega(t)$ is given by

$$S_\omega(s) = \frac{1}{s} G_\omega(s) = \frac{\Theta(s)}{I_a(s)} = \frac{1}{s(s+1)} = \frac{1}{s(s+1)} = \frac{1}{s} - \frac{1}{s+1}$$

Taking the inverse Laplace transform, we get

$$s_\omega(t) = (1 - e^{-t})u(t)$$


The $\pm 5\%$ settling time is approximately equal to three time constants: $t_s \approx 3 \text{ s}$.

(c) [7 marks] Based on the above figure, find the gain B of the joint angle sensor (potentiometer) in Volts/radian. Assume, as shown in the figure above, that there is a gain B^{-1} in the feedback path canceling out the sensor gain, and thus the link angle $\theta(t)$ is measured perfectly, i.e.,

$\theta_m(t) = \theta(t)$. We want to analyze the feedback controller $K(s) = \lambda(s + \alpha)$ to control the robot's joint angle. That is, we want $\theta(t)$ to track the desired angle $\theta_d(t)$.

Answer:

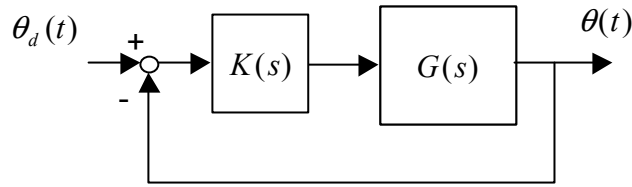Sensor gain is $B = \frac{10}{\pi} \text{ V/rad}$



Find the closed-loop transfer function $H(s) := \Theta(s)/\Theta_d(s)$. Find expressions for the closed-loop damping ratio ζ and undamped natural frequency ω_n in terms of the controller parameters α and λ . For $\alpha = 4$, find a value of λ that will result in a closed-loop damping ratio of $\zeta = \frac{1}{\sqrt{2}}$.

Closed-loop transfer function:

$$\begin{aligned} H(s) &= \frac{K(s)G(s)}{1 + K(s)G(s)} \\ &= \frac{\frac{\lambda(s + \alpha)}{s(s + 1)}}{1 + \frac{\lambda(s + \alpha)}{s(s + 1)}} \\ &= \frac{\lambda(s + \alpha)}{s(s + 1) + \lambda(s + \alpha)} \\ &= \frac{\lambda(s + \alpha)}{s^2 + (1 + \lambda)s + \alpha\lambda} \end{aligned}$$

We get $\omega_n = \sqrt{\alpha\lambda}$ and $\zeta = \frac{1 + \lambda}{2\sqrt{\alpha\lambda}}$.

For $\alpha = 4$ and given $\zeta = \frac{1}{\sqrt{2}}$, we have:

$$\begin{aligned} \zeta &= \frac{1}{\sqrt{2}} = \frac{1 + \lambda}{2\sqrt{4\lambda}} \\ \Rightarrow \frac{1}{2} &= \frac{(1 + \lambda)^2}{16\lambda} \Rightarrow 8\lambda = 1 + 2\lambda + \lambda^2 \\ \Rightarrow 1 - 6\lambda + \lambda^2 &= 0 \\ \Rightarrow \lambda_{1,2} &= \frac{6 \pm \sqrt{36 - 4}}{2} = 3 \pm 2\sqrt{2} \end{aligned}$$

both values are positive (for stability) and hence acceptable.

END OF EXAMINATION