

Outline of Section 1.3

1.1 Analog Amplifiers

1.2 Frequency Response of Amplifiers


1.3 Digital Logic Inverters

- Voltage transfer characteristic
- Noise margins
- Ideal Inverter

Inverter


- Inverts the logic value of the input signal
 - logical ‘0’ input becomes a logical ‘1’ at the output
 - logical ‘1’ input becomes a logical ‘0’ at the output
- Logic levels represented by voltage magnitudes:
 - V_{IH} : minimum input voltage corresponding to logical ‘1’
 - V_{IL} : maximum input voltage corresponding to logical ‘0’
 - V_{OH} : minimum output voltage corresponding to logical ‘1’
 - V_{OL} : maximum output voltage corresponding to logical ‘0’

Symbol:

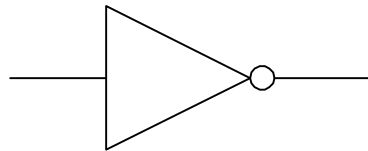

Digital circuits enjoy reduced sensitivity to exact value of the input than their analog amplifier counterparts


Voltage Transfer Characteristic

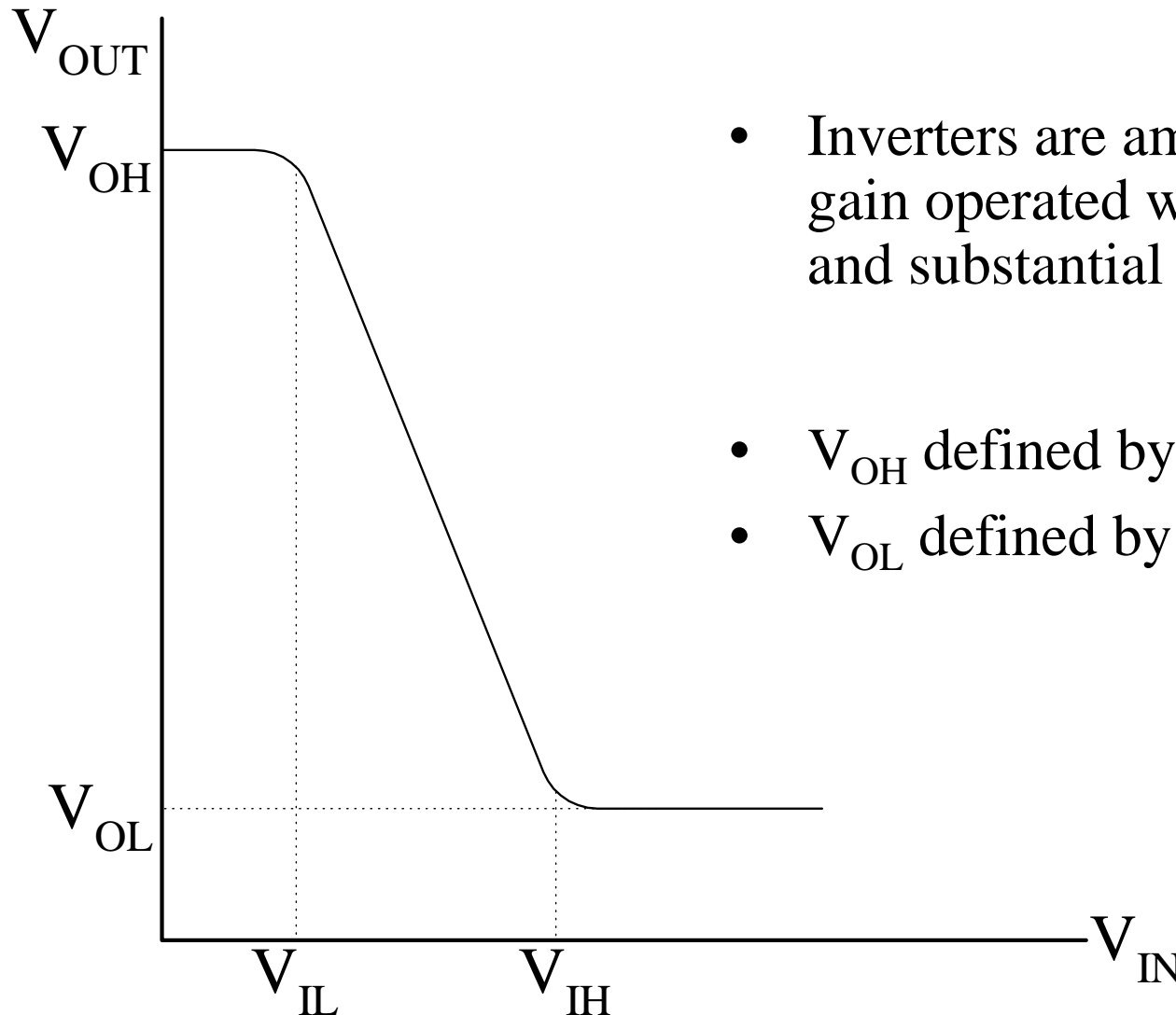

- Inverters are amplifiers with negative gain operated with large signal inputs and substantial signal distortion
- V_{OH} defined by V_{OUT} for $V_{IN} \leq V_{IL}$
- V_{OL} defined by V_{OUT} for $V_{IN} \geq V_{IH}$


Noise Margins - Cascaded Inverters

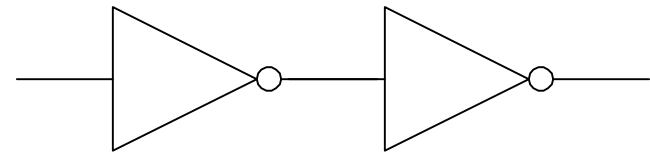- Noise margins a measure of the ability of digital circuits to be cascaded and their sensitivity to noise
- Consider scenario where one inverter drives an identical inverter




$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

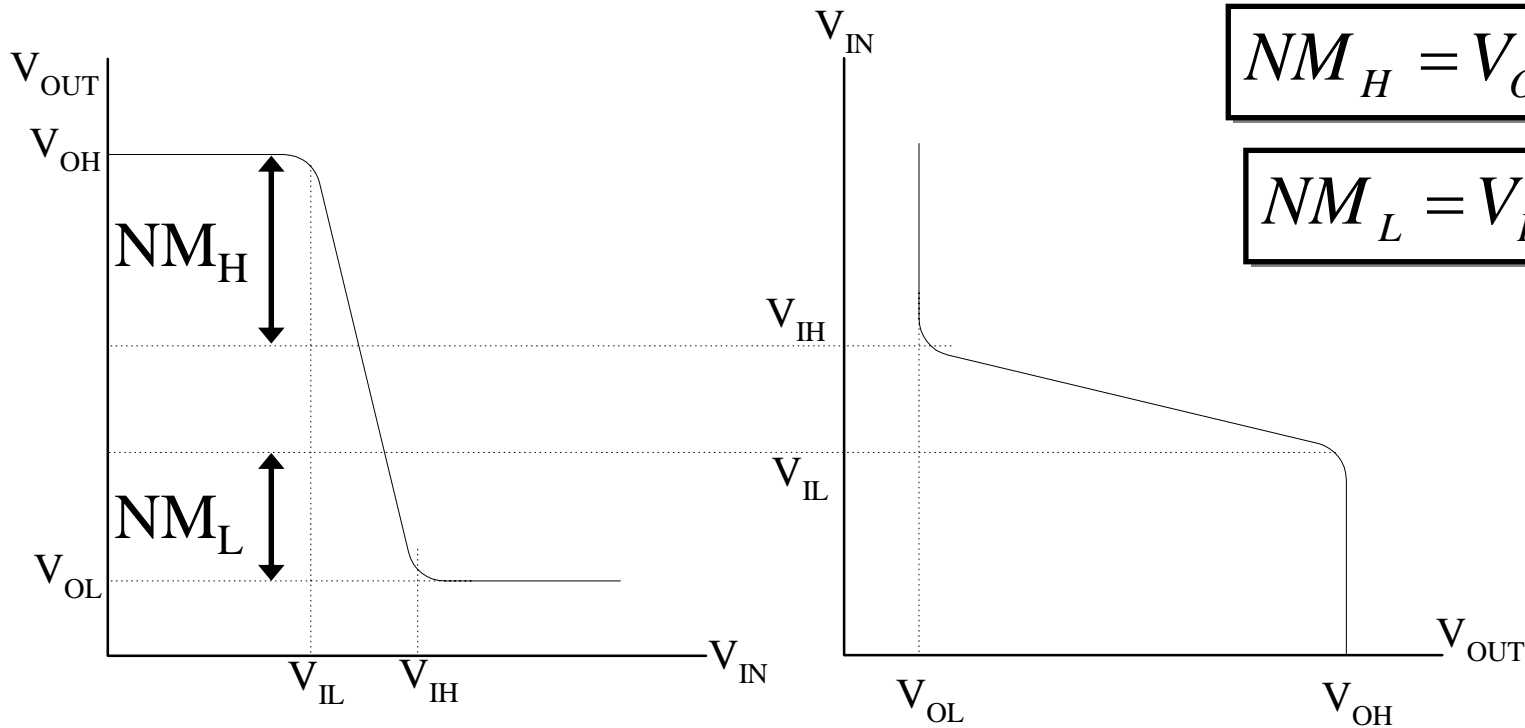

Ideal Inverter

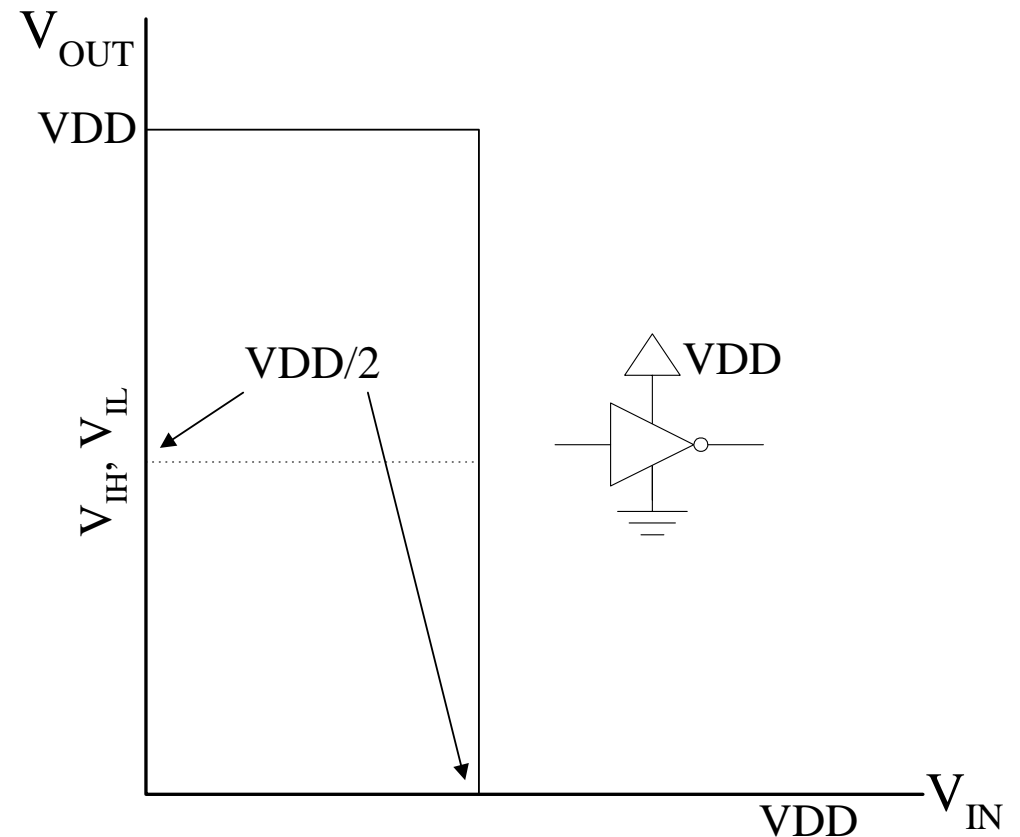- The ideal inverter has the following characteristics:
 - Symmetric VTC
 - V_{OH} and V_{OL} correspond to the supply voltages
 - Equal NM_H and NM_L
 - $V_{IH} = V_{IL} = VDD/2$



Corresponds to infinitely steep linear region

Simple Inverter Model

- Fig 1.31 Text book: Voltage controlled switch


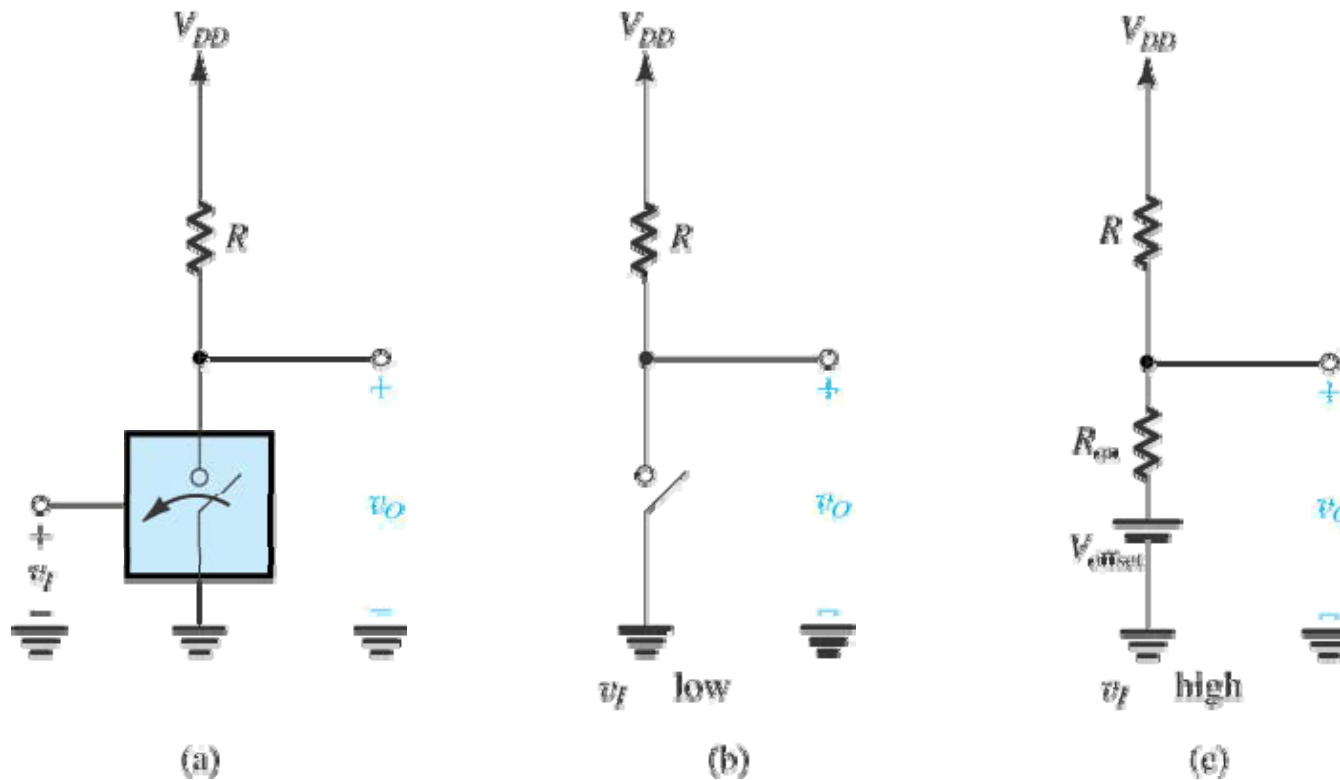


Figure 1.31 (a) The simplest implementation of a logic inverter using a voltage-controlled switch; (b) equivalent circuit when v_i is low; and (c) equivalent circuit when v_i is high. Note that the switch is assumed to close when v_i is high.


Simple Inverter Model

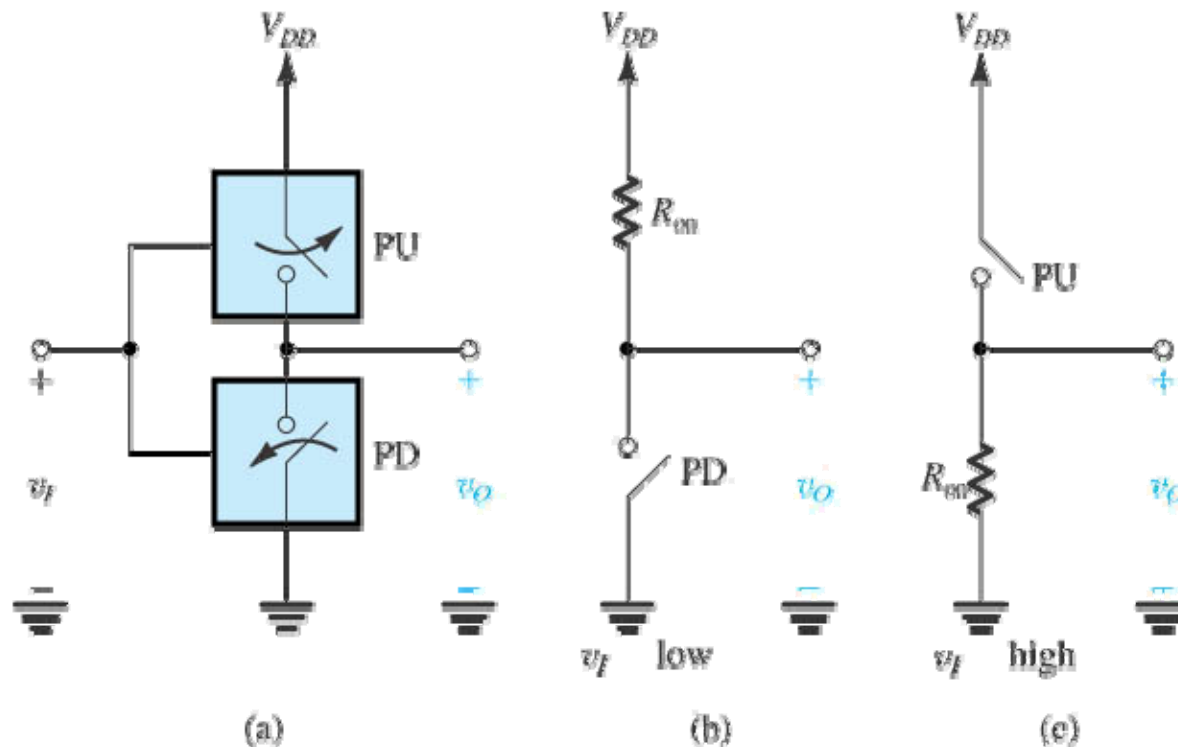- Fig 1.32 Text book: Two complementary switches- The basic model for a CMOS inverter



Inverter Timing

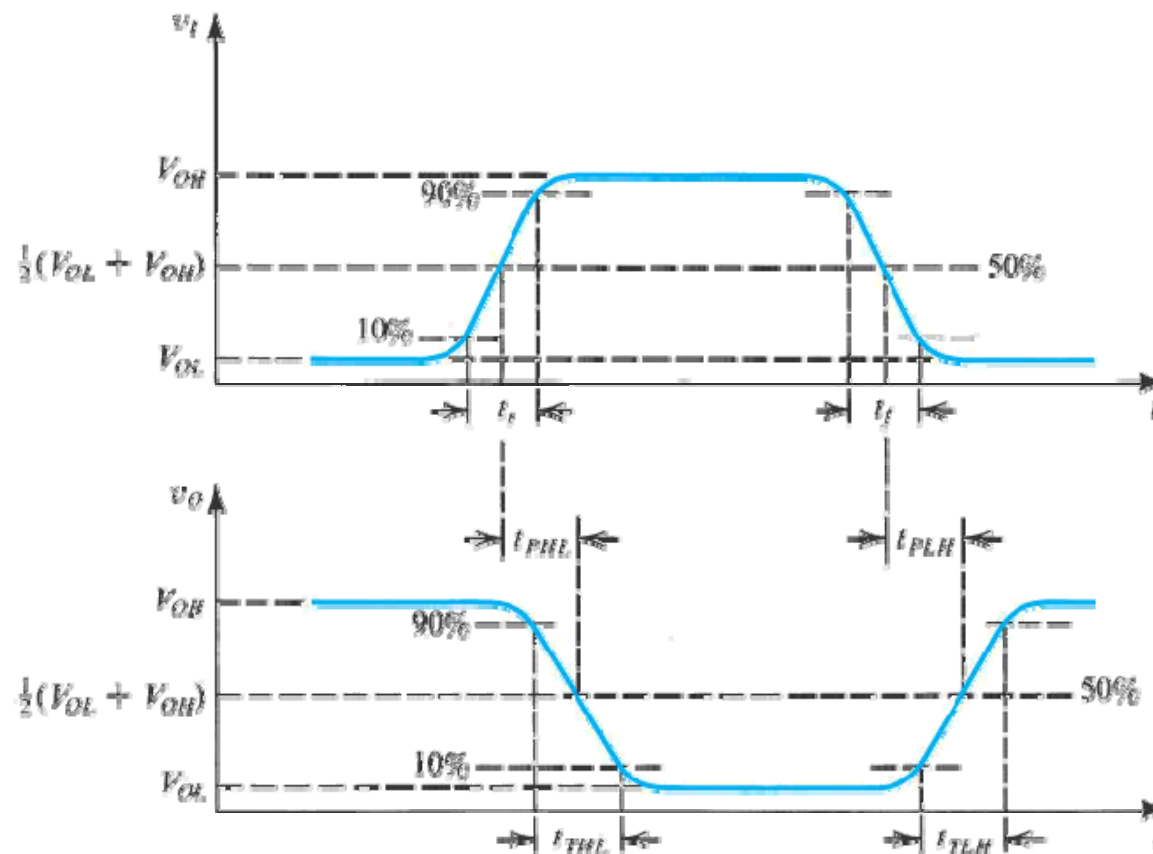- Fig 1.35 Text book: Definitions of propagation delays and transition times of the logic inverter.



1.3 Digital Logic Inverters - Summary

- Basic function of an inverter
- Input and output high and low voltages
- Voltage transfer characteristic of an inverter
- Meaning of noise margins
- Characteristics of an ideal inverter
- Simple inverter model