



Section 3

The pn Junction and Diodes

Sedra/Smith, Sections 3.1-3.7



Outline of Section 3 - Diodes

- Other two terminal devices
- Diode models
- Exponential model
- Constant voltage drop model
- Reverse breakdown
- Applications
- Small-signal model
- PN junctions




Resistors, Capacitors, Inductors

- Resistor: R $V=IR$
- Capacitor: C $i = c \frac{dv}{dt}$
- Inductor: L $v = l \frac{di}{dt}$
- Devices are two terminals and do not have a required orientation.



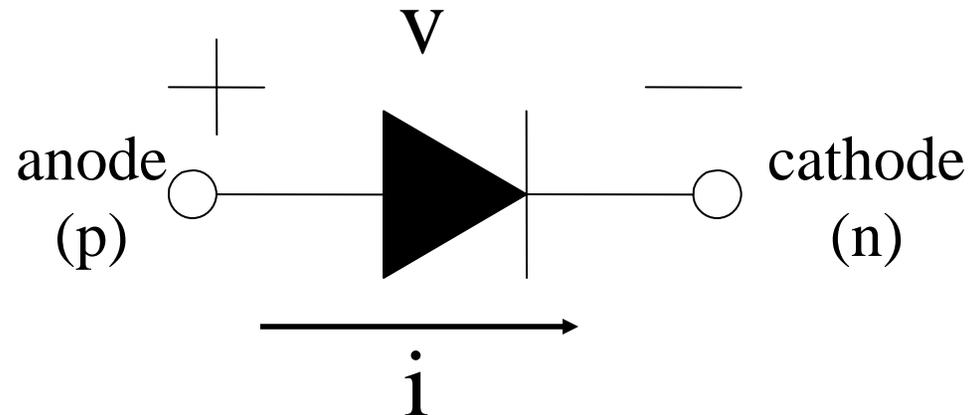Diode Symbol and Terminal Characteristics




Exponential i-v relation: $i = I_S \left(e^{\frac{v}{nV_T}} - 1 \right)$

Exponential Model



Exponential Characteristic Equation

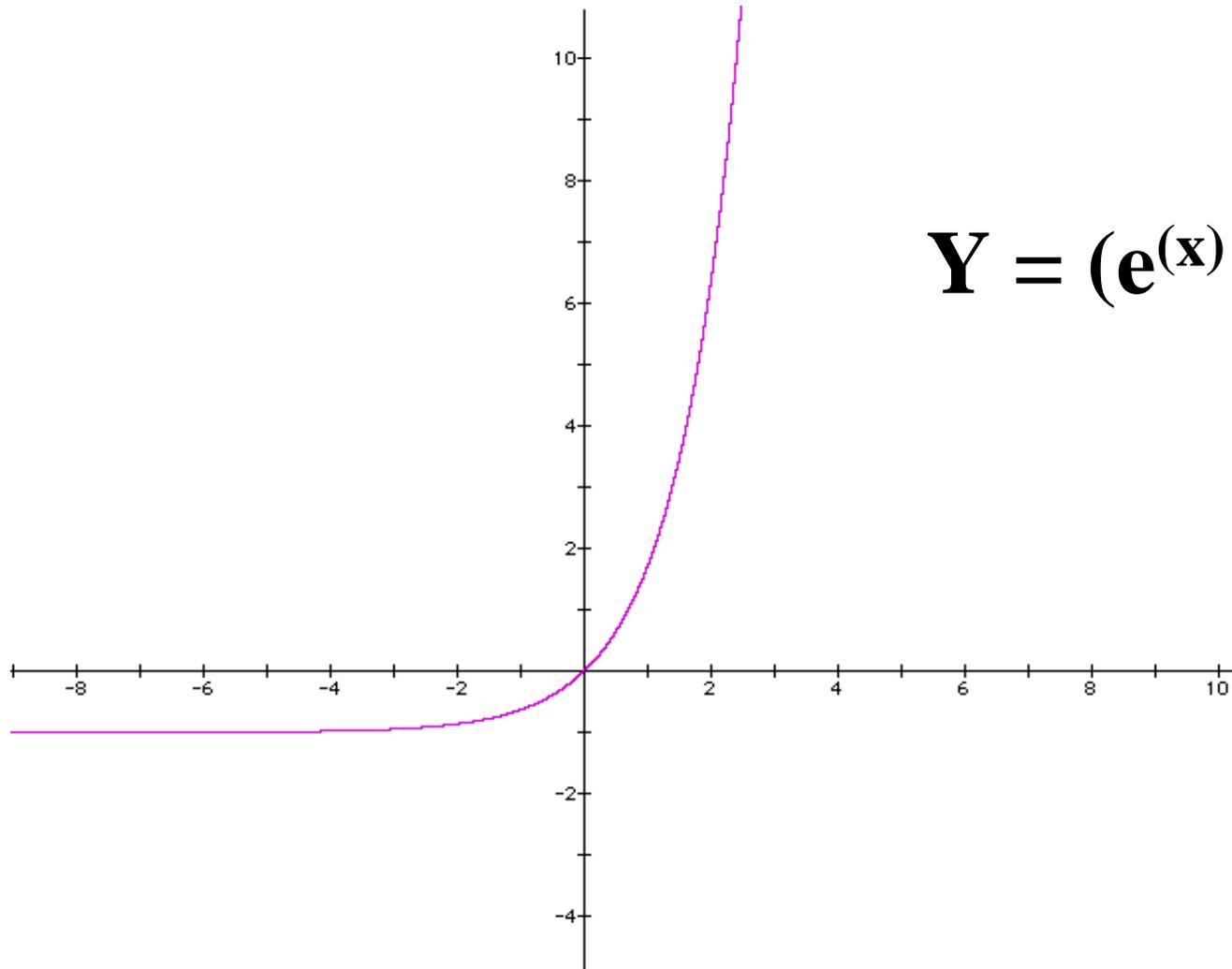

$$Y = (e^{(x)} - 1)$$




Diodes

- It is a nonlinear device
- How to model the nonlinear behavior?
 - Ideal model
 - Exponential model
 - Constant voltage drop model
 - Piecewise-linear (we don't work with this model much, except for Zener diode)




Ideal Model

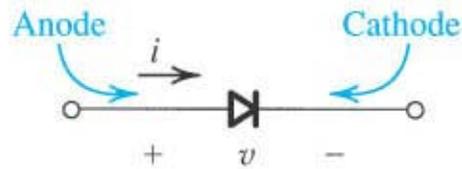
- Diode is considered to be an ideal switch
 - Used for fast and approximate analysis



(a)

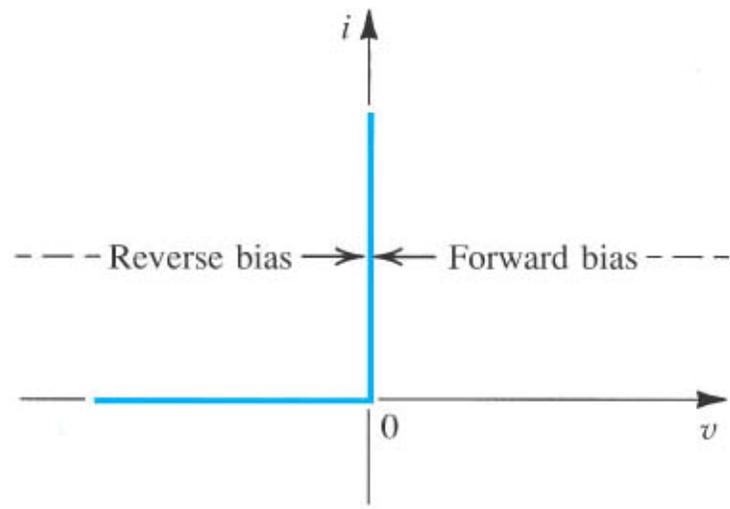


(b)

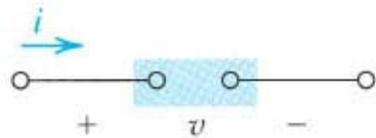

$$v < 0 \Rightarrow i = 0$$

(c)

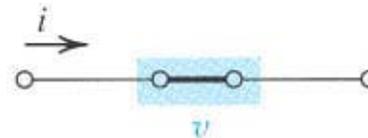





$$i > 0 \Rightarrow v = 0$$

(d)




Ideal Model Application

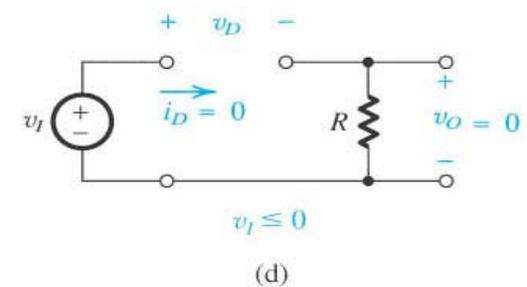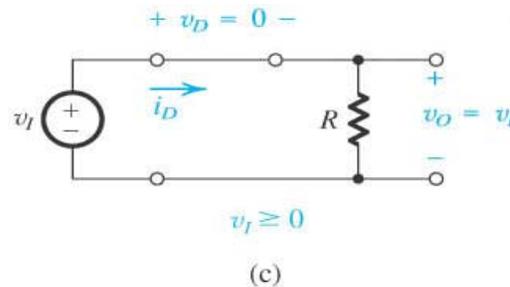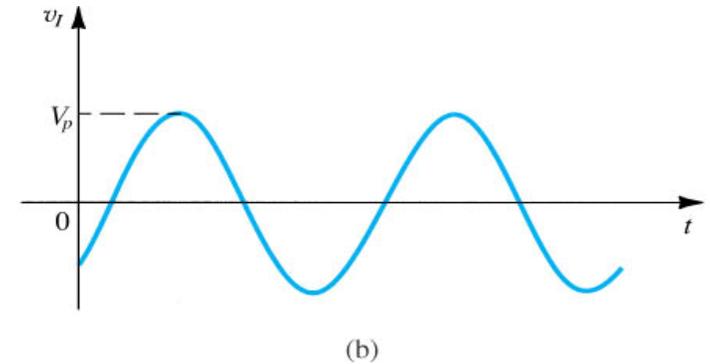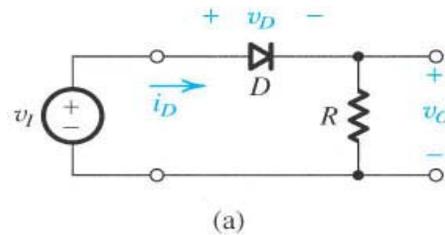- Example: Simple rectifier circuit
 - We will see a more accurate analysis of this circuit later



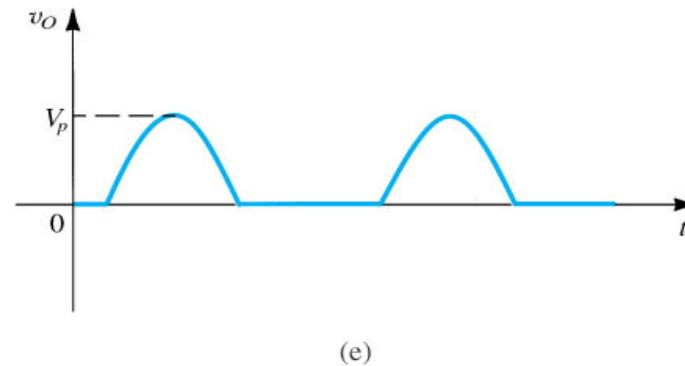- Example: Logic gates
 - This model is actually very useful in analysis of logic circuits and is often used






Outline of Section 3 - Diodes

- Other two terminal devices
- Diode models
- Exponential model
- Constant voltage drop model
- Reverse breakdown
- Applications
- Small-signal model
- PN junctions



I-V Characteristic of a Diode

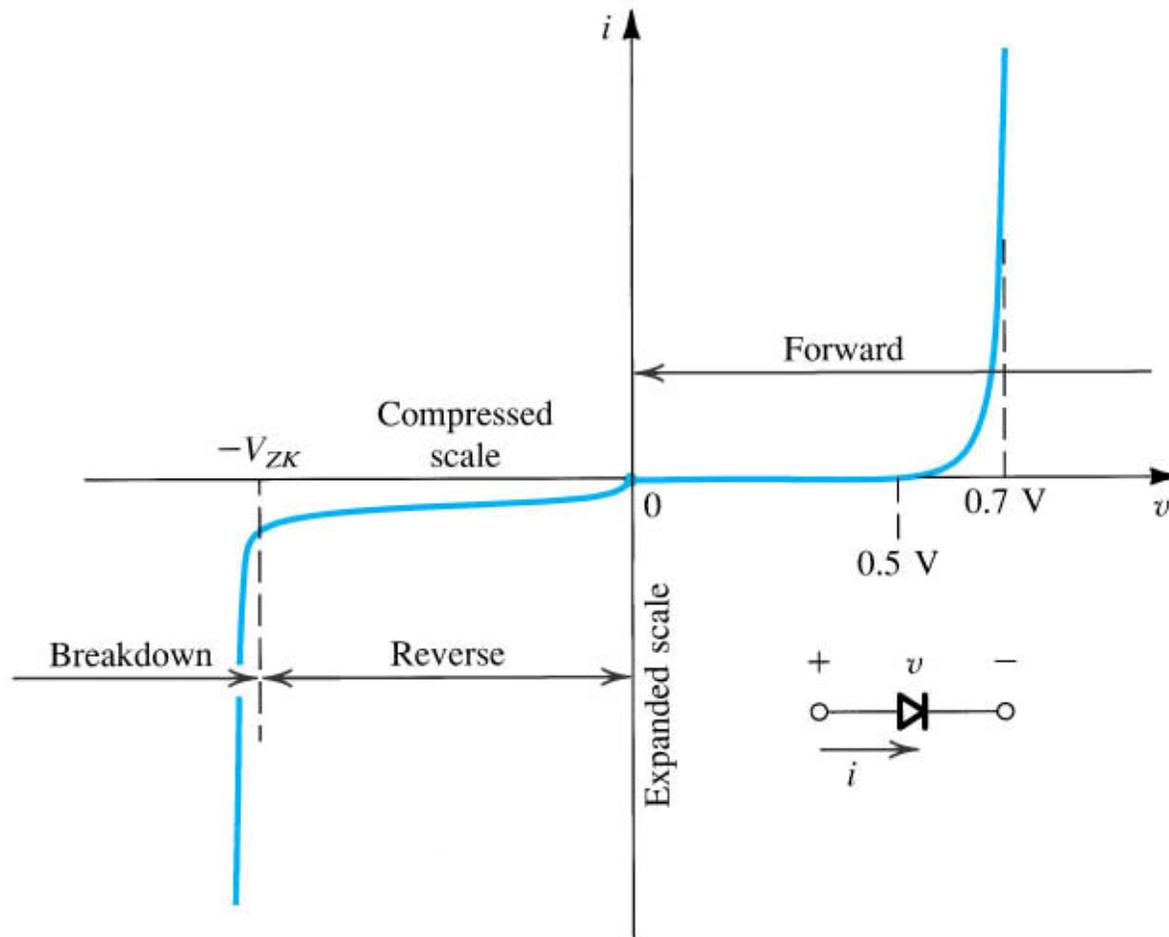

This nonlinear i-v characteristic can be described for most of its parts with the Exponential Model



Exponential Model Definitions

Exponential Model: $i = I_S \left(e^{\frac{v}{nV_T}} - 1 \right)$

- **I_S : reverse saturation current**

- proportional to cross-sectional area of current flow
- discrete Si devices:
 $I_S \sim 10^{-9}$ - 10^{-13} A
- IC Si devices: $I_S \leq 10^{-15}$ A

- **n : fitting parameter**

- normally between 1 and 2 for Si
- discrete Si devices: $n \sim 2$
- IC Si devices: $n \sim 1$

- **V_T : Thermal Voltage**

- from device physics:

$$V_T = \frac{k \cdot T}{q}$$

- **k : Boltzmann constant**
(1.38×10^{-23} J/K)
- **T : Temperature** (Kelvin)
- **q : electron charge**
(1.6×10^{-19} C)

- At room temperature,
 $V_T \sim 25$ mV




Exponential Model – Forward Bias

As V increases, $\exp\left(\frac{v}{n \cdot V_T}\right) \gg 1$

$$i \cong I_S e^{\frac{v}{nV_T}}$$

- The voltage at which the diode starts to conduct appreciably is called the *cut-in voltage*; value is $\sim .5V$ for silicon diodes

When diode is fully conducting, V remains constant at $\sim 0.7V$ for silicon diodes

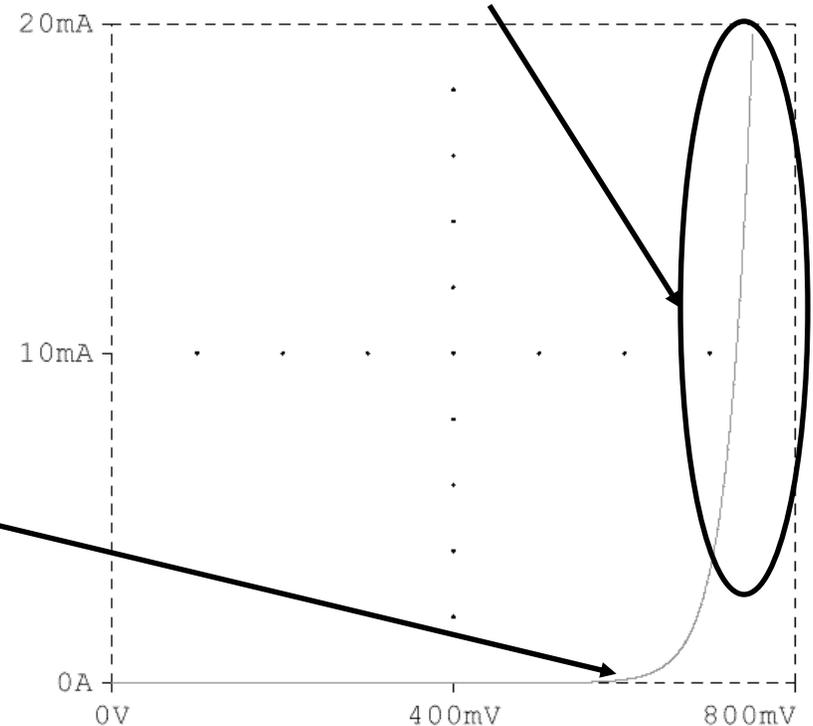

Diodes 3.12




Forward Bias Analysis

$$i = I_S e^{\frac{v}{nV_T}} \longleftrightarrow v = nV_T \ln\left(\frac{i}{I_S}\right)$$

Consider two points on
I-V curve above cut-in
voltage: (V_1, I_1) and
 (V_2, I_2)

$$\frac{I_2}{I_1} = \exp\left(\frac{V_2 - V_1}{n \cdot V_T}\right)$$
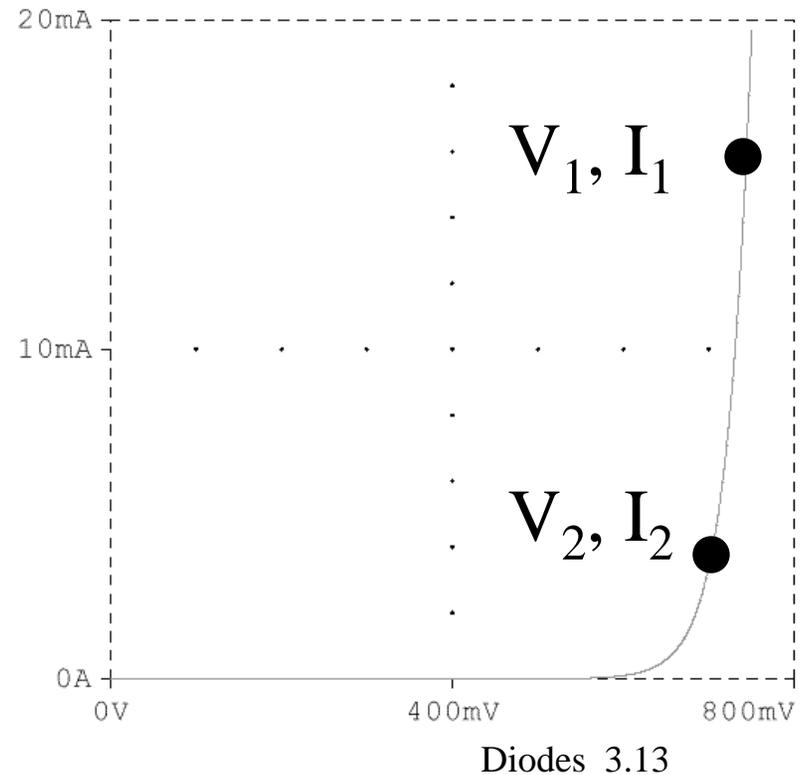
$$V_2 - V_1 = n \cdot V_T \cdot \ln\left(\frac{I_2}{I_1}\right)$$





Strong Forward Bias

- Given: a diode with $n = 1$ and $I = 1\text{mA}$ at $V = 0.7\text{V}$
- Question: determine the *voltage drop* across diode when the *current* flowing through the diode is doubled:
- I-V data points for $n = 1$ and $I_S = 6.9 \times 10^{-16}\text{A}$:

I	V
1pA	0.180V
10pA	0.239V
100pA	0.297V
1nA	0.355V
10nA	0.412V
100nA	0.470V
1μA	0.527V
10μA	0.585V
100μA	0.642V
1mA	0.700V
10mA	0.758V
100mA	0.815V

Note from data, above 10mA, a 10X increase in I results in only a 57mV increase in V

$$V_2 - 0.7 = n \cdot V_T \cdot \ln\left(\frac{2\text{mA}}{1\text{mA}}\right)$$

$$V_2 - 0.7 = (1)(25\text{mV})\ln(2)$$

$$V_2 = 0.717\text{V}$$



Reverse Bias


- Recalling exponential model
$$i = I_S \left(e^{\frac{v}{nV_T}} - 1 \right)$$
- As v becomes negative,

$$e^{\left(\frac{v}{nV_T}\right)} \ll 1 \quad i = -I_S$$

- Exponential model predicts approximately constant current under reverse bias; IC Si devices: $I_S \sim 10^{-15}$
- Usually, consider a reverse-biased diode to be *nonconductive; open circuit*



Circuit Analysis

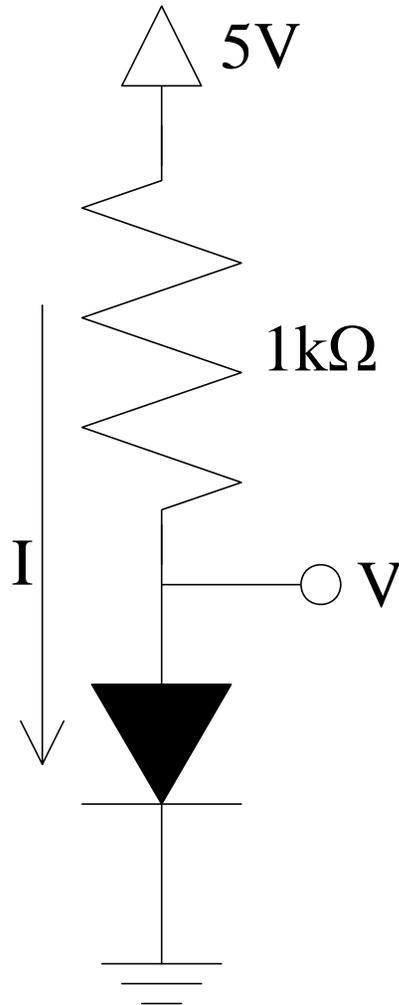

Given: $n = 1$, $I_S = 6.9 \times 10^{-16} \text{ A}$

Find: I and V


- For resistor: $I = \frac{5 - V}{1k}$
- For diode: $I = I_S \exp\left(\frac{V}{n \cdot V_T}\right)$

$$I = \frac{5 - V}{1k} = 6.9 \times 10^{-16} \exp\left(\frac{V}{25mV}\right)$$

- This is generally best for a circuit simulator to solve (like SPICE)



Iteration

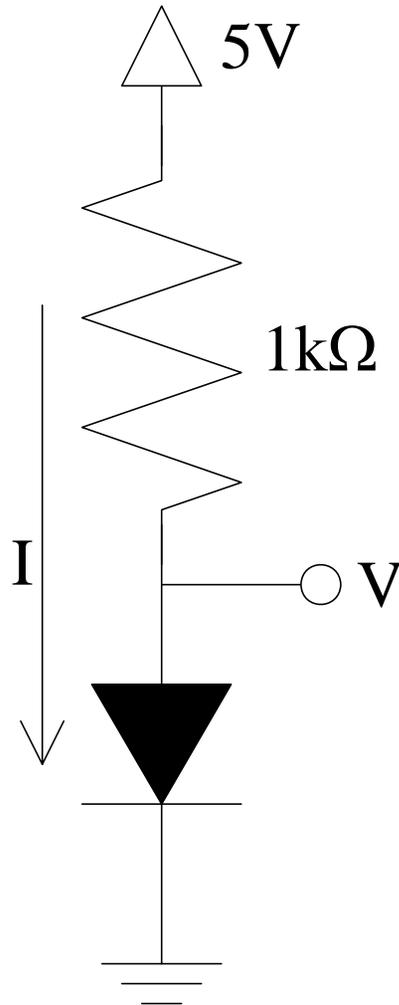

$n = 1, I_s = 6.9 \times 10^{-16} \text{A}$ Find I and V

- Iterative analysis procedure:

- Start with a guess for diode voltage drop

$$V \approx 0.7 \text{ is reasonable}$$

- Use guess for V to get corresponding I

$$I = \frac{5 - V}{1k}$$


- Use I to get better approximation for V

$$V = (25mV) \ln\left(\frac{I}{6.9 \times 10^{-16}}\right)$$

- Repeat procedure until V and I no longer change



Iteration (cont')

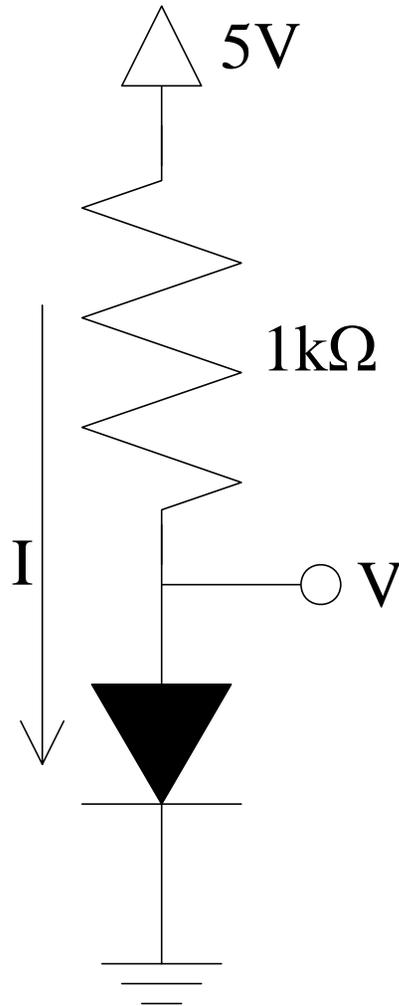

$n = 1, I_s = 6.9 \times 10^{-16} \text{A}$ **Find I and V**

- Iteration #1
($V = 0.7\text{V}$)

$$I = \frac{5 - 0.700}{1k} = 4.300 \text{mA}$$

$$V = (25m) \ln\left(\frac{4.300m}{6.9 \times 10^{-16}}\right) = 0.737\text{V}$$

- Iteration #2
($V = 0.737\text{V}$)

$$I = \frac{5 - 0.737}{1k} = 4.263 \text{mA}$$

$$V = (25m) \ln\left(\frac{4.263m}{6.9 \times 10^{-16}}\right) = 0.736\text{V}$$

- Iteration #3
($V = 0.736\text{V}$)



$$I = \frac{5 - 0.736}{1k} = 4.264 \text{mA}$$

$$V = (25m) \ln\left(\frac{4.264m}{6.9 \times 10^{-16}}\right) = 0.736\text{V}$$

$\therefore I = 4.264 \text{mA}, V = 0.736 \text{V}$



Graphical Analysis

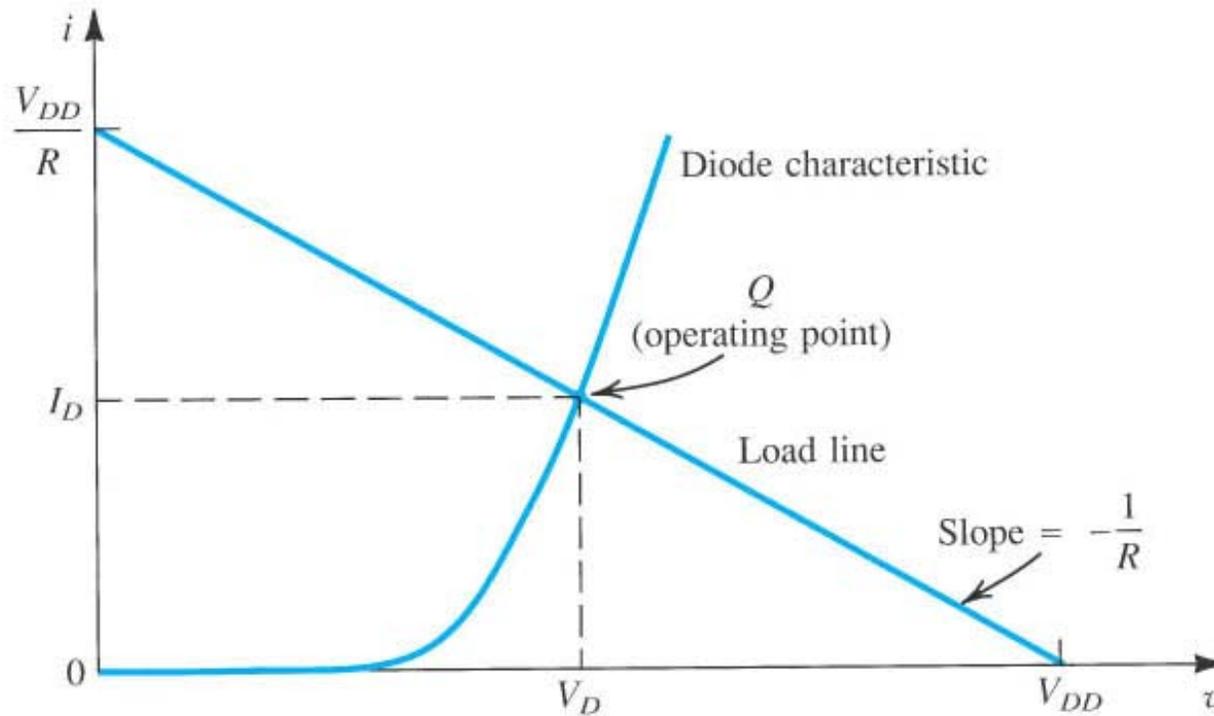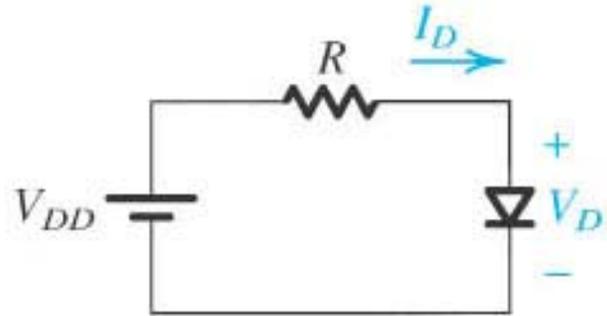

- 1) Plot two relationships on the i - v plane.
- 2) The solution is the intersection of the two graphs; ***operating point***




Outline of Section 3 - Diodes

- Other two terminal devices
- Diode models
- Exponential model
- Constant voltage drop model
- Reverse breakdown
- Applications
- Small-signal model
- PN junctions



The Constant Voltage Drop Model (CVDM)

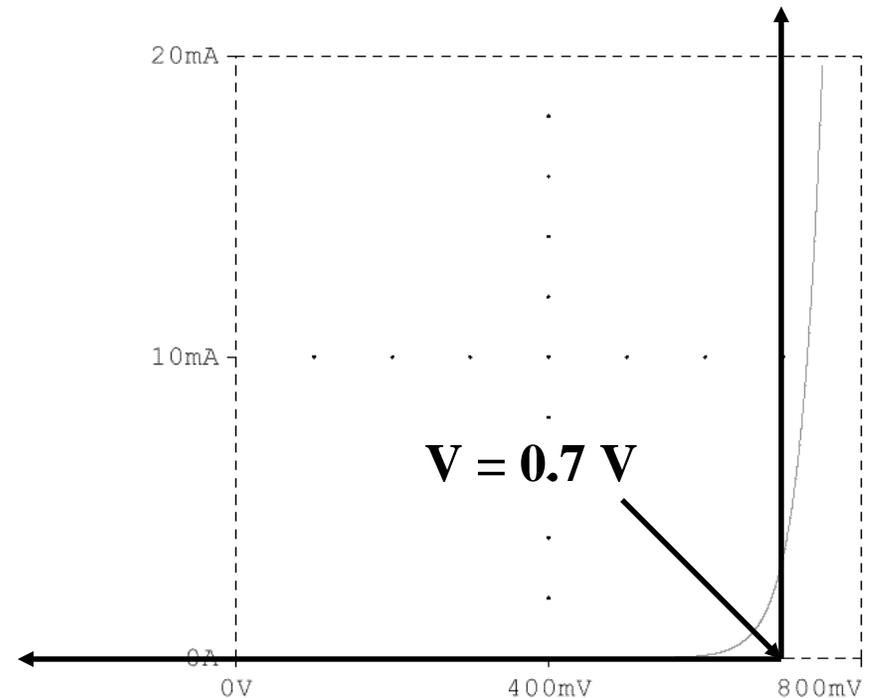- Exponential model gives accurate results; requires hand computation or a simulator
- The constant voltage drop model (CVDM) used to perform quick analysis of a diode circuit by hand
- CVDM approximates diode I-V curve piecewise-linearly






CVDM

- “Voltage” perspective of CVDM:
 - $V = 0.7V$ when diode is conducting
 - $V < 0.7V \Rightarrow$ diode is not conducting
- “Current” perspective of CVDM:
 - When $V = 0.7V$, diode supplies whatever current is required by the circuit
 - When $V < 0.7V$, diode supplies no current



How to use CVDM to Find I and V

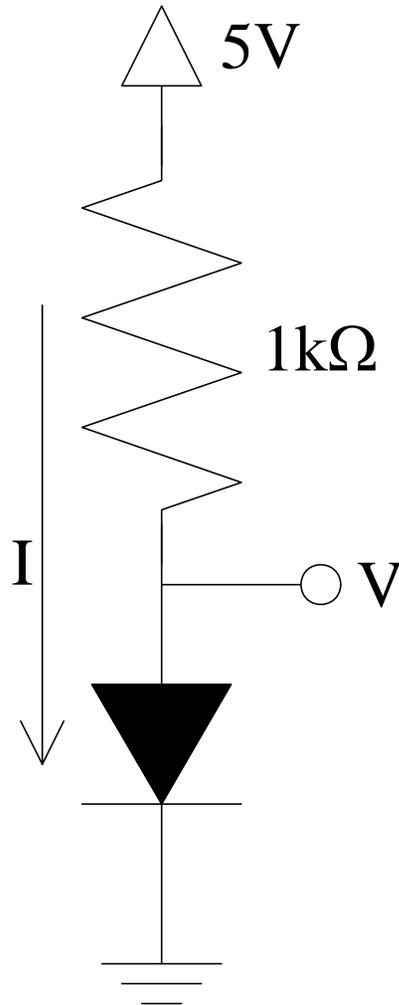

1) Make assumptions about whether diodes are *conducting or not*

2) Solve circuit:

use *0.7V drops* for conducting diodes

treat non-conducting diodes as *open-circuits*


3) Check validity of assumptions:

If consistent \Rightarrow DONE

If inconsistent \Rightarrow repeat with new assumptions



Example 1 – Find I and V

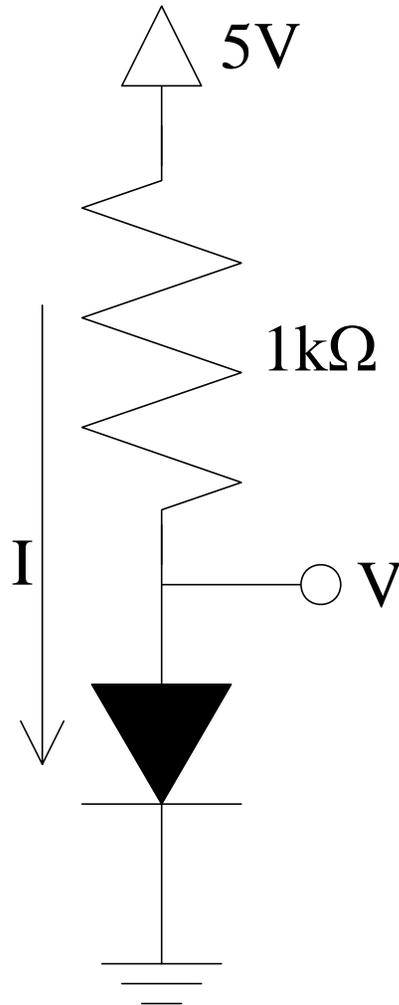

Assume that diode is conducting:


$$V = 0.7V$$

$$I = \frac{5 - 0.7}{1k} = 4.3mA$$

Result indicates that diode voltage drop 0.7V and diode current is 4.3 mA – acceptable.



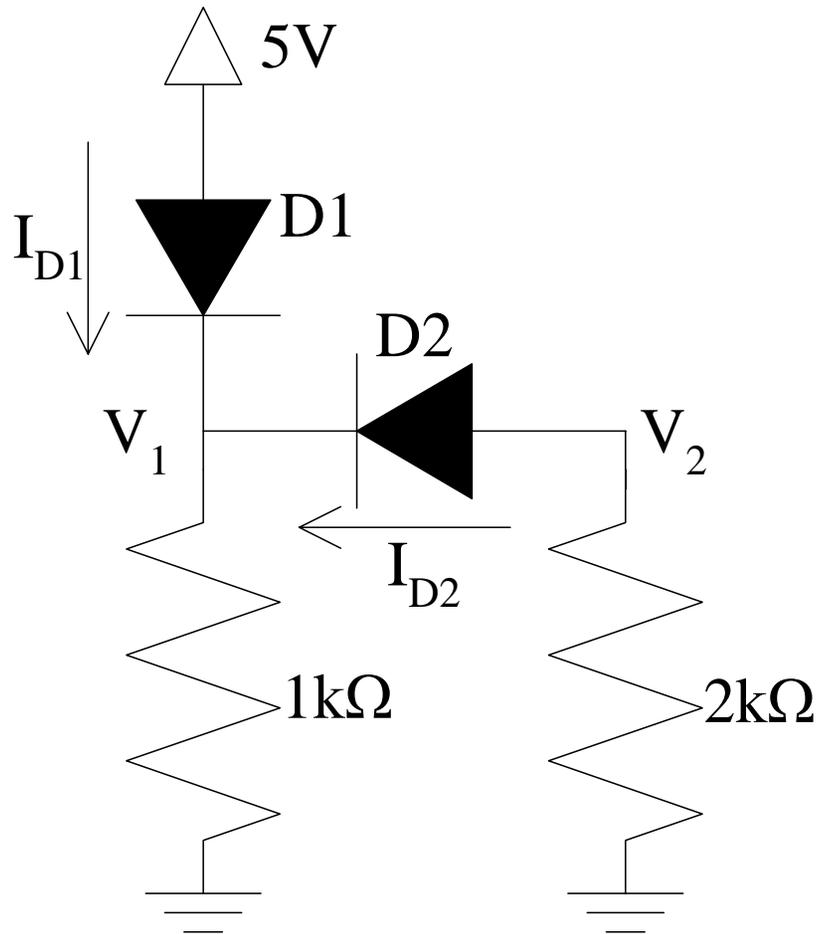Example 2 - Find V_1 , V_2 , I_{D1} and I_{D2}



Assume that both diodes are conducting

$$V_1 = 5 - 0.7 = \underline{4.3V}$$

$$V_2 - V_1 = 0.7 \Rightarrow \underline{V_2 = 5V}$$


$$I_{D2} = \frac{0 - V_2}{2k} = \frac{-5}{2k} = \underline{\underline{-2.5mA}}$$

Results *not* consistent for D_2



New Assumptions

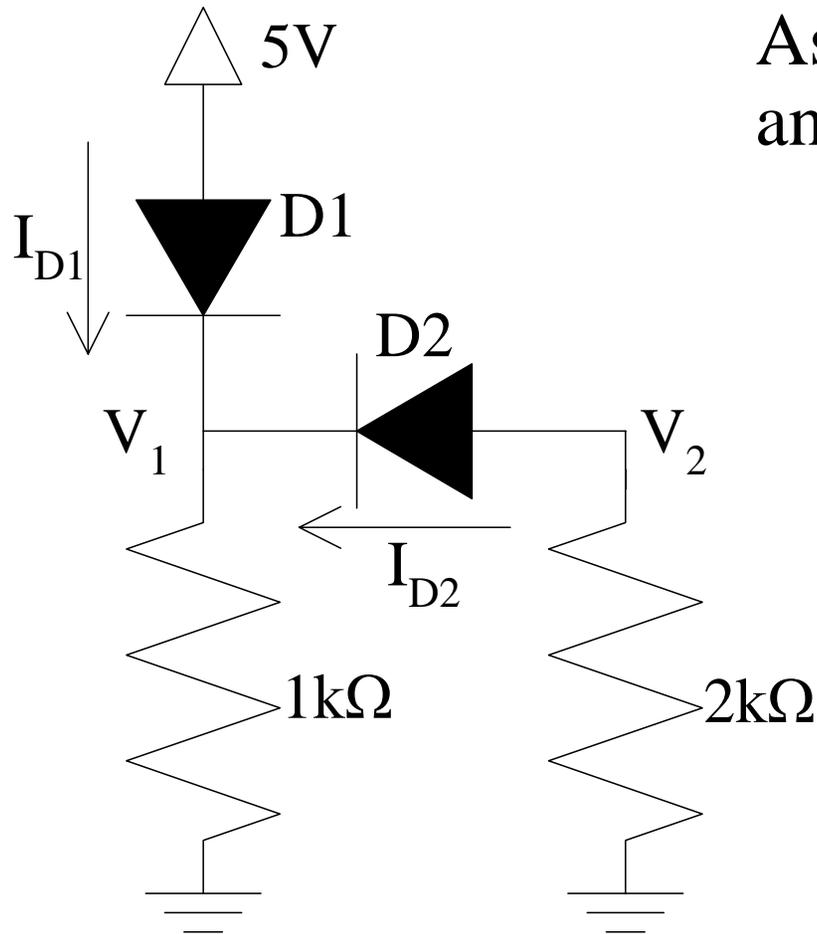Assume that D_1 is conducting
and that D_2 is not conducting



$$V_1 = 5 - 0.7 = \underline{4.3V}$$

$$\underline{I_{D2} = 0A}$$


$$\underline{V_2 = 0V}$$

$$I_{D1} = \frac{V_1 - 0}{1k} = \underline{4.3mA}$$

Results are acceptable



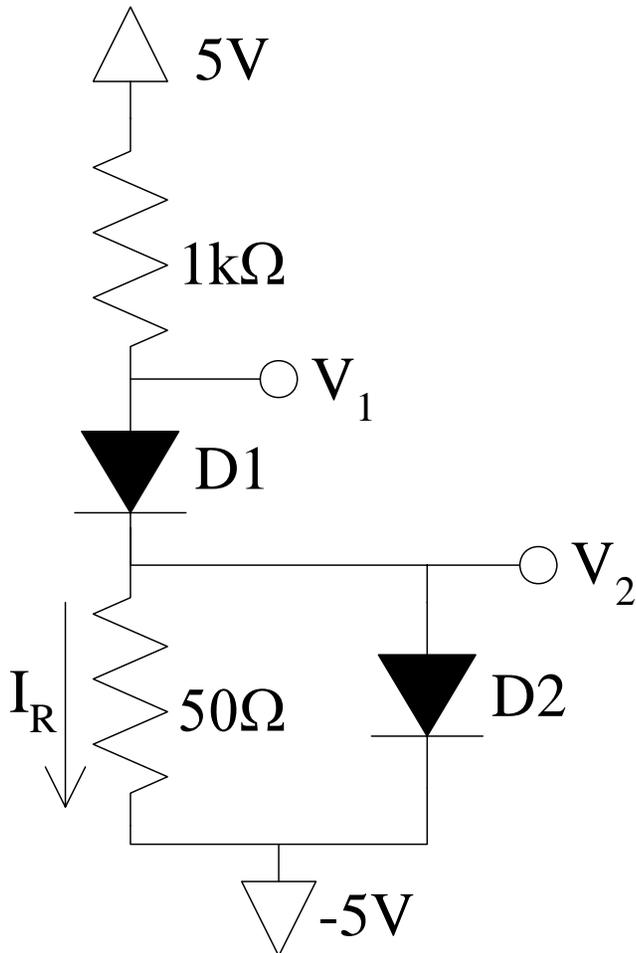Example 3 - Find V_1 , V_2 , I_{D1} and I_{D2}



Assume both D1 and D2 conducting

$$V_2 = -5 + 0.7 = \underline{-4.3V}$$

$$V_1 = V_2 + 0.7 = \underline{-3.6V}$$

$$I_{D1} = \frac{5 - V_1}{1k} = \frac{5 + 3.6}{1k} = \underline{8.6mA}$$

$$I_R = \frac{0.7}{50} = \underline{14mA}$$


$$I_{D2} = I_{D1} - I_R = \underline{-5.4mA}$$

Results *not* consistent for D2



New Assumptions

Assume D1 on, D2 off

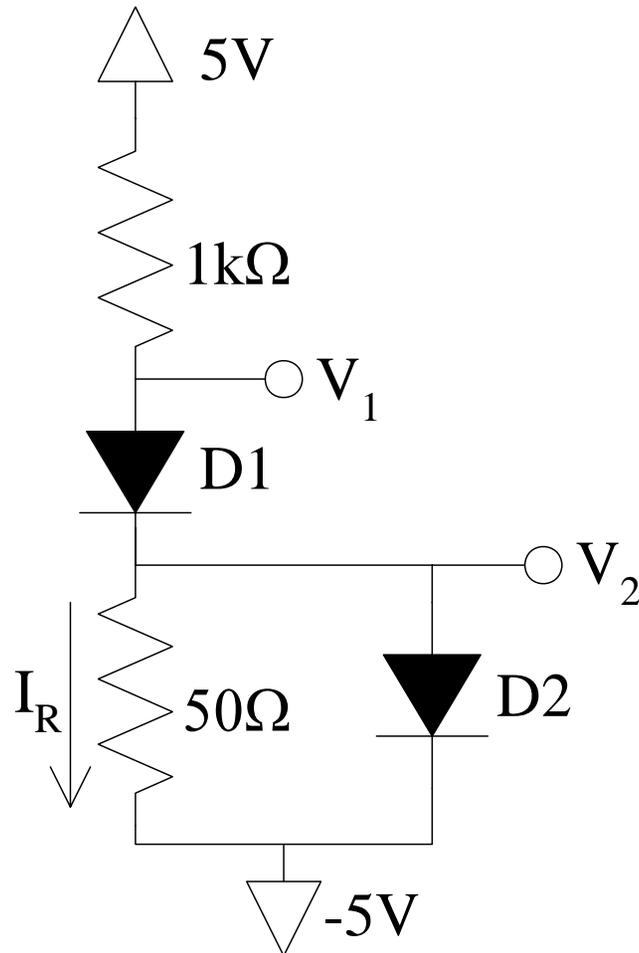

$$I_{D1} = I_R = \frac{5 - V_1}{1k} = \frac{V_2 + 5}{50}$$

$$V_1 - V_2 = 0.7V$$

$$\frac{5 - (V_2 + 0.7)}{1k} = \frac{V_2 + 5}{50} \Rightarrow V_2 = \underline{-4.557V}$$

$$V_1 = \underline{-3.857V}$$

$$I_{D1} = \frac{5 - V_1}{1k} = \underline{8.857mA}$$

Check D2: $V_2 + 5 = 0.443V < 0.7V \rightarrow D2 \text{ off}$

Results acceptable





Outline of Section 3 - Diodes

- Other two terminal devices
- Diode models
- Exponential model
- Constant voltage drop model
- Reverse breakdown
- Applications
- Small-signal model
- PN junctions



Reverse-Breakdown Region – Characteristics

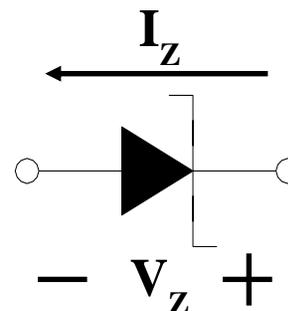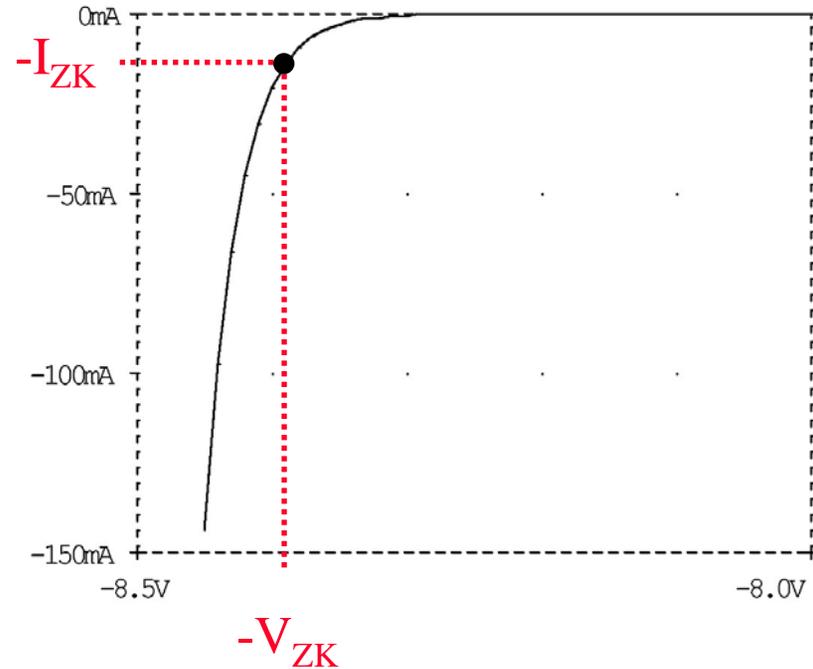
- Point on I-V curve where breakdown occurs called *Zener knee* ($-V_{ZK}$, $-I_{ZK}$)
- *Zener* diodes designed specifically for operation in reverse-breakdown.
- This means that they can handle large currents, hence they are physically larger.






Reverse-Breakdown Region – Modeling

- Model for Zener diode:

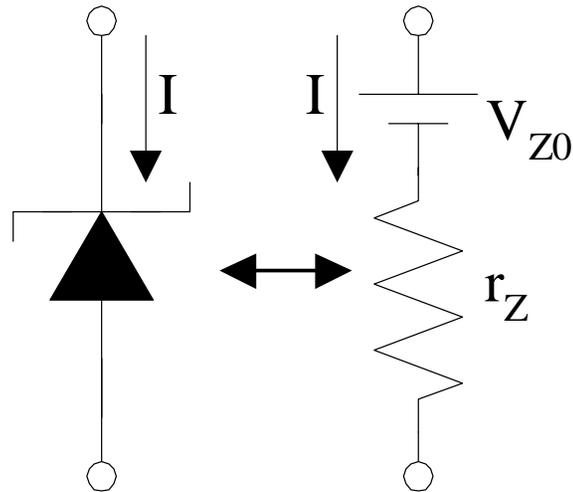

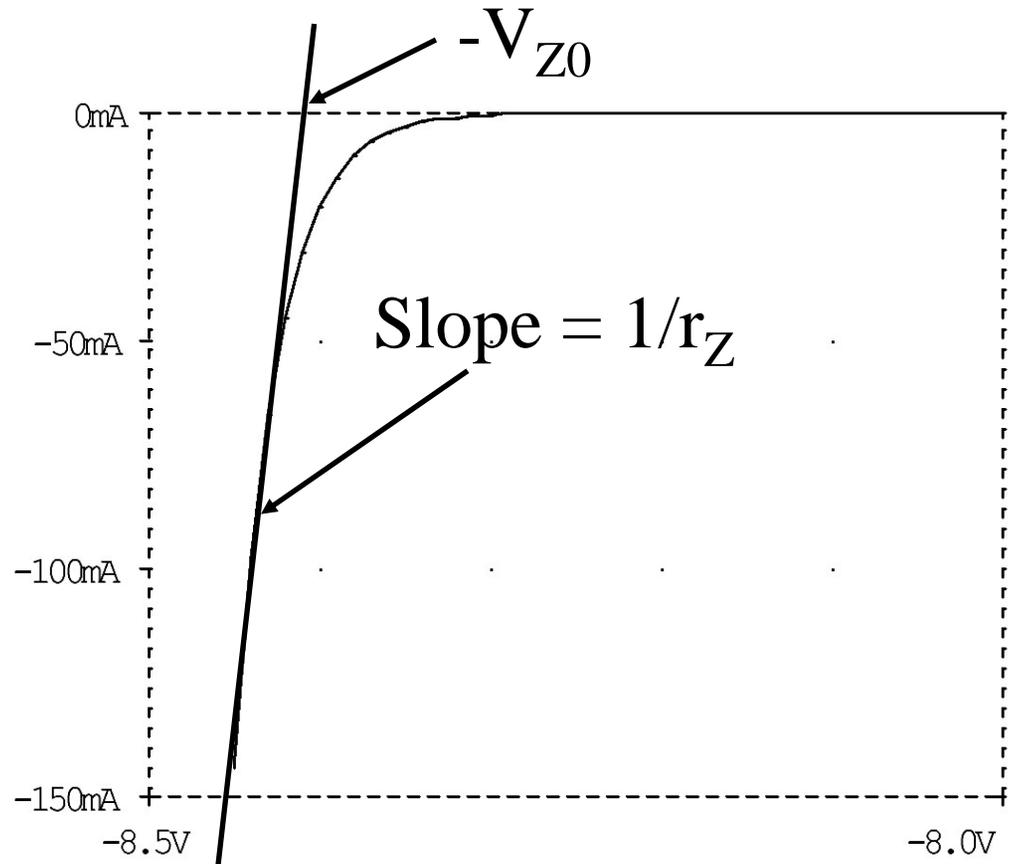- Typical Zener application : voltage regulation




- Slope of I-V curve in reverse-breakdown region very steep; r_Z very small



Zener Example

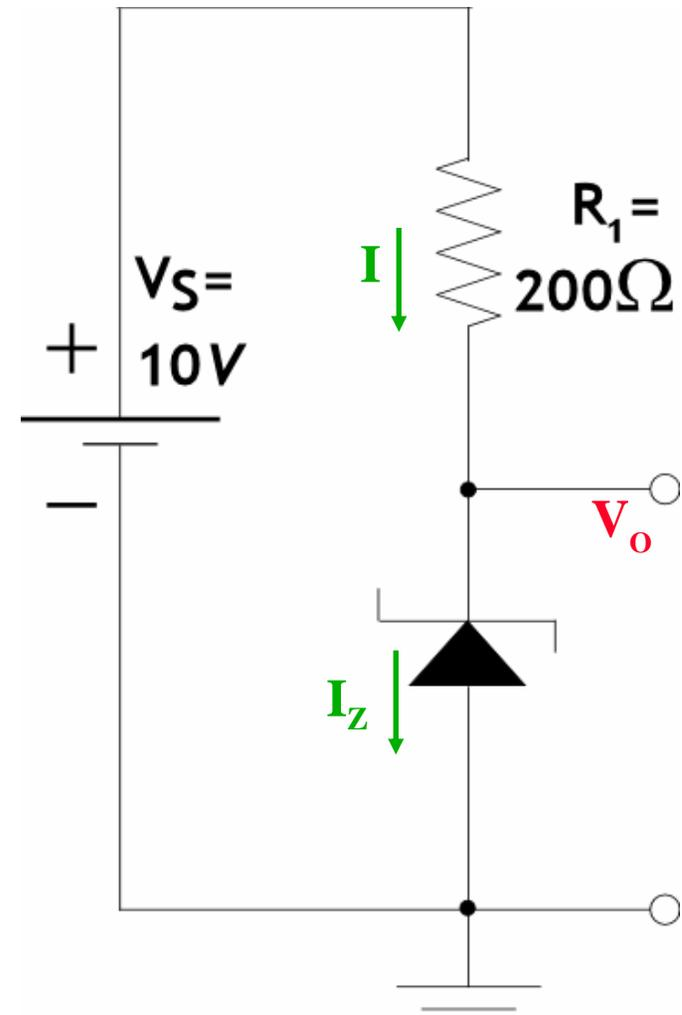Question: given a Zener Diode with $V_{Z0} = 5.5V$ and an incremental resistance of $r_z = 40\Omega$, calculate the output voltage V_o .





Example (cont')

- 1) Replace Zener with model
- 2) Perform circuit analysis by solving for I in the network:

$$V_S = IR_1 + V_{Z0} + Ir_Z$$

$$10 = I(200) + 5.5 + I(40)$$

$$\Rightarrow I = 18.75mA$$

- 3) Compute V_o :

$$V_o = V_S - IR_1 = 10 - (18.75mA)(200)$$

$$\Rightarrow V_o = 6.25V$$

