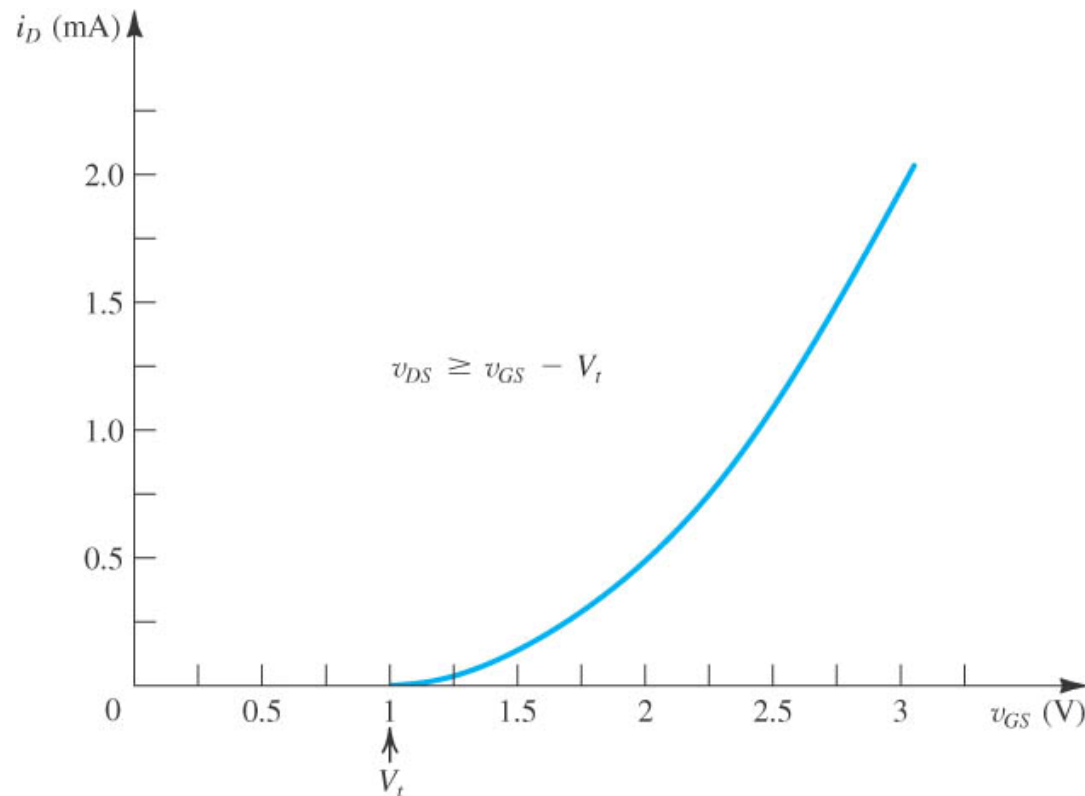




# More MOSFETs from the Text Book

- Current-Voltage Characteristics



**Figure 4.12** The  $i_D$ - $v_{GS}$  characteristic for an enhancement-type NMOS transistor in saturation ( $V_t = 1$  V,  $k'_n W/L = 1.0$  mA/V<sup>2</sup>).



# More MOSFETs from the Text Book

- Circuit representation of Current-Voltage Characteristics in the **Saturation Region** *ignoring channel length modulation effect*

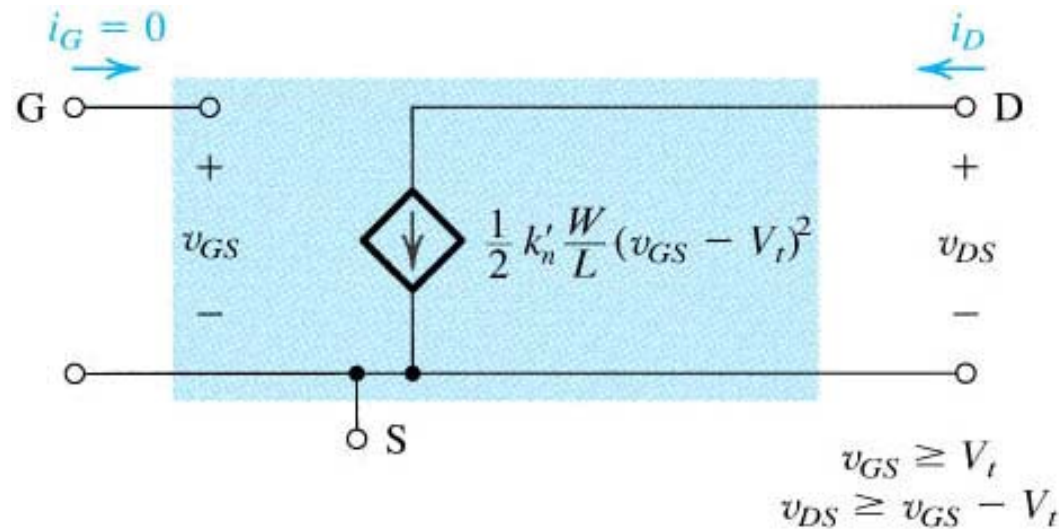


Figure 4.13 Large-signal equivalent-circuit model of an  $n$ -channel MOSFET operating in the saturation region.

- This circuit is called **Large-Signal equivalent circuit**
- **Note:** This circuit is **NOT USED** in most of our practical MOSFET problems



## Outline of Chapter 4

- *1- Intro to MOS Field Effect Transistor (MOSFET)*
- 2- NMOS FET
- 3- PMOS FET
- 4- DC Analysis of MOSFET Circuits
- 5- MOSFET Amplifier
- 6- MOSFET Small Signal Model
- 7- MOSFET Integrated Circuits
- 8- CSA, CGA, CDA
- 9- CMOS Inverter & MOS Digital Logic




## MOSFET DC Analysis

1. Make an assumption about the state of operation
  - There are three possibilities
  - The mostly used case is saturation mode
  - This is the mode used in designing amplifiers
2. Solve to find DC voltages and currents
  - Namely,  $I_D$ ,  $V_D$ ,  $V_S$ , and  $V_G$
3. Verify the found values with the inequalities describing the state of operation
4. If not correct, start solving the circuit again with another assumption about the state of operation



## Example 1

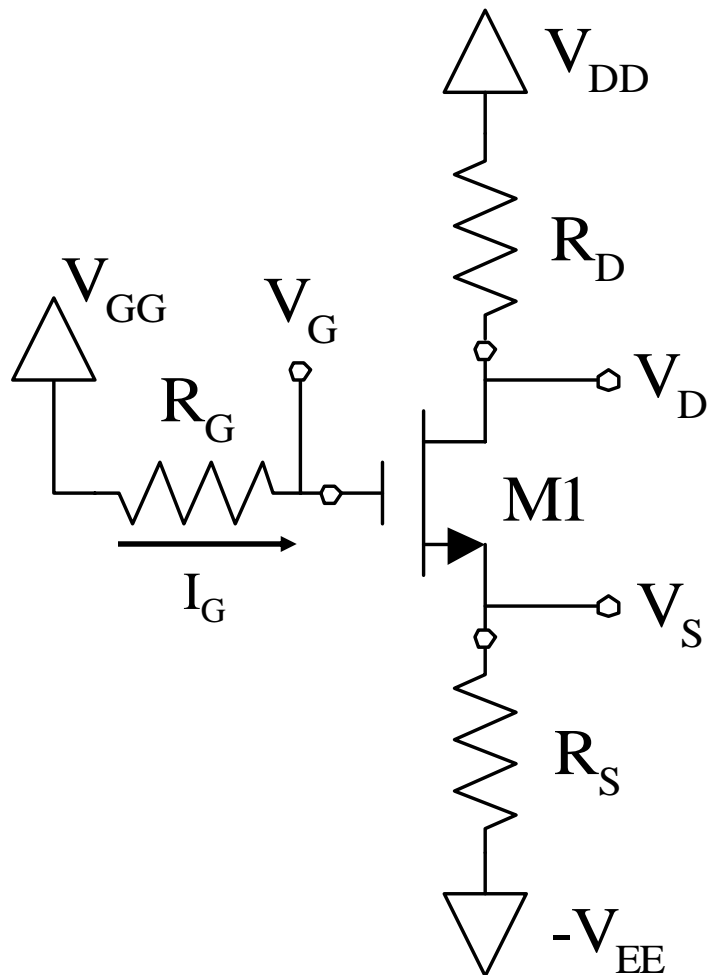

- No gate current:  $I_G = 0 \Rightarrow V_G = V_{GG}$
- Have expressions for  $I_D$ :

$$I_D = \frac{V_{DD} - V_D}{R_D} = \frac{V_S + V_{EE}}{R_S}$$

- Assume saturation mode:


$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

- Body effect:  $V_B = -V_{EE} \Rightarrow V_S \neq V_B$

$$V_t = V_{t0} + \gamma \left( \sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$$



## Example 1 – con't

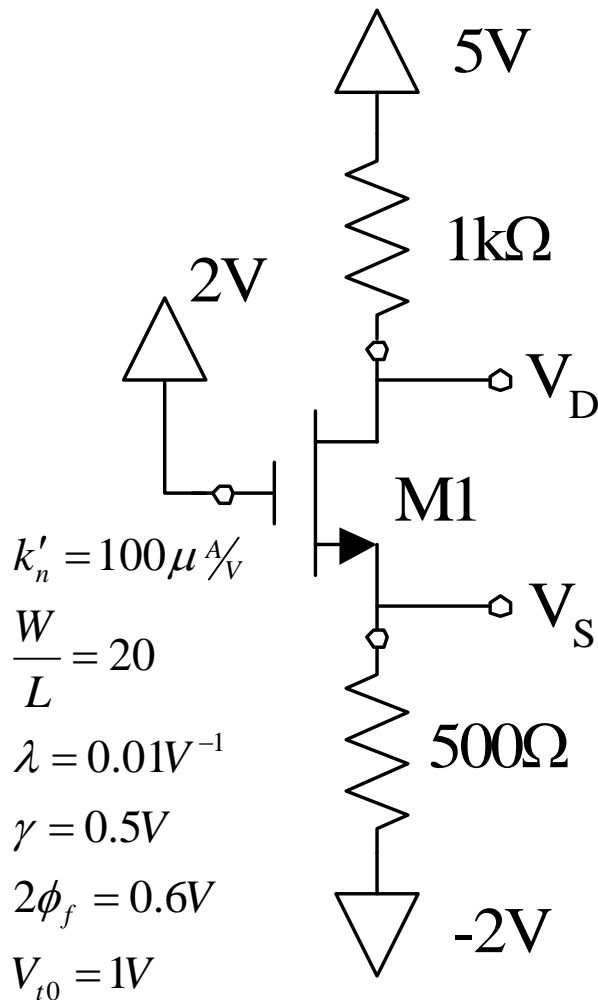

$$I_D = \frac{5 - V_D}{1k} = \frac{V_S + 2}{500}$$

- **Assume saturation** mode:

$$I_D = 1m(2 - V_S - V_t)^2 [1 + \lambda(V_D - V_S)]$$


$$V_t = 1 + 0.5(\sqrt{0.6 + V_S + 2} - \sqrt{0.6})$$

- With  $V_D$  in terms of  $V_S$ , get cubic  $I_D$  expression
- Neglect CLM and Body Effect.

$$I_D = 1m(2 - V_S - 1)^2$$



## Example 1 – con't

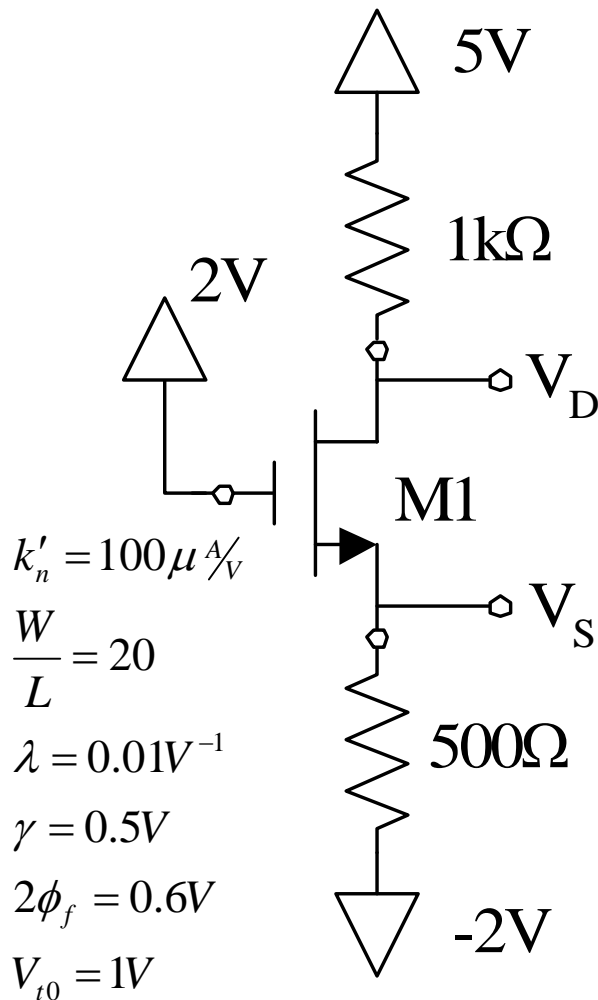

$$I_D = 1m(2 - V_S - 1)^2 = \frac{V_S + 2}{500}$$

$$V_S^2 - 4V_S - 3 = 0$$

$$V_S = 4.646V \text{ or } V_S = -0.646V$$

### Check conditions for saturation


$$V_{GS} > V_t \Rightarrow 2 - V_S > 1 \Rightarrow V_S < 1V$$

$$V_S = -0.646V$$

$$I_D = 2.708mA$$



## Example 1 – con't

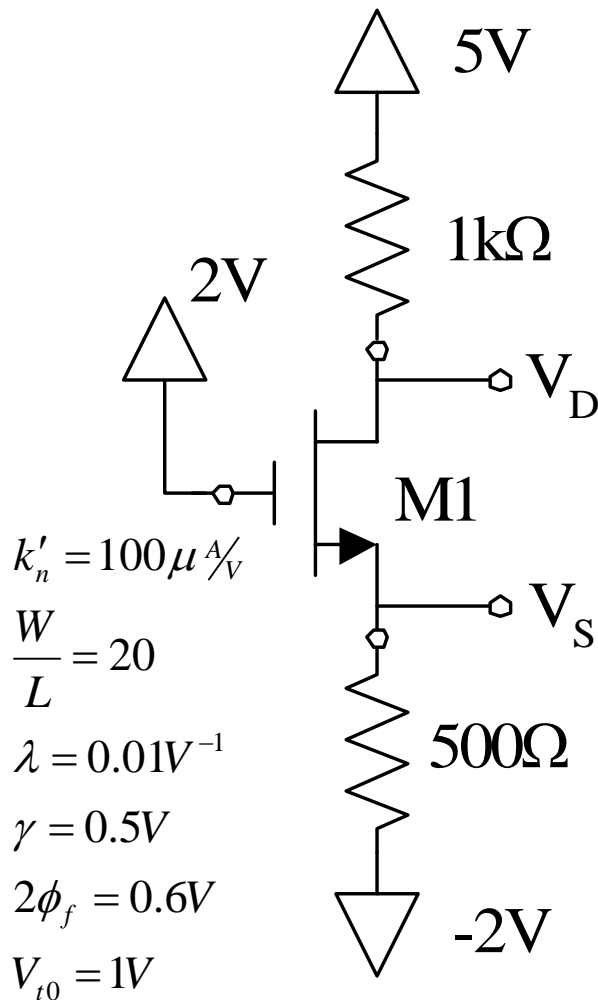

$$V_D = 5 - I_D R_D = \underline{2.292 V}$$

- **Verify saturation :**

$$V_{DS} > V_{GS} - V_t$$

$$V_D - V_S > V_G - V_S - V_t$$

$$2.292 > 2 - 1 = 1$$

- Maximum  $R_D$  that sustains saturation mode:  $V_D > 1 V$ ?


$$V_D = 5 - (2.708 m) R_D > 1 V$$

$R_D < 1.477 k\Omega$





## Example 2

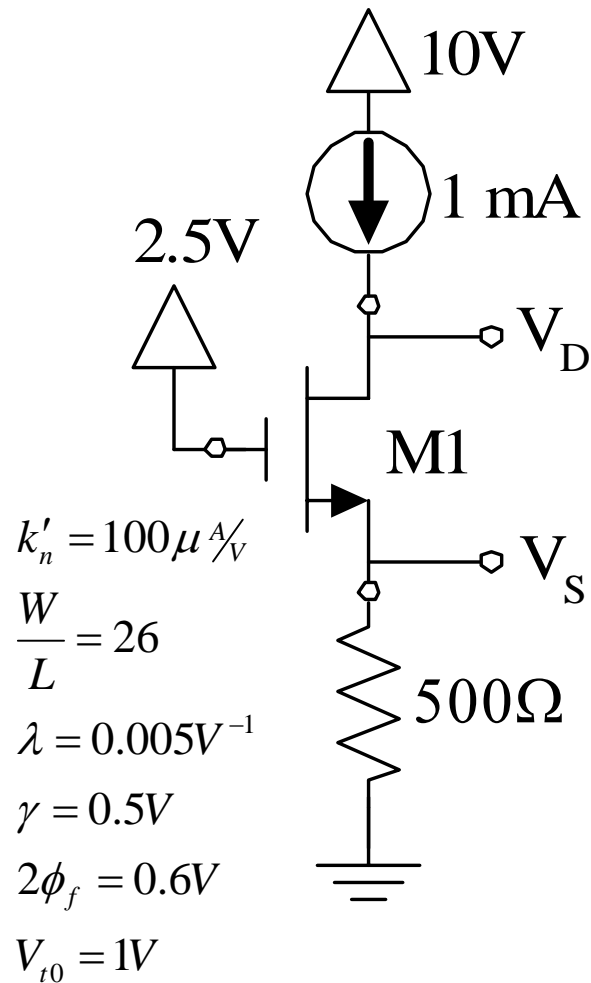

$$I_D = 1mA = \frac{V_S}{500} \Rightarrow V_S = 0.5V$$

- Calculate  $V_t$ :

$$V_t = 1 + 0.5(\sqrt{0.6 + 0.5} - \sqrt{0.6}) = 1.137V$$

- **Assume saturation mode:**

$$I_D = 1.3m(2.5 - 0.5 - 1.137)^2 [1 + 5m(V_D - 0.5)]$$


- Solve for  $V_D$ :

Verify the assumption

$$\boxed{V_D = 7.07V} > V_G - V_t$$



## Example 3

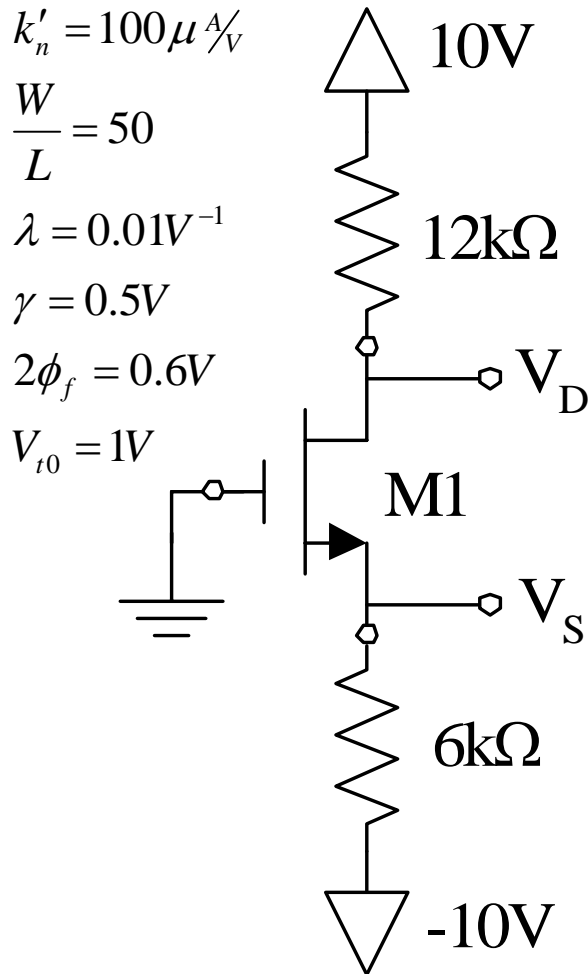

$$I_D = \frac{10 - V_D}{12k} = \frac{V_S + 10}{6k}$$

- **Assume saturation mode:**

$$I_D = 2.5m(-V_S - V_t)^2 [1 + \lambda(V_D - V_S)]$$

- No simple way to find  $V_S$ ; neglect Body effect
- With  $V_D$  in terms of  $V_S$ , get cubic for  $I_D$ ; neglect CLM

$$I_D = 2.5m(-V_S - 1)^2 = \frac{V_S + 10}{6k}$$

$$15 \cdot V_S^2 + 29 \cdot V_S + 5 = 0$$

$$V_S = -0.191V \quad \text{or} \quad V_S = -1.742V$$



## Example 3 – con't

$$k'_n = 100 \mu A/V$$


$$\frac{W}{L} = 50$$

$$\lambda = 0.01 V^{-1}$$

$$\gamma = 0.5 V$$

$$2\phi_f = 0.6 V$$

$$V_{t0} = 1 V$$

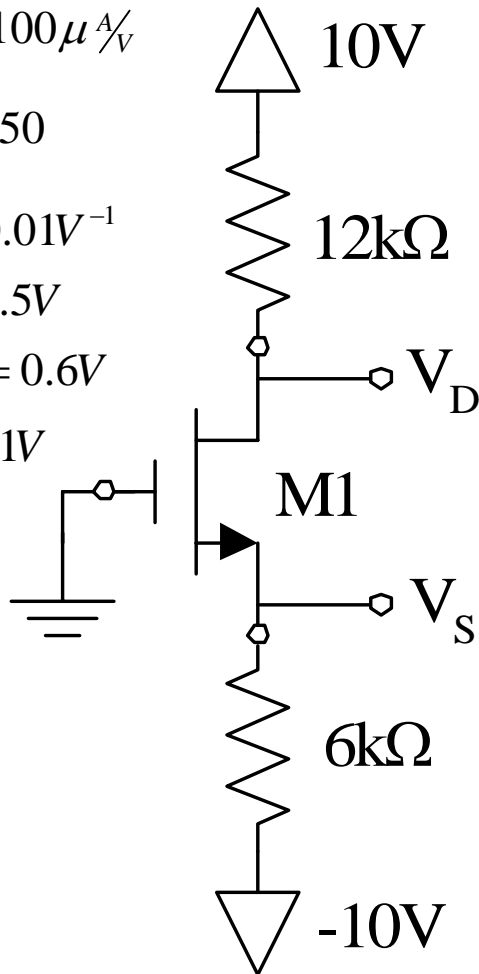

- Require  $V_{GS} > V_t$   $V_S = -1.742V$
- Solve for  $I_D$ :  $I_D = \frac{V_S + 10}{6k} = \underline{1.376mA}$
- Solve for  $V_D$ :  $V_D = 10 - I_D R_D = \underline{-6.51V}$

But, require  $V_D > V_G - V_t = -1V$

*∴ Cannot be in saturation*

- Assume triode region :

$$I_D = 5m \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Need expression for  $V_{DS}$



## Example 3 – con't

$$k'_n = 100 \mu A/V$$


$$\frac{W}{L} = 50$$

$$\lambda = 0.01 V^{-1}$$

$$\gamma = 0.5 V$$

$$2\phi_f = 0.6 V$$

$$V_{t0} = 1 V$$

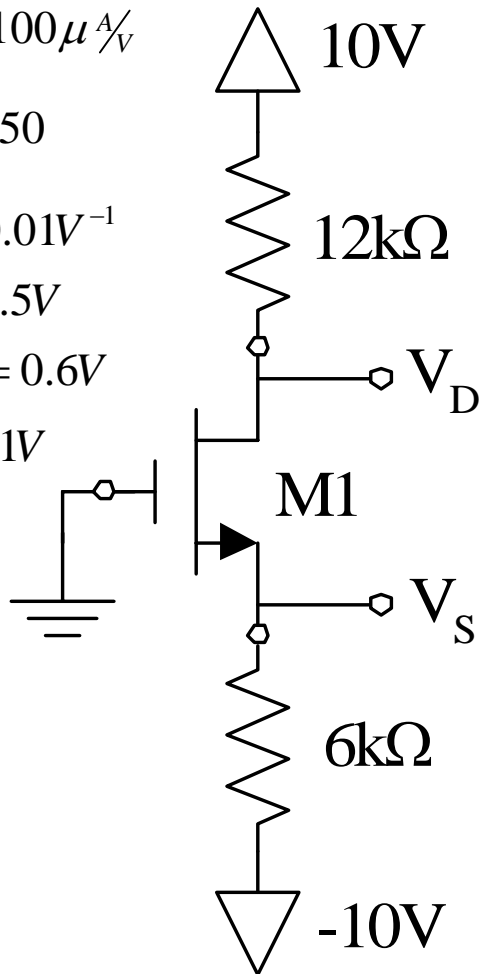

$$I_D = \frac{10 - V_D}{12k} = \frac{V_S + 10}{6k} \quad V_D = -2V_S - 10$$

$$V_{DS} = -3V_S - 10$$

- Substitute & solve for  $V_S$ :

$$45 \cdot V_S^2 + 511 \cdot V_S + 1210 = 0$$

$$V_S = -3.365 V \quad \text{or} \quad V_S = -7.991 V$$

- Find corresponding  $V_D$ 's:

$$V_D = -3.27 V \quad \text{or} \quad V_D = 5.982 V$$

But, require  $V_D < V_G - V_t = -1 V$

$$V_D = -3.27 V \quad \& \quad V_S = -3.37 V$$

$$I_D = 1.11 mA$$



## DC Analysis – General Comments

What should we do in our engineering calculations?

- CLM generally has small effect at DC (a few percent)
- Can usually be safely ignored
- Neglecting Body effect can result in significant errors in DC analysis
- Rules of thumb (DC Analysis):
  - Ignore CLM unless easy to include
  - Include Body effect unless  $V_S$  not easy to find



## Outline of Chapter 4

- *1- Intro to MOS Field Effect Transistor (MOSFET)*
- 2- NMOS FET
- 3- PMOS FET
- 4- DC Analysis of MOSFET Circuits
- 5- MOSFET Amplifier
- 6- MOSFET Small Signal Model
- 7- MOSFET Integrated Circuits
- 8- CSA, CGA, CDA
- 9- CMOS Inverter & MOS Digital Logic



# Small Signal Analysis

$$k_n = 100\mu\text{A/V}$$

$$W/L = 50$$


$$\lambda = 0.01\text{V}^{-1}$$

$$V_{t0} = 1\text{V}$$

$$V_{DD} = 6\text{V}$$

$$R_D = 1\text{k}\Omega$$

$$V_{GS} = 2\text{V}$$

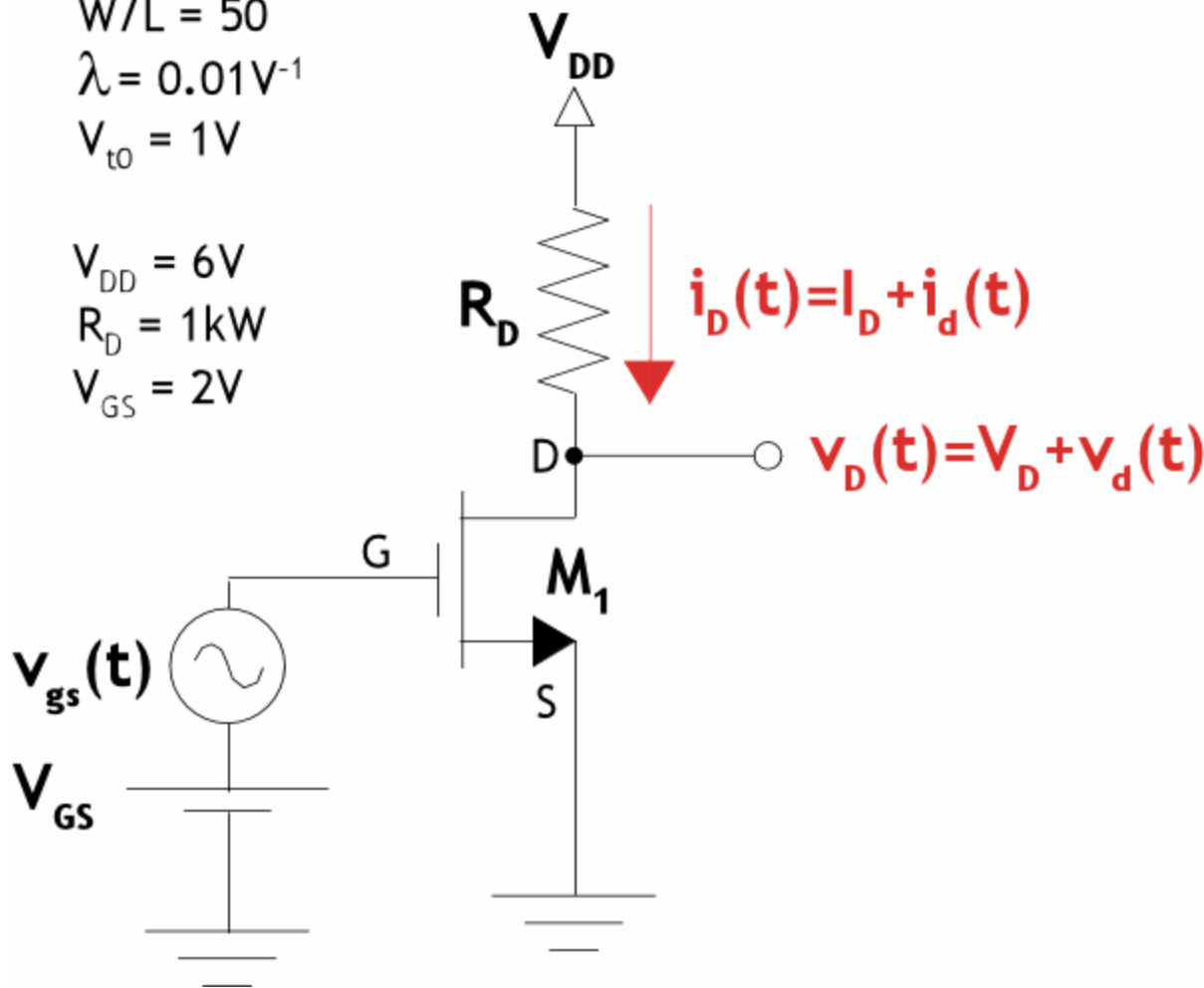

- Gate input has DC and AC components
- So will the drain voltage and current
- Develop small signal model





# Operating Point $I_D$ vs $V_{GS}$

$k_n = 100\mu\text{A/V}$   
 $W/L = 50$   
 $\lambda = 0.01\text{V}^{-1}$   
 $V_{t0} = 1\text{V}$

$V_{DD} = 6\text{V}$   
 $R_D = 1\text{k}\Omega$   
 $V_{GS} = 2\text{V}$

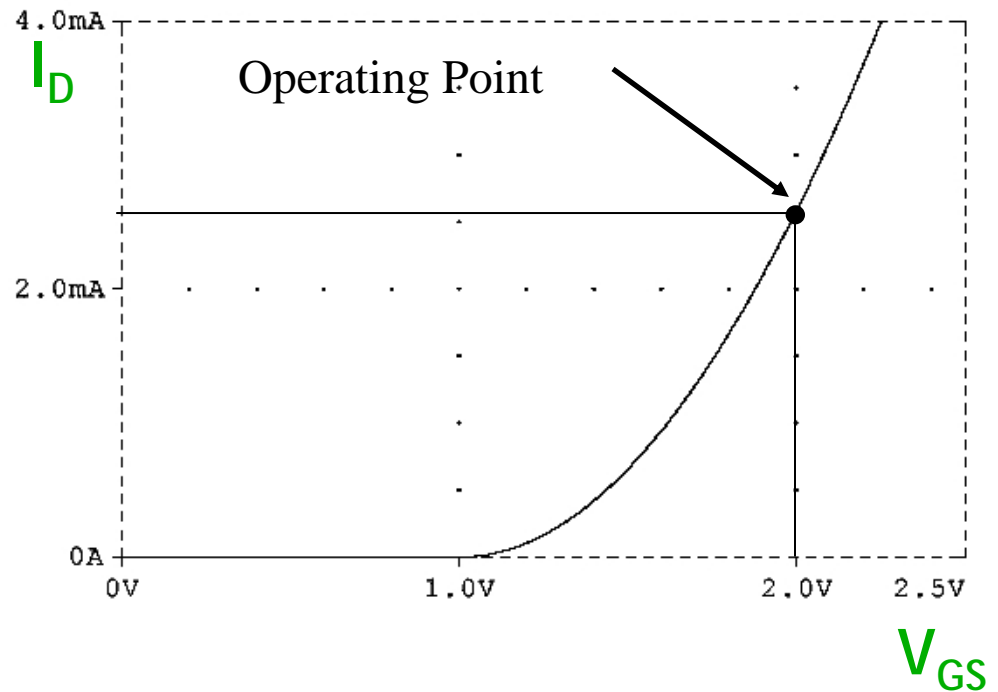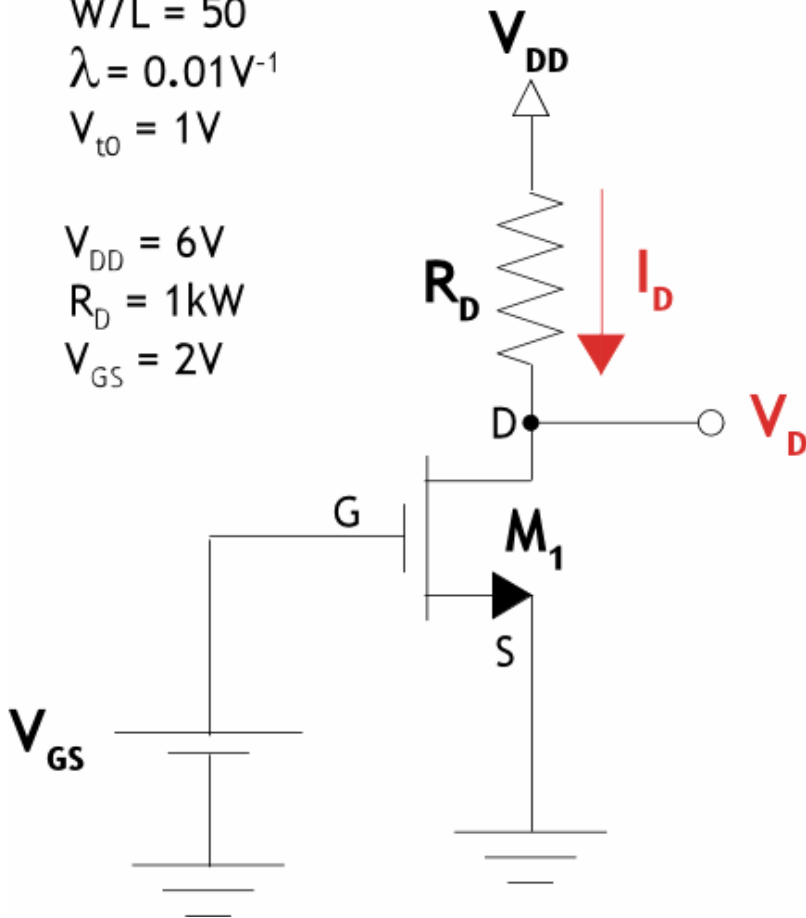
- DC analysis, AC sources off
- Operating point determined by  $V_{GS} - V_t$  in saturation






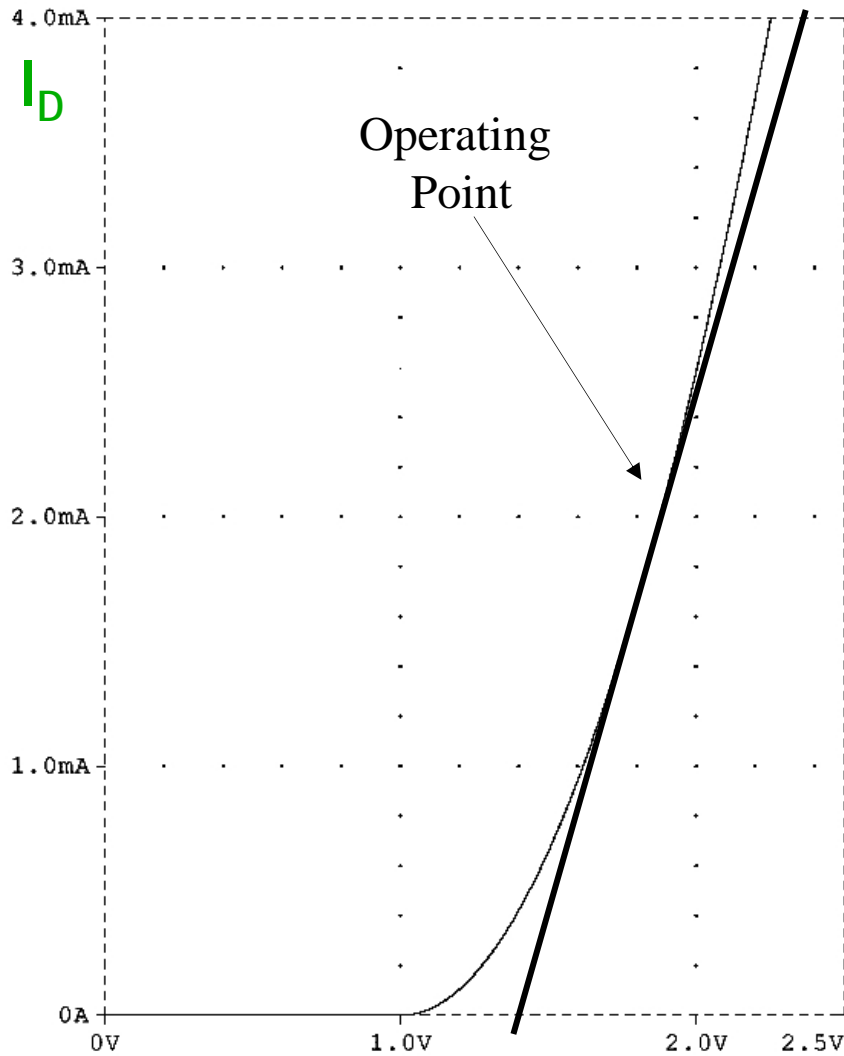
# Small Signal Superposition – $I_D$ vs $V_{GS}$



Consider superposition of an AC signal at the DC operating point

Slope of  $i_d$ - $v_{gs}$  curve at operating defined as MOSFET transconductance,  $g_m$

$$g_m \equiv \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{OP} \approx \frac{\Delta I_D}{\Delta V_{GS}}$$

$V_{GS}$



## MOSFET Transconductance – $g_m$

- To derive an expression for  $g_m$ :

$$g_m \equiv \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{i_D=I_D}$$

- Start with full  $I_D$  equation

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda \cdot V_{DS})$$

- Take derivative and simplify

$$\frac{\partial i_D}{\partial v_{GS}} = \underbrace{k'_n \frac{W}{L} (V_{GS} - V_t)}_{\frac{2 \cdot I_D}{(V_{GS} - V_t)}} (1 + \lambda \cdot V_{DS})$$

$$g_m = \frac{2 \cdot I_D}{V_{GS} - V_t}$$



## Summary of $g_m$

- Sedra & Smith use several expressions for  $g_m$

$$g_m = \frac{2 \cdot I_D}{V_{GS} - V_t}$$

$$g_m = k'_n \frac{W}{L} (V_{GS} - V_t)(1 + \lambda \cdot V_{DS})$$

$$g_m = \sqrt{2k'_n} \sqrt{\frac{W}{L}} \sqrt{1 + \lambda \cdot V_{DS}} \sqrt{I_D}$$



# Basic MOSFET Amplifier Operation

$$k_n = 100\mu\text{A/V}$$

$$W/L = 50$$


$$\lambda = 0.01\text{V}^{-1}$$

$$V_{t0} = 1\text{V}$$

$$V_{DD} = 6\text{V}$$

$$R_D = 1\text{k}\Omega$$

$$V_{GS} = 2\text{V}$$

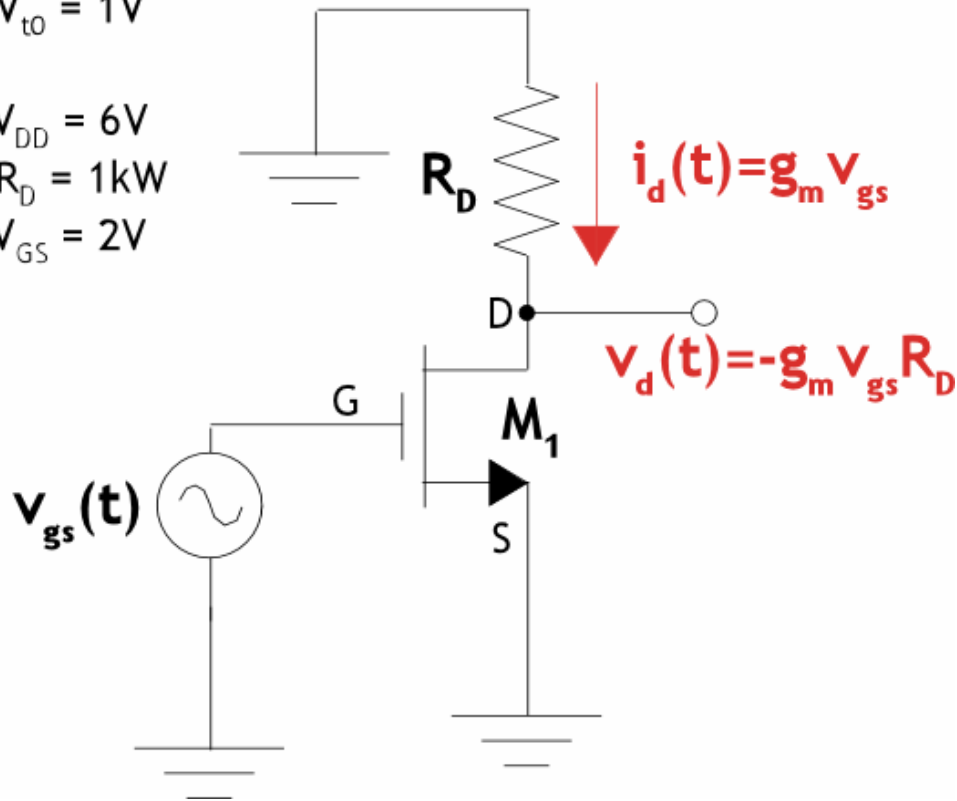

- Apply small signal at gate:  $v_{gs}$
- Results in signal current flow at drain  $i_d$ ;  $g_m$  proportionality constant
- Signal current through  $R_D$  produces output voltage
- Output signal voltage equal to:  $v_d = -g_m v_{gs} R_D$