





Outline of Chapter 4

- *1- Intro to MOS Field Effect Transistor (MOSFET)*
- 2- NMOS FET
- 3- PMOS FET
- 4- DC Analysis of MOSFET Circuits
- 5- MOSFET Amplifier
- 6- MOSFET Small Signal Model
- 7- MOSFET Integrated Circuits
- 8- CSA, CGA, CDA
- 9- CMOS Inverter & MOS Digital Logic



Small Signal Modeling

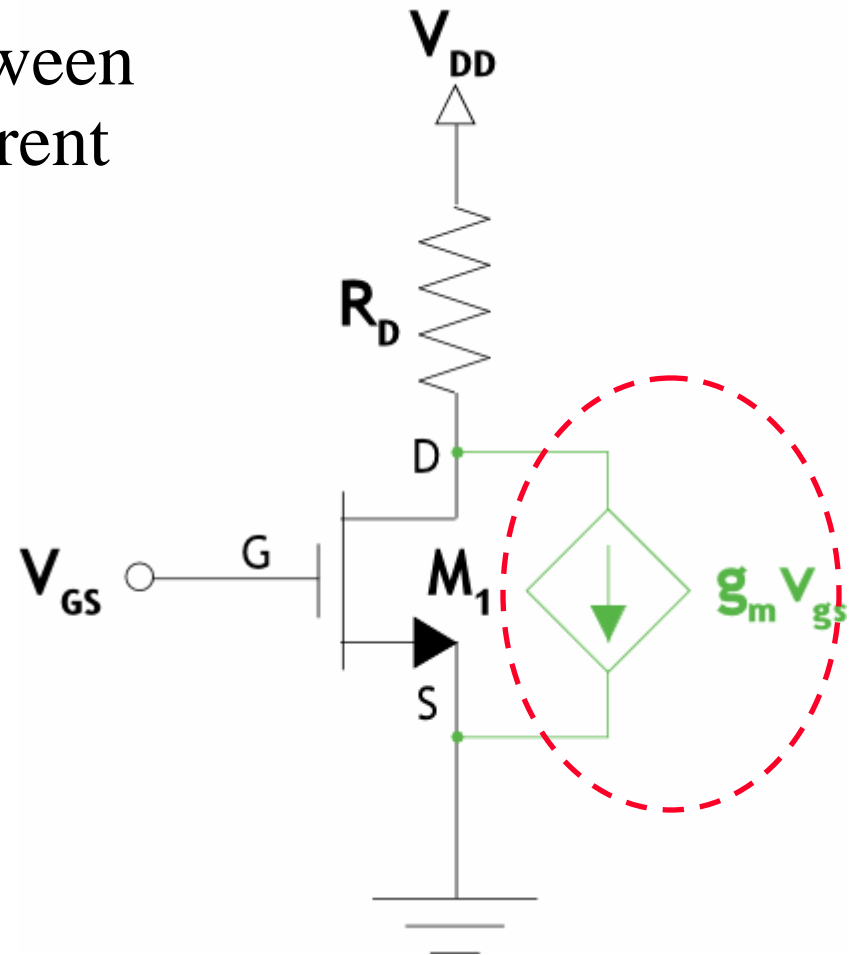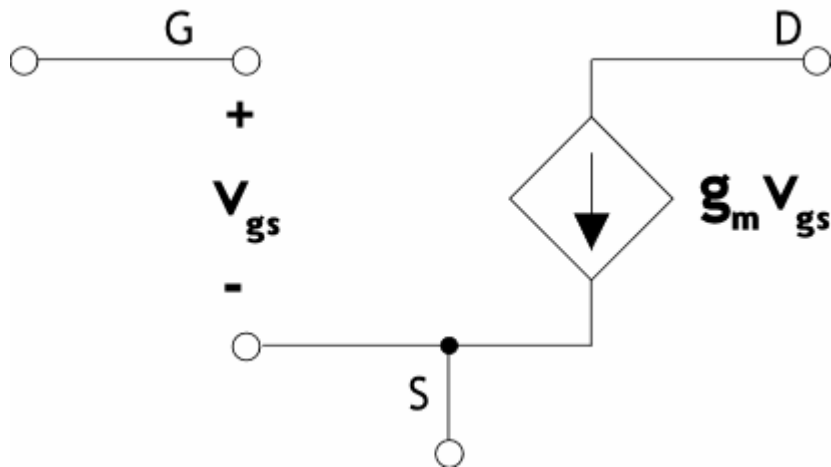- In response to signal input between gate and source, v_{gs} , signal current flows in drain, i_d




- Still to be determined:
- output resistance (r_o)
 - input resistance
 - body terminal



Small Signal Output Resistance

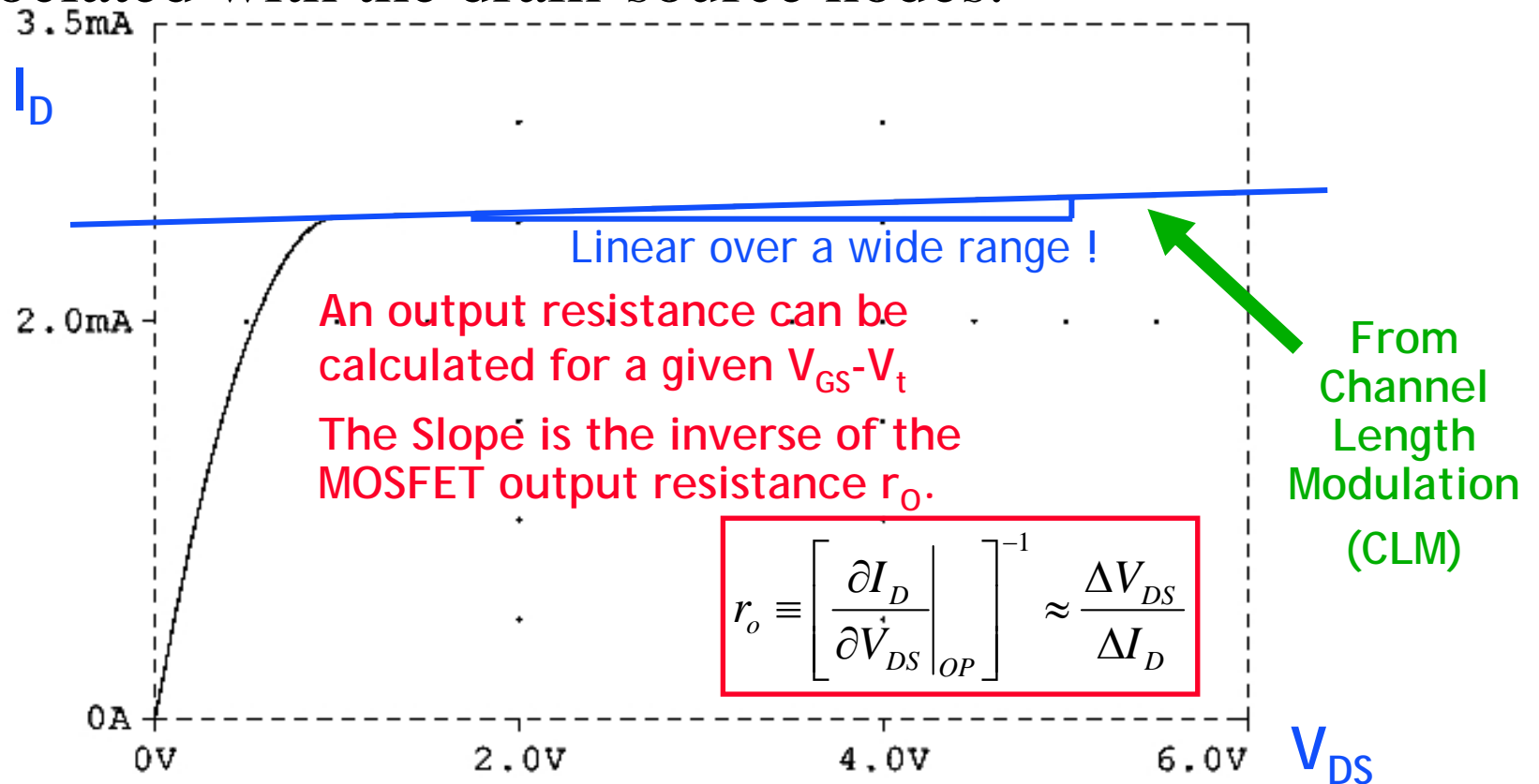- Since the characteristic curve for I_D - V_{DS} indicates a slope when in saturation, there is an output resistance associated with the drain-source nodes.





Output Resistance – r_o

- To derive an expression for r_o :
- Start with full I_D equation
- Take derivative and simplify
- Plug in the operating point

$$r_o \equiv \left[\frac{\partial i_D}{\partial v_{DS}} \Big|_{OP} \right]^{-1}$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda \cdot v_{DS})$$

$$\frac{\partial i_D}{\partial v_{DS}} = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 \cdot \lambda$$



$$\frac{\partial i_D}{\partial v_{DS}} \Big|_{OP} = \frac{\lambda \cdot I_D}{1 + \lambda \cdot V_{DS}} = \frac{I_D}{\frac{1}{\lambda} + V_{DS}} = \frac{I_D}{V_A + V_{DS}} \approx \lambda \cdot I_D$$

$$r_o \approx \frac{1}{\lambda \cdot I_D}$$



Small Signal Modeling

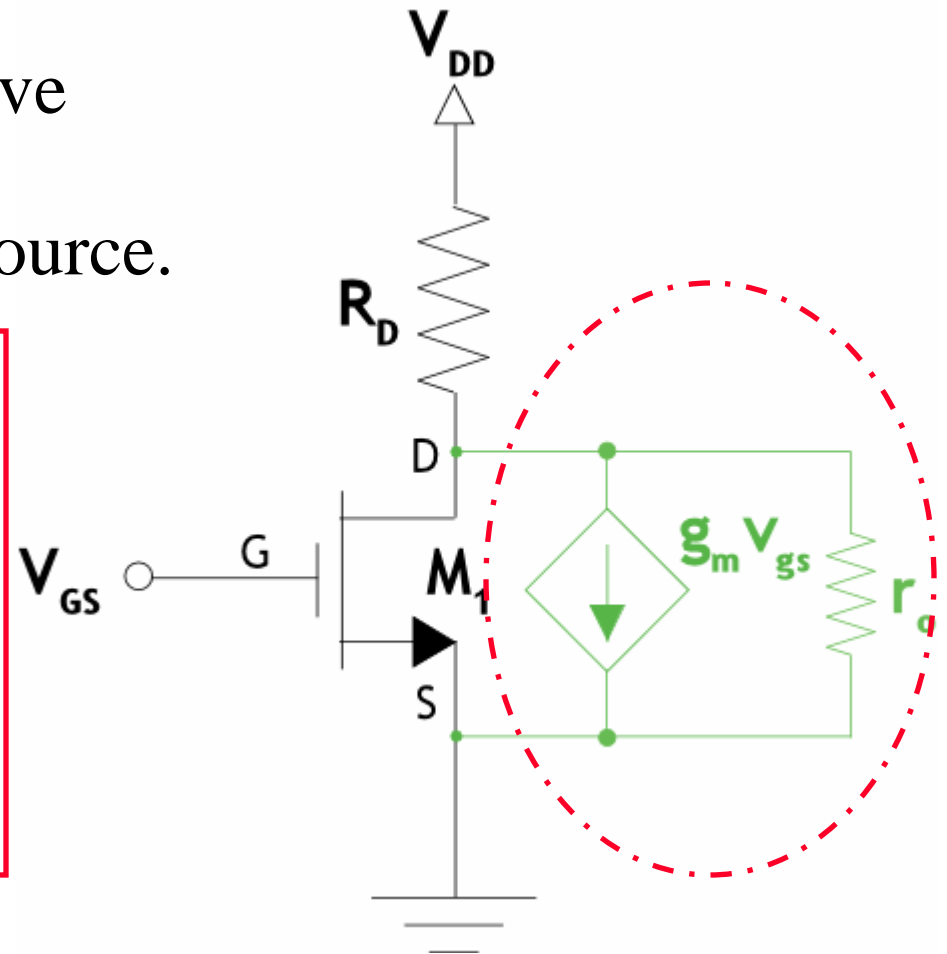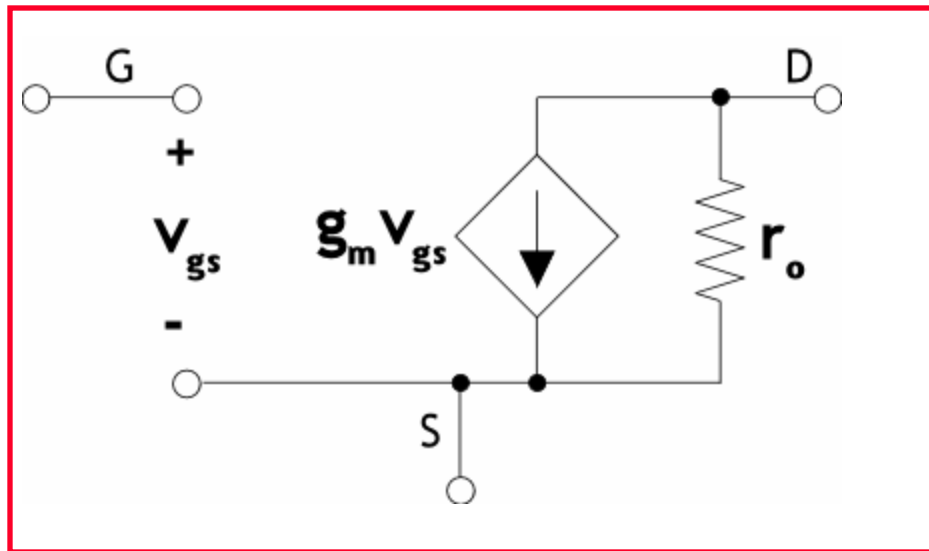- The slope of the I_D - V_{DS} curve indicates a finite resistance between the drain and the source.





The MOSFET T-Model


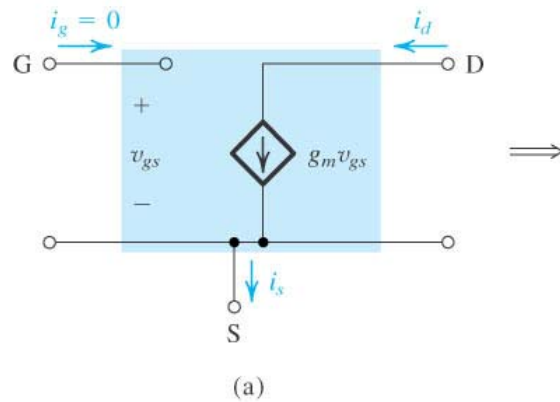


Figure 4.39 Development of the T equivalent-circuit model for the MOSFET. For simplicity, r_o has been omitted but can be added between D and S in the T model of **(d)**.

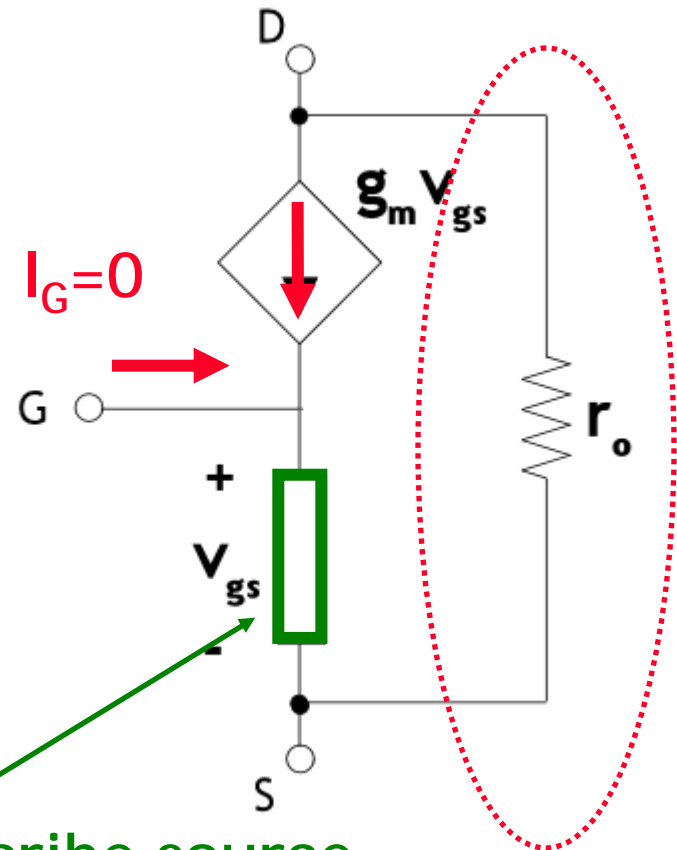

The MOSFET T-Model

- When input signal (voltage or current) is applied at source terminal, use the **T-model**.
- Non-zero signal current flows in source
- Input resistance looking into source is finite when we do not consider the frequency response
- Need to determine source resistance parameter




How describe source input resistance ?



Source Resistance for T-model

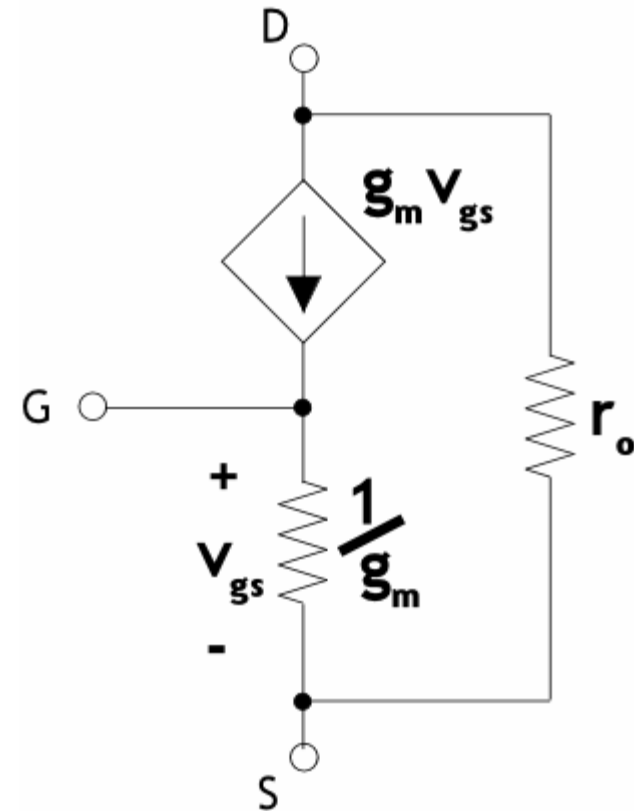
- Find the relationship between source current and gate-source voltage. We can identify a $V=IR$ relationship
- Define r_s as the input resistance looking into the source
- Can compute: $r_s = v_{gs}/i_s$
- Since $i_s = i_d$, and $i_d = g_m v_{gs}$, recognize that $r_s = 1/g_m = v_{gs}/i_s$



Source Absorption Theorem



The MOSFET T Small Signal Model

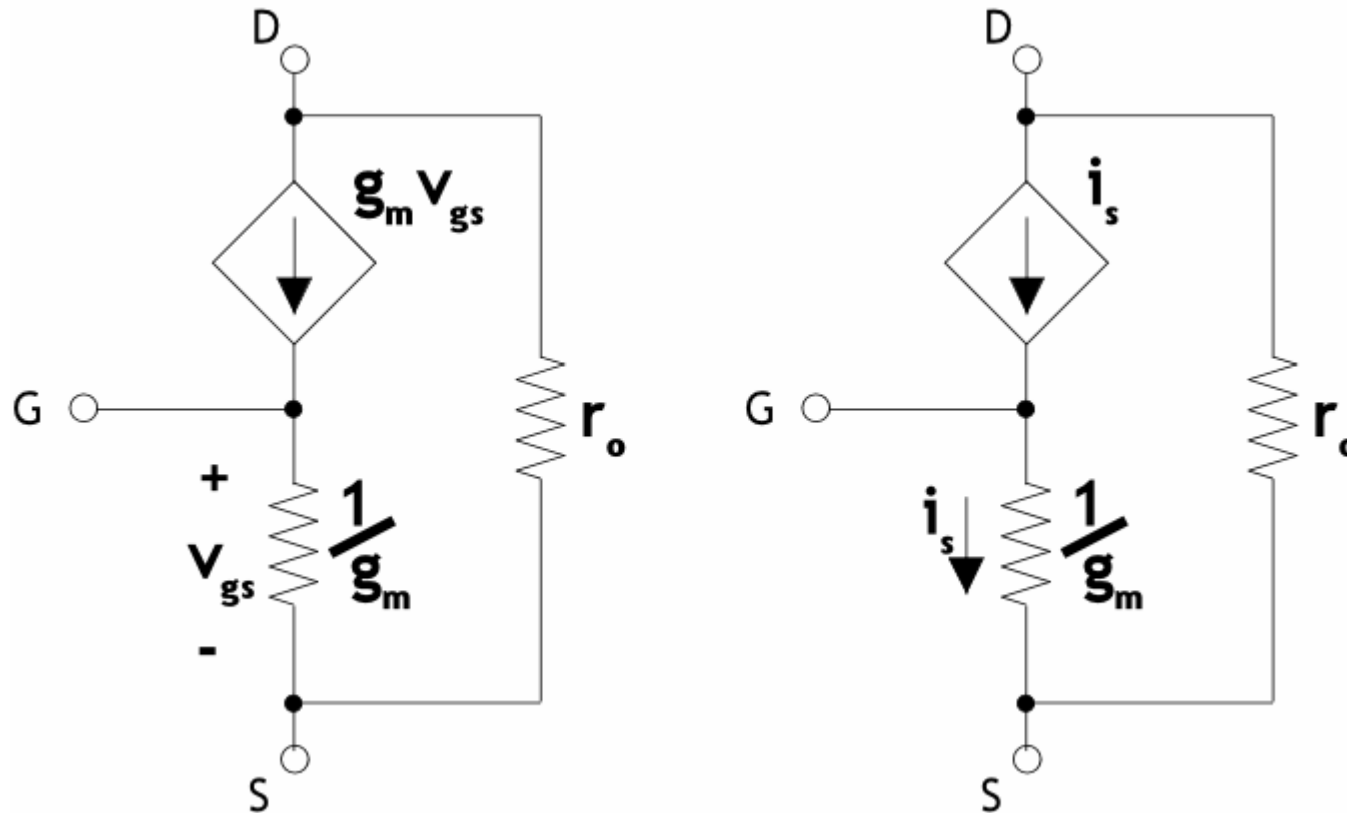



The Body Effect – Small Signal

- Recall that DC Body effect occurs because Body and Source not always maintained at same potential
- The same thing can apply to AC analysis
 - The body terminal always connected to the most negative DC power supply;
 - Body terminal will always be at signal (AC) ground.
 - The small signal body effect occurs when the source is not at signal ground.
 - Result: the body behaves like a second – albeit weaker – gate



Modeling the Small Signal Body Effect

- Consider effect of small changes in V_{BS} on I_D :
- V_{BS} dependence is in V_t :
- Start with full I_D expression
- Take derivative and simplify

$$\left. \frac{\partial i_D}{\partial v_{BS}} \right|_{OP}$$

$$V_t = V_{t0} + \gamma \left(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$$

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - v_t)^2 (1 + \lambda \cdot v_{DS})$$

$$\frac{\partial i_D}{\partial v_{BS}} = \frac{\partial i_D}{\partial v_t} \cdot \frac{\partial v_t}{\partial v_{BS}} = \left[2 \cdot \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - v_t)(1 + \lambda \cdot V_{DS})(-1) \right] \cdot \left[\frac{1}{2} \cdot \gamma (2\phi_f + v_{SB})^{-1/2} (-1) \right]$$

Insert the operating point


Body transconductance

$$= \left[\frac{\gamma}{2} \frac{1}{\sqrt{2\phi_f + V_{SB}}} \right] \cdot g_m = \chi \cdot g_m$$

$$\begin{aligned} g_{mb} &= \chi \cdot g_m \\ \chi &= \frac{\gamma}{2} \cdot \frac{1}{\sqrt{2\phi_f + V_{SB}}} \end{aligned}$$



Hybrid- π Small Signal Model

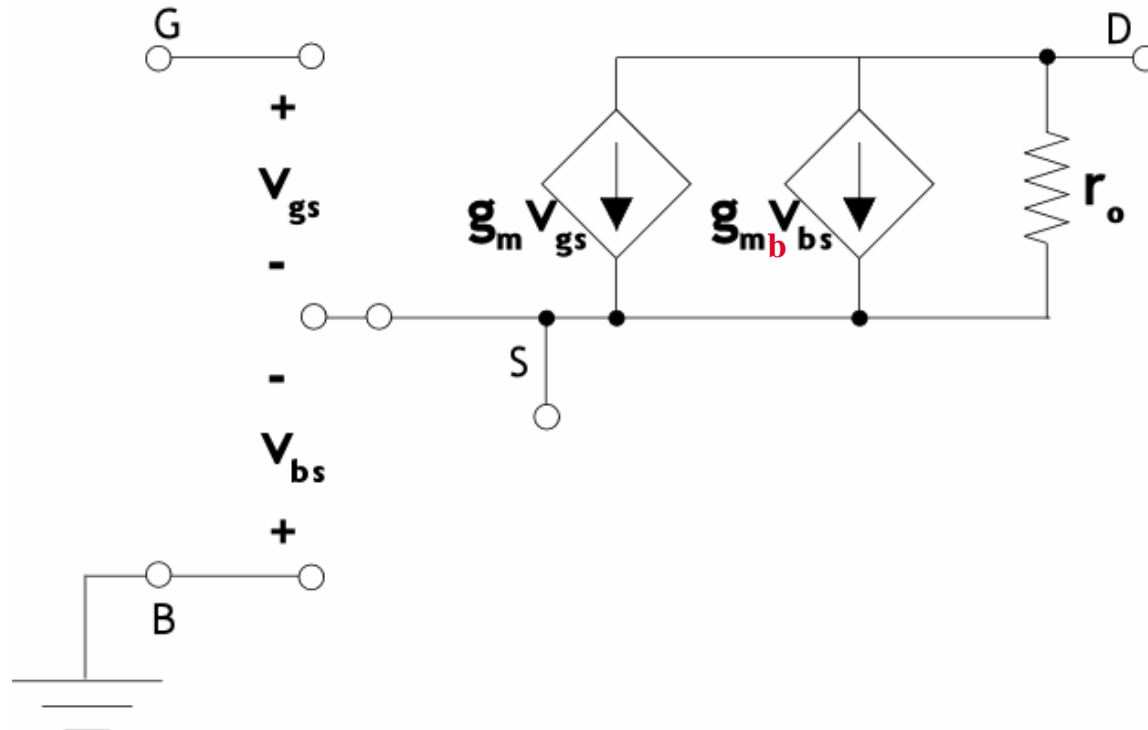


- AC Body effect: another VCCS (dependent on g_{mb}) in parallel with the one dependent on g_m
- T model generally not used when modeling Body effect, regardless of circuit topology



pMOS Small Signal Model

- Small signal model for PMOS is identical to that for NMOS
- Be careful of location of G, D, and S terminals

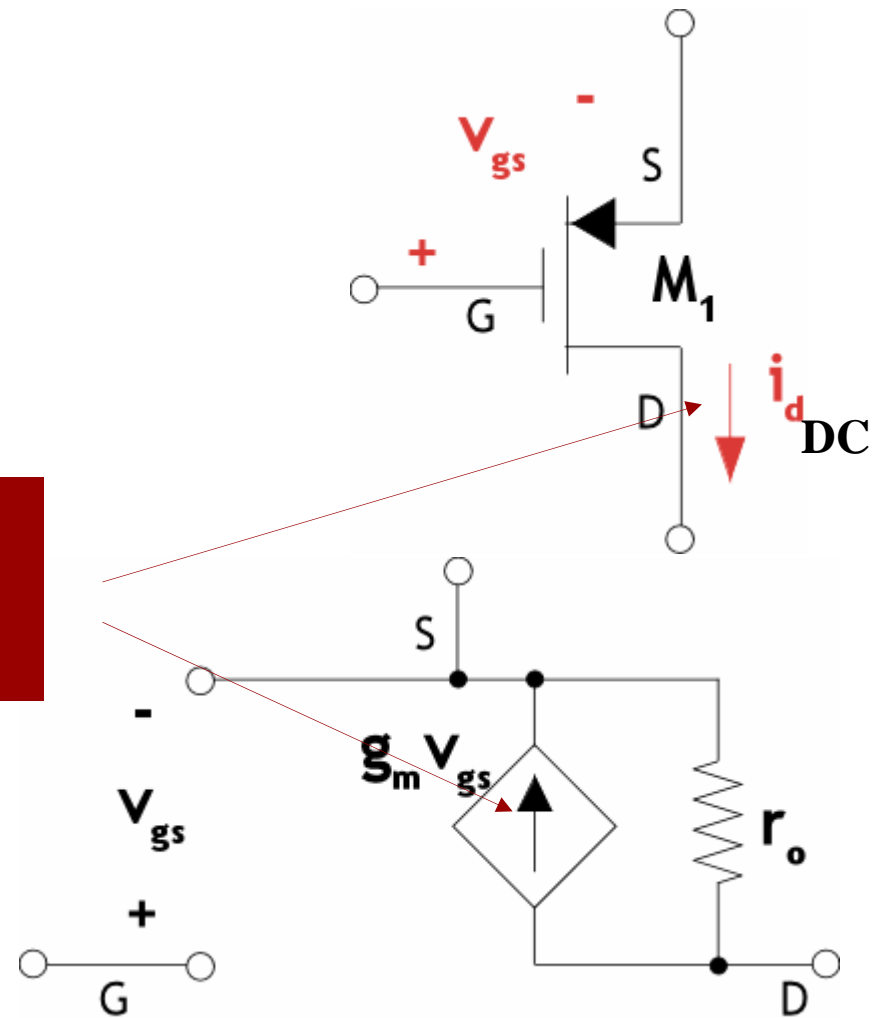– DC current flows one way, signal current flows the other way







Common Source MOSFET Amplifier

$k_n = 100\mu\text{A/V}$
 $W/L = 50$
 $\lambda = 0.01\text{V}^{-1}$
 $V_{t0} = 1\text{V}$

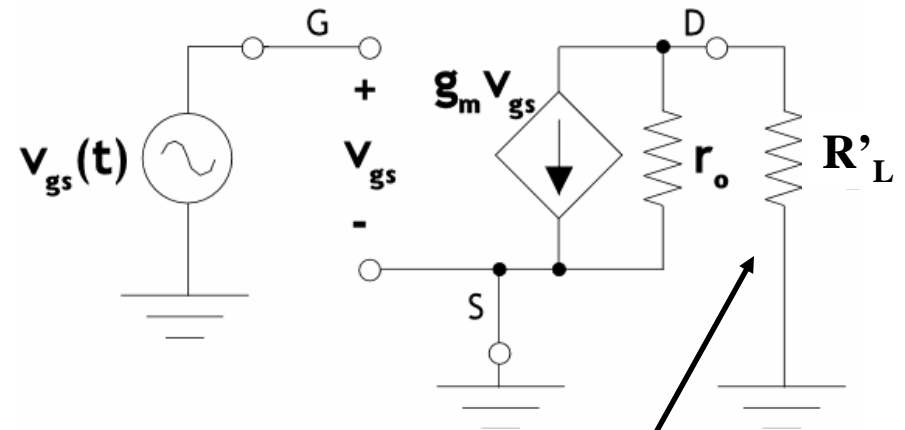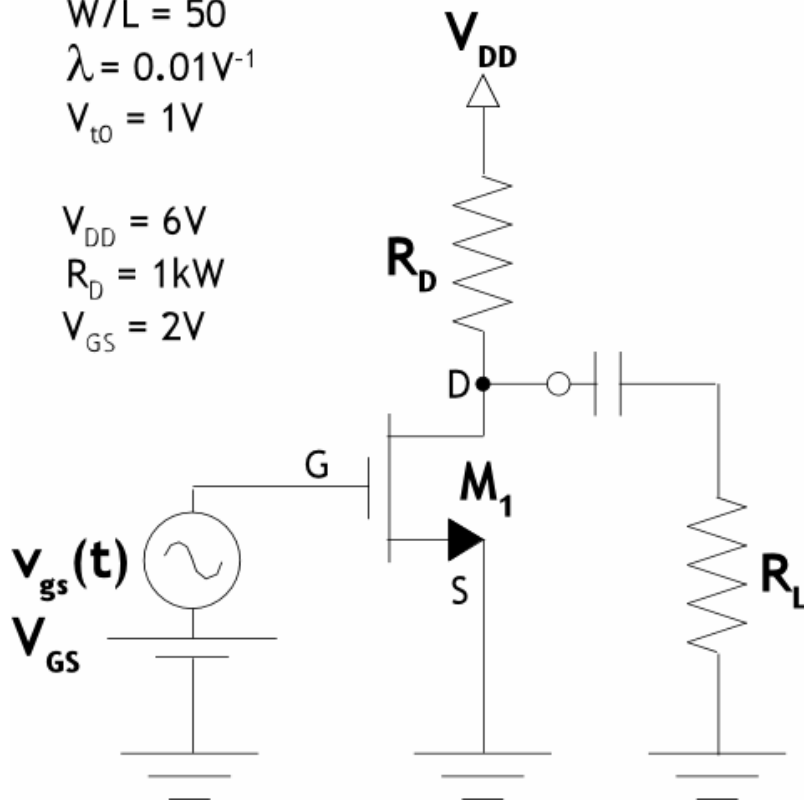$V_{DD} = 6\text{V}$
 $R_D = 1\text{k}\Omega$
 $V_{GS} = 2\text{V}$



$$R'_L = R_D \parallel R_L$$



Small Signal Operation

- Small signal analysis requires the use of “small” signals to be valid
- Start with expression for drain current:

$$i_D = \frac{1}{2} k'_n \frac{W}{L} (v_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

- Substitute $v_{GS} = \bar{V}_{GS} + v_{gs}$, $i_D = I_D + i_d$
- Expand quadratic term:

$$I_D + i_d = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} + v_{gs} - V_t)^2 (1 + \lambda V_{DS})$$

$$\begin{aligned} (V_{GS} + v_{gs} - V_t)^2 &= [(V_{GS} - V_t) + v_{gs}]^2 \\ &= (V_{GS} - V_t)^2 + 2v_{gs}(V_{GS} - V_t) + v_{gs}^2 \end{aligned}$$

$$v_{gs}^2 \ll 2v_{gs}(V_{GS} - V_t) \quad v_{gs} \ll 2(V_{GS} - V_t)$$