




Outline of Chapter 4

- 1- Intro to MOS Field Effect Transistor (MOSFET)
- 2- NMOS FET
- 3- PMOS FET
- 4- DC Analysis of MOSFET Circuits
- 5- MOSFET Amplifier
- 6- MOSFET Small Signal Model
- 7- MOSFET Integrated Circuits
- 8- CSA, CGA, CDA
- 9- CMOS Inverter & MOS Digital Logic



Common Drain Amplifier (CDA)

 - A nMOS current mirror is used as I_{REF} including the output resistance.
- Voltage signal source DC-coupled to gate terminal
- Drain terminal held at a DC voltage
- Since source terminal not at signal ground, Body effect exists



R_I is the resistance from previous stage




CDA

- Replace with a “real” current source including output resistance r_{o2}
- No problem including AC CLM

Two types of analysis:


Neglect AC Body-Effect

Use AC Body-Effect

 



CDA Without Body Effect

 


$$A_V = \frac{v_o}{v_I} = \frac{r_{o2} \parallel r_{o1}}{r_{o2} \parallel r_{o1} + \frac{1}{g_{m1}}}$$

$$R_{IN} \Rightarrow \infty$$

$$R_{OUT} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m1}}$$




CDA With Body Effect

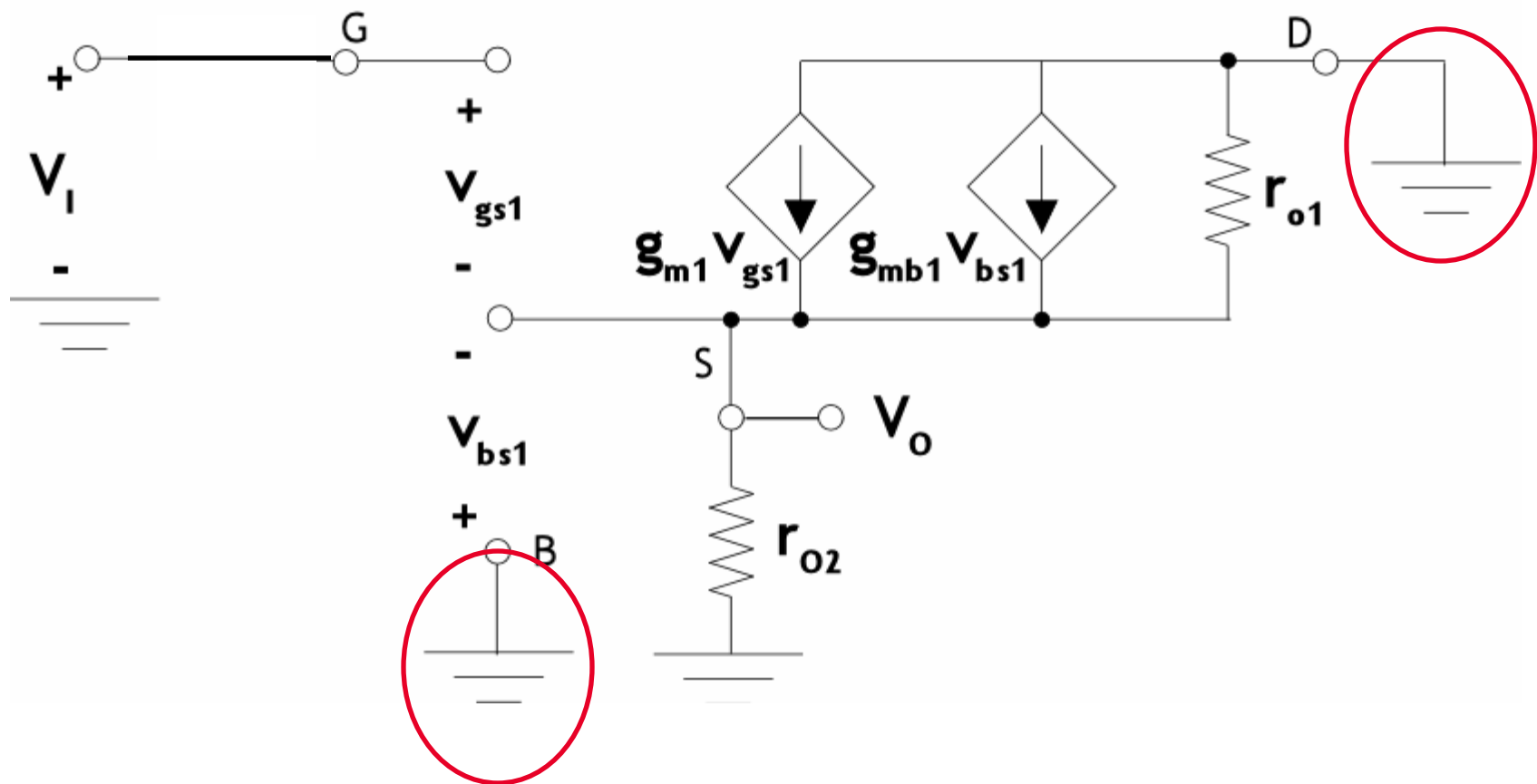



CDA With Body Effect

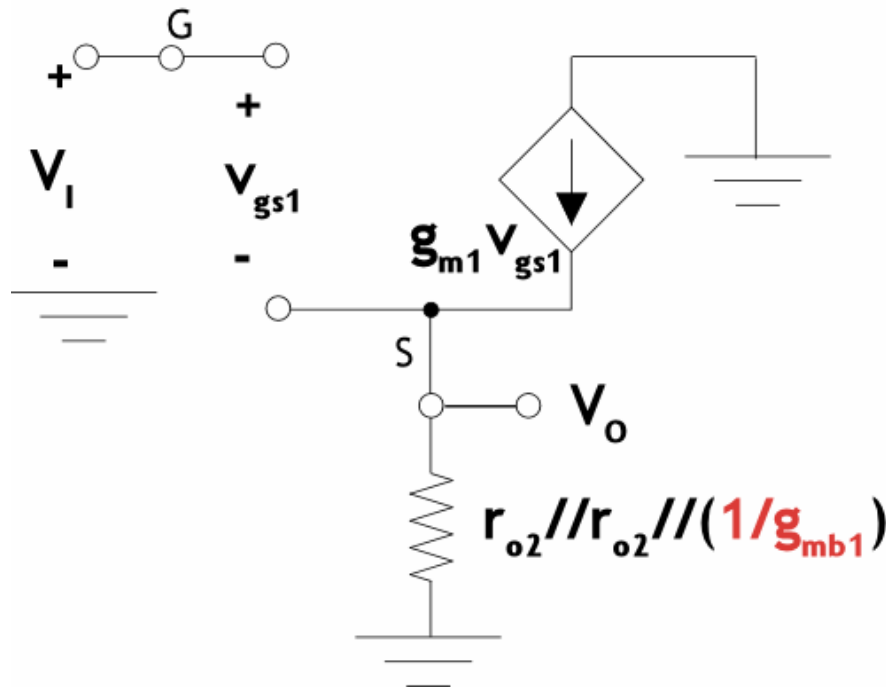

$$R_{IN} \Rightarrow \infty$$

$$v_{gs1} = v_I - v_o$$


$$\begin{aligned} v_o &= \left(g_{m1} v_{gs1} \right) \left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} \right) \\ &= g_{m1} (v_I - v_o) \left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} \right) \end{aligned}$$

$$\frac{v_o}{v_I} = \frac{\left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} \right)}{\left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} \right) + \frac{1}{g_{m1}}}$$



CDA With Body Effect - R_{OUT}

Short input voltage source

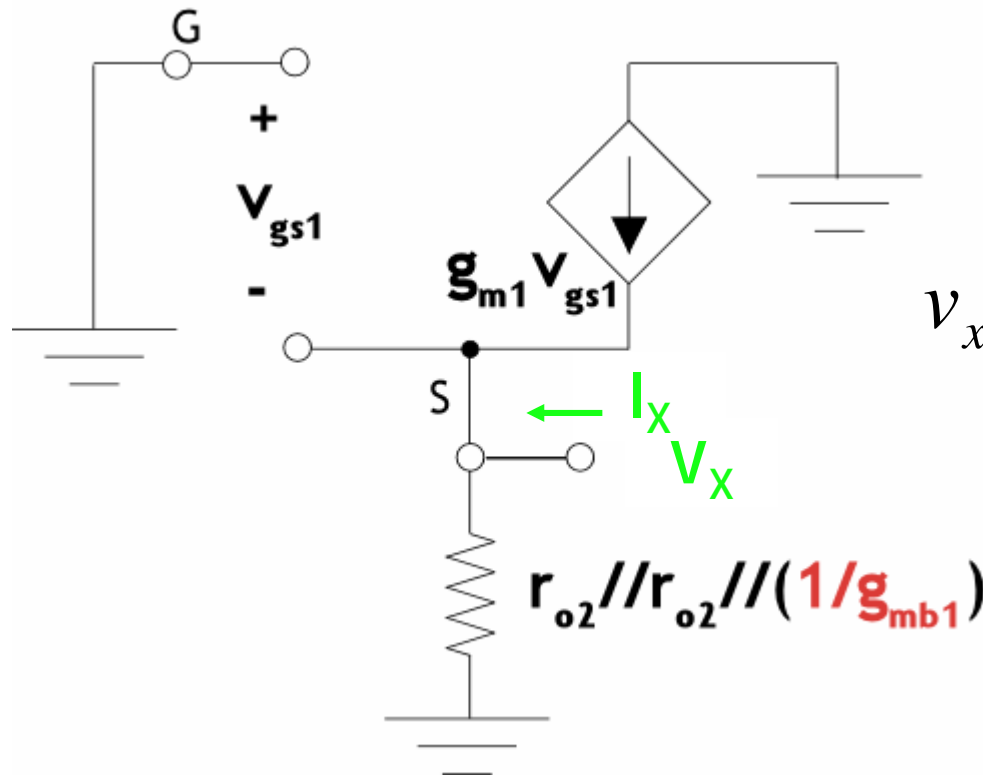

$$v_{gs1} = -v_x$$

$$v_x = (g_{m1} v_{gs1} + i_x) \left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} \right)$$

$$R_{OUT} = \frac{v_x}{i_x} = \frac{r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}}}{1 + g_{m1} \left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{mb1}} \right)}$$

By source-absorption:

$$R_{OUT} = r_{o1} \parallel r_{o2} \parallel (1/g_{m1}) \parallel (1/g_{mb1})$$




Outline of Chapter 4

- 1- Intro to MOS Field Effect Transistor (MOSFET)
- 2- NMOS FET
- 3- PMOS FET
- 4- DC Analysis of MOSFET Circuits
- 5- MOSFET Amplifier
- 6- MOSFET Small Signal Model
- 7- MOSFET Integrated Circuits
- 8- CSA, CGA, CDA
- 9- CMOS Inverter & MOS Digital Logic



CMOS Inverter

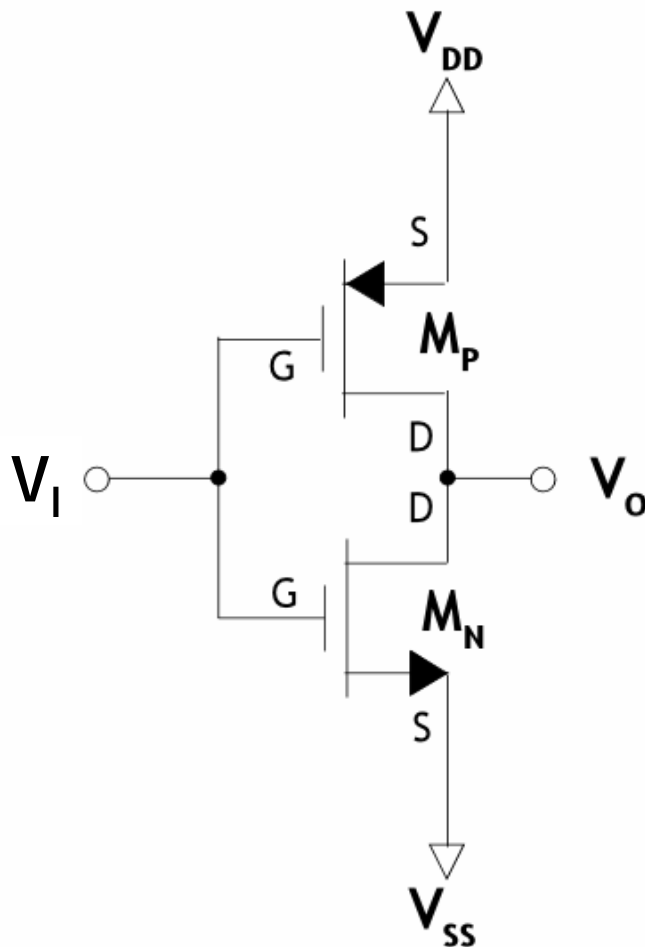


- MOSFETs can act as almost ideal current switches with symmetric VTCs.
- Matching of M_P and M_N : $|V_{tP}| = V_{tN} = V_t$
- Since typically k'_p is 2-3 times smaller than k'_n , the widths of the transistors are used to compensate:

$$W_P = 3W_N \implies k'_p \frac{W_P}{L_P} = k'_n \frac{W_N}{L_N}$$

- This is definition of matched devices; equal current driving and sinking capabilities when charging & discharging capacitive loads



CMOS Inverter – Operation

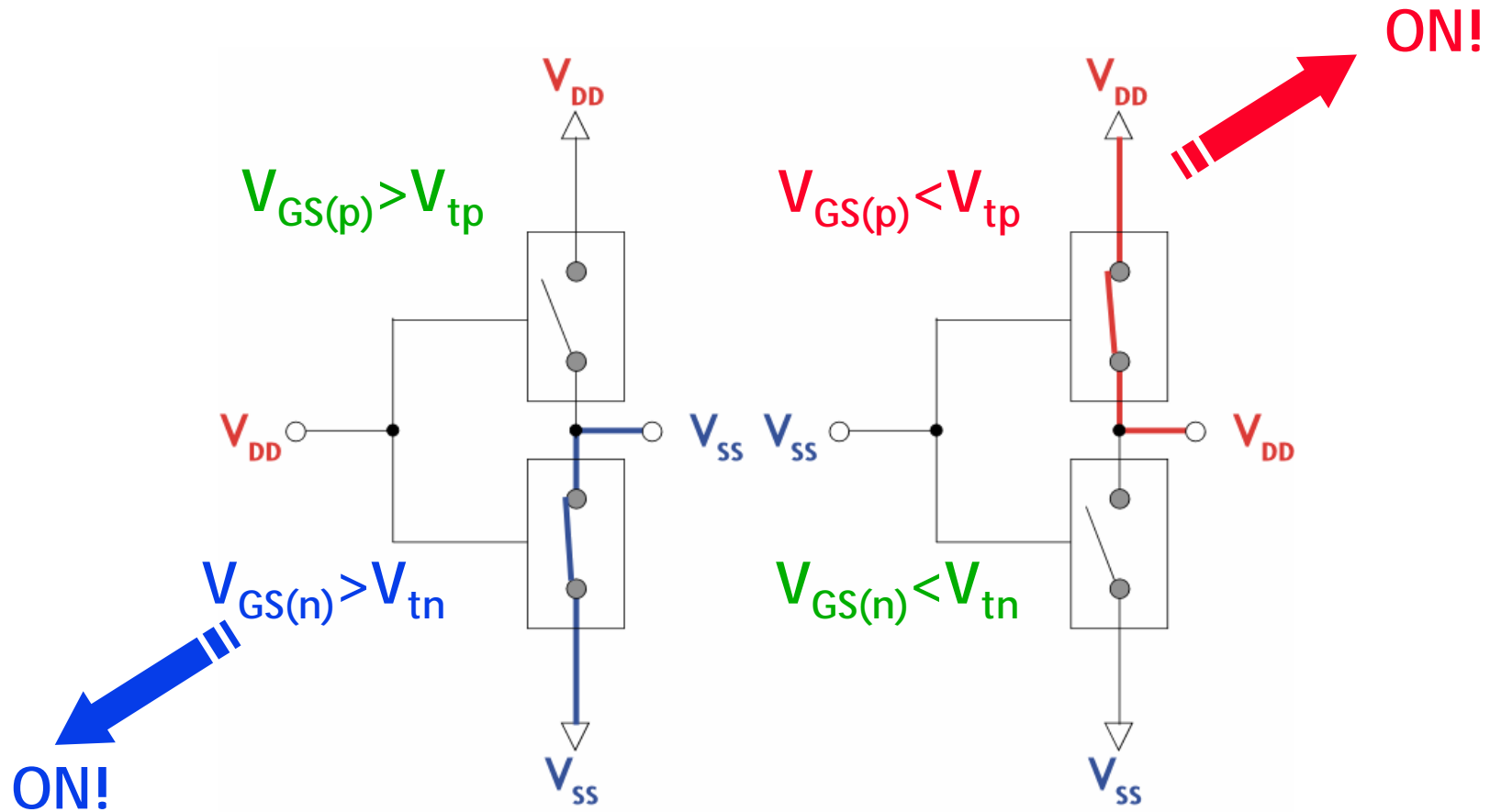


nMOS transistor pulls output voltage to the most negative rail.

pMOS transistor pulls output voltage to the most positive rail.




Inverter VTC

 

- Region I: $V_{IN} < V_t$
 - M_N cutoff, M_P in triode
 - Low-resistance path from V_{DD} to V_{OUT} pulls output high
 - No current flow
- Region II: $V_{IN} > V_t$
 - M_N enters saturation
 - M_P still in triode
 - Current flows, V_{OUT} starts to fall
- Region III:
 - High-gain region
 - M_N & M_P saturated
 - VTC slope = gain




Inverter VTC

 

- Region IV:
 - M_N enters triode
 - M_P still in saturation
- Region V: $V_{IN} > V_{DD} - V_t$
 - M_P cutoff, M_N in triode
 - Low-resistance path from V_{OUT} to ground pulls output low
 - No current flow



VTC Characteristics

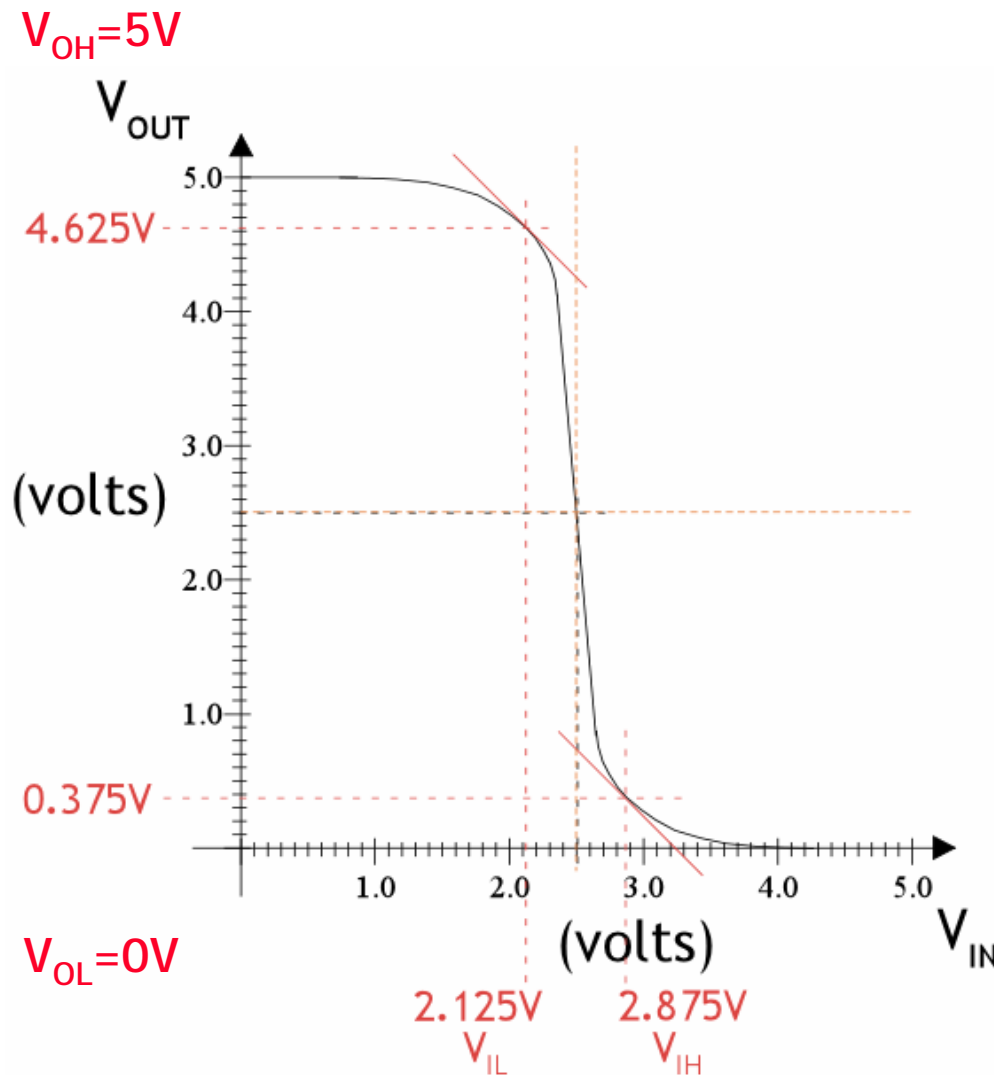

- A matched inverter has symmetric voltage transfer characteristic.
- V_{OL} and V_{OH} are defined as 0V and 5V respectively.
- V_{IH} and V_{IL} defined as location where VTC slope = -1
 - V_{IL} is in region II
 - V_{IH} is in region IV



Finding V_{IH} – Matched Devices

- In region IV, M_P saturated, M_N in triode:

$$\cancel{k'_n} \frac{W_N}{L_N} \left[(V_{IN} - V_t)V_{OUT} - \frac{1}{2}V_{OUT}^2 \right] = \frac{1}{2} \cancel{k'_p} \frac{W_P}{L_P} (V_{IN} - V_{DD} + V_t)^2$$

$$(V_{IN} - V_t)V_{OUT} - \frac{1}{2}V_{OUT}^2 = \frac{1}{2}(V_{IN} - V_{DD} + V_t)^2 \quad \textcircled{1}$$

- $V_{IN} = V_{IH}$ when $\frac{\partial V_{OUT}}{\partial V_{IN}} = -1 \quad \therefore$ Take derivative wrt V_{IN}

$$V_{OUT} + (V_{IN} - V_t) \frac{\partial V_{OUT}}{\partial V_{IN}} - V_{OUT} \frac{\partial V_{OUT}}{\partial V_{IN}} = (V_{IN} - V_{DD} + V_t)$$

- Substitute $V_{IN} = V_{IH}$ & simplify to get: $V_{OUT} = V_{IH} - \frac{V_{DD}}{2}$



Finding V_{IH} – Matched Devices

- Take result for V_{OUT} when $V_{IN} = V_{IH}$

$$V_{OUT} = V_{IH} - \frac{V_{DD}}{2}$$

- Substitute into ①

$$(V_{IH} - V_t) \left(V_{IH} - \frac{V_{DD}}{2} \right) - \frac{1}{2} \left(V_{IH} - \frac{V_{DD}}{2} \right)^2 = \frac{1}{2} (V_{IH} - V_{DD} + V_t)^2$$

- Solving for V_{IH} , get: $V_{IH} = \frac{1}{8} (5V_{DD} - 2V_t)$



Finding V_{IL} – Matched Devices

- Can use similar procedure to find V_{IL}
 - Write equations for region II operation: M_P in triode, M_N in saturation
 - Solve for V_{OUT} when $V_{IN} = V_{IL}$ and substitute back into equations and solve for V_{IL}

- Result:
$$V_{IL} = \frac{1}{8}(3V_{DD} + 2V_t)$$

- Alternatively, can find V_{IL} using symmetry of VTC because V_{IL} and V_{IH} are symmetric about $V_{DD}/2$

$$V_{IH} - \frac{V_{DD}}{2} = \frac{V_{DD}}{2} - V_{IL}$$



Noise Margins

NM_H , High Noise Margin Definition:

$$NM_H = V_{OH} - V_{IH} = V_{DD} - V_{IH} \quad V_{IH} = \frac{1}{8}(5V_{DD} - 2V_t)$$

$$NM_H = V_{OH} - V_{IH} = \frac{1}{8}(3V_{DD} + 2V_t)$$

NM_L : Low Noise Margin Definition:

$$NM_L = V_{IL} - V_{OL} = V_{IL} - 0 \quad V_{IL} = \frac{1}{8}(3V_{DD} + 2V_t)$$

$$NM_L = V_{IL} - V_{OL} = \frac{1}{8}(3V_{DD} + 2V_t)$$

Conclusion: NMs equal for matched devices (Problem 4.107)



Mismatched Inverter Characteristics


- For mismatched devices:

$$\left| V_{tp} \right| \neq V_{tn} \quad k'_p \frac{W_P}{L_P} \neq k'_n \frac{W_N}{L_N}$$

- VTC not symmetric any longer
- V_{IL} and V_{IH} can be found using same approach as before, with more algebra
- Resulting VTC noise margins will not be equal, but V_{OH} and V_{OL} will be unchanged




Structure of CMOS Logic-Gates

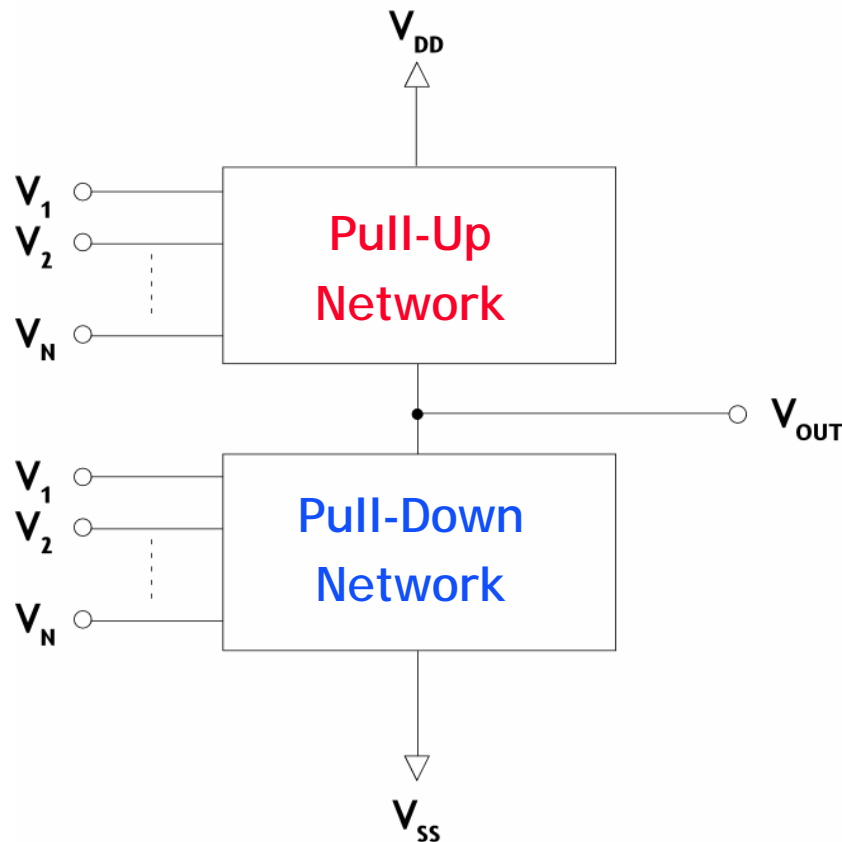

- **P-U-N: pull-up network**
(PMOS transistors)
- **P-D-N: pull-down network**
(NMOS transistors)
- P-U-N & P-D-N almost invariably made *complementary* networks
 - i.e. series-connected transistors in one network are parallel-connected in the other & vice versa
 - Facilitates formal design and logic synthesis techniques




Basic Pull-Up Structures

 

Parallel Structure

V_{OUT} is high when *either* V_A or V_B is low
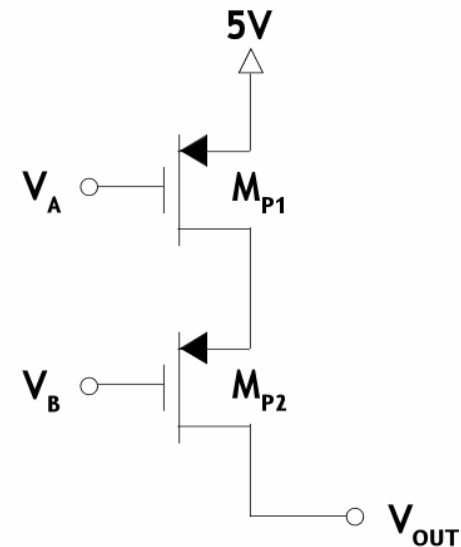
$$V_{OUT} = \overline{V_A} + \overline{V_B}$$




Serial Structure

V_{OUT} is high when *both* V_A and V_B are low

$$V_{OUT} = \overline{V_A} \cdot \overline{V_B}$$




Basic Pull-Down Structures

 

Parallel Structure

V_{OUT} is low when *either* V_A or V_B is high

$$\overline{V_{OUT}} = V_A + V_B$$

 

Serial Structure

V_{OUT} is low when *both* V_A and V_B are high

$$\overline{V_{OUT}} = V_A \cdot V_B$$





2-Input CMOS NAND Gate

Truth table:

V_A	V_B	V_{OUT}
0	0	1
1	0	1
0	1	1
1	1	0

$$V_{OUT} = \overline{V_A \cdot V_B}$$

Logic Symbol:

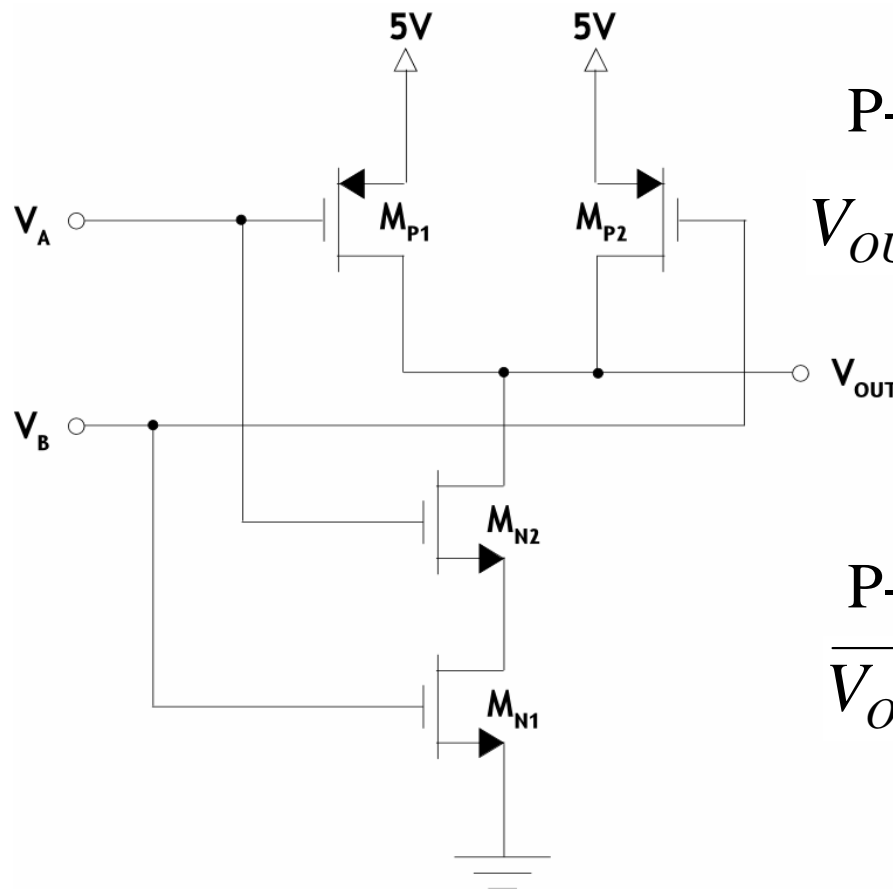 

P-U-N:

$$V_{OUT} = \overline{V_A} + \overline{V_B}$$

P-D-N:

$$\overline{V_{OUT}} = V_A \cdot V_B$$





2-Input CMOS NOR Gate

Truth table:

V_A	V_B	V_{OUT}
0	0	1
1	0	0
0	1	0
1	1	0

$$V_{OUT} = \overline{V_A + V_B}$$

Logic Symbol:

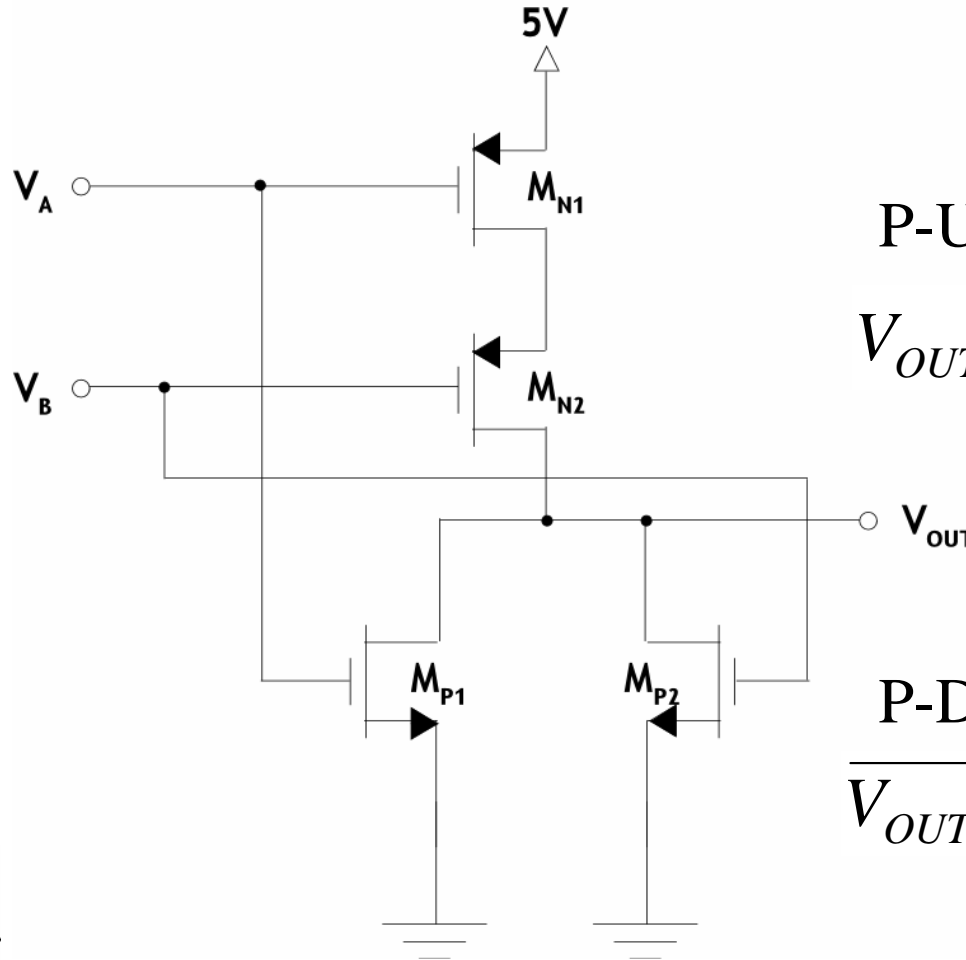 

P-U-N:

$$V_{OUT} = \overline{V_A} \cdot \overline{V_B}$$

P-D-N:

$$\overline{V_{OUT}} = V_A + V_B$$



Outline of Chapter 4, Sections 4.8-4.9

- 1- High-Frequency Model of MOSFET
- 2- Frequency Response of CSA
- Note: Frequency response of CGA and CDA are covered in EC2



High-Frequency Model

- The small signal model discussed so far didn't include internal capacitances and resulted in constant gain without accounting for frequency changes.
- Internal capacitances:
 - The gate capacitive (C_{ox}) effect is modeled by three capacitors C_{gs} , C_{gd} and C_{gb}
 - The source-body and drain-body depletion layer capacitances: Reverse biased pn junctions



Gate Capacitive Effect

- In Triode region the channel has a uniform depth:

$$C_{gs} = C_{gd} = \frac{1}{2}WLC_{ox}$$

- In saturation region: Channel is pinched off:

$$C_{gs} = \frac{2}{3}WLC_{ox} \qquad C_{gd} = 0$$

- In the cutoff region: $C_{gs} = C_{gd} = 0$
- Often there is overlap area underneath the gate in the S and D diffusion (n^+ or P^+) regions.
 - This adds to C_{gs} and C_{gd}



Junction Capacitances

- The two pn junction in MOSFET are reverse biased, so the depletion regions creates junction capacitances
- Junction capacitance in a reverse-biased diode or pn junction is defined by:

$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_R}{V_0}\right)^m} \quad \frac{1}{3} \leq m \leq \frac{1}{2} \quad C_j = \frac{C_{j0}}{\sqrt{1 + \frac{V_R}{V_0}}}$$

- Where V_0 is the junction built-in voltage, C_{j0} is the value of C_j when zero voltage is applied and m is the grading coefficient



Junction Capacitances

- The two junction capacitances in MOSFET are:

$$C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{V_0}}}$$


$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_0}}}$$

- Assuming $m=1/2$
- V_0 is the junction built-in voltage (0.6 to 0.8 V)
- C_{sb0} is the value of C_{sb} at $V_{SB}=0$
- C_{db0} is the value of C_{db} at $V_{DB}=0$
- Formulas are for small-signal operation




High-Frequency MOSFET Model

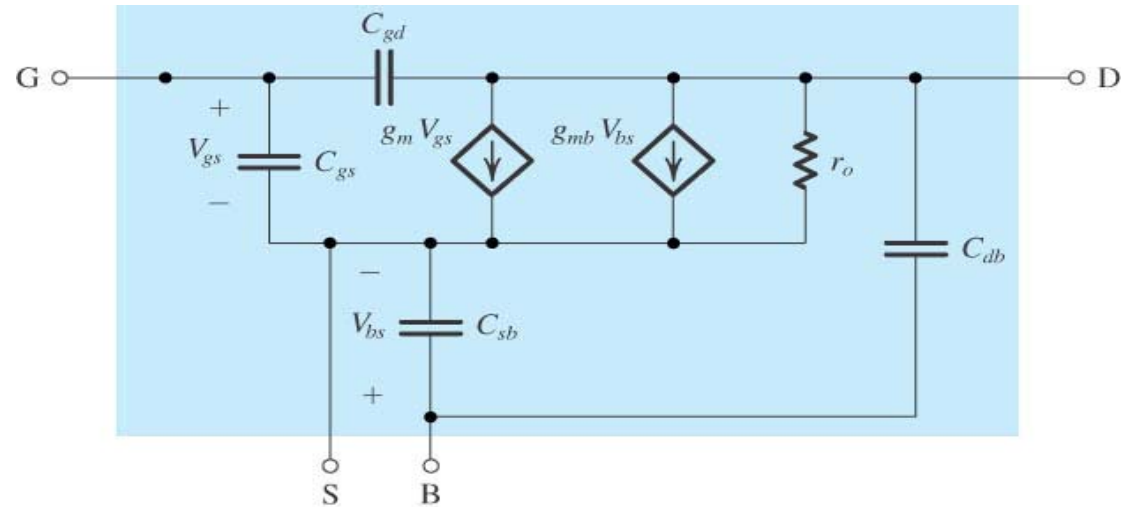- Complete Model used in SPICE (Fig. 4.47):



(a)

- When S is connected to B:

 


(b)



High-Frequency MOSFET Model

 - Capacitance C_{db} is usually neglected and for hand calculations and circuit solutions the following model is used




(c)

- Note: Hybrid- π model is used



MOSFET Unity-Gain Frequency

 - Unity-gain frequency, f_T , is a figure of merit for high-frequency operation.
- It is defined as the frequency at which the short circuit current gain in the Common Source amplifier is 1.



$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

Goes up to few GHz



Frequency Response of CSA



- Gain expressions derived previously were assumed to be independent of frequency.
- In reality gain is constant only over the midband frequencies
- The midband gains are the gain relations we found earlier
- Low frequency falloff is due to coupling and bypass capacitors
- High frequency gain falloff is due to internal capacitances.



Frequency Response of CSA

- Midband gain:
 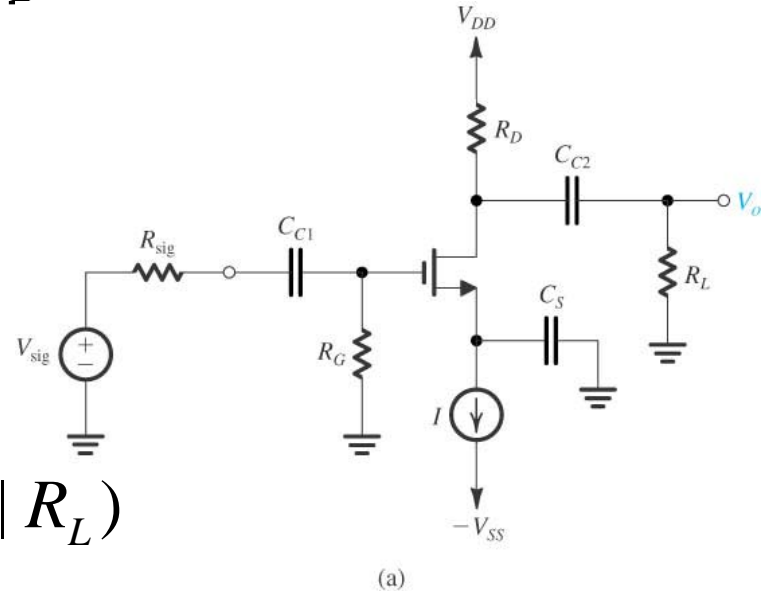
$$A_M = \frac{V_o}{V_{sig}} = - \frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L)$$





High-Frequency Response (CSA)

- f_H and f_L are frequencies at which gain is 3 dB lower than the midband value
- 3dB bandwidth is:

$$BW \equiv f_H - f_L$$



- If $f_L \ll f_H$ then
- Another figure of merit for an amplifier is gain-bandwidth product

$$GB \equiv |A_M| BW$$



High-Frequency Response (CSA)

- CSA
- Using Thevenin Theorem

  




High-Frequency Response (CSA)

- Lowpass STC circuit

Miller Effect

 

- Corner frequency

$$\omega_H = \omega_0 = \frac{1}{C_{in} R'_{sig}} = \frac{1}{(C_{gs} + C_{eq}) R'_{sig}}$$

- High-frequency gain of CSA

$$\frac{V_o}{V_{sig}} = \frac{A_M}{1 + \frac{s}{\omega_H}} = -\frac{R_G}{R_G + R_{sig}} (g_m R'_L) \frac{1}{1 + \frac{s}{\omega_H}}$$



Low-Frequency Response (CSA)


- Voltage divider at the G

$$V_g = V_{sig} \frac{R_G}{R_G + \frac{1}{sC_{C1}} + R_{sig}}$$

$$V_g = V_{sig} \frac{R_G}{R_G + R_{sig} \left(s + \frac{1}{C_{C1}(R_G + R_{sig})} \right)}$$

High-pass STC

$$\omega_0 = \omega_{p1}$$

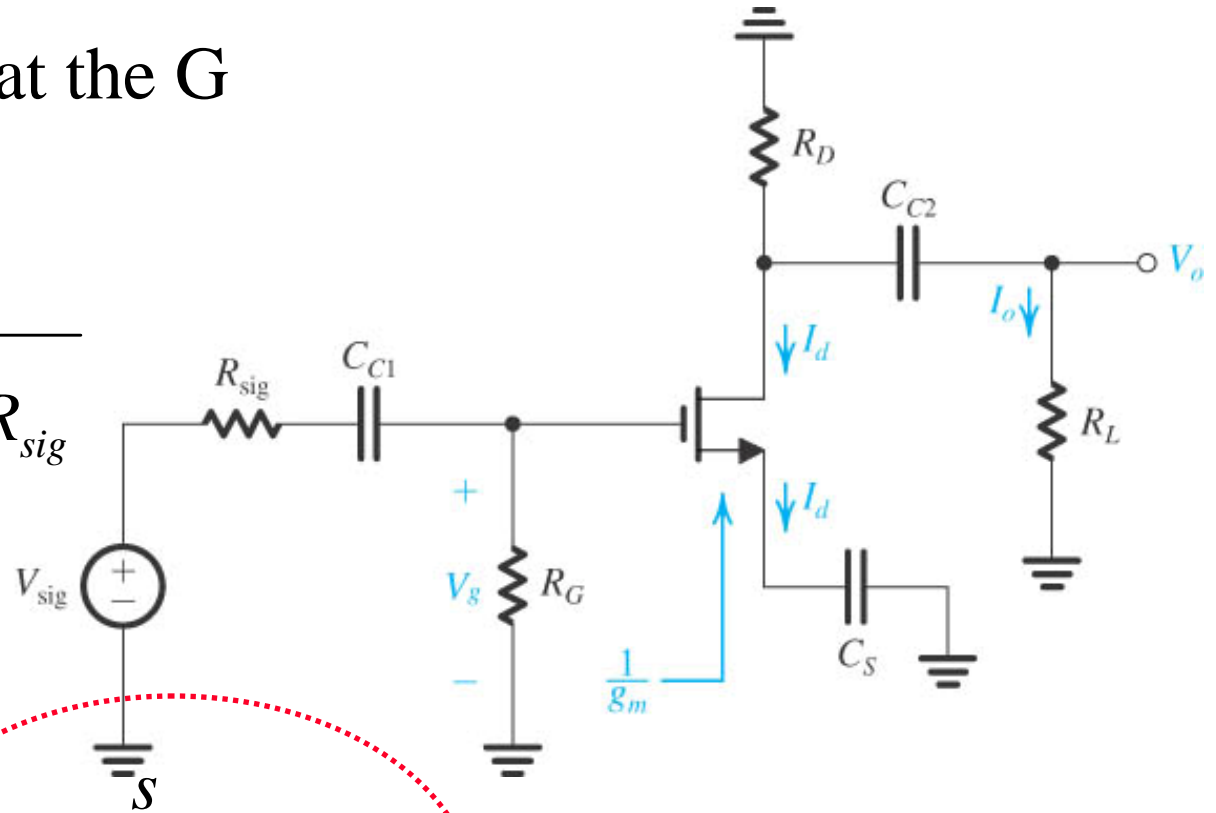



Low-Frequency Response (CSA)

- Two other high-pass factors are due to:

- Source bypass capacitance

$$\omega_{p2} = \frac{g_m}{C_S}$$

- Load coupling capacitance

$$\omega_{p3} = \frac{1}{C_{C2}(R_D + R_L)}$$

- Low-frequency transfer function or low-frequency gain of CSA

$$\frac{V_o}{V_{sig}} = -\frac{R_G}{R_G + R_{sig}} (g_m R_D \parallel R_L) \frac{s}{s + \omega_{P1}} \frac{s}{s + \omega_{P2}} \frac{s}{s + \omega_{P3}}$$



Low-Frequency Response (CSA)

- To find the time constant for poles f_{p1} , f_{p2} and f_{p3}
 - Set source to zero
 - Consider each C separately (others are short circuit)
 - Find the total resistance seen between the two terminals of C

