



## Outline of Chapter 5

- 1- Introduction to The Bipolar Junction Transistor
- 2- Active Mode Operation of BJT
- 3- DC Analysis of Active Mode BJT Circuits
- 4- BJT as an Amplifier
- 5- BJT Small Signal Models
- 6- CEA, CEA with  $R_E$ , CBA, & CCA
- 7- Integrated Circuit Amplifiers




# DC Analysis – Requires Assumptions

Find voltages & currents


Process:

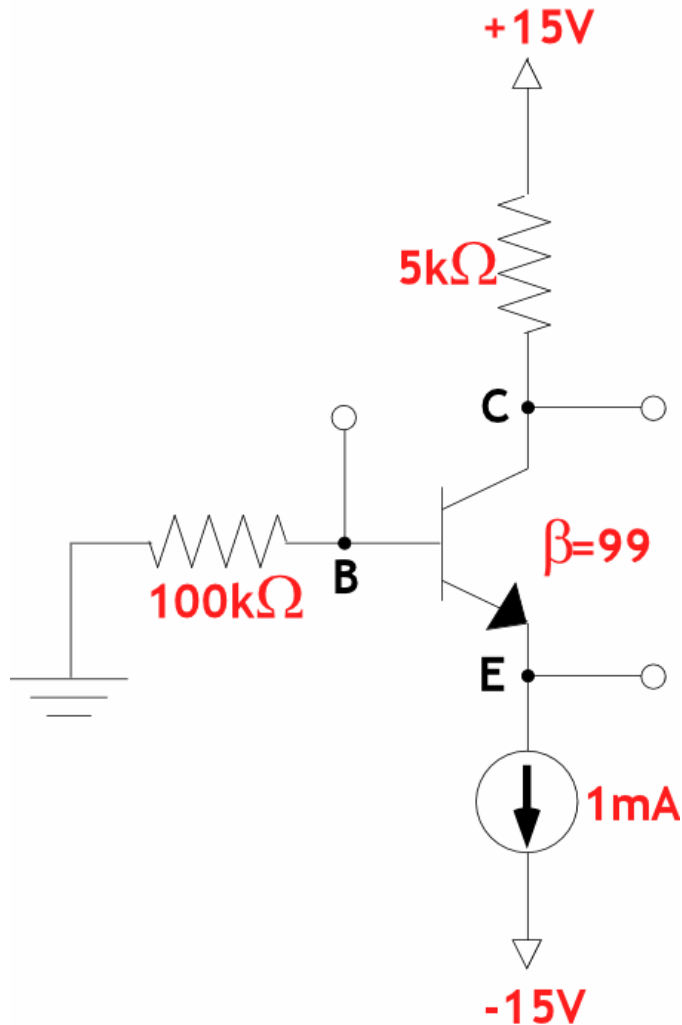- Assume *active* mode operation;  $V_{BE} = 0.7V$
- Based on assumption, calculate branch voltages and currents
- Verify *active* mode by checking  $V_{CB} > 0V$





## Perform Analysis

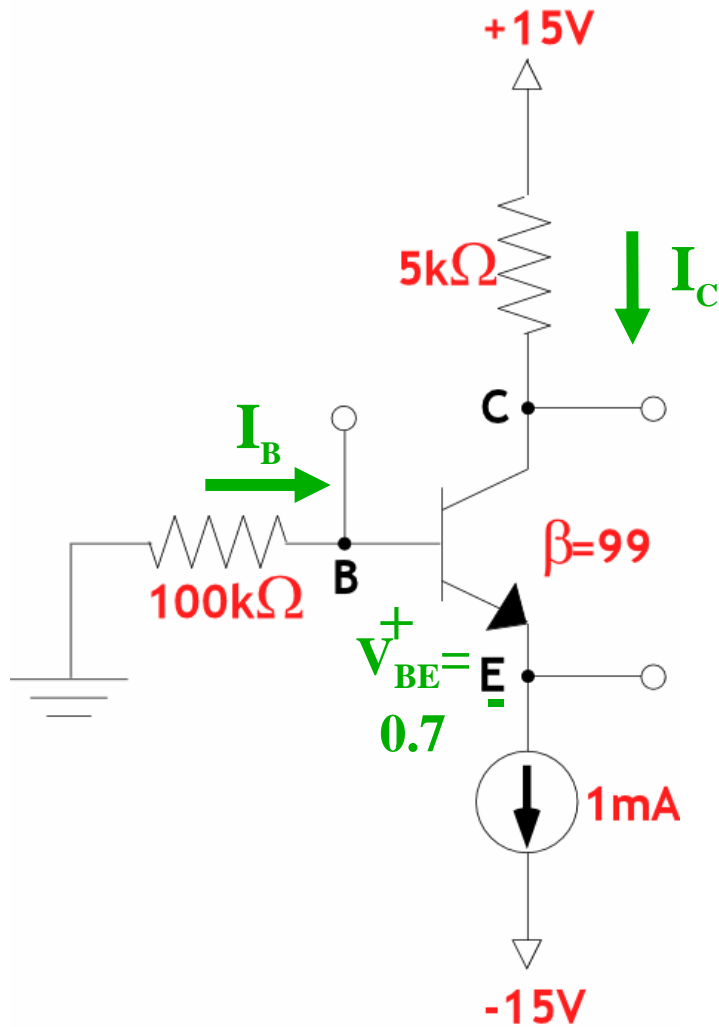

$$I_B = \frac{I_E}{\beta + 1} = \frac{1mA}{99 + 1} = \underline{10\mu A}$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{99}{99 + 1} 1mA = \underline{0.99mA}$$

$$V_C = 15 - I_C R_C = 15 - (0.99mA)(5k) = \underline{10.05V}$$

$$V_B = 0 - I_B R_B = -(10\mu A)(100k) = \underline{-1V}$$


**Check  $V_{BE}$  (0.7V) and  $V_{CB}$  (reverse):**

$$V_E = V_B - V_{BE} = (-1) - 0.7 = -1.7V$$

$$V_{CB} = V_C - V_B = 10.05 - (-1) = 11.05V$$



# DC Analysis

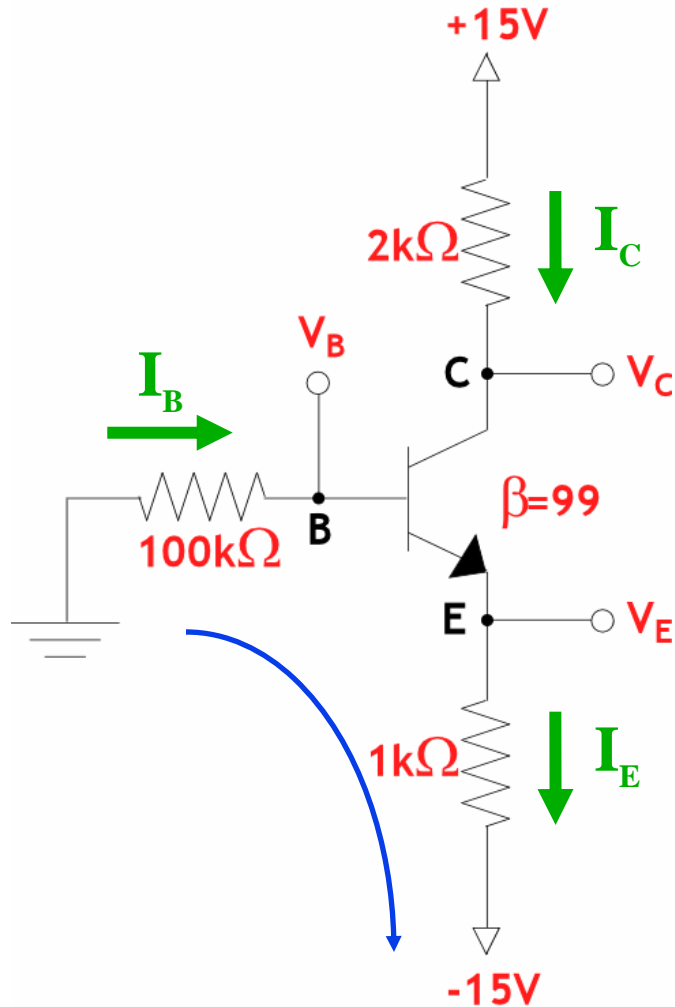


Find voltages & currents

Process:

- Assume ACTIVE mode operation;  $V_{BE} = 0.7V$
- Based on assumption, calculate branch voltages and currents
- Verify ACTIVE mode by checking  $V_{CB}$



# DC Analysis

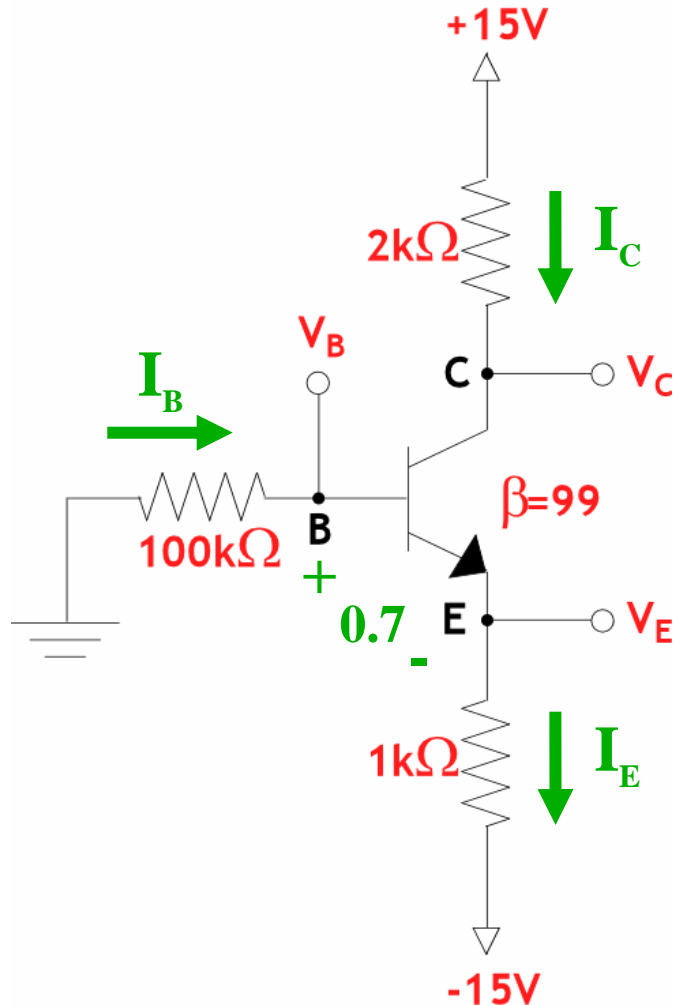

$$I_E = \frac{V_E + 15}{1k} \quad I_B = \frac{0 - V_B}{100k}$$

$$I_E = (\beta + 1)I_B \rightarrow \frac{V_E + 15}{1k} = (\beta + 1) \frac{0 - V_B}{100k}$$

$$\boxed{V_B = V_E + 0.7} \rightarrow \frac{V_E + 15}{1k} = (100) \frac{-V_E - 0.7}{100k}$$

$V_E = -7.85V$	$I_E = 7.15mA$
$V_B = -7.15V$	$I_B = 71.5\mu A$

Get:


$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{99}{100} (7.15m) = \underline{7.08mA}$$

$$V_C = 15 - I_C R_C = 15 - (7.08m)(2k) = \underline{0.84V}$$

**Check:**  $V_{CB} = 7.99V$  (reverse biased) – OK



## Edge of Active Mode

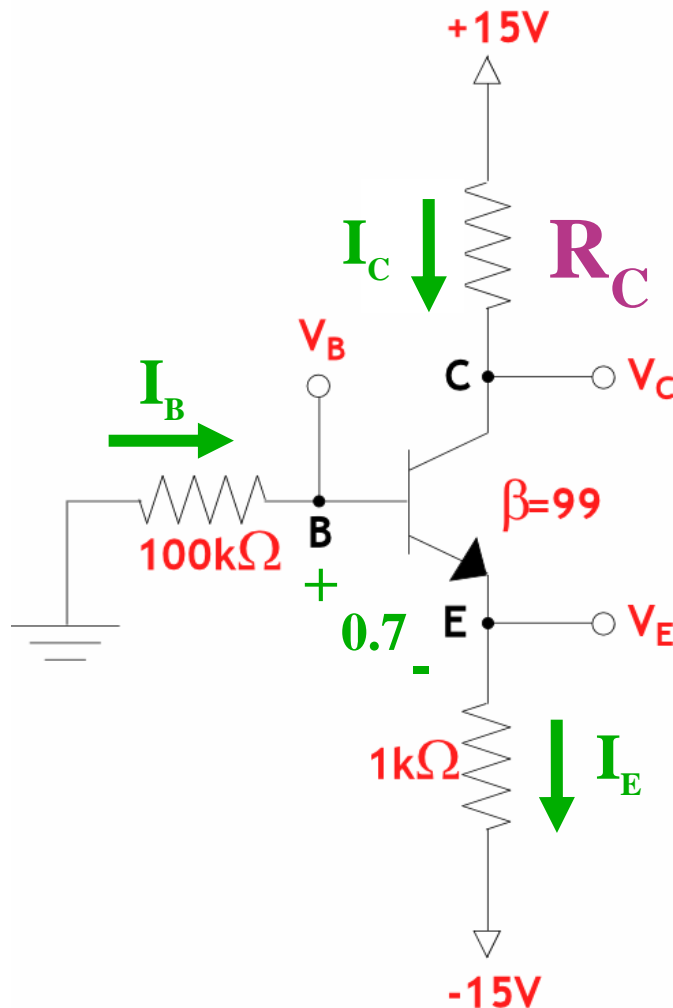


- From previous slide, found:

$$V_C = 15 - I_C R_C = 15 - (7.08m)R_C$$

- In general, *increasing*  $R_C$  will not change  $I_C$  significantly
- More significant consequence of *increasing*  $R_C$  is a *decrease* of  $V_C$
- If  $R_C$  is too large, *decrease* of  $V_C$  will cause BJT to leave *active* mode and transition to *saturation* mode
- Recall, *active/saturation boundary* occurs for  $V_C > V_B$ ;  $V_{CB} > 0V$



# Calculate Transition Point

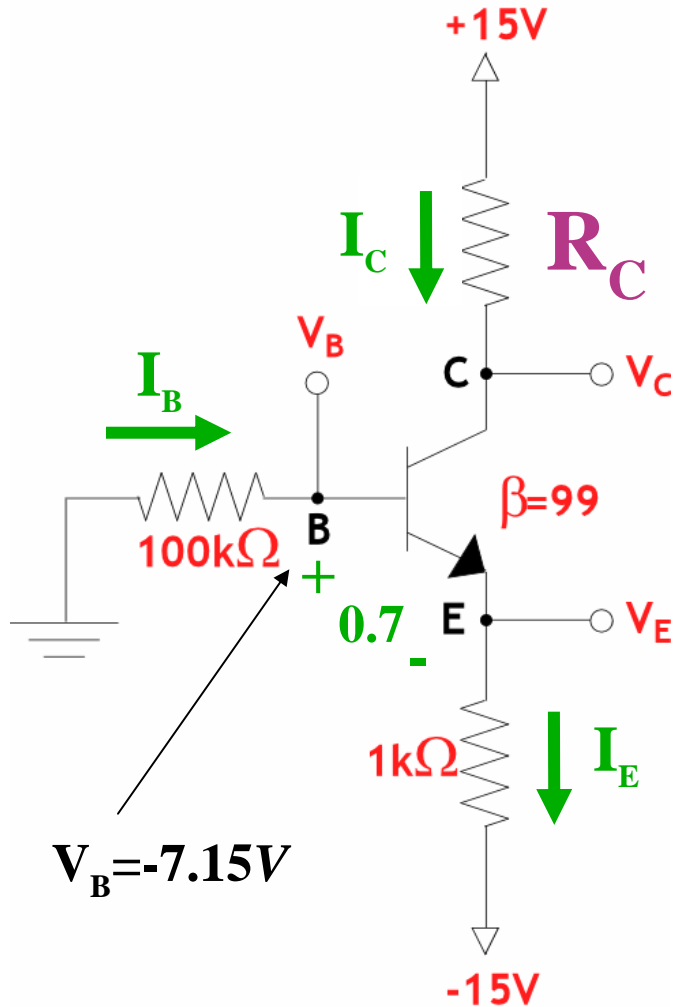

-Use relationship for  $V_C$  &  $I_C$ :

$$V_C = 15 - I_C R_C = 15 - (7.08mA)R_C$$

-Use previous result for  $V_B = -7.15V$ , and write expression for  $R_C$  as a function of  $V_C$ ; solve for maximum  $R_C$  in order to stay in *active* mode:

$$V_C = V_B ; 15 - (7.08mA)R_C = -7.15V$$

-For active mode operation:

$$R_C \leq 3.13k\Omega$$




## DC Analysis Comments

- Do not know a priori that BJT is in active mode
- Use approach similar to diode CVDM analysis
  - Assume active mode operation ( $V_{BE} = 0.7V$ )
  - Solve circuit
  - Verify active mode operation (check  $V_{CB}$ )
- Generally never use exponential model for  $I_C$  in basic DC analysis
- Generally neglect Early Voltage effect in DC analysis





# pnP Transistor Biasing

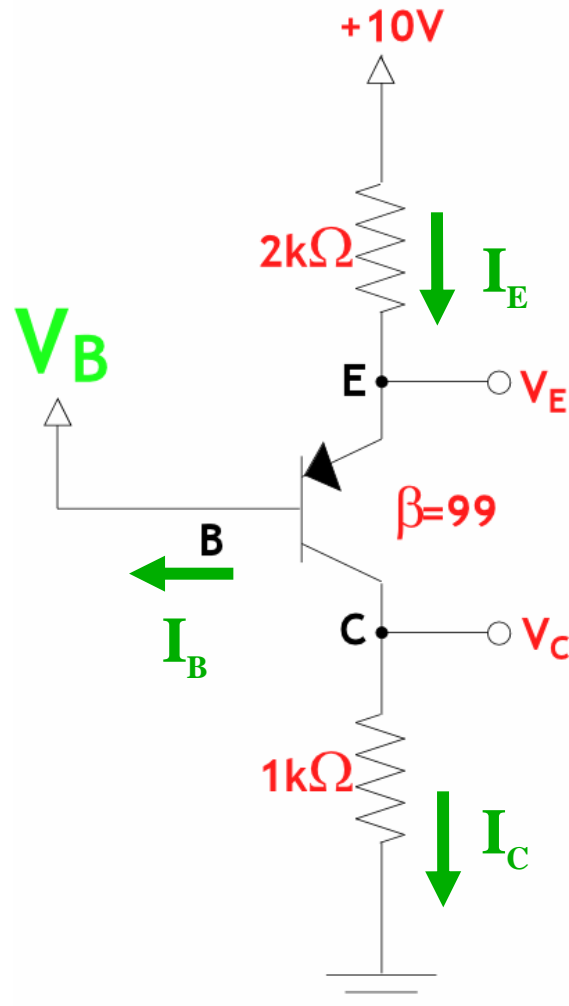


Process:

- Assume *active* mode operation;  $V_{EB} = 0.7V$
- Based on assumption, calculate branch voltages and currents
- Verify *active* mode by checking  $V_{BC} \geq 0V$


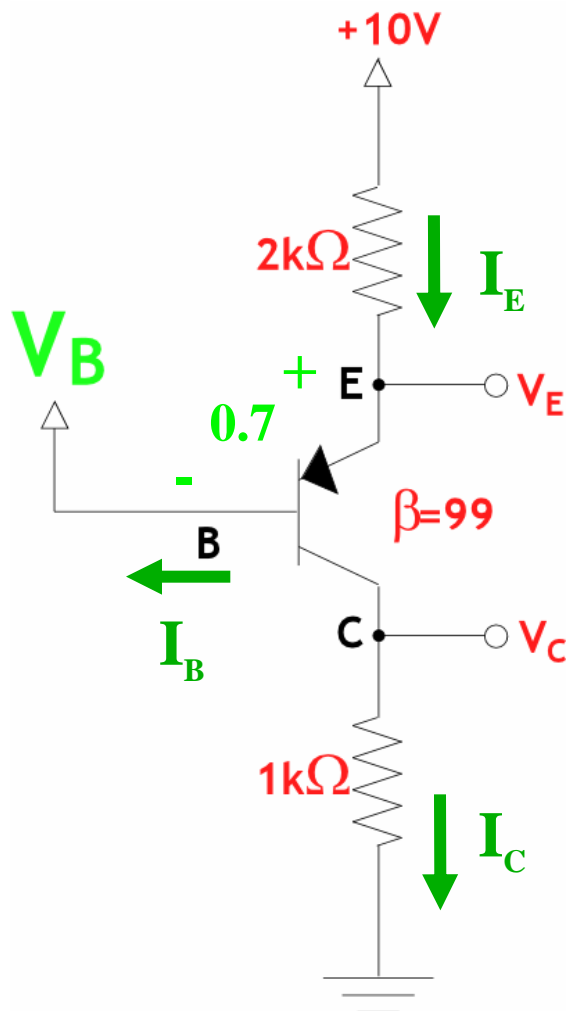
# Example: Find $V_B$ That Keeps BJT Active



- As  $V_B$  decreases,  $I_E$  &  $I_C$  increase,  $V_C$  increases
- Minimum  $V_B$  condition exists while maintaining  $V_{EB} = 0.7V$
- In active mode:  $V_E - V_B = 0.7V$

$$I_E = \frac{10 - V_E}{2k}$$

$$I_C = \frac{V_C}{1k} = \alpha I_E = 0.99 \cdot \frac{10 - (V_B + 0.7)}{2k}$$

$$V_C = 4.6 - 0.495V_B$$


At *active/saturation* boundary,  $V_C = V_B$ :

$$V_B \geq 3.08V$$



# Transistor Sensitivity to $I_B$

$\beta$  is 107

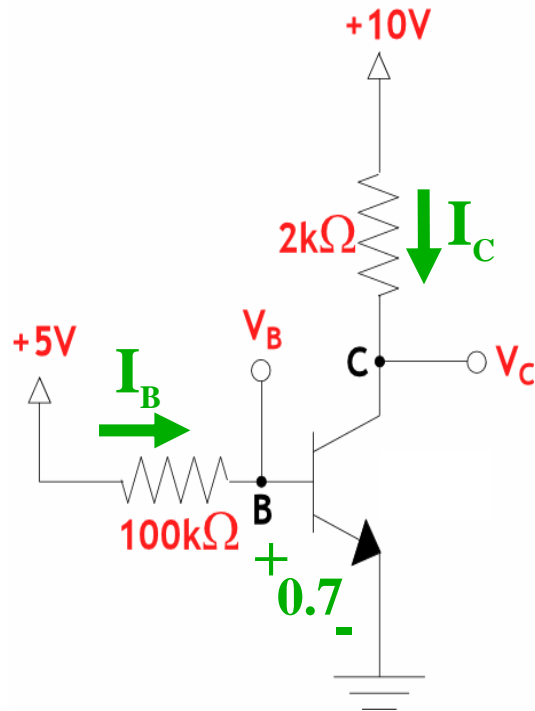

$$R_B = 100k\Omega$$

$$V_B = 0.7V$$

$$I_B = \frac{5 - 0.7}{100k} = 43\mu A$$

$$I_C = \beta I_B = (107)(43\mu A) = 4.601mA$$

$$V_C = 10 - (4.601mA)(2k\Omega) = 0.798$$

$$R_B = 200k\Omega$$

$$V_B = 0.7V$$

$$I_B = \frac{5 - 0.7}{200k} = 21.5\mu A$$

$$I_C = \beta I_B = (107)(21.5\mu A) = 2.4075mA$$

$$V_C = 10 - (2.4075mA)(2k\Omega) = 5.185$$

- Small changes in base current result in large current changes in the collector:  $I_C = \beta I_B$ .
- Doubling the base current, causes the collector voltage to decrease more than 6.5 times.



# Transistor Sensitivity to $\beta$

Find  $\beta$  condition to keep BJT active


$$V_B = 0.7V \quad I_B = \frac{5 - 0.7}{100k} = 43\mu A$$

$$I_C = \beta I_B = \beta \cdot 43\mu A$$

$$V_C = 10 - I_C(2k) = 10 - 0.086\beta$$

$$\text{Let } V_C = V_B = 0.7$$
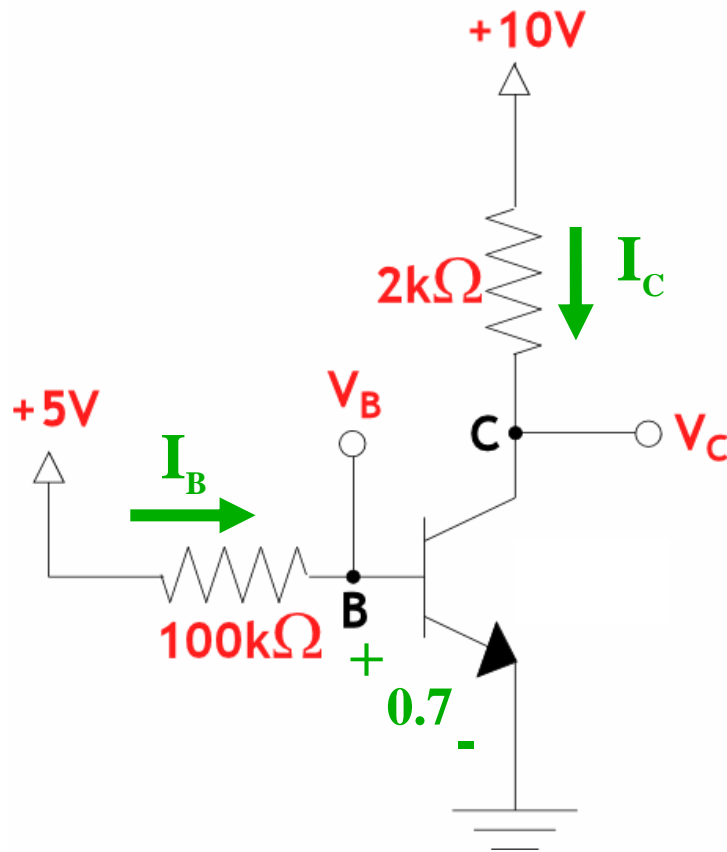
$$V_C \geq V_B \Rightarrow \beta \leq 108$$




- $\beta$  can vary; want designs with DC conditions that are insensitive to  $\beta$


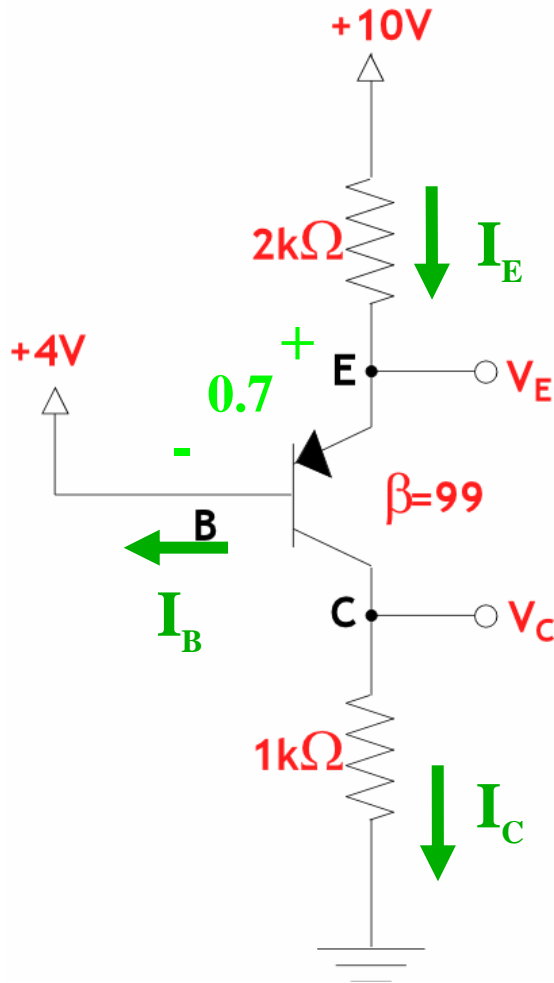
# Avoiding $\beta$ Sensitivity

Find  $\beta$  condition to keep BJT active



$$V_E = 4.7V \quad I_E = \frac{10 - 4.7}{2k} = 2.65mA$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} 2.65mA$$


$$V_C = I_C (1k\Omega) = (2.65) \frac{\beta}{\beta + 1} \quad \text{Let } V_C = V_B = 4V$$

$$V_C \leq V_B \Rightarrow \beta \geq -2.96 \quad \text{OK for any } \beta$$


- Putting resistance in the emitter generally stabilizes DC biasing



# Transistor Biasing

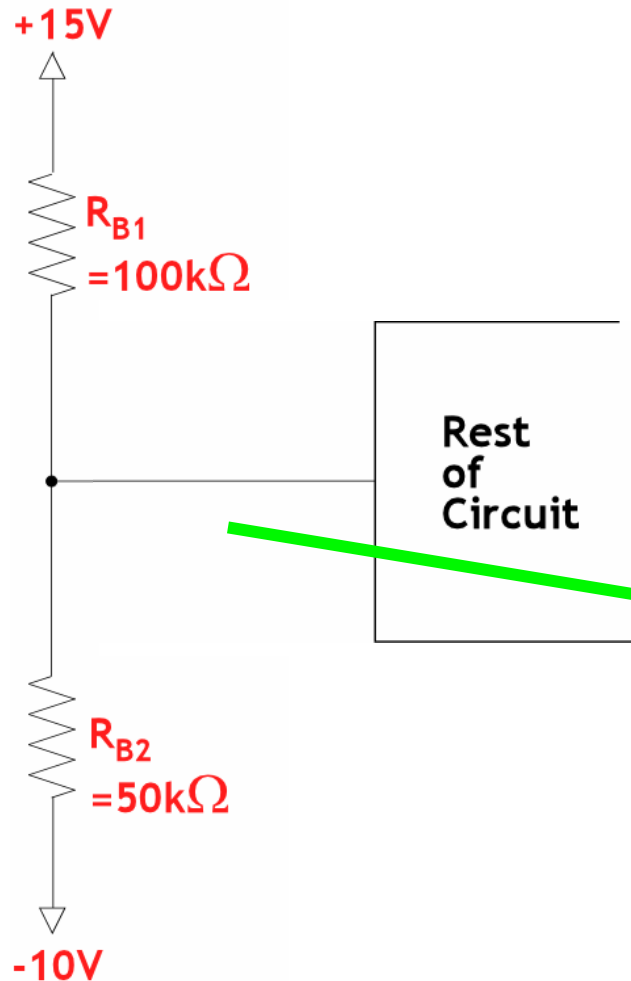

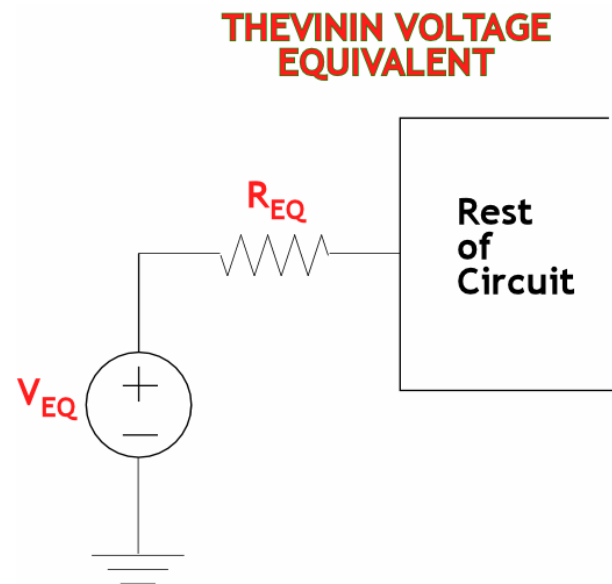- Typical resistor arrangement for base-biasing of the BJT amplifier configurations.
- Start by simplifying base network  $R_{B1}$  &  $R_{B2}$





# Thevenin Circuit for Transistor Biasing

- $V_{EQ}$ : use superposition


$$V_{EQ} \Big|_{+15V \text{ source}} = \frac{R_{B2}}{R_{B1} + R_{B2}} 15 = 5V$$

$$V_{EQ} \Big|_{-10V \text{ source}} = \frac{R_{B1}}{R_{B1} + R_{B2}} (-10) = -6.67V$$

$$\therefore V_{EQ} = -1.67V$$

- R: by inspection
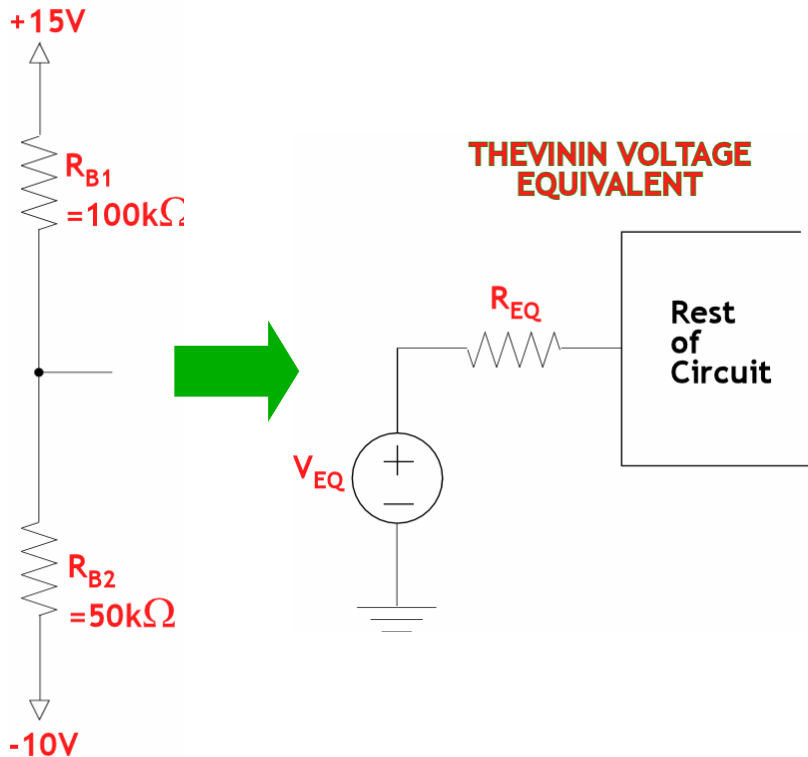
$$R_{EQ} = R_{B1} \parallel R_{B2} = 33.3k\Omega$$





# Example

$$I_E = \frac{V_E + 10}{3k} \quad I_B = \frac{-1.67 - V_B}{83.3k}$$

$$I_E = (\beta + 1)I_B \rightarrow \frac{V_E + 10}{3k} = (\beta + 1) \frac{-1.67 - V_B}{83.3k}$$

$$V_B = V_E + 0.7 \rightarrow \frac{V_E + 10}{3k} = (100) \frac{-V_E - 2.37}{83.3k}$$


Get:

$V_E = -4.03V$	$I_E = 1.99mA$
$V_B = -3.33V$	$I_B = 19.9\mu A$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} I_E = \frac{99}{100} (1.99m) = 1.97mA$$

$$V_C = 15 - I_C R_C = 15 - (1.97m)(2k) = 5.15V$$

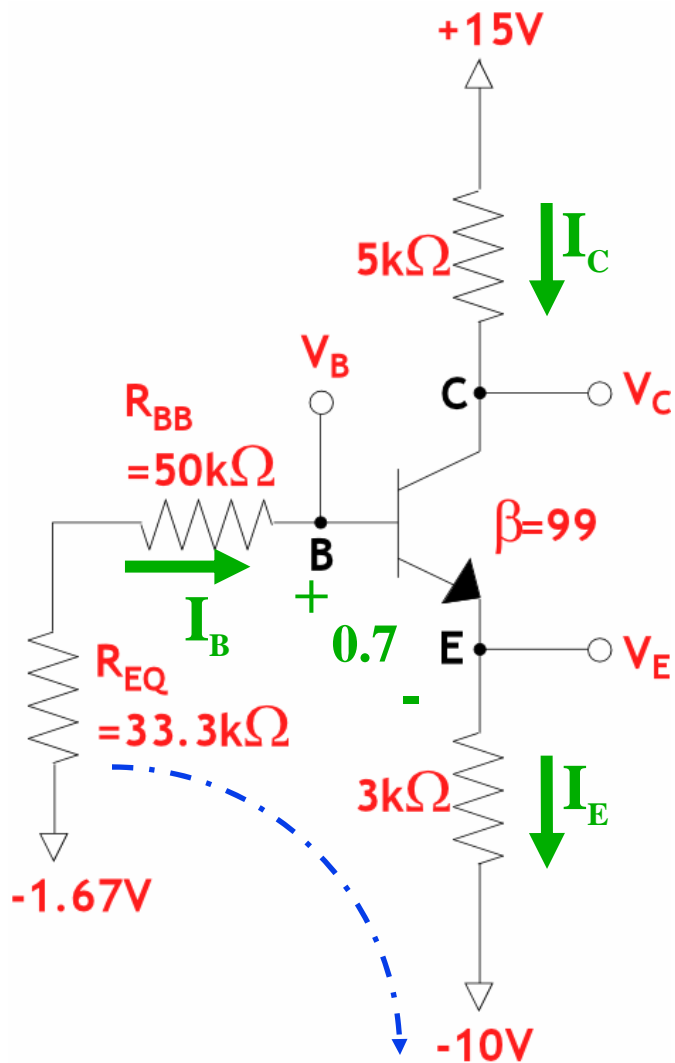
**Check:**  $V_{CB} = 8.48V$  (reverse biased) – OK








# AC-Signal Coupling

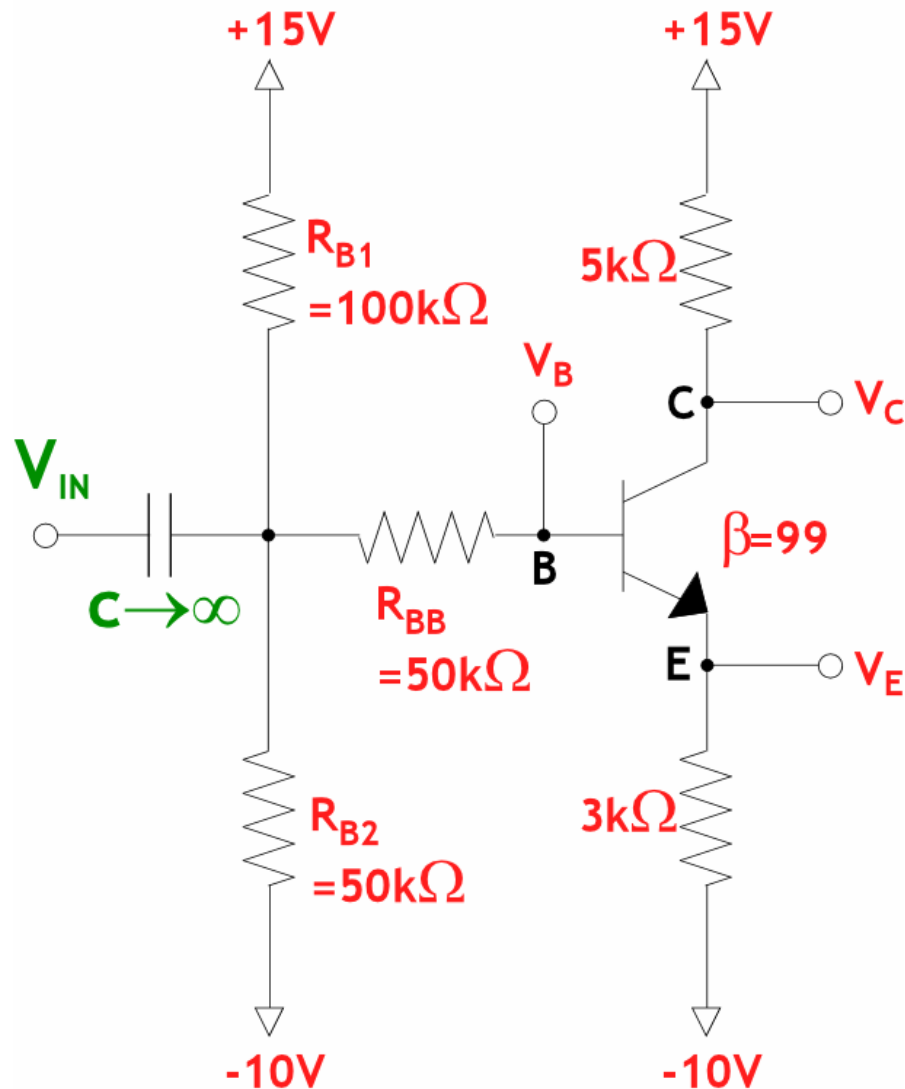

- Couple an input signal via a coupling capacitor:
  - $C \rightarrow \infty$  is open circuit at DC, short circuit for AC signals.
  - If  $R_{B1}$  &  $R_{B2}$  not present, BJT would not be DC biased
  - $C$  prevents signal source from having to provide DC current
  - Completely decouples DC biasing from signal source



# Two-Stage BJT DC Circuits Analysis

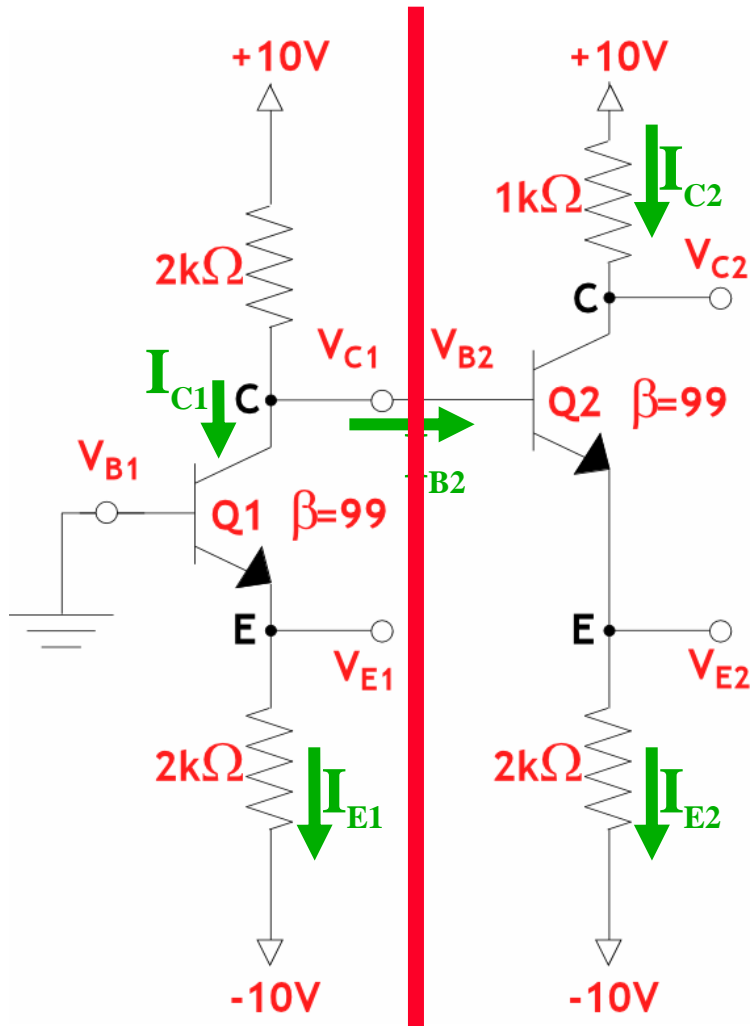


- Analysis approach: perform DC analysis on individual transistors.
- In this example, decouple at  $V_{C1} - V_{B2}$  circuit connection
- Assume that  $I_{B2} = 0$  and calculate  $V_{B2}$
- Analyze each BJT separately
- Compare results for  $I_{B2}$  and  $I_{C1}$
- Through iteration/simulation, can verify approximation


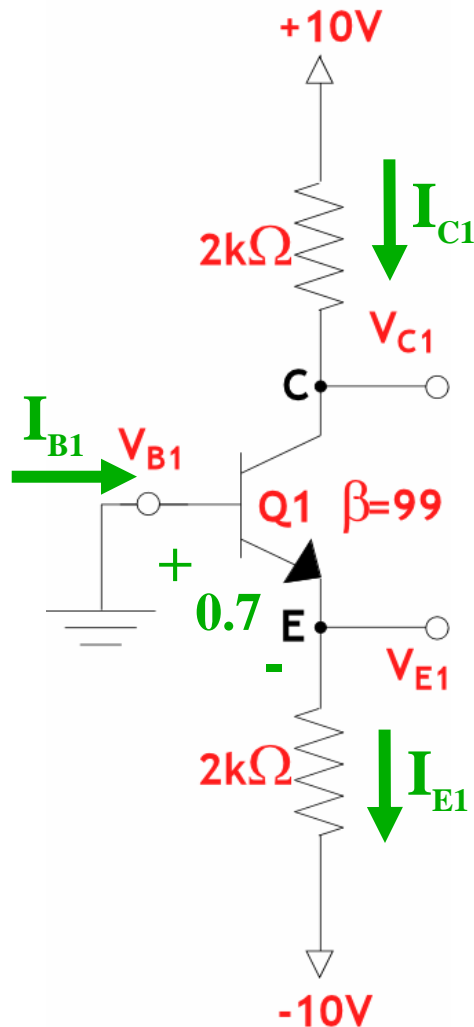
## Q1 Analysis

2 assumptions: a) *active mode*, and b) *no current flowing into Q2 via  $V_{C1}$  node:  $I_{B2}=0$*



$$V_E = -0.7V \quad I_E = \frac{-0.7 + 10}{2k} = 4.65mA$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} 4.65mA = 4.604mA$$

$$V_C = 10 - I_C (2k\Omega) \\ = 10 - (4.605mA)(2k\Omega) = 0.79V$$


$$V_{E1} = \underline{-0.7V} \quad I_{E1} = \underline{4.65mA}$$

$$I_{B1} = \underline{46.5\mu A}$$

$$V_{C1} = \underline{0.79V} \quad I_{C1} = \underline{4.60mA}$$



## Q2 Analysis – Same Assumptions

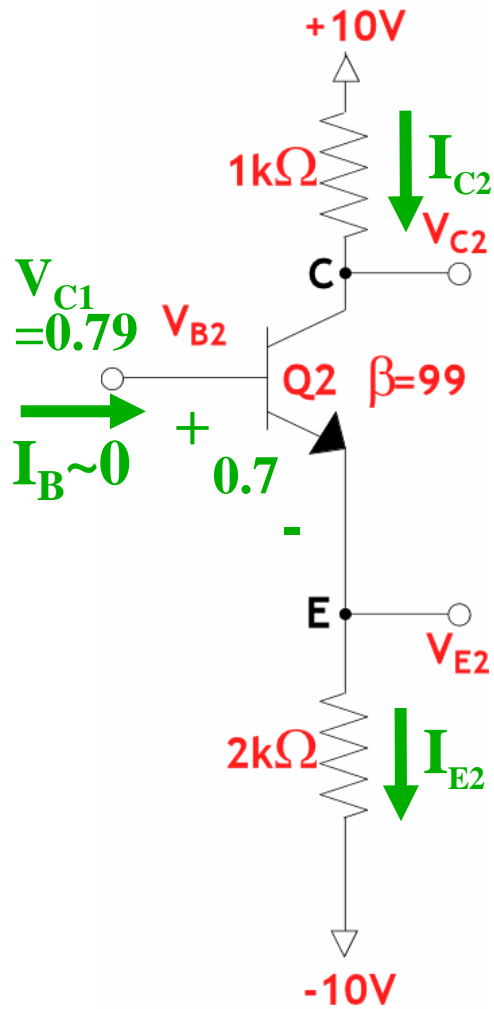

2 assumptions: a) *active mode*, and b) *no current flowing into Q2 via  $V_{C1}$  node:  $I_{B2}=0$*

$$V_E = 0.79 - 0.7 = 0.09V$$

$$I_E = \frac{0.09 + 10}{2k} = 5.045mA$$

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} 5.045mA = 4.995mA$$


$$V_C = 10 - I_C(1k\Omega) = 10 - (4.995mA)(1k\Omega) = 4.995V$$

$$V_{E2} = \underline{0.09V} \quad I_{E2} = \underline{5.05mA}$$

$$V_{C2} = \underline{4.995V} \quad I_{C2} = \underline{4.995mA}$$



# Compute Q2 Base Current

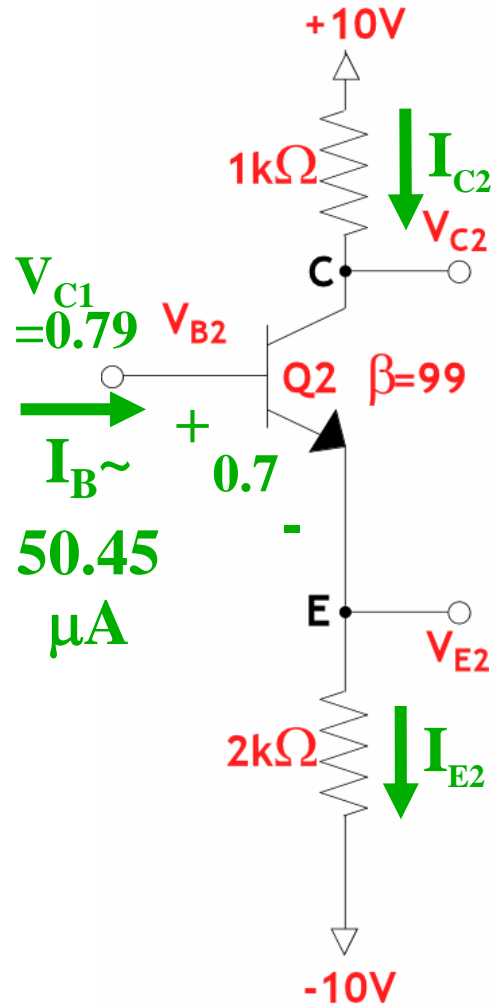


From previous:

$$I_C = \alpha I_E = \frac{\beta}{\beta + 1} 5.045 \text{mA} = 4.995 \text{mA}$$

$$I_B = \frac{I_C}{\beta} = \frac{4.995 \text{mA}}{99} = 50.45 \mu\text{A}$$


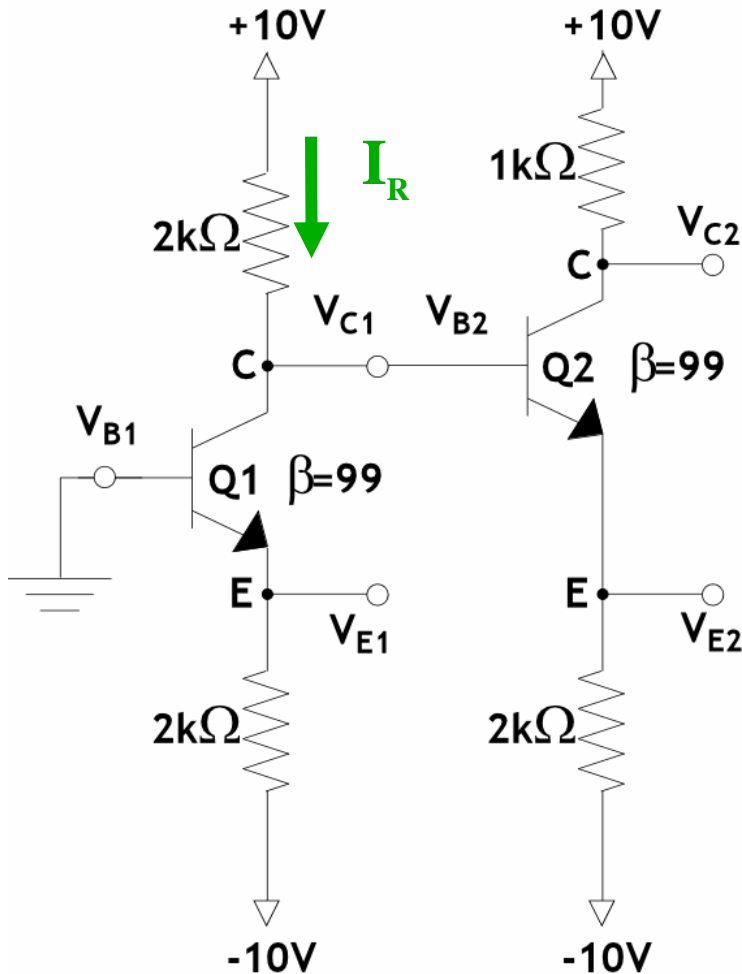
# Iterate to Get Exact Solution; Verify On Own



Add  $I_{B2}$  to  $I_{C1}$  current flowing in  $2k\Omega$

$$I_R = I_{C1} + I_{B2} = 4.604 + 0.0505 = 4.6545 \text{ mA}$$

$$V_{C1} = 10 - I_R(2k\Omega) \\ = 10 - (4.6545 \text{ mA})(2k\Omega) = 0.691$$

Re-DO the calculations for Q2:

$$V_{E2} = 0.691 - 0.7 = -0.01 \text{ V}$$

$$I_{E2} = \frac{-0.01 + 10}{2k} = 4.995 \text{ mA}$$

$$I_{C2} = \alpha I_{E2} = \frac{\beta}{\beta + 1} 4.995 \text{ mA} = 4.945 \text{ mA}$$

$$V_{C2} = 10 - I_{C2}(1k\Omega) \\ = 10 - (4.945 \text{ mA})(1k\Omega) = 4.945 \text{ V}$$

$$I_{B2} = \frac{I_{C2}}{\beta} = \frac{4.945 \text{ mA}}{99} = 49.95 \mu\text{A}$$



# DC Analysis of Active Mode BJT Circuits – Summary

- General approach to active mode DC analysis
- Collector resistance and its effect on active mode operation
- Sensitivity of BJT DC bias to variations in  $\beta$ , and how to avoid it
- Practical biasing arrangement for coupling AC signals
- Analysis approach to DC analysis of circuits involving multiple BJTs




## Outline of Chapter 5

- 1- Introduction to The Bipolar Junction Transistor
- 2- Active Mode Operation of BJT
- 3- DC Analysis of Active Mode BJT Circuits
- 4- BJT as an Amplifier
- 5- BJT Small Signal Models
- 6- CEA, CEA with  $R_E$ , CBA, & CCA
- 7- Integrated Circuit Amplifiers





# BJT Signal Analysis


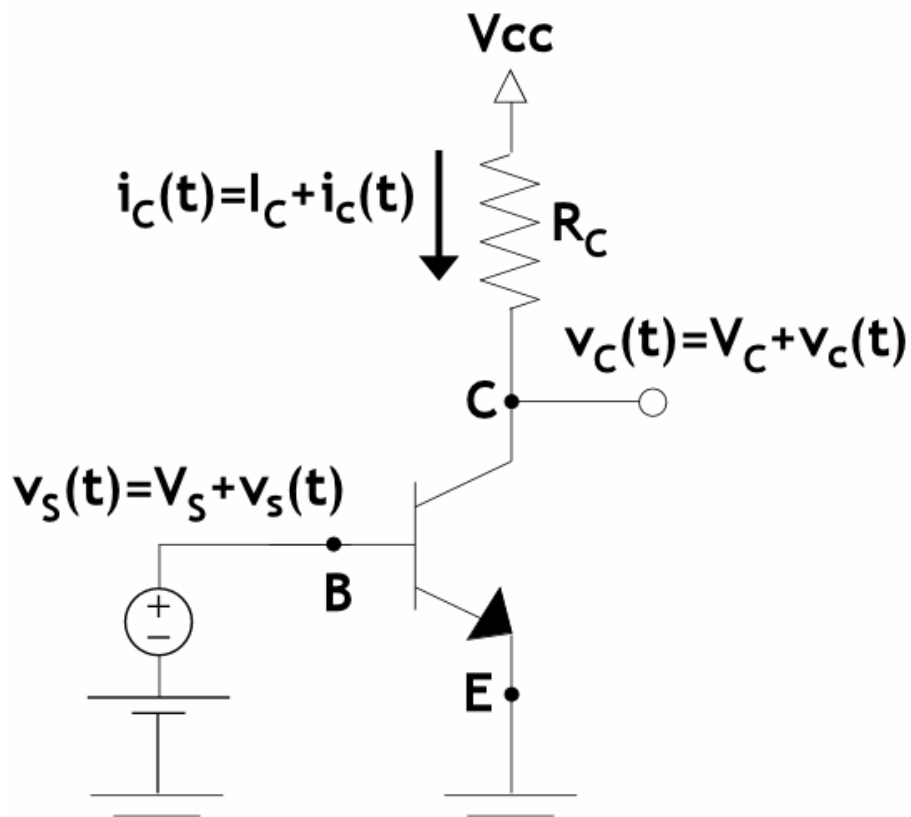


- Input has DC and AC components
- Output has DC and AC components
- Because the two are linearly superimposed, can separate DC and AC analysis as did with diode



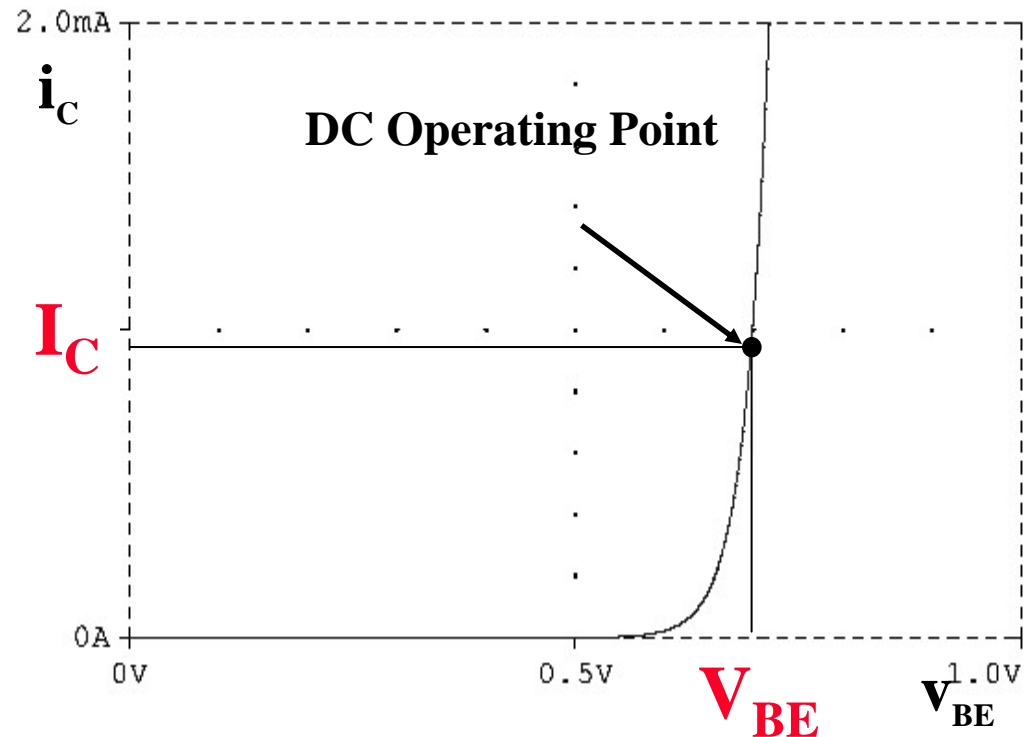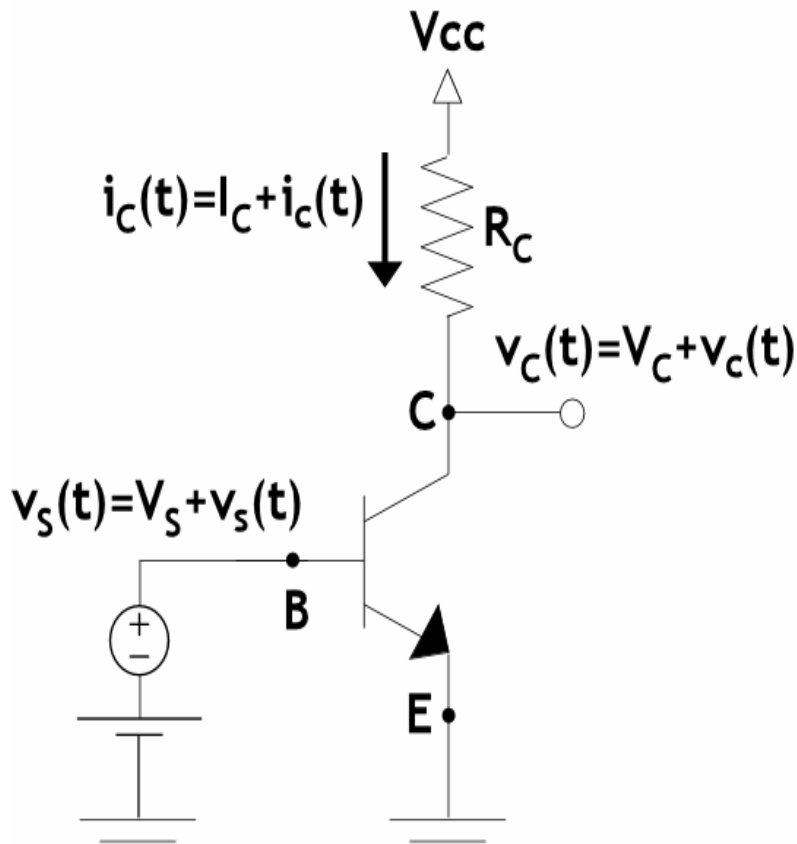
# DC Analysis – Operating Point, $I_C$ vs $V_{BE}$

- Kill AC sources
- Operating point determined by  $V_{BE}$




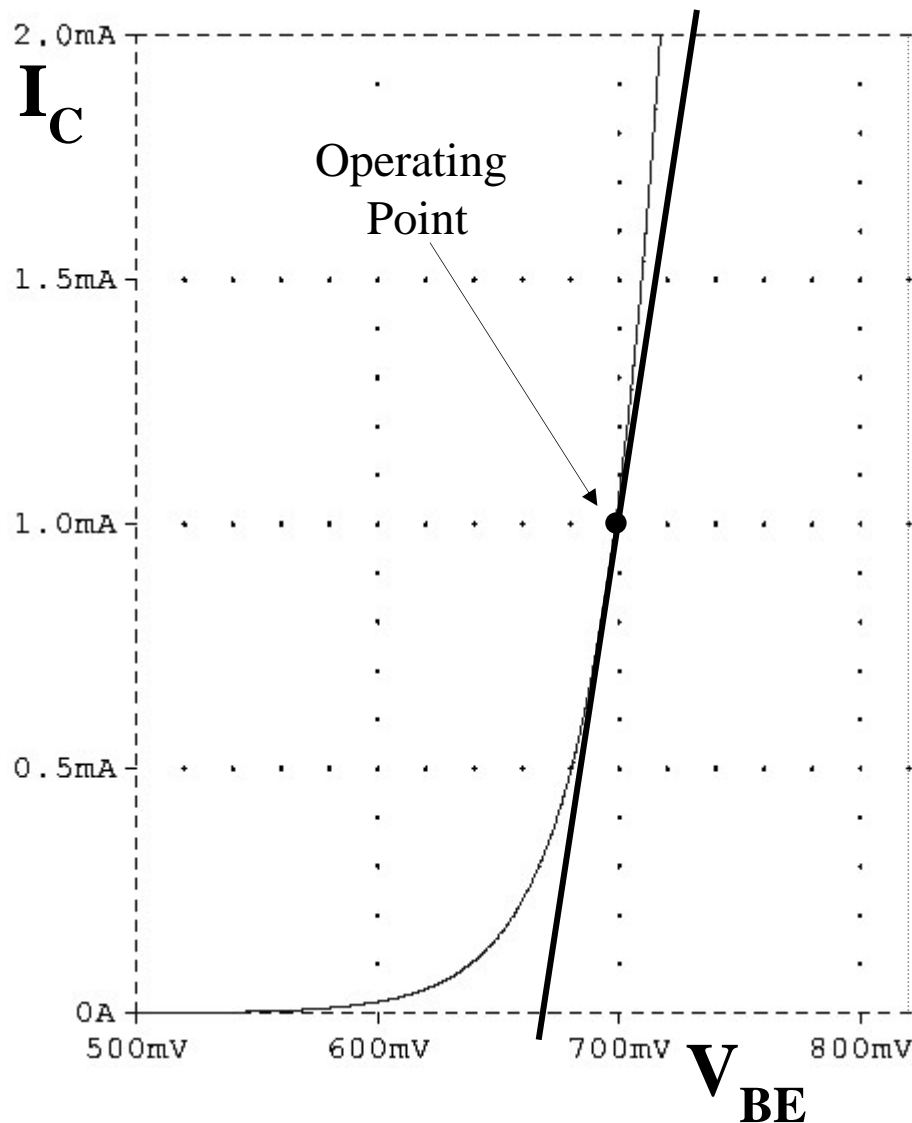
## BJT Signal Analysis – $i_C$ vs $V_{BE}$



Consider superposition of an AC signal at the DC operating point

- Slope of  $i_C$ - $v_{BE}$  curve at operating defined as BJT transconductance,  $g_m$

$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$$



## $g_m$ Operating Point Dependence

- Since  $g_m$  represents slope at a fixed *operating point*, can derive an expression for  $g_m$ , at this operating point
- Take derivative and simplify
- Final expression for  $g_m$  indicates BJT operating point dependence based on  $I_C$ , the DC collector current.

$$g_m \equiv \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{i_C=I_C}$$


$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$$

$$\left. \frac{\partial i_C}{\partial v_{BE}} \right|_{i_C=I_C} = \underbrace{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}_{I_C} \cdot \frac{1}{V_T}$$

$$g_m = \frac{I_C}{V_T}$$



# BJT Small Signal – $i_C$ vs $V_{BE}$

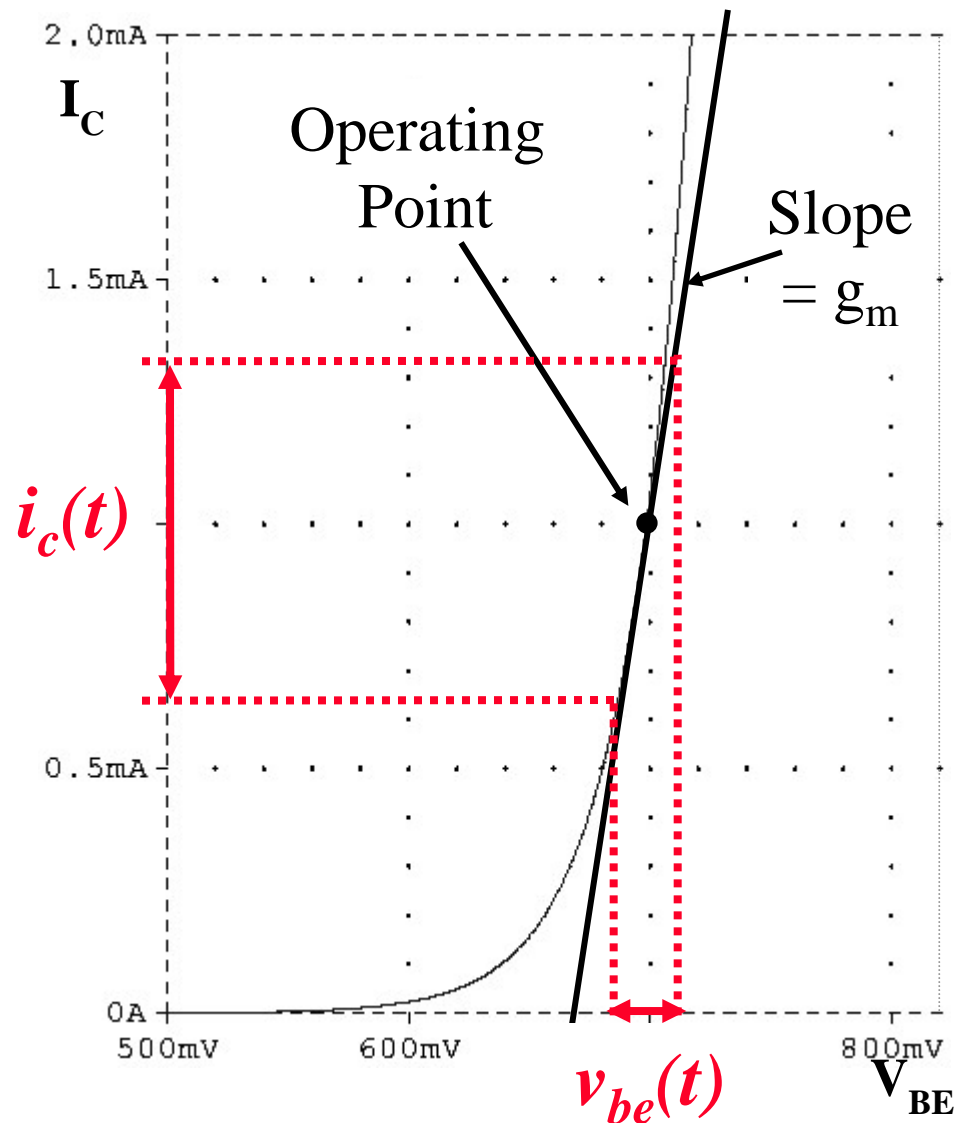

Define transconductance as slope of the  $i_C$ - $V_{BE}$  curve at an operating point:


In the *small signal* limit, can write expression for  $g_m$  as follow:

$$g_m = \frac{i_c(t)}{v_{be}(t)}$$

$g_m$  determines the BJT gain



# Common Emitter BJT Amplifier

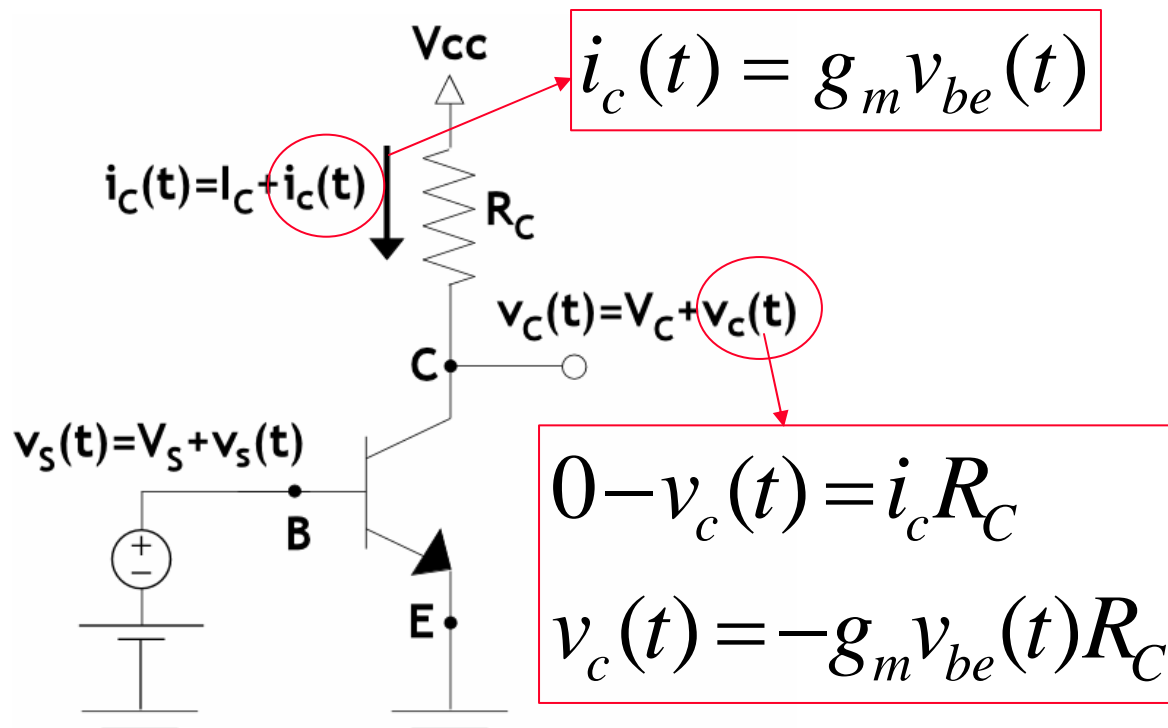


- Apply small signal at base:  $v_s(t) = v_{be}(t)$
- Results in signal current,  $i_c(t)$ , at collector
- Signal current through  $R_C$  produces output voltage at BJT collector terminal


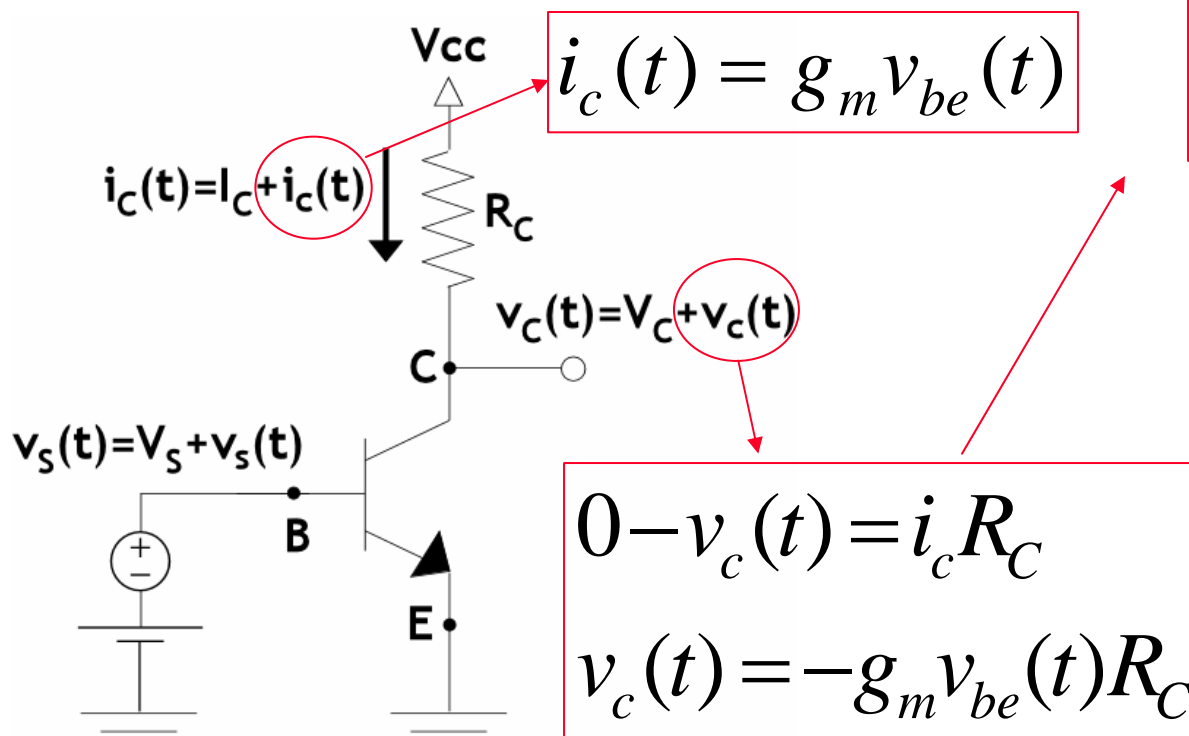
# Common Emitter BJT Voltage Gain

- Define voltage gain:


$$A_V = \frac{v_c(t)}{v_{be}(t)} = -g_m R_C$$





# Common Emitter BJT Voltage Gain

- From SPICE:

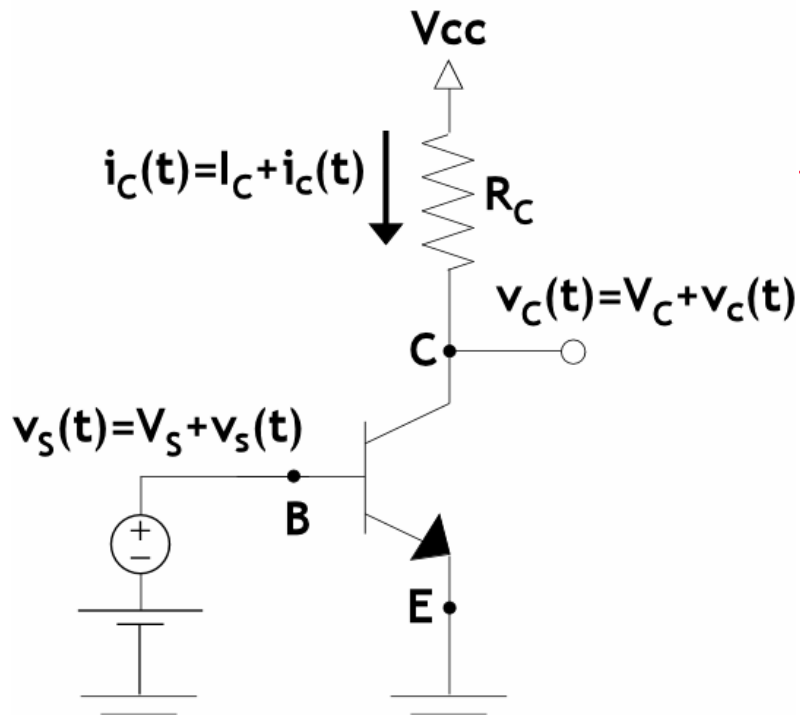

*Input*

*Output*

