




Outline of Chapter 5

- 1- Introduction to The Bipolar Junction Transistor
- 2- Active Mode Operation of BJT
- 3- DC Analysis of Active Mode BJT Circuits
- 4- BJT as an Amplifier
- 5- BJT Small Signal Models
- 6- CEA, CEA with R_E , CBA, & CCA
- 7- Integrated Circuit Amplifiers



CBA with r_o (Resistance Coupling C-E)

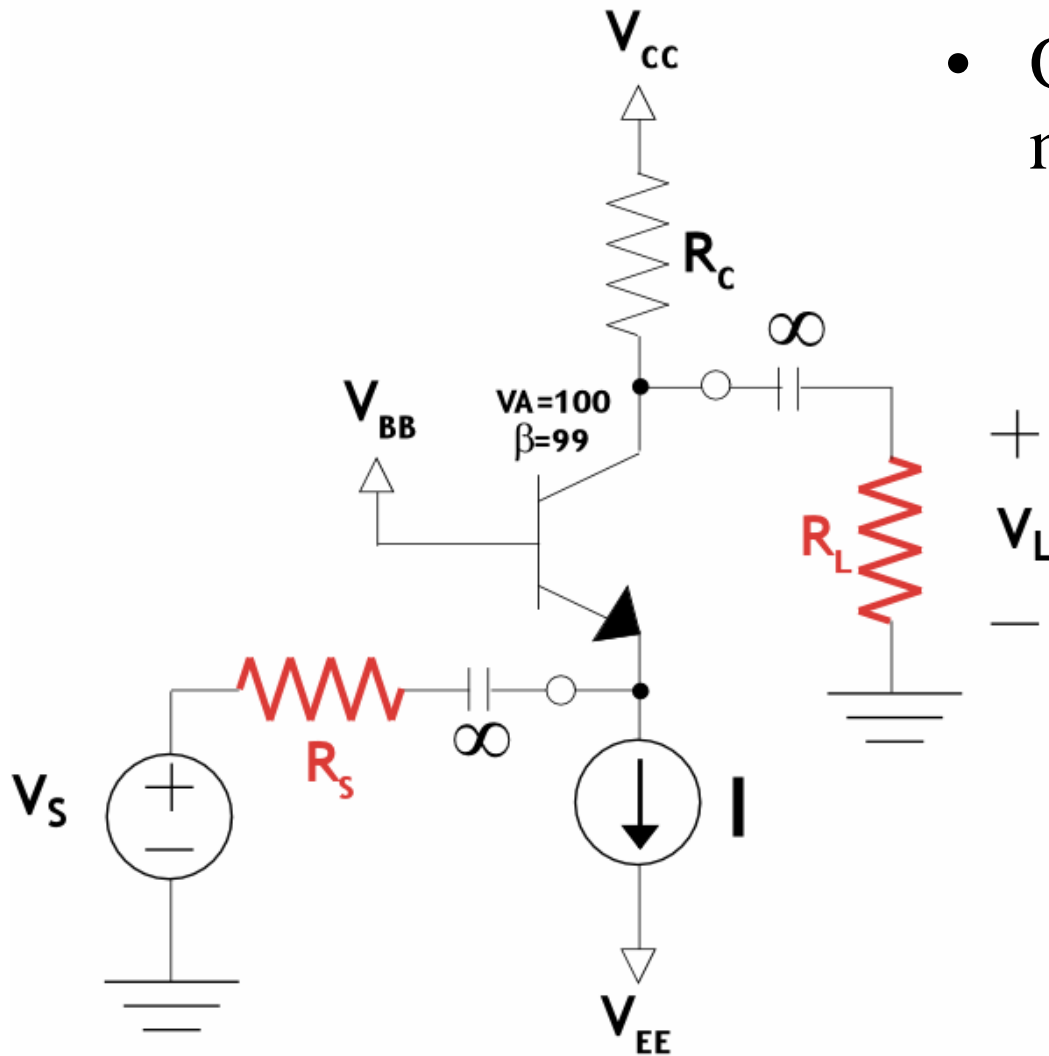- Original results neglecting R_S , R_L , & r_o :



Open circuit voltage gain

$$A_{VO} = \frac{v_{out}}{v_{in}} = g_m R_C$$

Short circuit current gain


$$A_{IS} = \frac{i_{out}}{i_{in}} = \alpha$$

$$R_{IN} = r_e$$

$$R_{OUT} = R_C$$



CBA with r_o -Voltage Gain

 

$$v_{be} = -v_{Input}$$

$$g_m v_{be} + \frac{(v_{Output} - v_{Input})}{r_o} + \frac{v_{Output}}{R_C} = 0$$


$$-g_m v_{Input} + \frac{(v_{Output} - v_{Input})}{r_o} + \frac{v_{Output}}{R_C} = 0$$

$$A_{VO} = \left(g_m + \frac{1}{r_o} \right) (r_o \parallel R_C)$$

Large r_o has little effect on gain



CBA with r_o Short-Circuit Current Gain

 

$$\alpha i_e + i_x + i_{Output} = 0$$

$$-i_{Input} - i_e - i_x = 0$$


$$i_e r_e = i_x r_o$$

$$A_{IS} = \frac{i_{out}}{i_{in}} = \frac{\alpha + \frac{r_e}{r_o}}{1 + \frac{r_e}{r_o}}$$

If r_o is large, it will have little effect on the overall gain



CBA with r_o -Input Resistance

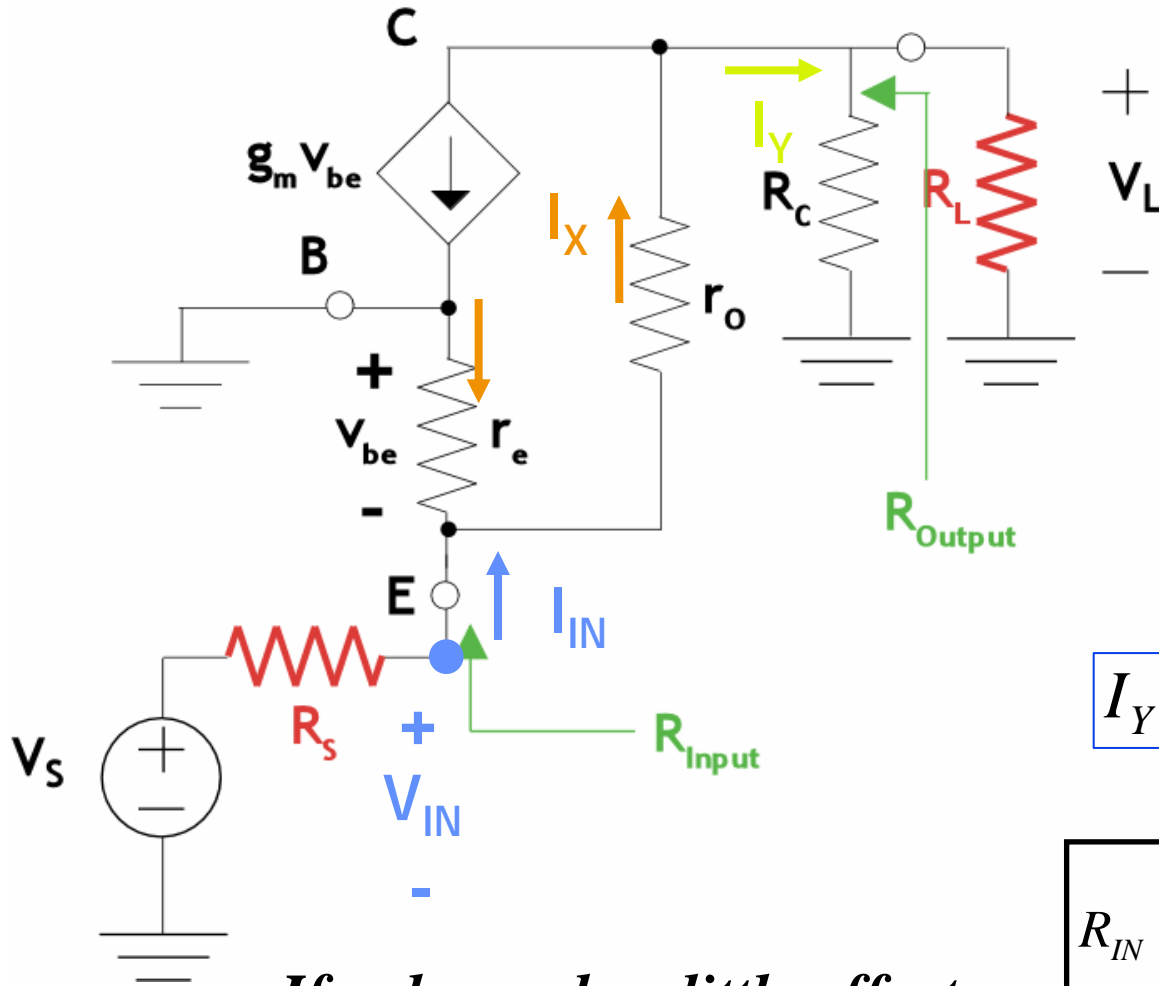

If r_o large, has little effect

$$R_{IN} = V_{IN} / I_{IN}$$

$$V_{IN} = -v_{be}$$

$$I_{IN} + \frac{v_{be}}{r_e} - I_X = 0$$


$$-g_m v_{be} + I_X - I_Y = 0$$

$$I_Y (R_C // R_L) + I_X r_o + v_{be} = 0$$

$$R_{IN} = r_e \parallel \left[r_o / 1 - \left(g_m + \frac{1}{r_o} \right) (r_o \parallel R_C \parallel R_L) \right]$$



CBA with r_o -Output Resistance

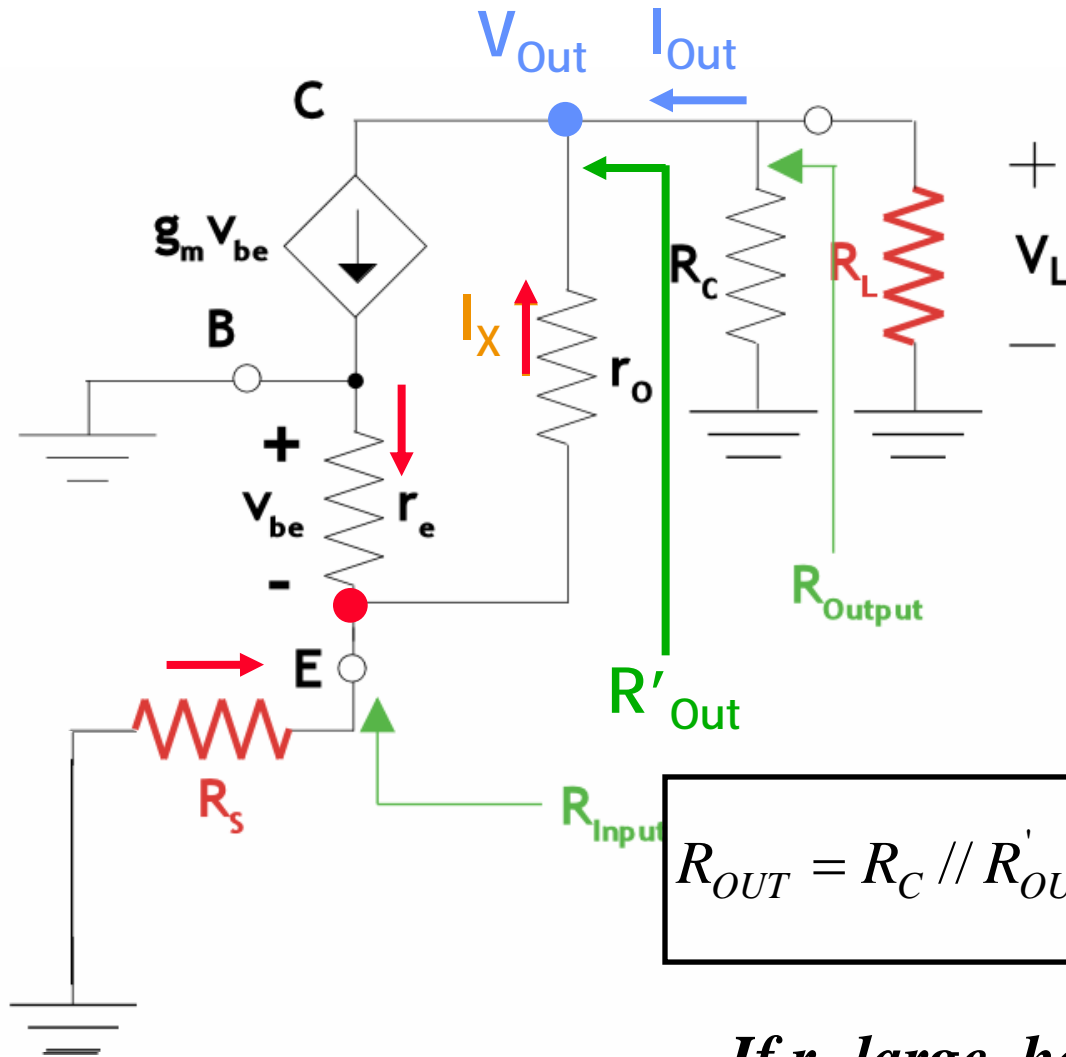

$$R'_{Out} = V_{Out} / I_{Out}$$

$$-I_{Out} - g_m v_{be} + I_X = 0$$

$$\frac{v_{be}}{r_e} + \frac{v_{be}}{R_S} - I_X = 0$$


$$I_X = \frac{(-V_{Out} + (-v_{be}))}{r_o}$$

$$R_{OUT} = R_C // R'_{OUT} = R_C // \frac{(r_o + r_e // R_S)}{1 + g_m (r_e // R_S)} \approx R_C // \frac{r_o}{2}$$

If r_o large, has little effect



CCA Operation – Voltage Buffer

 

- Good voltage buffer
 - The VOLTAGE gain is almost unity, and the DC component is only reduced by 0.7V
 - Large short circuit current gain
 - High input resistance (which reduces loading to the circuits before)
 - Low output resistance (which reduces the loading to the circuits after)




CCA with r_o – Voltage-Gain Analysis

Voltage Division:


$$v_{out} = v_{in} \left(\frac{r_o // 4k\Omega}{r_o // 4k\Omega + r_e} \right)$$

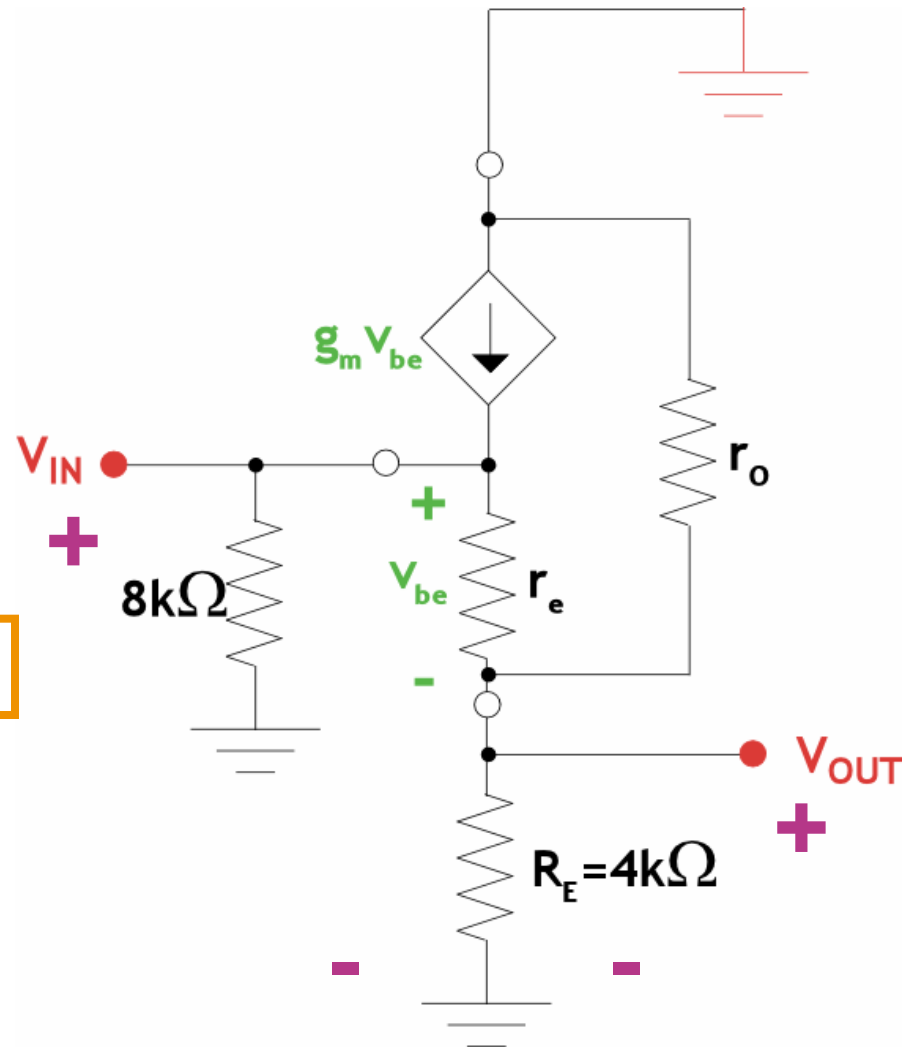Since r_e small, Almost $v_{out} = v_{in}$





CCA with r_o - Input/Output Resistance

 

- Input Resistance; by inspection using $\beta+1$ rule:

$$R_{IN} = 8k\Omega // \{(\beta + 1)(r_e + r_o // R_E)\}$$

HIGH INPUT RESISTANCE

- Output Resistance, $v_{in} = 0$


$$R_{OUT} = r_e // r_o // R_E$$

LOW OUTPUT RESISTANCE



CCA with r_o , Source and Load
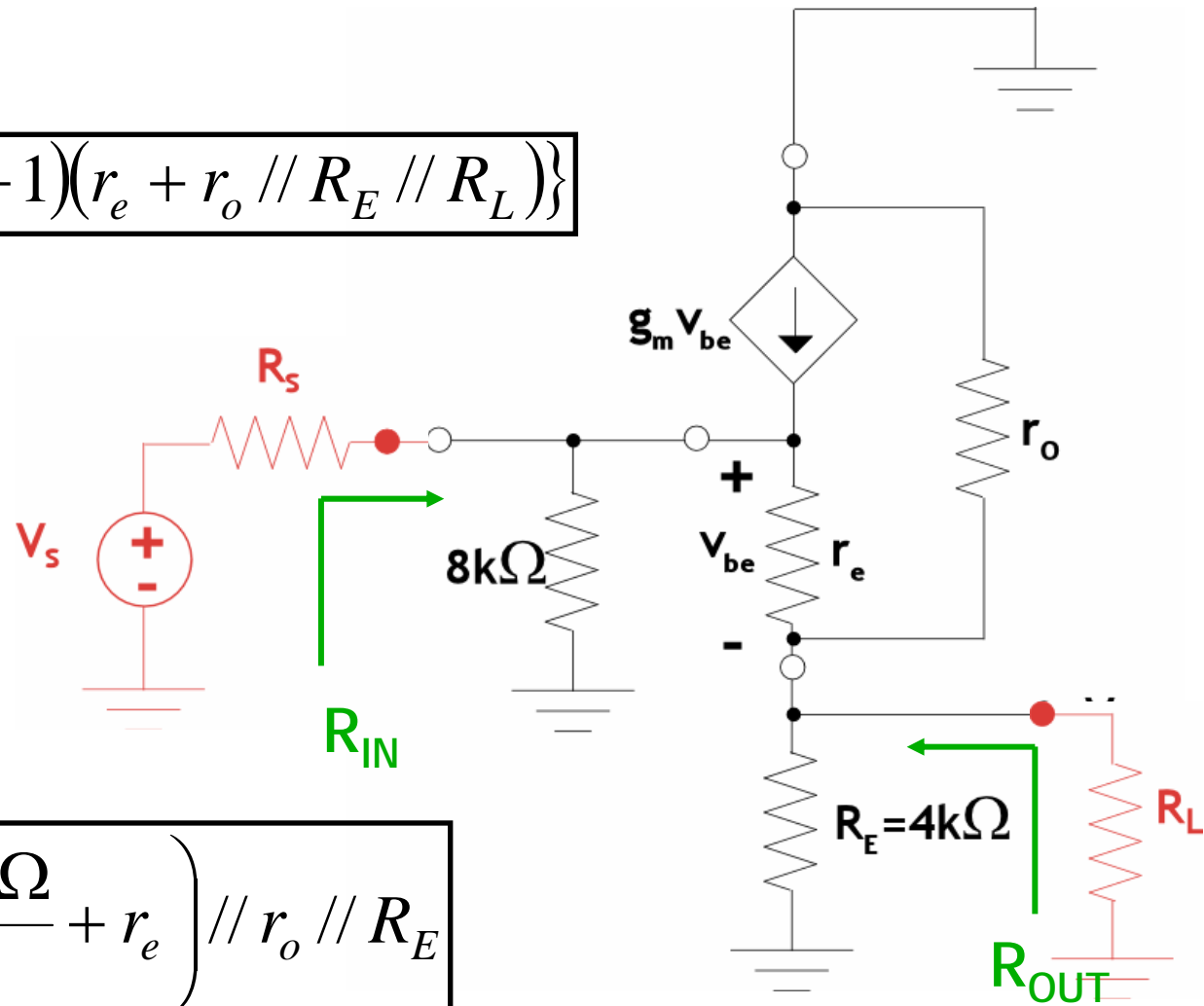
$$R_{IN} = 8k\Omega // \{(\beta + 1)(r_e + r_o // R_E // R_L)\}$$




$$R_{OUT} = \left(\frac{R_s // 8k\Omega}{\beta + 1} + r_e \right) // r_o // R_E$$



CEA with RE- Internal Feedback

 - Consider the small-signal T-model for the CEA configuration
- Base is input, collector is output
- r_e (or r_π – in Hybrid- π model) **AND** r_o both represent internal feedbacks from output to input; if emitter is grounded, feedback broken; if RE is present, feedback exists.






Internal Feedback – Summary

- CBA configuration:
 - r_o produces internal feedback between C & E terminals
 - expect effects to be *weak* since r_o large
- CCA configuration:
 - r_π or r_e produces internal feedback between B & E terminals
 - expect *strong* effect on R_{IN} & R_{OUT}
- CEA with R_E amplifier configuration:
 - r_o provides internal feedback between E & C terminals
 - occurs because emitter not at signal ground
 - expect *weak* effects since r_o large (More in EC2)
- CEA (no R_E) amplifier configuration:
 - no internal feedback between B & C terminals



Multistage Amplifier – DC Analysis

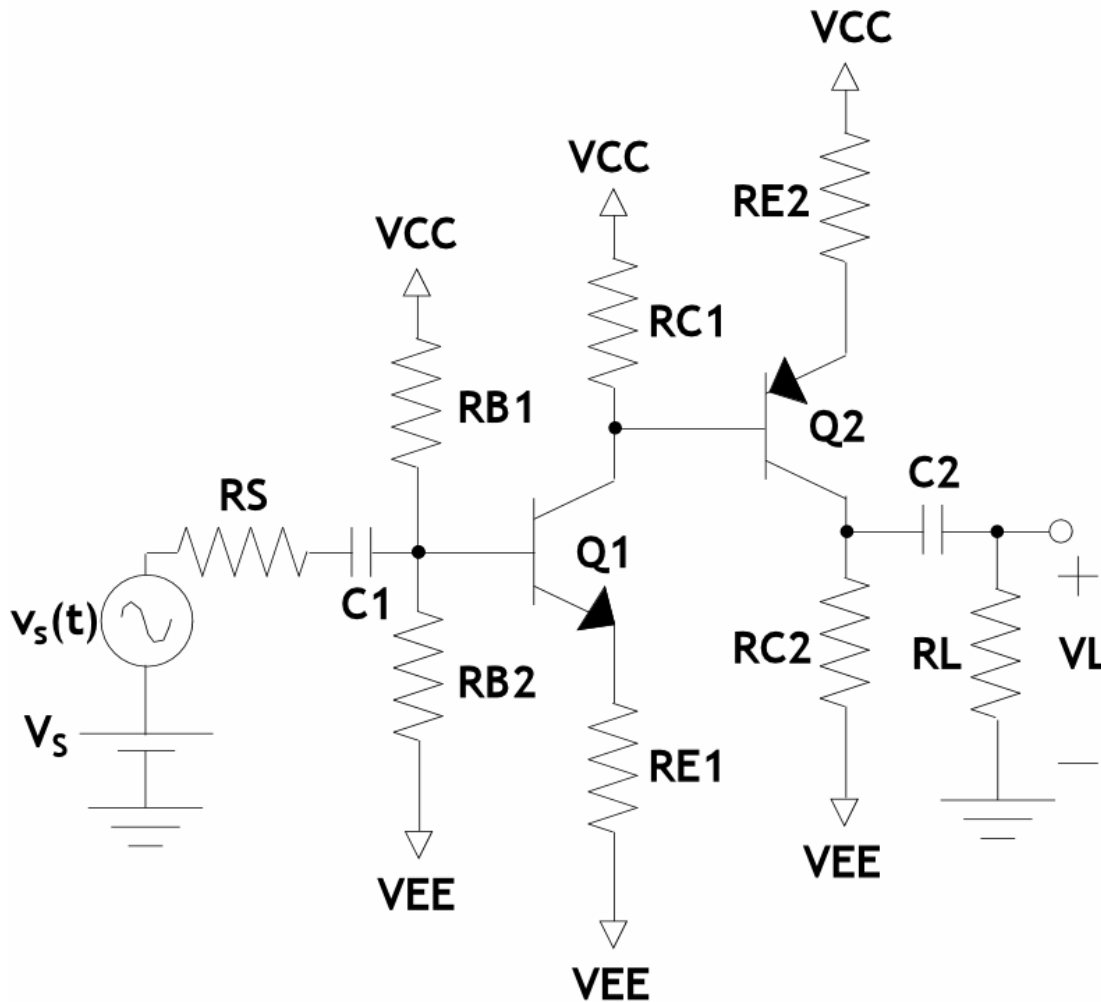


- Cascade of C-E stages
- Output of Q_1 stage is direct-coupled (DC) to input of Q_2 stage
- Coupled DC analysis!



Multistage Amplifier – R_{IN} & R_{OUT}

 Find: R_{IN1} , R_{IN2} ,
 R_{OUT1} , R_{OUT2} , A_{V01} ,
 A_{V02}






Outline of Chapter 5

- 1- Introduction to The Bipolar Junction Transistor
- 2- Active Mode Operation of BJT
- 3- DC Analysis of Active Mode BJT Circuits
- 4- BJT as an Amplifier
- 5- BJT Small Signal Models
- 6- CEA, CEA with R_E , CBA, & CCA
- 7- Integrated Circuit Amplifiers




Integrated Circuits

 

- Issues:
 - Limited area available
 - Size of R's and C's limited
 - Process variations
- Concept:
 - Integrate multiple transistors and passive components (R's and C's) on a single chip
 - Circuit performs application-specific function (ASIC)
 - Physically smaller, faster
- Coupling capacitors:
 - On-chip: \sim pF's only
 - Off-chip: \sim μ F's
- Resistors:
 - Pure resistors are difficult to make on an IC
 - Alternative: a transistor




Active Loads

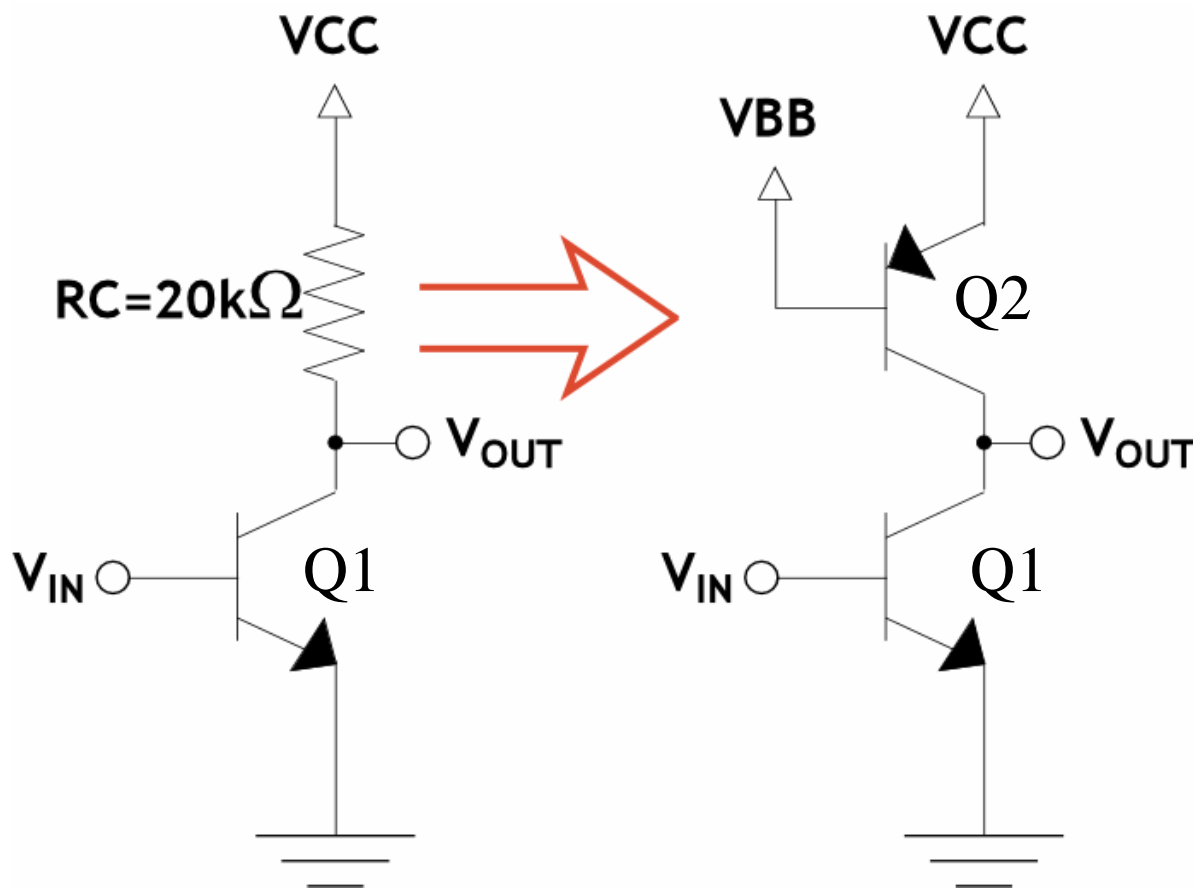

- Replace R_C with PNP transistor, $Q2$
- $Q2$ base held at constant voltage.
- $Q1$ load resistance becomes r_o of $Q2$.




CEA Gain with Active Load

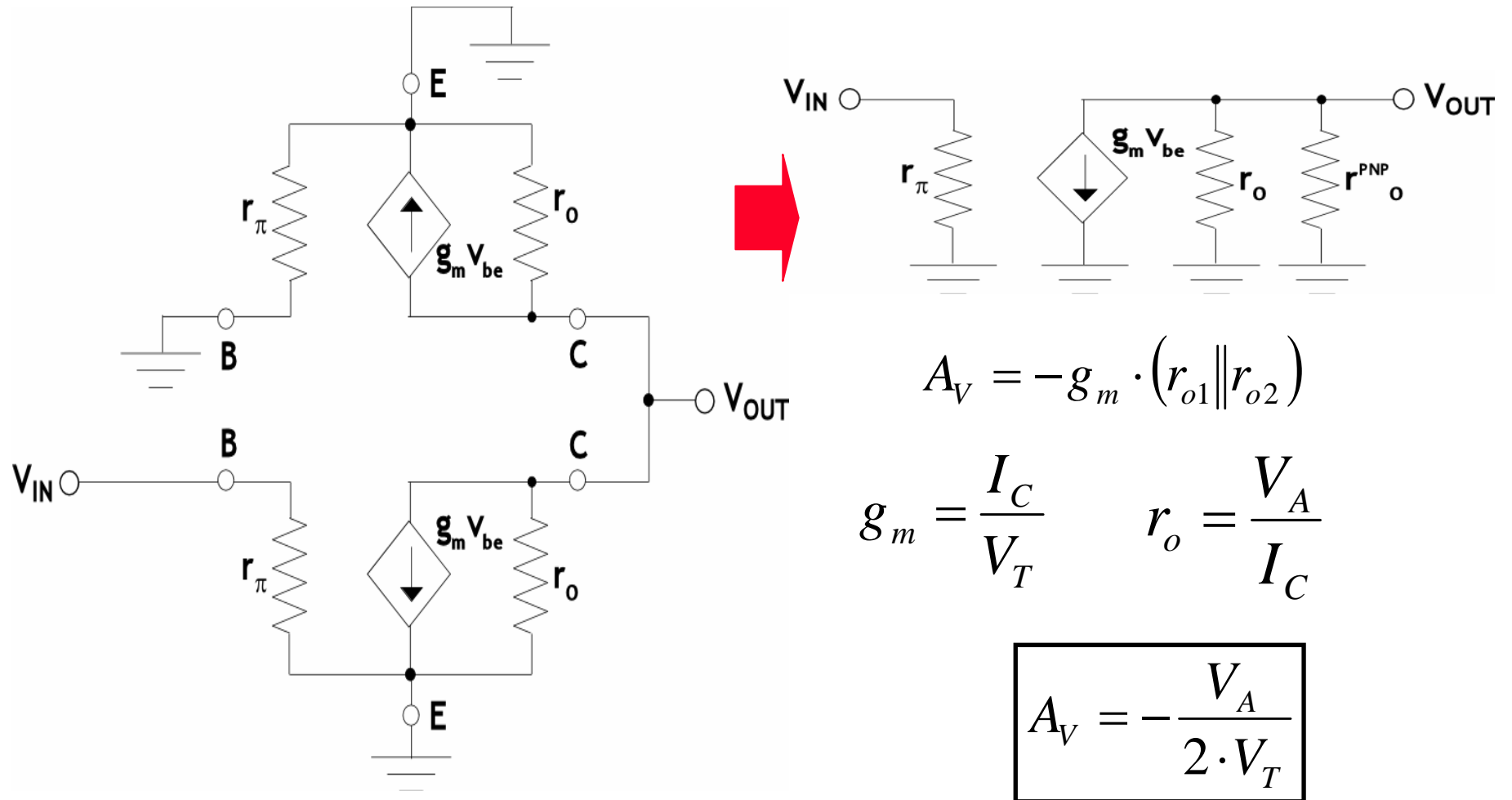



Current Mirrors

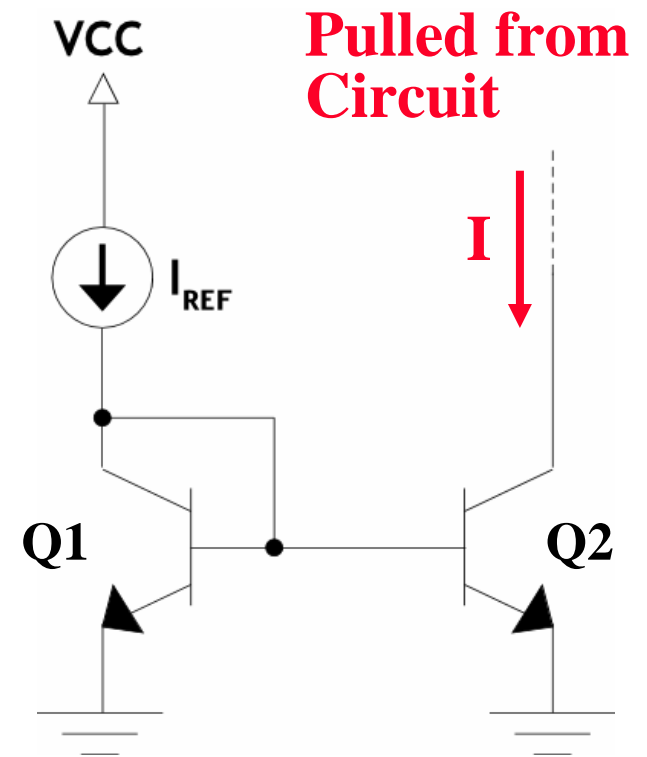- CBA and CCA conveniently biased with current sources
- On an IC, a current source is implemented using transistors
- I_{REF} can be implemented off-chip, resistor
- Transistor Q2 pulls current from attached circuit
- Collector current of Q1 and Q2 identical because of V_{BE} is the same (r_o neglected)






Current Mirror DC Analysis

- Neglect r_o (in EC1 DC analysis) and assume Q1 and Q2 active
- If Q1 has a collector current of I , then there must be a base current of I/β .
- This sets-up a Q1 V_{BE1} that is “mirrored” across to the base emitter of Q2, V_{BE2} .
- V_{BE2} draws a current of I from the Q2 collector.


$$I_{REF} = I + 2 \frac{I}{\beta}$$
 
$$\frac{I}{I_{REF}} = \frac{1}{1 + \frac{2}{\beta}}$$






Current Mirror DC Analysis

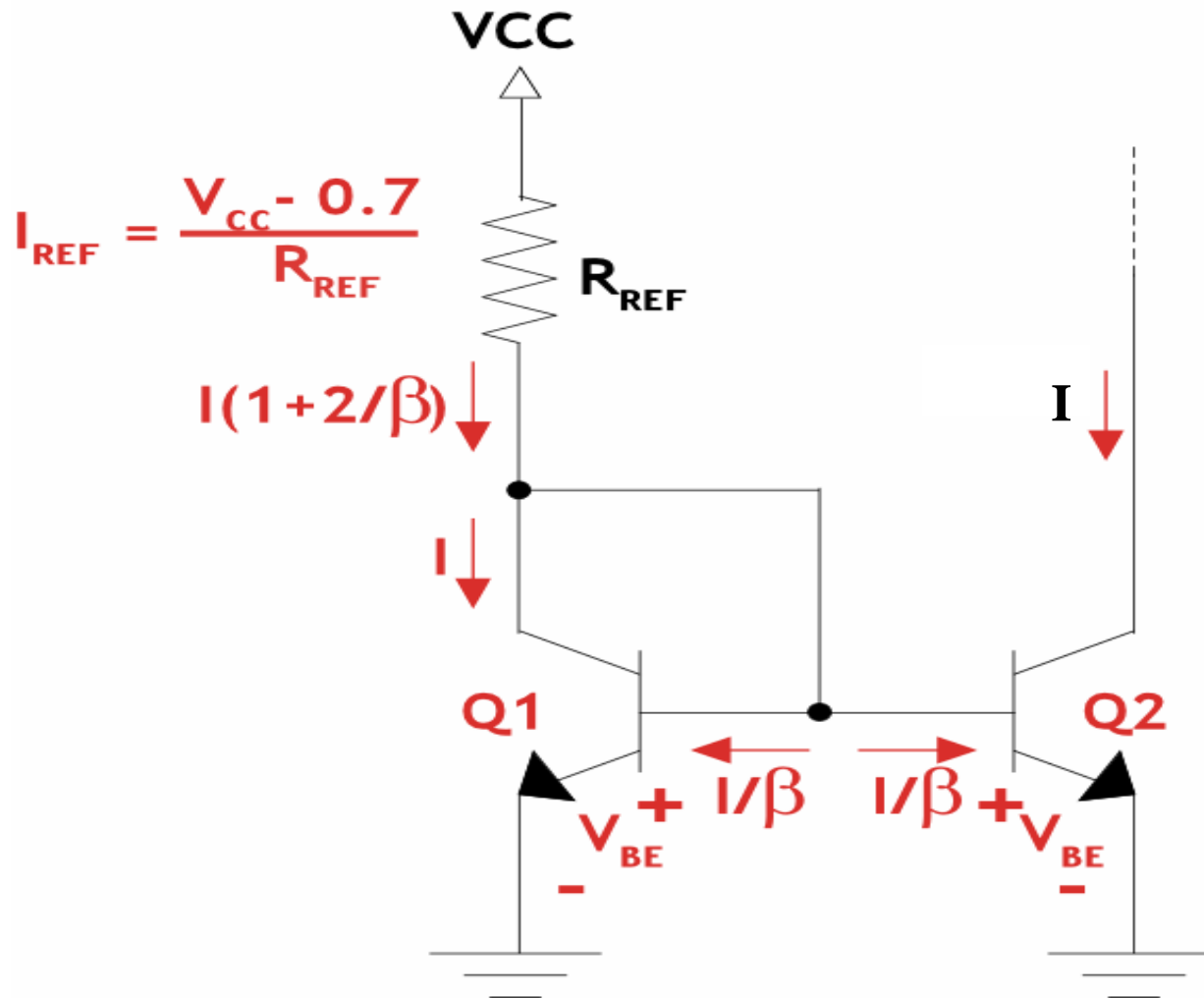



Current Mirror AC Analysis

 


Impact of current mirror is to add a load r_o to circuit that is drawing current

Note: In AC analysis r_o is included



Current Mirroring – Multiple Copies

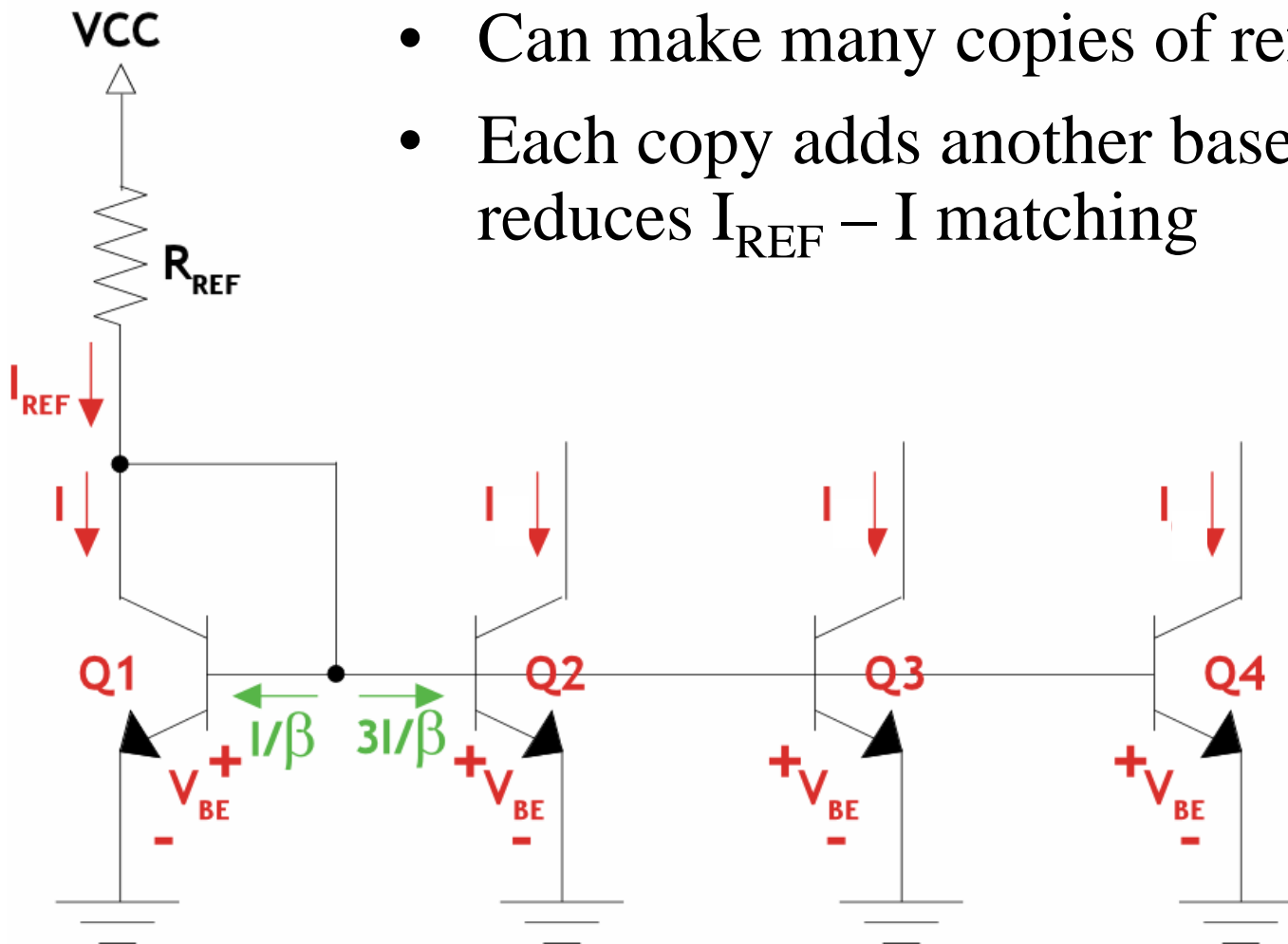- Can make many copies of reference current
- Each copy adds another base current draw, reduces $I_{REF} - I$ matching




$$\frac{I}{I_{REF}} = \frac{1}{1 + \frac{N+1}{\beta}}$$




Current Mirroring – Scaling

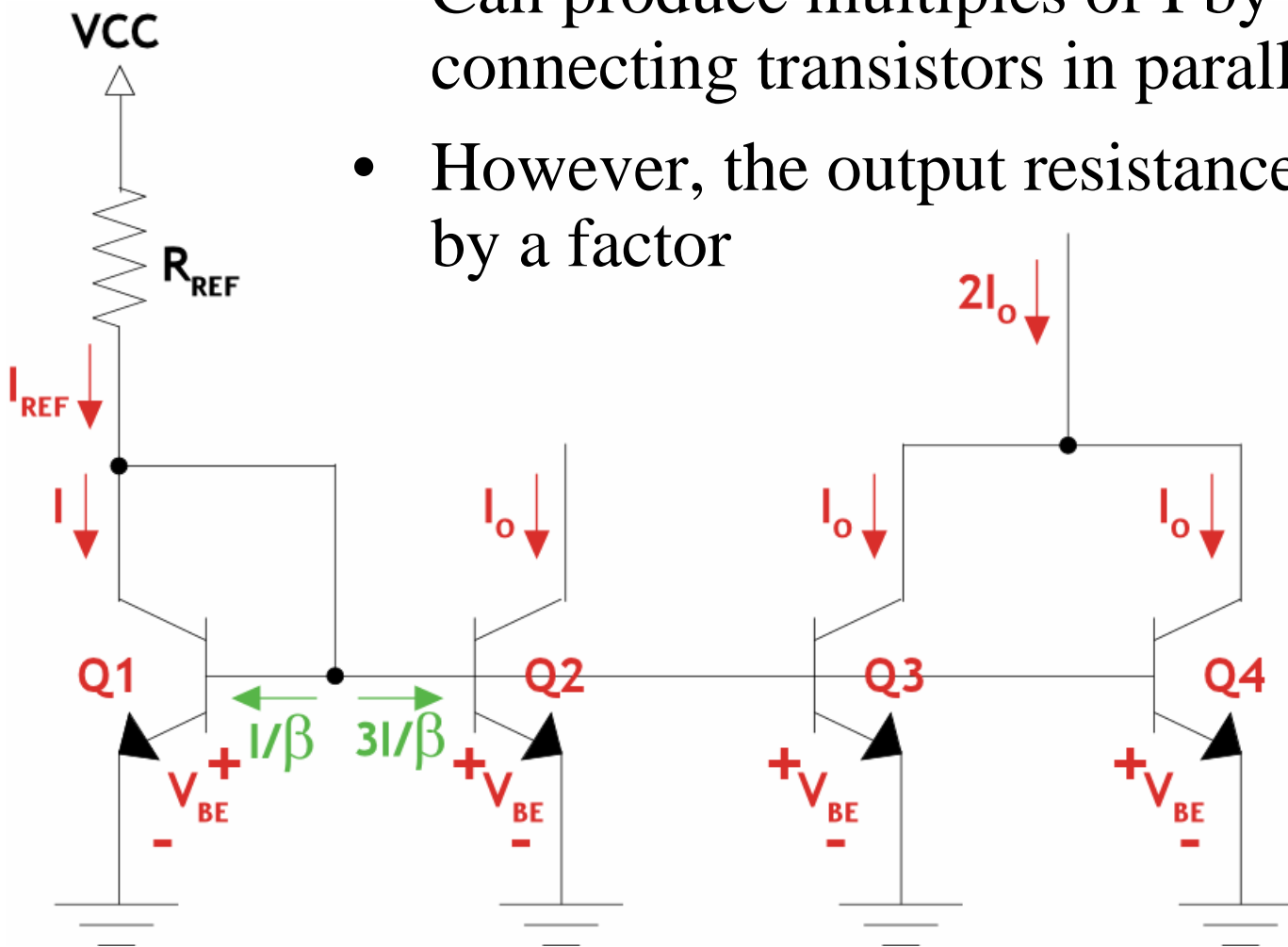- Can produce multiples of I by connecting transistors in parallel
- However, the output resistance is decreased by a factor





Current Mirroring – Pushing and Pulling

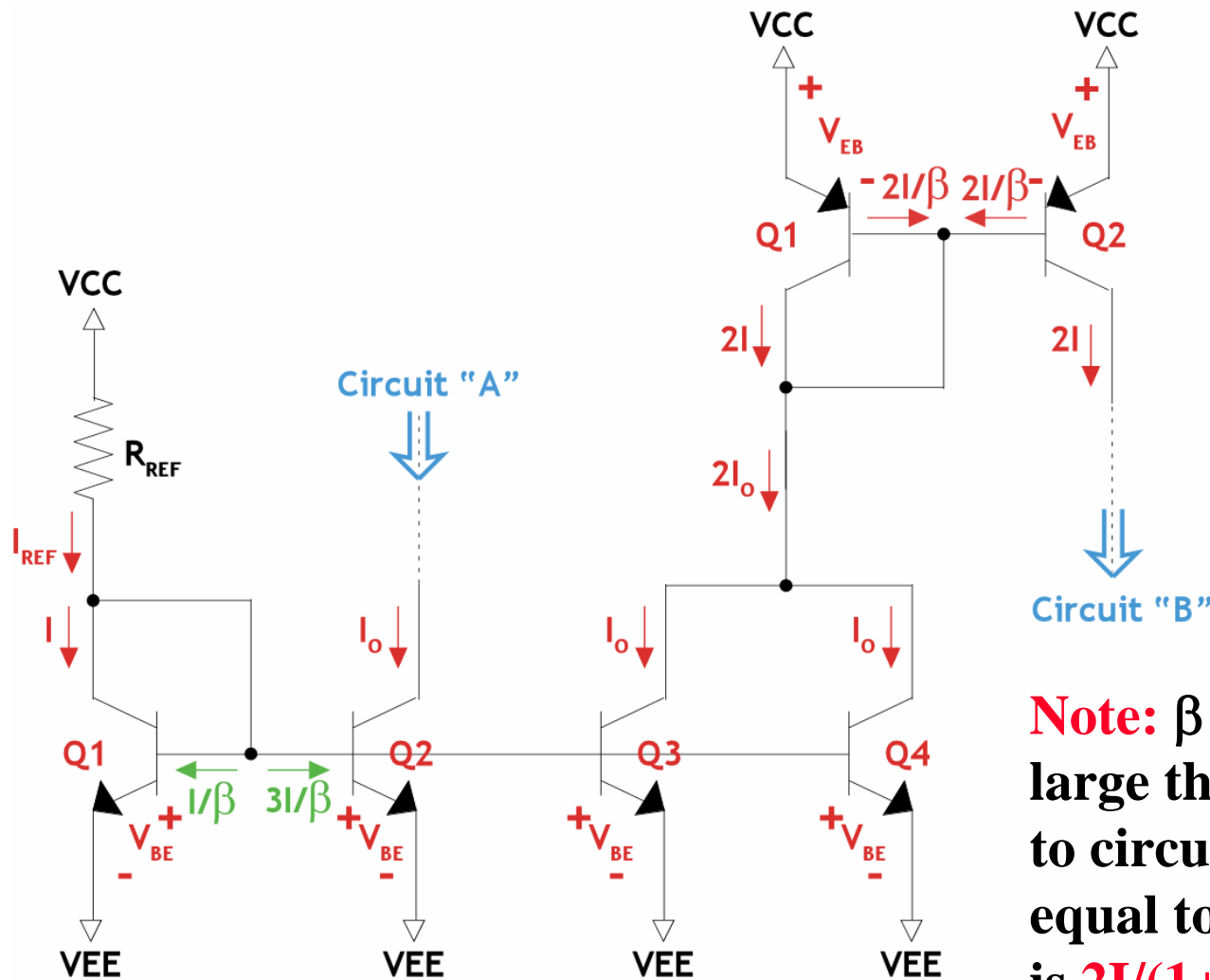

Note: β is assumed to be very large thus the current pushed to circuit B is approximated equal to $2I$. The exact answer is $2I/(1+2/\beta)$




Outline of Chapter 5

- 1- Cut-off and Saturation Modes
- 2- Digital Circuits



The npn BJT Operational Modes

 


4 Modes of operation

	B-E Junction	B-C Junction
Cutoff	reverse	reverse
Active	forward	reverse
Saturation	forward	forward
Reverse Active	reverse	forward



Cutoff Mode

 

- Cutoff mode:
 - B-E pn junction reverse-biased
 - B-C pn junction reverse-biased

- Reverse-bias drift currents are *SMALL*


- Drift currents:
 - From E to B
 - From C to B

4 Modes of operation

	B-E Junction	B-C Junction
Cutoff	reverse	reverse
Active	forward	reverse
Saturation	forward	forward
Reverse Active	reverse	forward



Saturation Mode

 


4 Modes of operation

	B-E Junction	B-C Junction
Cutoff	reverse	reverse
Active	forward	reverse
Saturation	forward	forward
Reverse Active	reverse	forward




Saturation Mode – Operation (1)

 

- Saturation mode:
 - B-E pn junction forward-biased
 - B-C pn junction forward-biased
- Electron diffusion current from E to B
 - Base recombination
 - Traverses base into collector
- Electron diffusion current from C to B
 - Base recombination
 - Traverses base into emitter



Saturation Mode – I_C , I_B , and I_E

 

- β (and α) as we know it only applies in active mode
- “new” β (β_{forced}) set by external components


$$V_{CE-SAT} = 0.2V$$

$$I_E = I_C + I_B$$

$$\beta_{forced} = \frac{I_C}{I_B}$$



Saturation DC Analysis

 

- For $R_C = 5k\Omega$, BJT enters saturation
- Apply voltage drop criteria, solve for currents

$$I_E = \frac{-0.7 + 5}{3.3k} = 1.303mA$$

$$I_C = \frac{5 + 0.5}{5k} = 1.1mA$$

$$I_B = I_E - I_C = 203\mu A$$

$$\beta_{forced} = \frac{I_C}{I_B} = \frac{1.1m}{203\mu} = 5.4 \ll \beta$$




Comments

- $\beta_{\text{forced}} \ll \beta$ in saturation
- Current directions (I_C , I_B , I_E) same as for active mode
- All concepts & expressions same for **PNP** in saturation

$$V_{EC-SAT} = 0.2V$$

$$I_E = I_C + I_B$$
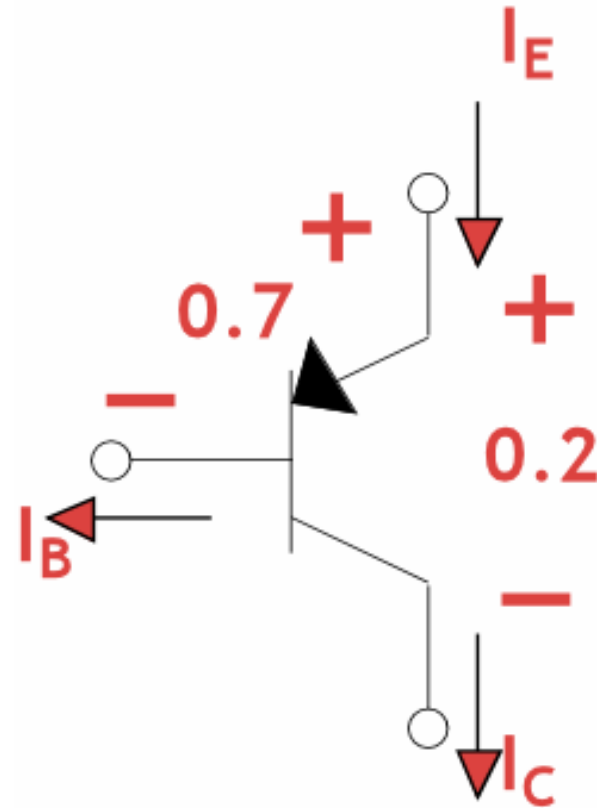
$$\beta_{\text{forced}} = \frac{I_C}{I_B}$$






CEA as an Inverter

- The large negative voltage gain of the CEA was:



$$A_{VO} = \frac{v_{out}}{v_{be}} = -g_m (r_o \parallel R_C)$$

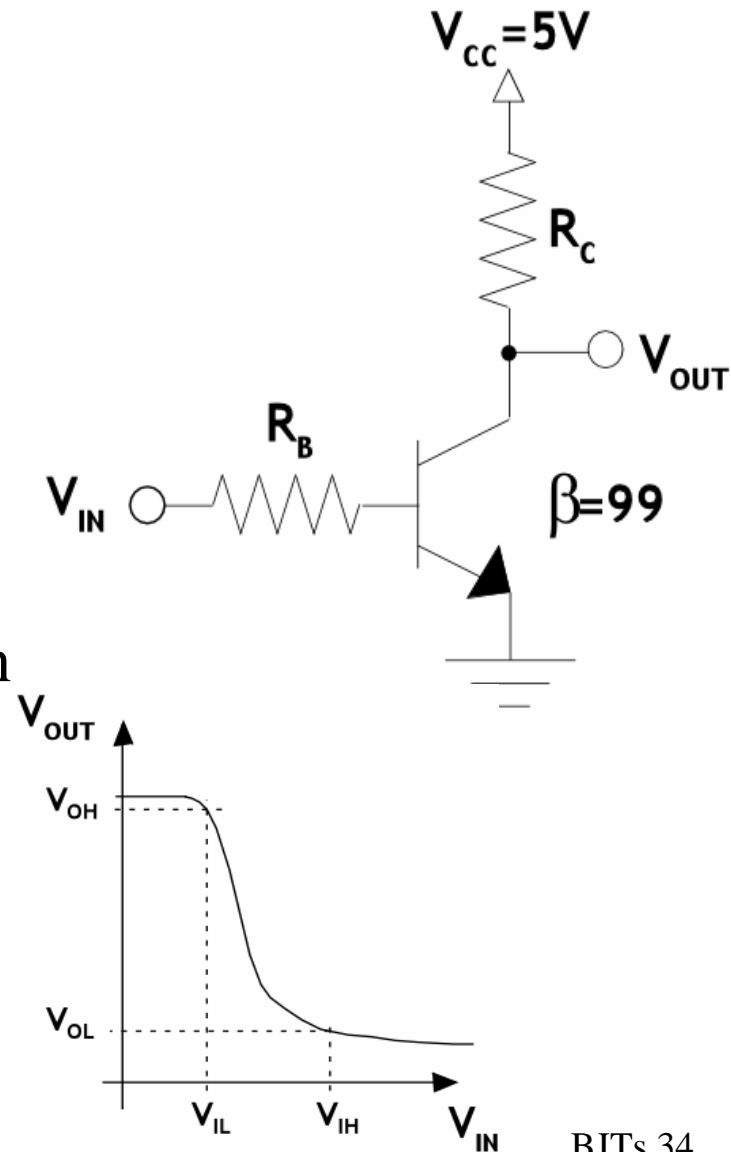- This produces a sharp linear region that describes V_{out}/V_{in} for device in active-mode.
- Max. output (cut-off) and min. output (saturation).
- Through analysis, we can describe the Voltage Transfer Characteristic (VTC)





CEA Inverter

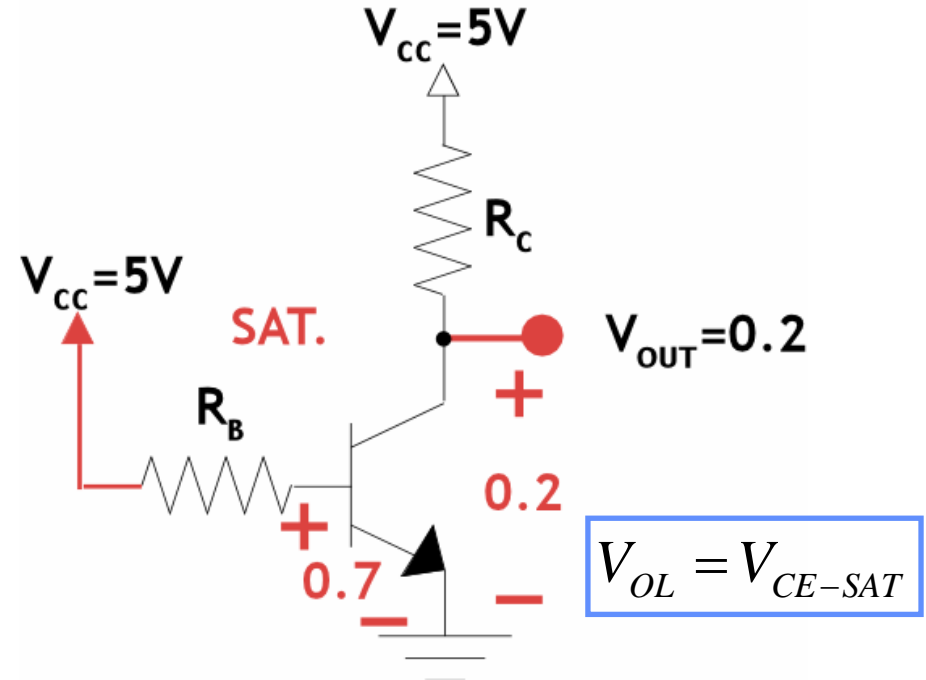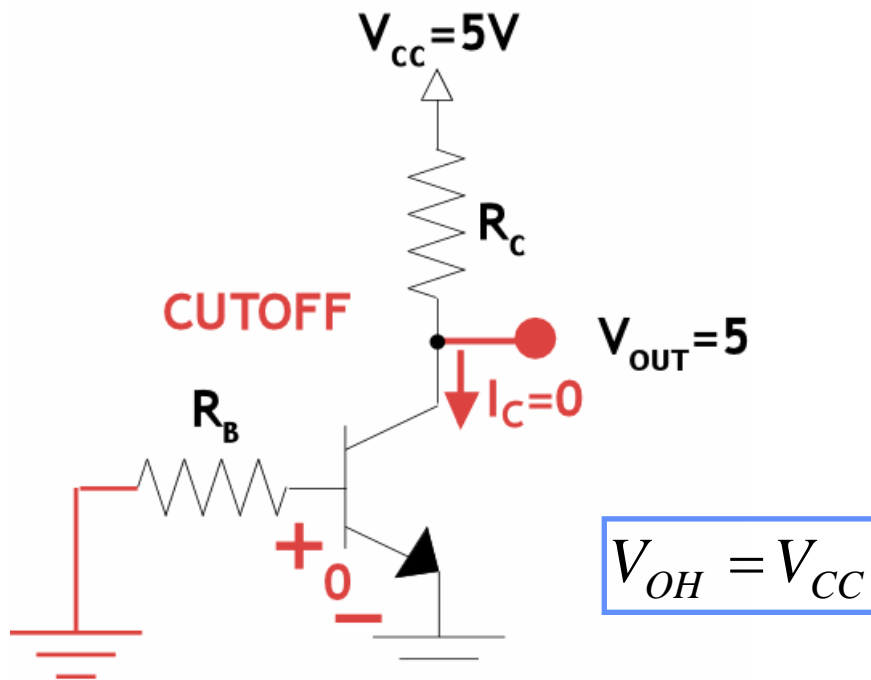

- When $V_{IN} = 0$
 - BJT is in cutoff
 - $I_C = 0$
 - $V_{OUT} = V_{CC}$


- When $V_{IN} = 5$
 - BJT is in saturation
 - $V_{OUT} = 0.2$



CEA Inverter - V_{IL}

- BJT remains in cutoff until $V_{IN} \approx 0.7V$, then enters active mode because B-E junction goes into FWD bias
- As V_{IN} rises in active mode, V_{OUT} decreases

$$V_{IL} \approx 0.7V$$

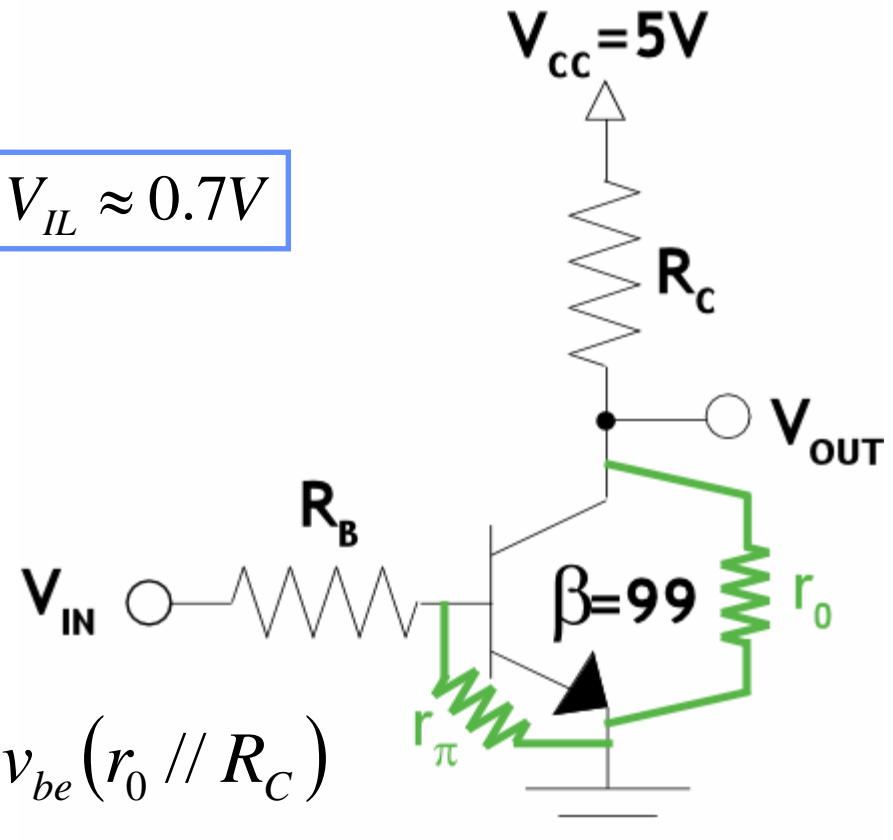

$$v_{be} = \frac{r_{\pi}}{r_{\pi} + R_B} v_{IN} \quad v_{OUT} = -g_m v_{be} (r_o // R_C)$$

$$A_V = \frac{v_{OUT}}{v_{IN}} = \frac{-g_m r_{\pi}}{r_{\pi} + R_B} (r_o // R_C) = \frac{-\beta}{r_{\pi} + R_B} (r_o // R_C)$$




CEA Inverter - V_{IH}

- To find V_{IH} :
 - Must use the “Edge-of-Saturation” (EOS)
 - The Max. I_B at the threshold of Active/Sat. defined as I_{B-EOS}

$$V_{IN} = 0.7 + I_B R_B$$
 
$$I_{B-EOS} = \frac{I_{C-SAT}}{\beta} = \frac{V_{CC} - V_{CE-SAT}}{\beta R_C}$$



$$V_{IH} = 0.7 + I_{B-EOS} R_B = 0.7 + \frac{V_{CC} - V_{CE-SAT}}{\beta R_C} R_B$$



CEA Inverter Voltage Transfer Characteristic (VTC)

Consider $V_{CC}=5V$, $R_B=10k\Omega$, $R_C=1k\Omega$, $\beta=100$, $V_A=100V$

Hand-analysis:

$$V_{IL} \approx 0.7V$$

$$V_{OL} \approx 0.2V$$

$$V_{OH} = 5V$$

$$V_{IH} = 1.18V$$


Noise margins:

$$NM_H = V_{OH} - V_{IH} = V_{CC} - 0.7V - I_{B-EOS}R_B$$

$$NM_L = V_{IL} - V_{OL} = 0.7V - V_{CE-SAT} = 0.5V$$

$$NM_H = 3.82V \quad NM_L = 0.5V$$


VTC (simulation)

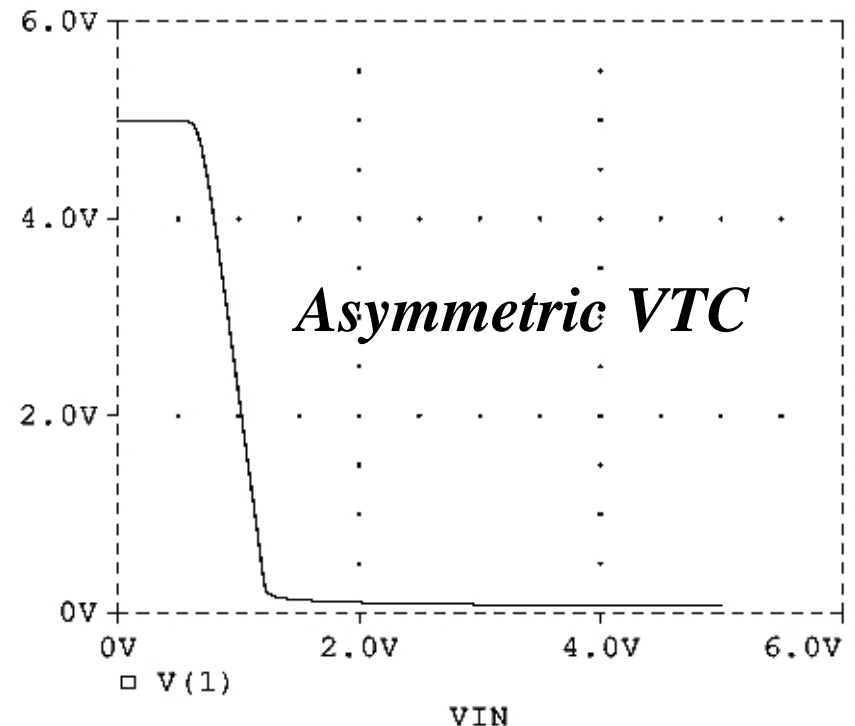



Resistor-Transistor Logic (RTL) Inverter

- Popular technology in 1960's

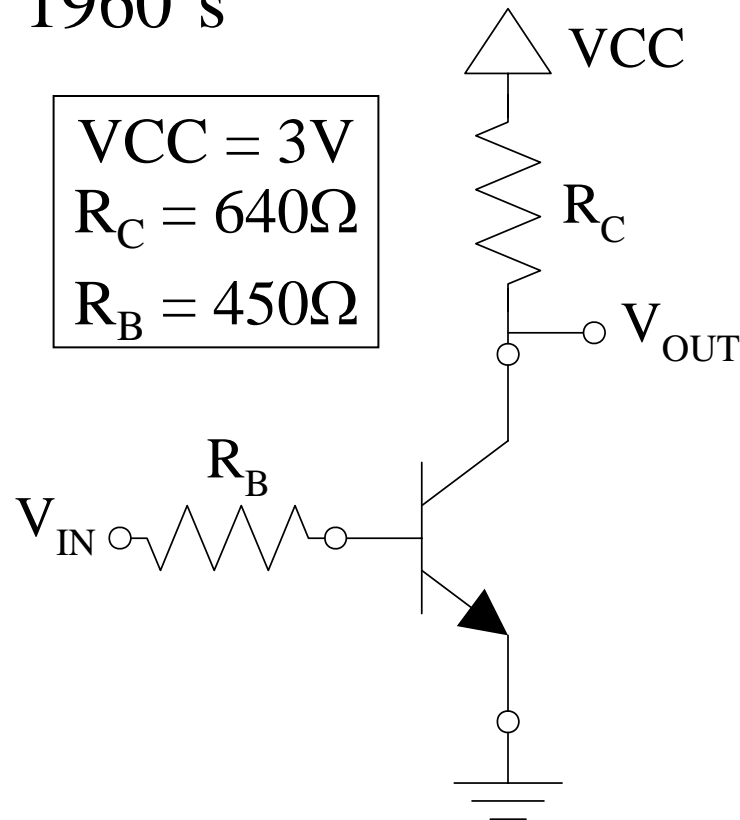

- Using equations:

$V_{IL} \approx 0.7V$	$V_{OL} \approx 0.2V$
$V_{OH} = 3V$	$V_{IH} = 0.72V$
$NM_H = 2.28V$	$NM_L = 0.5V$

More in EC2