



Course Evaluation

- On line course evaluation
- Accessible through WebCT account



ECSE-330: Introduction to Electronics Winter Session, 2008



What You Already Know (ECSE-210)

- Circuit models – resistors, capacitors, inductors
- KVL and KCL
- Branch relationships
- Resistive circuit analysis
- Network theorems including one and two port networks
- Steady state, transient and frequency analysis



What Was Covered

Chapter 1) Introduction to Analog and Digital Electronics

Sections 1.4-1.7

Chapter 3) The PN Junction and Diodes

Sections 3.1-3.7

Chapter 4) Field-Effect Transistors

Sections 4.1-4.10, (also 10.3, 6.3)

Chapter 5) Bipolar Junction Transistors

Sections 5.1-5.10, (also 6.3)

Chapter 2 was NOT covered



Upon Completion of the Course

- Design and analysis of circuits:
 - *Rectify signals* – diodes
 - *Amplify signals* – analog functions
 - *Digital circuits* – digital signal processing
- Design principles behind the realization of modern *Integrated Circuits (ICs)*
- An understanding of physical principles behind the operation of transistors and diodes
- Everything you need to know for ECSE-334, Electronic Circuits II.



Outline of Chapter 1

Analog Amplifiers

- Linear amplifiers and transfer characteristics
- Classification of ideal amplifier topologies and desirable properties
- Input/Output resistance

Digital Logic Inverters


- Voltage transfer characteristic
- Noise margins

Frequency Response

- STC circuits
- Transfer function
- Bode plots



Attach Source and Output Loads

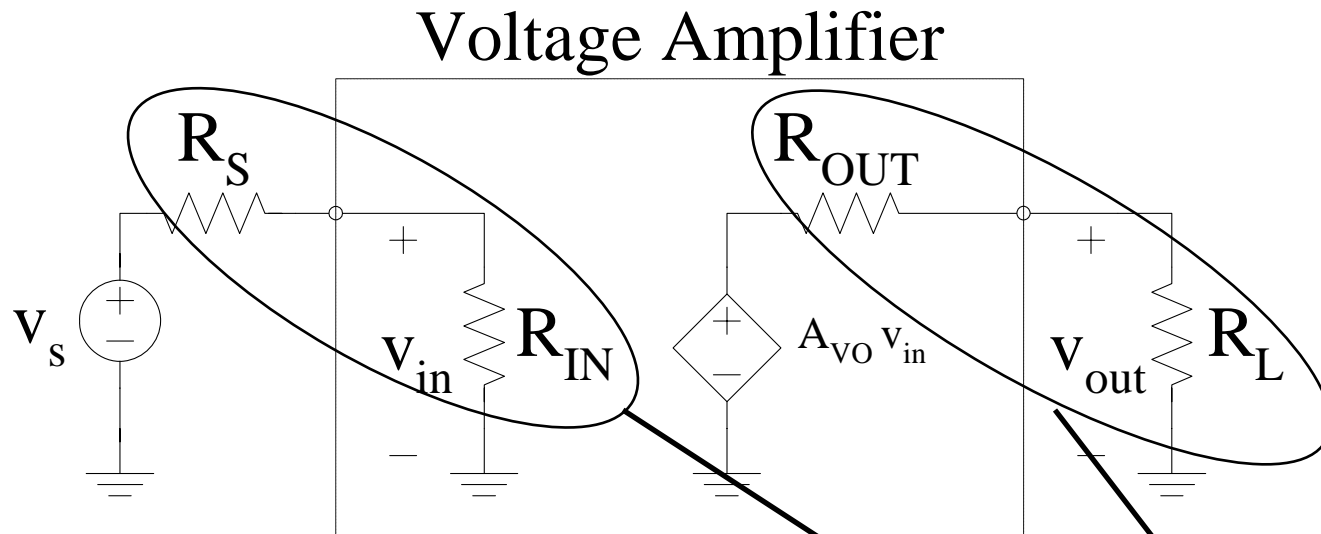

Compute Voltage Gain:
$$A_V = \frac{v_{out}}{v_s} = \frac{R_{IN}}{R_{IN} + R_S} \cdot \frac{R_L}{R_L + R_{OUT}} \cdot A_{VO}$$


- 1) $A_V < A_{VO}$ due to two voltage divisions: source and load
- 2) A_V maximized with large R_{IN} , small R_{OUT}



Finding R_{IN}

R_{IN} is the resistance “seen” between the input node and ground

 With input signal applied, v_{in} and i_{in} signals are established



$$R_{IN} = \frac{v_{in}}{i_{in}}$$


Important:

R_{IN} can usually
be obtained by
inspection



Finding R_{OUT}

 - Alternatively, one can determine R_{OUT} as follows:
 - “Kill” the input signal (set v_{in} or i_{in} to zero)
 - Apply a test voltage signal v_x to the output node
 - Determine the current i_x it supplies to the circuit




$$R_{OUT} = \frac{v_x}{i_x}$$



Cascaded Amplifier Stages

- e.g. cascaded voltage amplifiers:

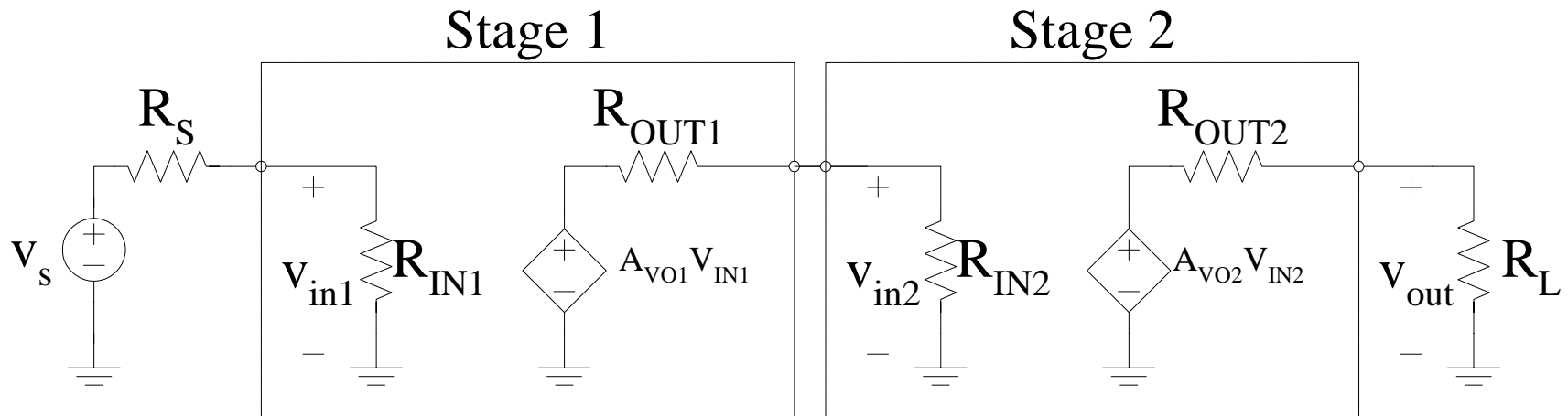

- By inspection, working from output to input:

$$A_V = \frac{v_{out}}{v_s} = \frac{R_L}{R_L + R_{OUT2}} \cdot A_{VO2} \cdot \frac{R_{IN2}}{R_{IN2} + R_{OUT1}} \cdot A_{VO1} \cdot \frac{R_{IN1}}{R_{IN1} + R_s}$$

- Equally simple for other amplifier cascades




Measuring Frequency Response

- The **frequency response** of an amplifier is completely known by the **magnitude (or amplitude) response** and **phase response**

$$|T(\omega)| = \frac{V_o}{V_i}$$

$$\angle T(\omega) = \phi$$

- Often the magnitude plot is given in decibels and $20\log|T(\omega)|$ is plotted versus frequency

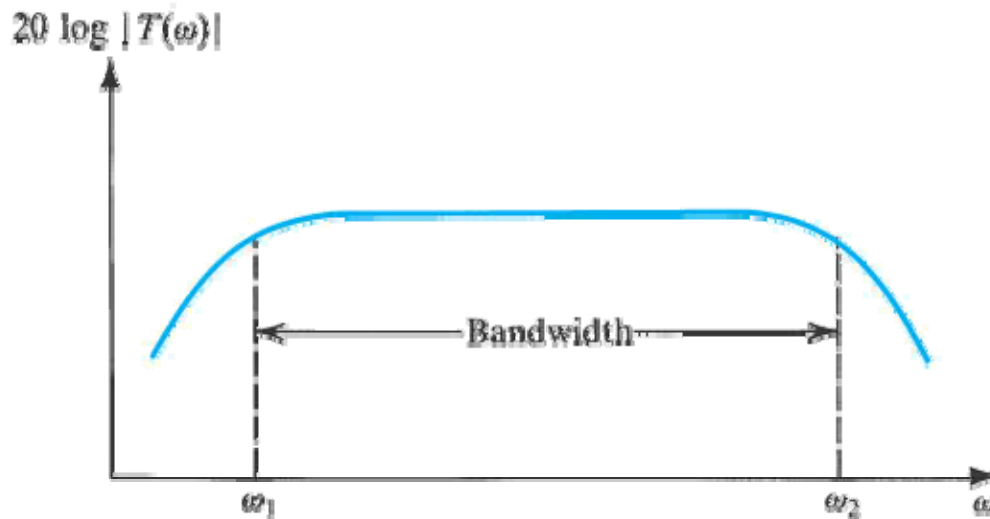




Outline of Chapter 3 - Diodes

- Exponential model
- Constant voltage drop model
- Applications
- Small-signal model
- PN junctions



 Diode Symbol and Terminal Characteristics




Exponential model:
$$i = I_S \left(e^{\frac{v}{nV_T}} - 1 \right)$$



The Constant Voltage Drop Model (CVDM)

 - Exponential model gives accurate results; requires hand computation or a simulator
- The constant voltage drop model (CVDM) used to perform quick analysis of a diode circuit by hand
- CVDM approximates diode I-V curve piecewise-linearly





Small-Signal Analysis Technique Summary

- Tool for analyzing the behavior of circuits that employ active devices and small signals
- Through linearization of exponential model, can separate DC & AC analysis; linear superposition
- Analysis procedure
 - Turn off AC sources, solve for DC operating point
 - Based on DC operating point parameters, solve for small signal-signal equivalent circuit model parameters
 - Construct small-signal equivalent circuit; short circuit voltage sources and open circuit current sources
 - Solve for AC parameters


Outline of Chapter 4

- Introduction to MOS Field Effect Transistor (MOSFET)
- NMOS FET
- PMOS FET
- DC Analysis of MOSFET Circuits
- MOSFET Amplifier
- MOSFET Small Signal Model
- MOSFET Integrated Circuits
- CSA, CGA, CDA
- CMOS Inverter & MOS Digital Logic
- High frequency model and Frequency response of CSA




nMOS Circuit Symbol

 - A MOSFET is a *four-terminal* device
- Body terminal *always* biased at *most negative* potential



 
- Simplified symbol with implicit Body terminal connection
- Arrow indicates direction of current






pMOS Circuit Symbol

 - A MOSFET is a *four terminal* device
- Body terminal *always* biased at *most positive* potential



 - Simplified symbol with implicit Body terminal connection
- Arrow indicates direction of current flow






Summary of Enhancement nMOS FET I-V Characteristics

Cutoff: $V_{GS} < V_t$ $I_D = 0$

Triode: $V_{GS} > V_t$
 $V_{DS} < V_{GS} - V_t$ $I_D = k'_n \frac{W}{L} \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$

Saturation: $V_{GS} > V_t$
 $V_{DS} > V_{GS} - V_t$ $I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$

 Body effect: $V_t = V_{t0} + \gamma \left(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$






Summary of pMOS FET I-V Characteristics

Cutoff: $V_{GS} > V_t$ $I_D = 0$

Triode: $V_{GS} < V_t$ $I_D = k'_p \frac{W}{L} \left[(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2 \right]$
 $V_{DS} > V_{GS} - V_t$

Saturation: $V_{GS} < V_t$ $I_D = \frac{1}{2}k'_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$
 $V_{DS} < V_{GS} - V_t$


Body effect: $|V_t| = |V_{t0}| + \gamma \left(\sqrt{2\phi_f + |V_{SB}|} - \sqrt{2\phi_f} \right)$

 

Note: V_{GS} , V_{DS} , V_{SB} , V_t , λ , are all NEGATIVE




Hybrid- π Small Signal Model

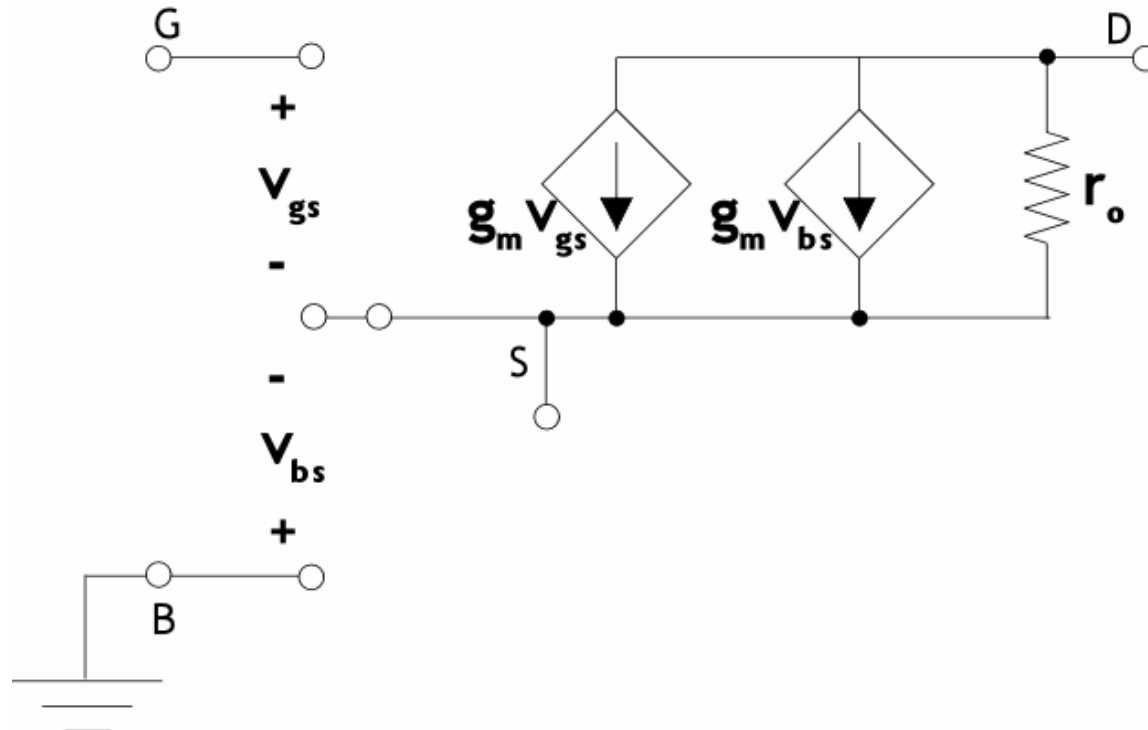

- AC Body effect: another VCCS (dependent on g_{mb}) in parallel with the one dependent on g_m
- T model generally not used when modeling Body effect, regardless of circuit topology



The MOSFET T Small Signal Model

 




Outline of Chapter 5

- Introduction to The Bipolar Junction Transistor
- Active Mode Operation of the npn and pnp BJTs
- DC Analysis of BJT Circuits
- BJT as an Amplifier
- BJT Small Signal Models
- CEA, CEA with R_E , CBA, & CCA
- Integrated Circuit Amplifiers
- High-frequency model and frequency response




Bipolar Junction Transistor (BJT)

 - 3 terminal device in which the voltage across 2 terminals controls the current flowing in/out of a 3rd terminal:



npn BJT

 

pnp BJT



Summary of npn Active Mode Characteristics


$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$I_B = \frac{I_C}{\beta} \quad r_o = \frac{V_A}{I_C}$$

$$I_C = \alpha I_E; \quad \alpha = \frac{\beta}{\beta + 1} \approx 1$$

$$I_E = (\beta + 1)I_B$$

$$I_E = I_C + I_B$$

 

$$V_C \geq V_B > V_E; \quad V_{BE} \approx 0.7V$$



Summary of pnp Active Mode Characteristics


$$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) \left(1 + \frac{V_{EC}}{V_A}\right)$$

$$I_B = \frac{I_C}{\beta} \quad r_o = \frac{V_A}{I_C}$$

$$I_C = \alpha I_E; \quad \alpha = \frac{\beta}{\beta + 1} \approx 1$$

$$I_E = (\beta + 1)I_B$$

$$I_E = I_C + I_B$$

 


$$V_E \geq V_B > V_C; \quad V_{EB} \approx 0.7V$$



Hybrid- π Small Signal Models


VCCS based model

 

$$i_b = \frac{v_{be}}{r_\pi}$$

$$r_\pi = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

CCCS based model

 


$$g_m v_{be} = (g_m r_\pi) i_b = \beta i_b$$




T-Models

VCCS based model

 

CCCS based model

 


$$i_e = \frac{v_{be}}{r_e} \quad r_e = \frac{\alpha}{g_m} = \frac{V_T}{I_E}$$

$$g_m v_{be} = (g_m r_e) i_e = \alpha i_e$$



Beginning of the Transistor Era

 
- 1st transistor – invented in 1947 at Bell Laboratories.
- Invented by Brattain and Bardeen.
- PNP point-contact germanium transistor.
- Operated as a speech amplifier with a power gain of 18.





And now?

 - The Pentium IV with 55 million transistors
- These transistors are located in an area of $\sim 12 \text{ mm} \times 12 \text{ mm}$
- $0.13 \mu\text{m}$ technology, $0.09 \mu\text{m}$ technology is also available







And now?


- Feb. 2005, *IEEE International Solid-State Conference (ISSCC)*
- CELL Processor (designed and developed by SONY, Toshiba, IBM):
 - The first consumer exposure was in Sony's PlayStation 3 game console
 - 4 GHz, 1.1V V_{dd}, BGA package (42.5 mm by 42.5 mm), 90 nm process
 - One sample operate at 5.6 GHz with 1.4V V_{dd}
- CMOS used for short-range wireless communications at 60 GHz, 0.13 μ m technology
 - Wireless-LAN ICs delivered as single-chip solutions, built in CMOS at foundries in Taiwan.
 - Texas Instruments Inc. shakes up the cost-sensitive handset market with baseband-plus-RF parts made in 90-nanometer CMOS.



Near Future

  - We want to develop Personal Area Networks using CMOS wireless electronics



 



Final Exam Topics

- Amplifiers
 - General amplifier analysis and frequency response
- Diodes:
 - DC analysis including exponential and CVD
 - Small signal analysis including diode small signal resistance
 - Applications and circuits
- FETs:
 - NMOS, PMOS
 - DC analysis
 - Cut-off/triode/saturation behavior
 - Small signal modeling including CSA, CGA, CDA
 - Multistage amplifiers
 - Body effect and Channel Length Modulation (DC and small signal)
 - Current mirrors – DC and small signal
 - High frequency model and frequency response of CSA



Final Exam Topics

- BJT's:
 - NPN, PNP
 - DC analysis
 - Cut-off/saturation/active behavior
 - Small signal modeling including CEA, CEA with RE, CBA, CCA
 - Early effect
 - Multistage amplifiers
 - Current mirrors – DC and small signal
 - High frequency model and frequency response of CEA

All topics including physics, derivations, problem solving and numerical calculation



ECSE-330: Electronic Circuits I
Winter Session, 2008

Good Luck,
and
Have a great
Summer!