



McGill

Introduction to SPICE

ECSE 330 Introduction to Electronics

**Department of Electrical and Computer Engineering
McGill University**

SPICE

- **SPICE (Simulation Program with Integrated Circuits Emphasis!):**
 - Circuit simulation program.
 - Provides detailed analysis of circuits containing lumped components (R, L, C) and active components (diodes, FETs, BJTs).

- **PC Version:**
 - Pspice A/D (part of Orcad 10.0)
 - Available on the machines on the 4th and 5th floor of the Trottier.
 - You can download PSPICE 9.1 (student edition) it from the following link at your own risk:
<http://electronics-lab.com/downloads/schematic/013/>

- **Resources:**
 - “Spice for Microelectronics” by Roberts and Sedra, 2nd edition.
 - Interactive User Guide from
<http://bwrc.eecs.berkeley.edu/Classes/IcBook/SPICE>

PSpice A/D

- Models the behavior of a circuit containing any mix of analog and digital devices.

- Basic analyses:
 - DC analysis: DC sweep, bias point, DC sensitivity, small-signal DC gain, and input and output resistances.
 - AC analysis: small-signal response over a range of frequencies and noise.
 - Transient analysis: time-domain response and Fourier analysis.

Spice Input File (Deck)

□ Suggested input format:

Title Statement
****Comment

*Title statement is always on the first line.
Comment always begins with an asterisk (*).*

Circuit Description
Power Supplies / Sources
Element Description
Model Statements

Elements must be uniquely labeled (up to 8 characters, 1st character identifies the type of the element). Connections are represented by nodes, which are usually numbered. Node "0" means ground.

Analysis Requests

Output Requests

.END

The last line must end with an .END.

□ Additional Notes:

- Order is not important, except the first and last lines.
- NOT case sensitive.
- Words can be separated by an arbitrary number of spaces.

Input File Example

Title → Low pass filter

The “+” sign means that the previous command is continued on this line.

```
** Circuit Description **  
* Power supply  
Vin 1 0 PWL(0s, 0V,1ms,0V,  
+ 1.0001ms, 1V)
```


```
* Elements description  
R1 1 2 1Kohm  
C1 2 0 1uF
```

Positive Terminal (n+)

Negative Terminal (n-)

```
*Analysis request  
.OP  
.Tran 0.1ms 5ms  
.END  
.end
```

← .END command

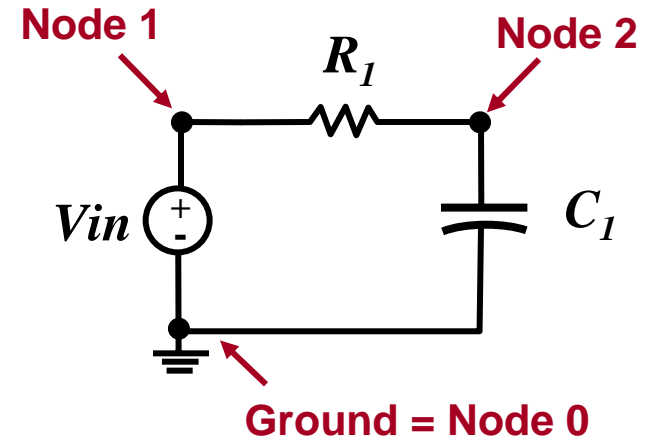

Basic Element Types in Spice

1st Letter Presentation

Element

B	GaAs field-effect transistor (MESFET)
C	Capacitor
D	Diode
E	Voltage-controlled voltage source (VCVS)
F	Current-controlled current source (CCCS)
G	Voltage-controlled current source (VCCS)
H	Current-controlled voltage source (CCVS)
I	Independent current source
J	Junction field-effect transistor (JFET)
K	Coupled inductors
L	Inductor
M	MOS field-effect transistor (MOSFET)
Q	Bipolar transistor (BJT)
R	Resistor
V	Independent voltage source

Scale-factor Abbreviations in Spice

<u>Power-of-Ten Suffix Letter</u>	<u>Metric Prefix</u>	<u>Multiplying Factor</u>
T	tera	10^{12}
G	giga	10^9
Meg	mega	10^6
K	kilo	10^3
M	mili	10^{-3}
U	micro	10^{-6}
N	nano	10^{-9}
P	pico	10^{-12}
F	femto	10^{-15}

Element Dimensions

<u>Spice Suffix</u>	<u>Units</u>
V	Volts
A	Amps
Hz	Hertz
Ohm	Ohm
H	Henry
F	Farad
Degree	Degree
S	Seconds

Circuit Elements – Two Terminal

□ **Resistor**

Rname n+ n- value



□ **Capacitor**

Cname n+ n- value [IC = initial_voltage_condition]



□ **Inductor**

Lname n+ n- value [IC = initial_current_condition]



□ **Diode**

Dname n+ n- dmodel

.model dmodel D (I_s=1nA n=1)



Independent Sources

Voltage source:




Spice Description

Type of Analysis

$Vname$ n+ n-	DC <i>value</i>	All types
$Vname$ n+ n-	AC <i>Magnitude Phase_deg</i>	AC Frequency Response
$Vname$ n+ n-	SIN (V_o V_a <i>freq</i> t_d <i>damp</i>)	Transient
$Vname$ n+ n-	PULSE (V_1 V_2 t_d t_r <i>PW</i> <i>T</i>)	Transient
$Vname$ n+ n-	PWL (t_1, V_1 t_2, V_2 ... t_n, V_n)	Transient


Current source:

 

The Spice description for an independent current source is the same as the voltage source, except replace “V” by “I”.

Field-Effect Transistors (FETs)

□ NMOS

 


Spice description:

Mname drain gate source substrate *MOS_model_name* L=*value* W=*value*
.MODEL *MOS_model_name* **NMOS** (*parameter_name=value ...*)

Example:

```
M1 2 0 3 3 nmos_enhancement_mosfet L=10u W=400u  
.model nmos_enhancement_mosfet nmos (kp=20u Vto=2V lamda=0)
```

□ PMOS

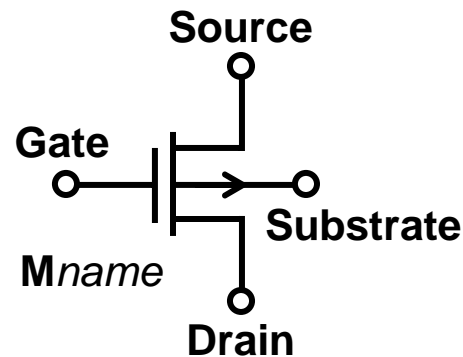


Spice description:

Mname drain gate source substrate *MOS_model_name* L=*value* W=*value*
.MODEL *MOS_model_name* **PMOS** (*parameter_name=value ...*)

Bipolar Junction Transistors (BJTs)

□ NPN Transistor

 


Spice description:

```
Qname collector base emitter [substrate] BJT_model_name [#_in_parallel]  
.MODEL BJT_model_name NPN (parameter_name=value ...)
```

Example:

```
Q1 2 0 3 npn_transistor  
.model npn_transistor npn (Is=1.8104e-15 Bf=100)
```

□ PNP Transistor

 

Spice description:

```
Qname collector base emitter [substrate] BJT_model_name [#_in_parallel]  
.MODEL BJT_model_name PNP (parameter_name=value ...)
```

Subcircuit

- Some circuit elements are not always available in the Spice library, *e.g.*, op-amps. To add an op-amp to the Spice deck, a “subcircuit” that represents this op-amp can be defined and incorporated into the main circuit.
- The definition in SPICE for a subcircuit is as follows:

```
.SUBCKT subcircuit_name list_of_nodes  
    Circuit Description  
.ENDS
```

- To incorporate the subcircuit into the main design, use the following statement, which starts with the letter “X”:
Xname node_connections *subcircuit_name*

Analysis Requests

Analysis Requests: specify the types of simulations to be performed.

Analysis Requests

Spice Command

Operating point

.OP

(Calculates DC node voltages and DC currents through voltage sources.)

Transfer Function

.TF

(Calculates small-signal gain from input to output, input resistance, and output resistance.)

DC sweep

.DC *[type] variable start_value stop_value step_value*

AC frequency response

.AC DEC *points_per_decade freq_start freq_stop*

.AC OCT *points_per_octave freq_start freq_stop*

.AC LIN *total_points freq_start freq_stop*

Transient response

.TRAN *time_step time_stop [(no_print_time Max_step_size)]*

DC Sweep

- ❑ **Syntax:** `.DC [type] variable start_value stop_value step_value`
- ❑ *Variable* can be a source name, a model parameter or temperature.
- ❑ DC operating point is calculated for each sweep.
- ❑ Sweep types:
 - LIN (linear sweep – default)
 - OCT (octave sweep)
 - DEC (sweep by decade)
 - LIST (list of values)
- ❑ Examples:
 - `.DC Vin -1.2 1.2 0.2`
 - ❑ Linearly sweeps Vin from -1.2V to +1.2V in 0.2V steps.
 - `.DC DEC Ibias 1u 5m 5`
 - ❑ Sweeps Ibias from 1uA to 5mA using 5 points/decade.

Output Requests

Output Requests: specify the outputs to be displayed.

Analysis Requests

Print data points
(tabulated data)

Spice Command

.PRINT DC *output_variables*
.PRINT AC *output_variables*
.PRINT TRAN *output_variables*

Plot data points
(tabulated data)

.Plot DC *output_variables* [(*lower_plot_limit* *upper_plot_limit*)]
.Plot AC *output_variables* [(*lower_plot_limit* *upper_plot_limit*)]
.Plot TRAN *output_variables* [(*lower_plot_limit* *upper_plot_limit*)]

Output Processing

.Probe
(saves simulated results for post-processing and plots)

Notes:


- 1) Spice *output_variables* can be a voltage at any node $V(\text{node})$, the voltage between two nodes $V(\text{node1}, \text{node2})$, or the current through a voltage source $I(V\text{name})$.
- 2) AC *output_variables* can also be
Vr, Ir: real part
Vi, li: imaginary part
Vm, Im: magnitude
Vp, Ip: phase
Vdb, Idb: decibels

Spice Implementation

- Steps to Identify your circuit:
 - Identify circuit elements
 - Identify node names
 - Write the netlist
 - Use appropriate models.
 - Specify the simulation type you want.


Spice Example 1 (1)

□ Circuit Schematic

 


Spice Example 1 (2)

□ Identify Circuit Elements

 

Spice Example 1 (3)

- Identify Node Names

 

Spice Example 1 (4)

□ Writing the Netlist

*Sources

```
VCC 3 0 10V
```

```
Vs1 1 0 SIN (5V 2.5V 50)
```

*Elements

```
M1 2 1 0 0 nmos_330 L=20u W=100u
```

```
Rd 3 2 10k
```

*Model statements

```
.MODEL nmos_330 nmos (kp=20u  
+Vto= +1V lambda=0.1)
```


*In the case of continuation in the
*new line use '+' at the first of new line.

*Analysis requests

```
.TRAN 1m 5 0 1m
```


```
.PROBE
```

```
.END
```

 

Spice Example 2 (1)

 - Identify circuit elements.
- Identify node names.
 - A Node name can be alphabetically named, such as VCC and VSS.



Spice Example 2 (2)

□ Netlist

```
*Sources
V1 VCC 0 10V
Vs1 1 0 SIN (5V 2.5V 50)
*Elements
M1 OUT 1 0 0 nmos_330 L=20u W=100u
M2 OUT 1 VCC VCC pmos_330 L=20u
+W=400u

*Model statements
.MODEL nmos_330 nmos (kp=20u
+Vto= +1V lambda=0.1)
.MODEL pmos_330 pmos (kp=20u
+Vto=-1V lambda=0.1)

*Analysis requests
.TRAN 1m 5 0 1m
.PROBE
.END
```

