
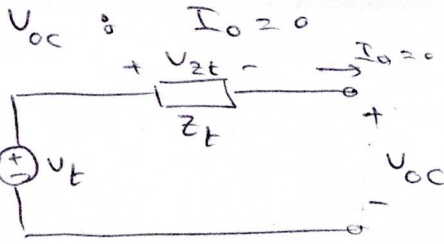


Solutions to Assigned Problems from Appendix C


C.1)

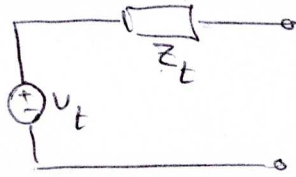

$$V_{oc} = V_t - V_{Z_t} = V_t - 0 \times Z_t$$

$$\Rightarrow V_{oc} = V_t$$


$I_{sc} : V_o = 0$

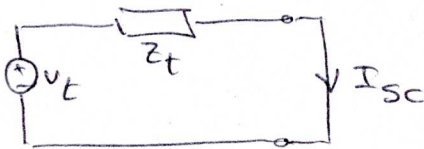


$$I_{sc} = \frac{V_t}{Z_t}$$

$$\Rightarrow Z_t = \frac{V_{oc}}{I_{sc}}$$

C.2)

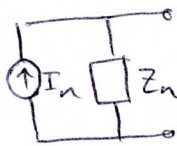


$V_{oc} : I_o = 0$

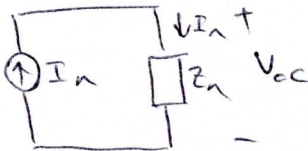

$$V_{oc} = Z_n I_n$$

$I_{sc} : V_o = 0$

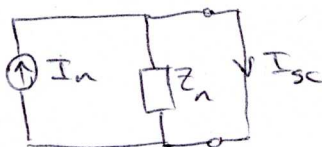


$$I_{sc} = \frac{Z_n}{Z_n + 0} I_n = I_n$$


$$\Rightarrow Z_n = \frac{V_{oc}}{I_{sc}}$$

Solutions to Assigned Problems from Appendix C

C.3)

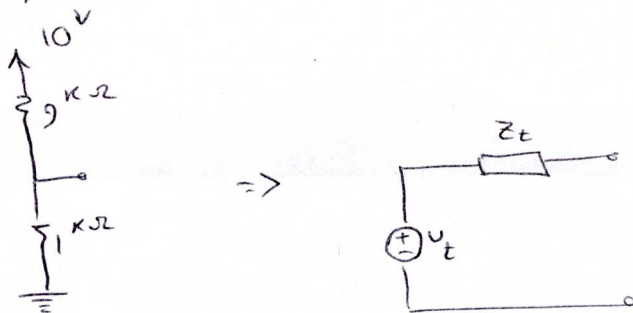


$V_t = V_{OC}$

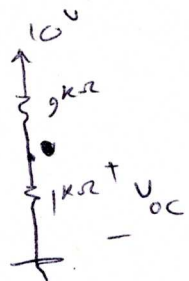


$$V_{OC} = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 9} \times 10 \text{ V} = 1 \text{ V}$$


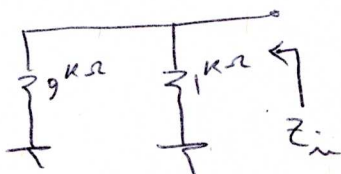
Z_t : independent sources $\rightarrow 0$


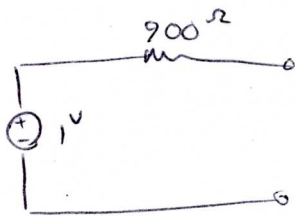
$$Z_{in} = Z_t = 1 \text{ k}\Omega \parallel 9 \text{ k}\Omega = 0.9 \text{ k}\Omega$$




$Z_{load} = 1 \text{ k}\Omega$

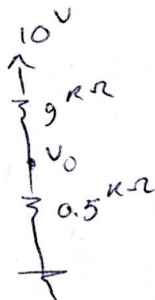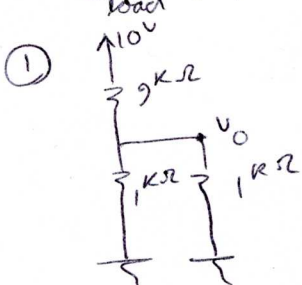

$$V_0 = \frac{0.5 \text{ k}\Omega}{9 \text{ k}\Omega + 0.5 \text{ k}\Omega} \times 1 \text{ V} = 0.526 \text{ V}$$


②

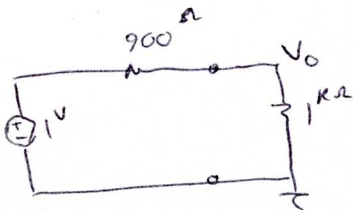

$$V_0 = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 0.9 \text{ k}\Omega} \times 1 \text{ V} = 0.526 \text{ V}$$


Solutions to Assigned Problems from Appendix C

C.4)

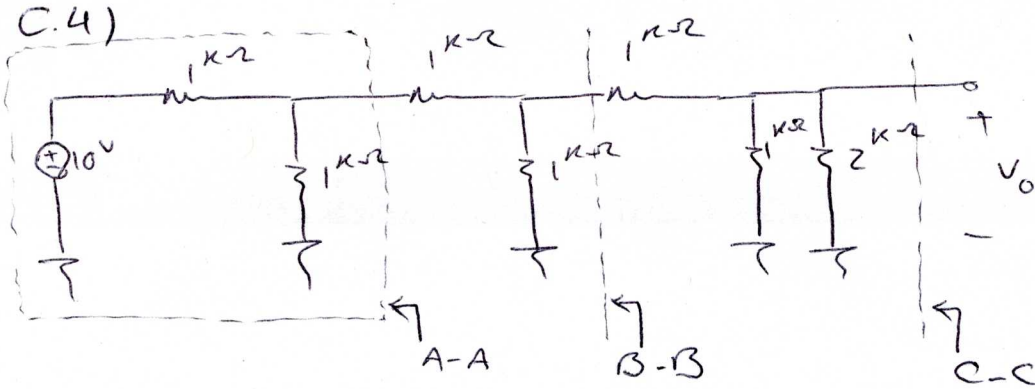


A-A :

$1 - V_{oc1} :$

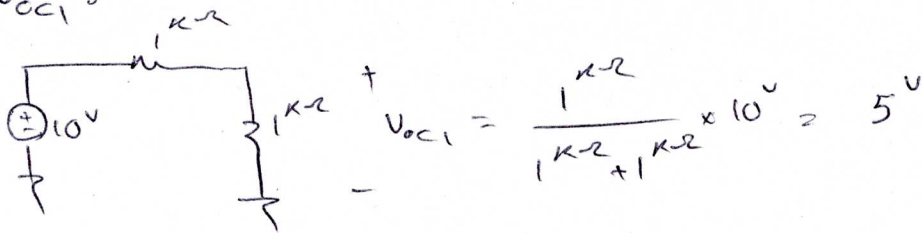


$$V_{oc1} = \frac{1\text{ k}\Omega}{1\text{ k}\Omega + 1} \times 10\text{ V} = 5\text{ V}$$


$Z_{t1} :$

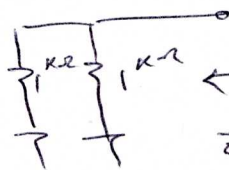

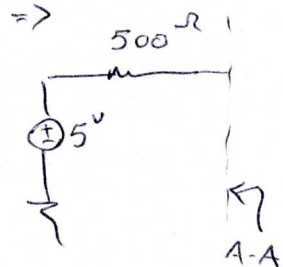
$$Z_{t1} = 1\text{ k}\Omega \parallel 1\text{ k}\Omega = 0.5\text{ k}\Omega$$



B-B :

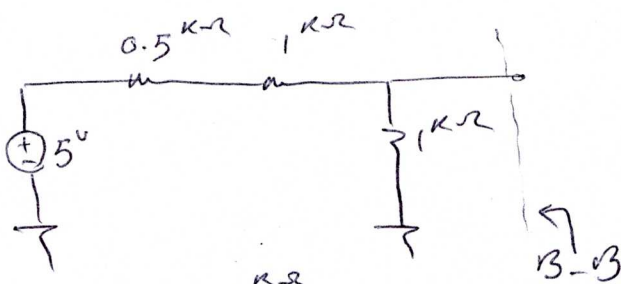


$V_{oc2} :$

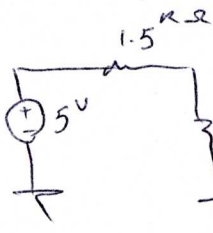


$$V_{oc2} = \frac{1\text{ k}\Omega}{1\text{ k}\Omega + 1.5} \times 5\text{ V} = 2\text{ V}$$

$Z_{t2} :$

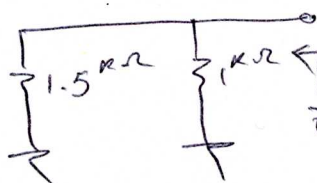

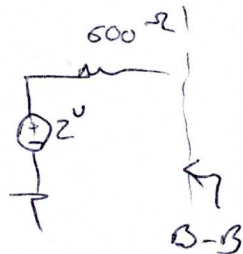
$$Z_{t2} = 1\text{ k}\Omega \parallel 1.5\text{ k}\Omega = 0.6\text{ k}\Omega$$




Solutions to Assigned Problems from Appendix C

C-C :

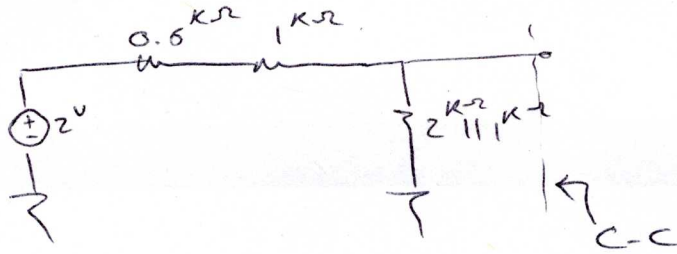


V_{OC3} :

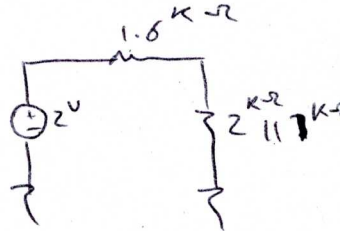

$$V_{OC3} = \frac{2 \text{ k}\Omega \parallel 2 \text{ k}\Omega}{2 \text{ k}\Omega \parallel 2 \text{ k}\Omega + 1.5 \text{ k}\Omega} \times 2 \text{ V} = 0.588 \text{ V}$$

Z_{L3} :

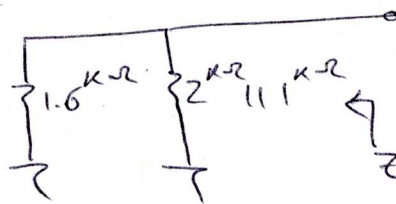

$$Z_{L3} = 2 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel 1.5 \text{ k}\Omega = 470.6 \Omega$$

