

## Chapter 5: Part 1 – Assignment Problems from S&S with Solutions

### Question 5.3

$$i_c = I_s e^{V_{BE}/V_T}$$

For Device #1

$$0.2 \times 10^{-3} = I_{s1} e^{0.72/0.025}$$

$$I_{s1} = \underline{\underline{6.214 \times 10^{-17} \text{ A}}}$$

For Device #2

$$12 \times 10^{-3} = I_{s2} e^{0.72/0.025}$$

$$I_{s2} = \underline{\underline{3.728 \times 10^{-15} \text{ A}}}$$

Since  $I_s \propto A$ , the relative junction areas is:

$$\frac{A_2}{A_1} = \frac{I_{s2}}{I_{s1}} = \frac{i_{c2}}{i_{c1}} = \frac{12}{0.2} = \underline{\underline{60}}$$

### Question 5.4


$$i_c = \beta i_B$$

$$400 = \beta \times 7.5$$

$$\beta = \frac{400}{7.5} = \underline{\underline{53.3}}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{53.3}{54.3} = \underline{\underline{0.982}}$$

Question 5.10

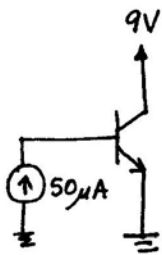

$$\beta = 60 \text{ to } 300$$

$$\begin{aligned} I_C &= \beta I_B \text{ ranges from} \\ &= 60 \times 50 \mu\text{A to} \\ &\quad 300 \times 50 \mu\text{A} \\ &= \underline{\underline{3 \text{ mA to } 15 \text{ mA}}} \end{aligned}$$

$$\begin{aligned} I_E &= I_C + I_B \text{ ranges from} \\ &= \underline{\underline{3.05 \text{ mA to } 15.05 \text{ mA}}} \end{aligned}$$

$$\begin{aligned} \text{Max Power} &= 9 \times I_{C \text{ max}} = 9 \times 15 \\ &= \underline{\underline{135 \text{ mW}}} \end{aligned}$$

Question 5.17



$$i_c = I_s e^{V_{EB}/U_T}$$

$$\text{Use } \frac{i_c}{1 \text{ A}} = e^{\frac{V_{EB} - 0.8}{0.025}}$$




to calculate  $V_{EB}$  for a particular  $i_c$

$$\text{for } i_c = 10 \text{ mA } \quad V_{EB} = 0.685 \text{ V}$$

$$i_c = 5 \text{ A } \quad V_{EB} = 0.840 \text{ V}$$

Question 5.20

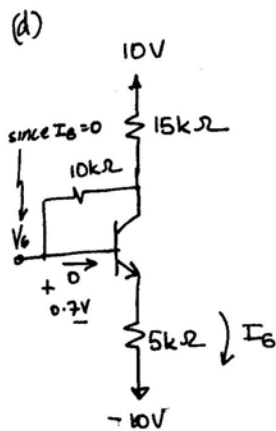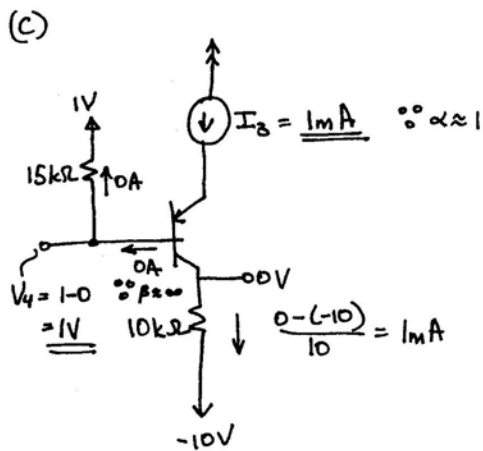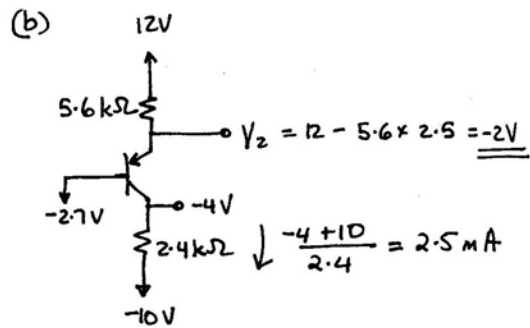(a)  $I_1 = \frac{10.7 - 0.7}{10} = \underline{1 \text{ mA}}$



$I_E = I_C$

$\frac{V_6 - 0.7 + 10}{5} = \frac{10 - V_6}{15}$


$15V_6 + 139.5 = 50 - 5V_6$

$V_6 = \underline{\underline{-4.475 \text{ V}}}$

$I_E = \frac{V_6 - 0.7 + 10}{5}$


$= \frac{-4.475 - 0.7 + 10}{5} = \underline{\underline{0.965 \text{ mA}}}$

Question 5.21

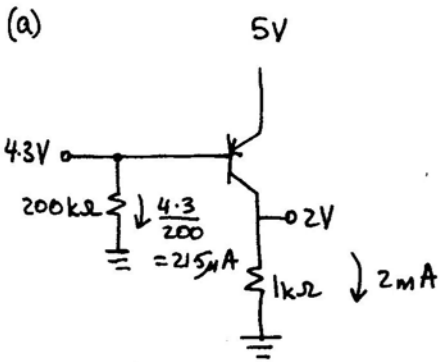


$$\frac{i_c}{i_B} = \beta = \frac{2}{0.0215} = \underline{\underline{93.0}}$$

(b)

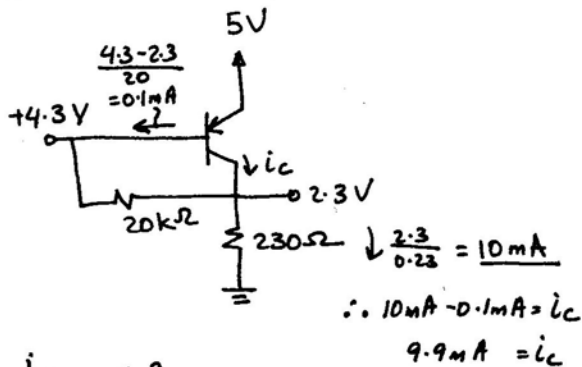

$$\frac{i_c}{i_B} = \frac{9.9}{0.1} = \beta$$

$$\beta = \underline{\underline{99}}$$

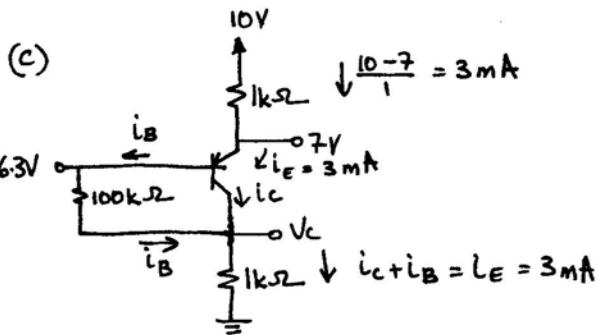



$$V_c = 3 \times 1 = 3 \text{ V}$$

$$i_B = \frac{6.3-3}{100} = \frac{3.3}{100}$$


$$\beta + 1 = \frac{i_E}{i_B} = \frac{3 \times 100}{3.3}$$

$$\beta = \frac{300}{3.3} - 1 = \underline{\underline{89.9}}$$


Question 5.79

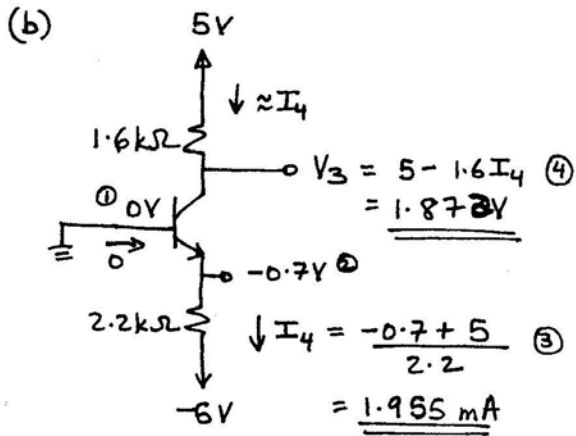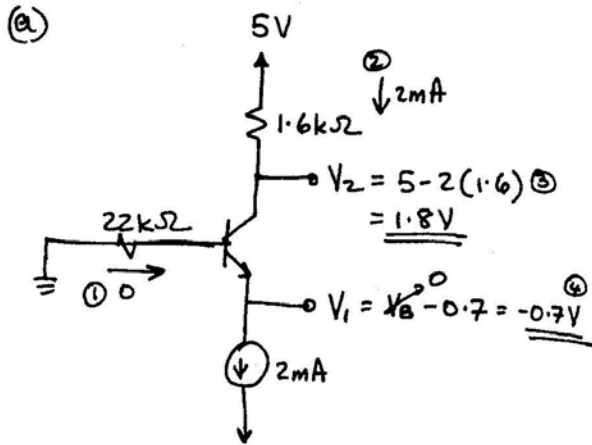


see below for part (c)

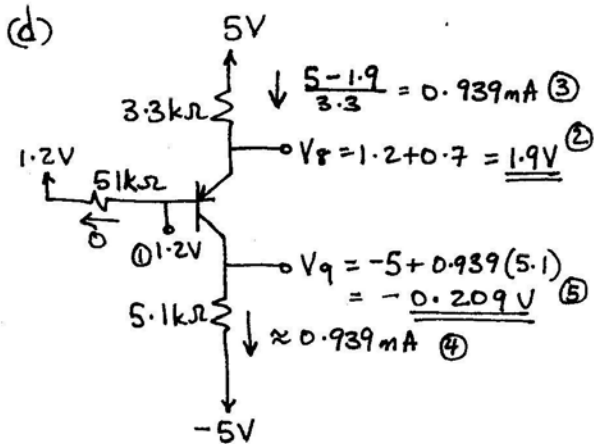

(C)

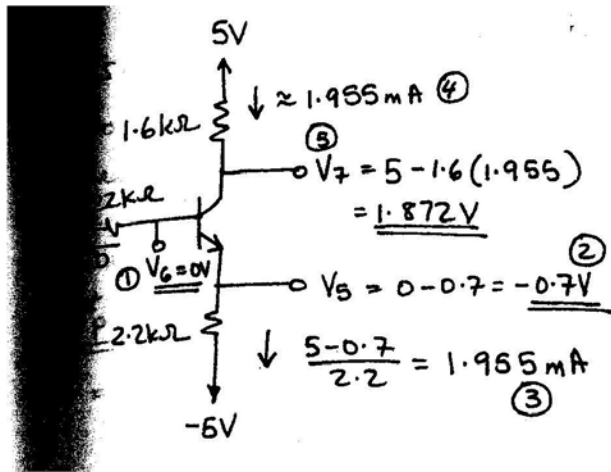

(D)

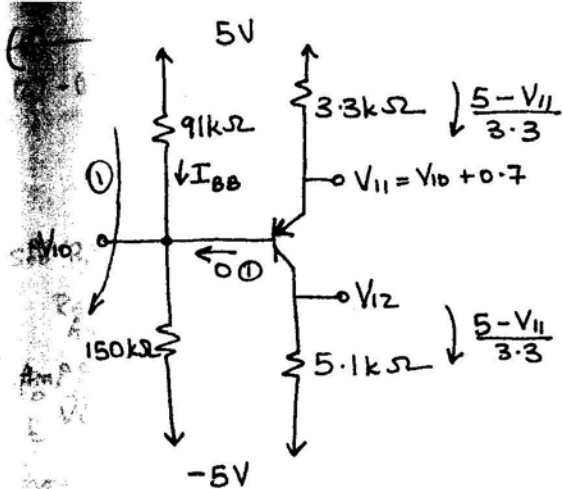

Loop ①

$$5 - 91I_{BB} - 150I_{BB} + 5 = 0$$

$$I_{BB} = \frac{10}{91 + 150}$$

$$V_{I0} = -5 + 150I_{BB}$$

$$= -5 + \frac{150}{91 + 150} \times 10$$




$$= \underline{\underline{1.224V}}$$

$$V_{I1} = V_{I0} + 0.7 = \underline{\underline{1.924V}}$$

$$\because I_C \approx I_E = \frac{5 - V_{I1}}{3.3}$$

$$V_{I2} = -5 + \left(\frac{5 - V_{I1}}{3.3}\right) 5.1 = \underline{\underline{-0.246V}}$$


Question 5.80

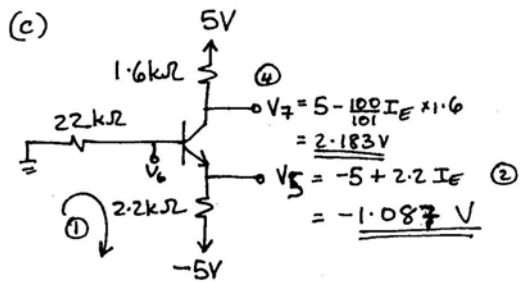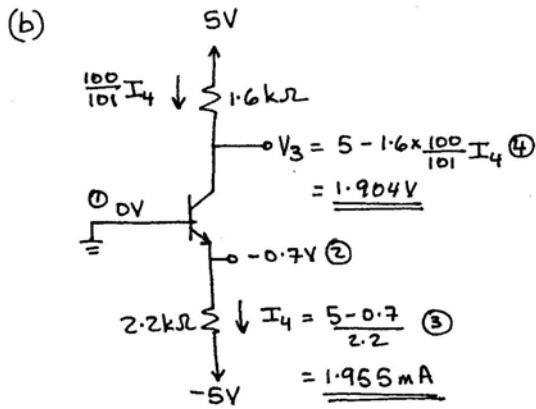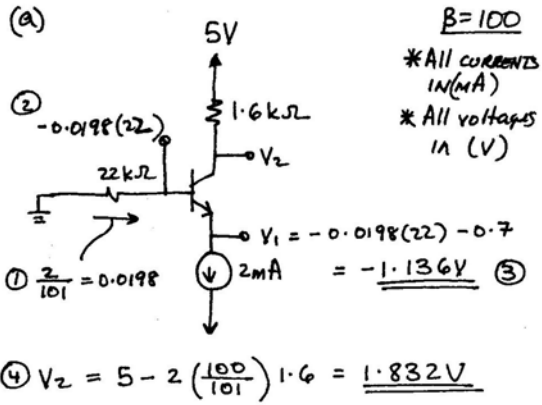

Loop ①  $0 - \frac{I_E}{101} 22 - 0.7 - 2.2 I_E + 5 = 0$

$I_E = 1.778mA$

③  $V_6 = V_5 + 0.7 = -0.387V$

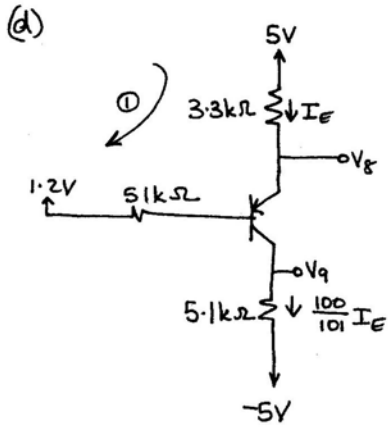

Loop ①

$$5 - 3.3 I_E - 0.7 - \frac{I_E}{101} 5.1 - 1.2 = 0$$

$$I_E = 0.8147 \text{ mA}$$


$$V_g = 5 - 3.3 I_E = \underline{2.3114 \text{ V}}$$

$$V_q = -5 + 5.1 \times \frac{100}{101} I_E = \underline{\underline{-0.8862 \text{ V}}}$$

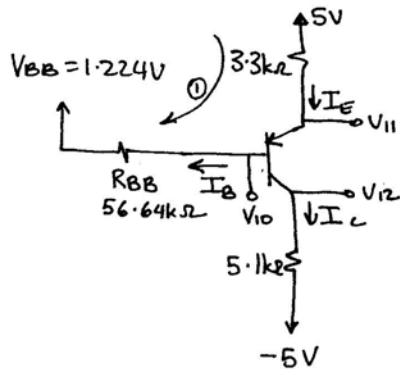(e) Use Thévenin's theorem to simplify the bias network:

$$V_{BB} = -5 + \frac{150}{150+91} \times 10 = 1.224 \text{ V}$$

$$R_{BB} = 150 \parallel 91 = 56.64 \text{ k}\Omega$$



Loop ①

$$5 - 3.3 I_E - 0.7 - \frac{I_E}{101} R_{BB} - 1.224 = 0$$

$$I_E = 0.7967 \text{ mA}$$

$$V_{11} = 5 - 3.3 I_E = \underline{\underline{2.371 \text{ V}}}$$


$$V_{12} = \frac{100}{101} I_E \times 5.1 - 5 = \underline{\underline{-0.977 \text{ V}}}$$

$$V_{10} = V_{11} - 0.7 = \underline{\underline{1.67 \text{ V}}}$$




Question 5.84

(a)  $\beta = \infty$

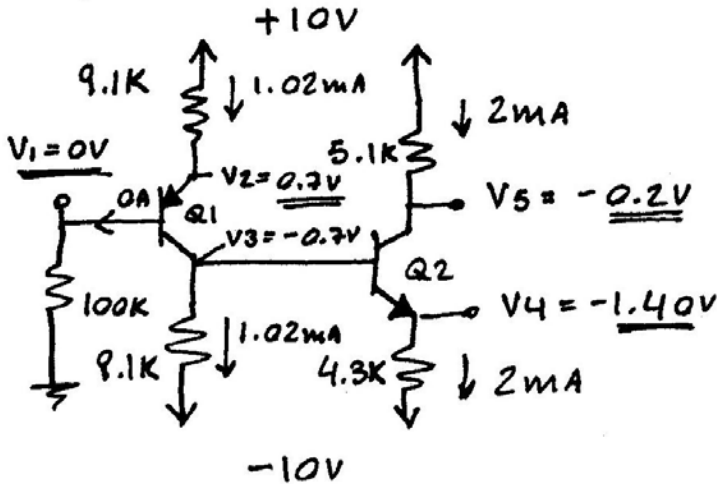

(b)  $\beta = 100$

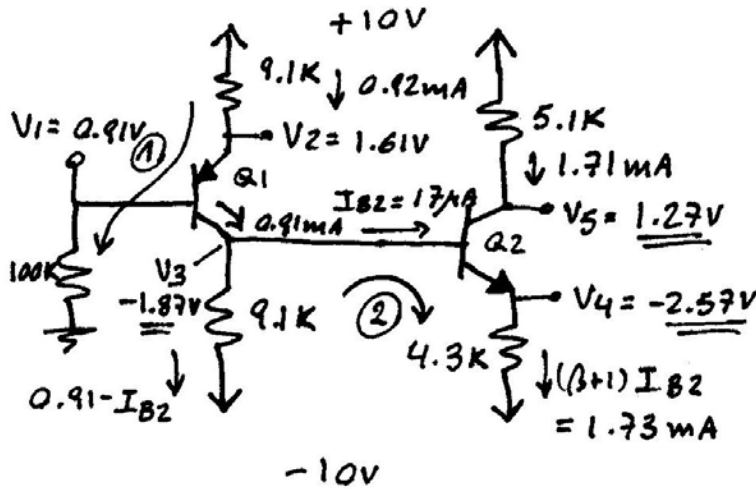

①  $10 - 9.1(\beta + 1)I_{B1} - 0.7 - 100I_{B1} = 0$



$\rightarrow I_{B1} = 0.009mA$

②  $(0.91 - I_{B2}) \times 9.1 = 0.7 + (\beta + 1)I_{B2} \times 4.3$

$\rightarrow I_{B2} = 0.017mA$

$\rightarrow I_{E2} = 1.73mA$


**Question 5.86**

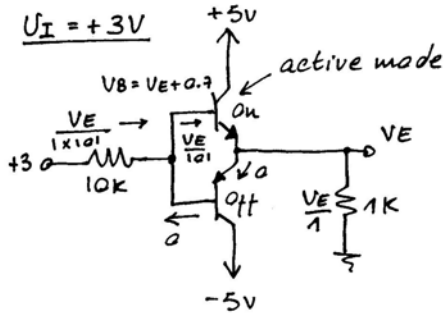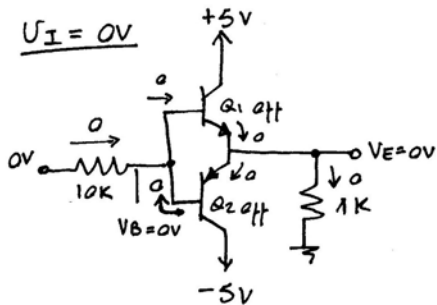

$$3 = \frac{V_E}{10} + 0.7 + V_E$$

$$\Rightarrow V_E = \underline{\underline{2.09V}}$$


$$V_B = \underline{\underline{2.79V}}$$

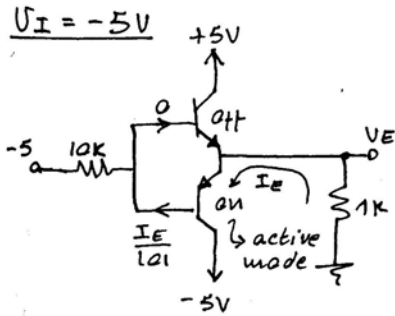

$$I_E = \frac{5 - 0.7}{1 + 10/101} = 3.91mA$$

$$V_E = -3.91V$$

$$V_B = \underline{\underline{-4.61V}}$$

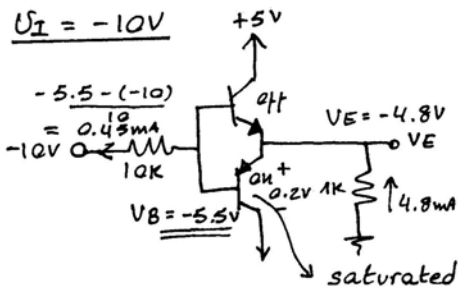

$$I_C = \frac{4.35}{\beta} = 9.7 < I_{B0}$$

thus, Q2 is saturated as assumed

$$V_E = \underline{\underline{-4.8V}} \quad V_B = \underline{\underline{-5.5V}}$$