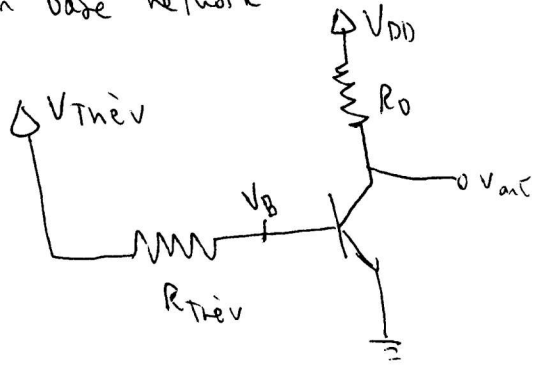


Q#1 design for max output swing: V_{CE} halfway between V_{CC} & V_B

① Transform base network



$$V_{Thév} = V_{CC} \left(\frac{R_{B2}}{R_{B2} + R_{B1}} \right)$$

$$R_{Thév} = R_{B1} \parallel R_{B2}$$

$$V_D = V_{CC} - I_C R_D \quad \text{and} \quad I_{C1} = \beta I_{B1} = \beta \frac{(V_{Thév} - V_B)}{R_{Thév}}$$

$$\text{Design for } V_D = \frac{V_{CC} + V_B}{2} = V_{CC} - R_D \beta \left(\frac{V_{CC} \left(\frac{R_{B2}}{R_{B2} + R_{B1}} \right) - V_B}{R_{B1} \parallel R_{B2}} \right) \quad \text{and note } V_B = 0.7V$$

choose R_{B2}, R_{B1}, \dots let's say we want a high input impedance

$$R_D = \left(\frac{V_{CC}}{2} - 0.45 \right) \left[\frac{\beta}{R_{B1}} \left(V_{CC} - 0.7 \left(\frac{R_{B1} + R_{B2}}{R_{B2}} \right) \right) \right]^{-1}$$


example: $V_{CC} = 10V, \beta = 100, R_{B1} = 9k, R_{B2} = 1k$

$$R_D = (4.55) \left[\frac{100}{9000} (10 - 7) \right]^{-1} = 136.5 \Omega$$

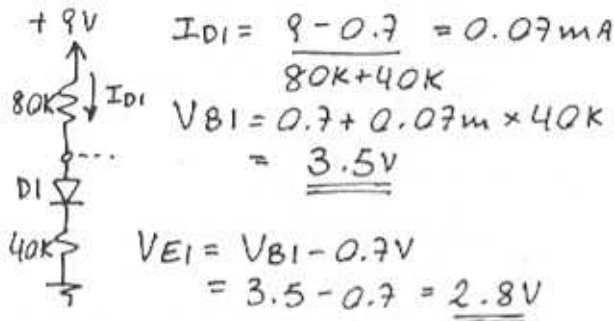5.83

For $\beta = \infty$ and R open:

$$I_{B1} = I_{B2} = 0, \alpha_1 = \alpha_2 = 1$$



$$I_{E1} = \frac{2.8 \text{ V}}{2k} = 1.4 \text{ mA}$$

$$I_{E1} = I_{C1} \text{ since } \alpha = 1$$

$$V_{C1} = 9 \text{ V} - 2k \times 1.4 \text{ mA} - 0.7 = \underline{5.5 \text{ V}}$$

$V_{CB} = 2 \text{ V} \rightarrow$ Transistor is in active mode.

$$V_{B2} = V_{C1} = \underline{5.5 \text{ V}}$$

$$V_{E2} = 5.5 + 0.7 = \underline{6.2 \text{ V}}$$


$$I_{E2} = \frac{9 - 6.2}{100} = 28 \text{ mA}$$

$$I_{E2} = I_{C2} \text{ since } \alpha = 1$$

$$\rightarrow V_{C2} = 28 \text{ mA} \times 100\Omega = \underline{2.8 \text{ V}}$$

For $\beta = \infty$ and R connected:

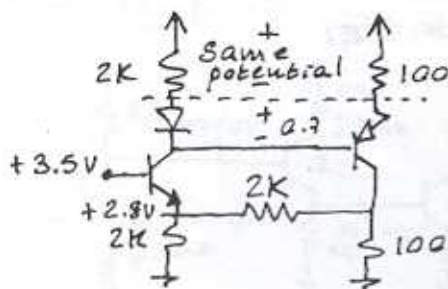Still: $V_{B1} = \underline{3.5 \text{ V}}, V_{E1} = \underline{2.8 \text{ V}}$




Since the voltage across the top two resistors is equal:

$$I_{C1} \times 2k = I_{E2} \times 100$$

$$I_{E2} = 20 I_{C1}$$

also: $I_{C1} = I_{E1}, I_{C2} = I_{E2}$

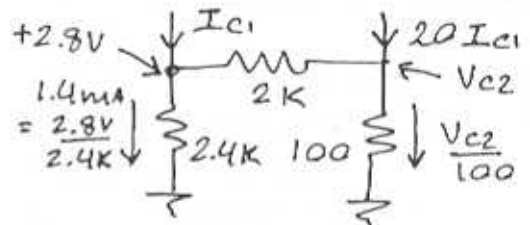

$$1.4 \text{ mA} - I_{C1} = 20 I_{C1} - \frac{V_{C2}}{100}$$

$$\rightarrow V_{C2} = 100 \times (21 I_{C1} - 1.4 \text{ mA}) \quad (1)$$

also:

$$\frac{V_{C2} - 2.8 \text{ V}}{2k} = 1.4 \text{ mA} - I_{C1}$$

$$\rightarrow V_{C2} = 5.6 - I_{C1} \times 2k \quad (2)$$

Solving for I_{C1} from (1) & (2)

$$I_{C1} = 1.4 \text{ mA}$$

Substituting in either (1) or (2)

$$V_{C2} = \underline{2.8 \text{ V}}$$

$$\text{and: } V_{E2} = 9 - 100 \times 1.4 \text{ mA} = \underline{8.86 \text{ V}}$$

$$V_{B2} = V_{C1} = 8.86 - 0.7 = \underline{8.16 \text{ V}}$$

For $\beta = 100$ and R open:

In the previous two cases

$$I_{D1} = 0.07 \text{ mA}, I_{E1} = 1.4 \text{ mA}$$

$$\text{if } \beta = 100 \rightarrow I_{B1} \approx 0.014 \text{ mA}$$

which is a significant amount compared to 0.07 mA
 \rightarrow must be taken into account

The bottom two resistors have equal voltage drops thus,
 CONT.

$$2K \times I_{E1} = 40K \times I_{D1}$$

$$\rightarrow I_{D1} = 0.05 \times I_{E1} \quad (3)$$

$$\text{also: } \frac{I_{D1} + I_{B1}}{\beta + 1} = \frac{9 - V_{B1}}{80K}$$

$$I_{E1} \left(\frac{1}{\beta + 1} + 0.05 \right)$$

for $\beta = 100$:

$$0.06 \times I_{E1} = \frac{9 - V_{B1}}{80K}$$

$$\rightarrow V_{B1} = 9 - 4800 \times I_{E1} \quad (4)$$

$$\text{also: } V_{B1} = 0.7 + I_{E1} \times 2K \quad (5)$$

$$\text{From (4) \& (5) } \begin{cases} V_{B1} = 3.14V \\ I_{E1} = 1.22mA \end{cases}$$

$$V_{E1} = 1.22m \times 2K \rightarrow V_{E1} = \underline{\underline{2.44V}}$$

$$I_{C1} = \alpha I_E = 0.99 \times 1.22m = 1.2mA$$

Again: voltage drop on top two resistors is equal

$$2K \cdot I_{D2} = 100 \cdot I_{E2}$$

$$I_{D2} = 0.05 I_{E2}$$

$$\text{but } I_{D2} = 1.2m - \frac{I_{E2}}{\beta + 1}$$

$$\Rightarrow 1.2mA = \left(0.05 + \frac{1}{\beta + 1} \right) I_{E2}$$

$$I_{E2} = 20mA \quad 0.06$$

$$V_{E2} = 9 - 100 \times 20m = \underline{\underline{7V}}$$


$$V_{B2} = V_{C1} = 7 - 0.7 = \underline{\underline{6.3V}}$$

$$I_{C1} = \alpha I_{E1} = 19.8mA$$

$$V_{C2} = 100 \times 19.8mA = \underline{\underline{1.98V}}$$

For $\beta = 100$ and R connected:

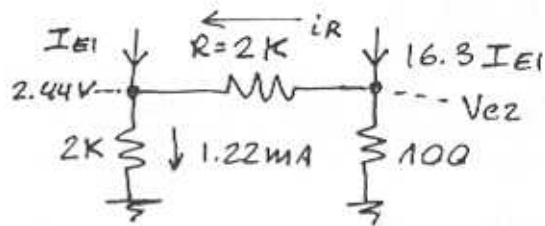To simplify the solution: assume I on R is $\ll I_{E1} \rightarrow V_{E1} = 2.44V$



From top of circuit:

$$I_{E2} = I_{C1} / 0.06$$

$$I_{C2} = \frac{\alpha^2}{0.06} \cdot I_{E1}$$

$$I_{C2} = 16.3 \times I_{E1}$$

To obtain I_{E1} :

$$1.22m - I_{E1} = 16.3 I_{E1} - \frac{V_{C2}}{100}$$

$$V_{C2} = 100 (17.2 I_{E1} - 1.22m) \quad (6)$$

also:

$$\frac{V_{C2} - 2.44}{2K} = 1.22m - I_{E1}$$

$$\rightarrow V_{C2} = 2.44 - 2000 I_{E1} + 2.44 = 4.88 - 2 \times 10^3 \cdot I_{E1} \quad (7)$$

$$\text{From (7) \& (8): } \begin{cases} I_{E1} = 1.34mA \\ V_{C2} = \underline{\underline{2.18V}} \end{cases}$$

thus,

$$I_{C1} = 1.33mA$$

$$I_{E2} = 22.1mA$$

$$V_{E2} = 9 - 22.1m \times 100 = 6.79V$$

$$V_{B2} = 6.79 - 0.7 = \underline{\underline{6.09V}}$$

To confirm initial assumption on I of R :

$$\frac{2.44 - 2.18}{2K} = 0.13mA$$

which is 10 times smaller than I_{E1}

Q #3

$V_C \geq V_B$ is the condition

$$-0.7 - R_E I_{C1} \geq -R_B I_{B1}$$

and use $I_{B1} = \frac{I_{C1}}{\beta}$ and $I_{C1} = \alpha I_{E1} = \frac{\beta}{\beta+1} I_{E1}$

$$-0.7 - 50 \left(\frac{\beta}{\beta+1} \right) 1 \text{mA} \geq -70 \text{k} \left(\frac{1 \text{mA}}{\beta+1} \right)$$

$$-(\beta+1) 0.7 - (50\text{m})\beta \geq -70$$

$$\beta \leq 92.4$$