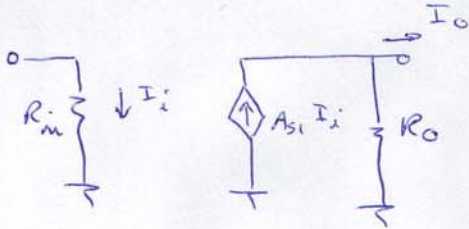


Quiz 1 Set A 8

Question 1)

a)




R_{in} : input resistance

R_o : output resistance

A_{SI} : short-circuit current gain

b)

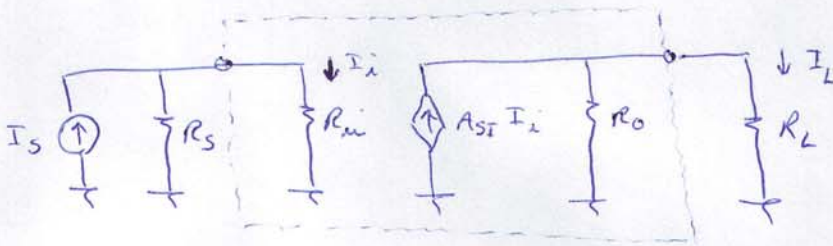

$$I_i = I_s \times \frac{R_s}{R_s + R_{in}}$$

$$\Rightarrow \frac{I_i}{I_s} = \frac{R_s}{R_s + R_{in}} \quad \textcircled{I}$$

$$I_L = A_{SI} I_i \times \frac{R_o}{R_o + R_L}$$

$$\Rightarrow \frac{I_L}{I_i} = A_{SI} \frac{R_o}{R_o + R_L} \quad \textcircled{II}$$


$$\textcircled{I}, \textcircled{II} \Rightarrow \frac{I_L}{I_s} = \frac{I_L}{I_i} \times \frac{I_i}{I_s} \Rightarrow \frac{I_L}{I_s} = \frac{R_s}{R_s + R_{in}} \times A_{SI} \times \frac{R_o}{R_o + R_L}$$

c) $R_s = 1 \text{ M}\Omega$, $R_{in} = 100 \text{ }\Omega$, $R_o = 1 \text{ M}\Omega$, $R_L = 100 \text{ }\Omega$, $A_{SI} = 100 \text{ A/A}$

$$\frac{I_L}{I_S} = \frac{R_S}{R_S + R_{in}} \times A_{SI} \times \frac{R_o}{R_o + R_L} = \frac{1000^k}{1000^k + 0.1} \times 100 \times \frac{1000^k}{1000^k + 1}$$

$$\frac{I_L}{I_S} = 99.98 \text{ A/A} \approx 100 \text{ A/A}$$

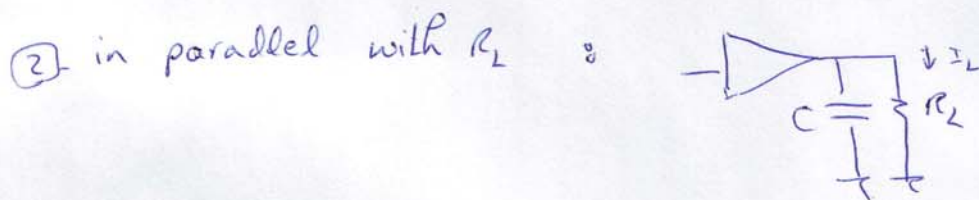
d) There are two ways to place a capacitor at the output of the current amplifier:




at dc ($f=0 \text{ Hz}$) the capacitor is open-circuit ($X_C = \frac{1}{j\omega C}$)
and at very high frequencies ($f \rightarrow \infty$) the capacitor is short-circuit

\Rightarrow { design ① is high-pass ($I_L \approx 0$ at low frequencies)
design ② is low-pass ($I_L \approx 0$ at high frequencies)

design ② :

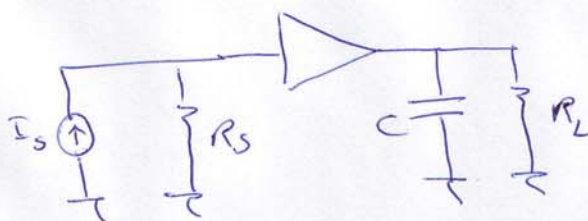

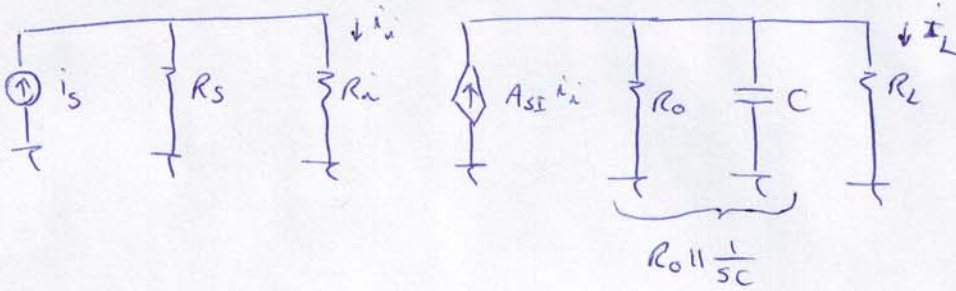

$$\left. \begin{aligned} \frac{i_i}{i_s} &= \frac{\frac{1}{R_{in}}}{\frac{1}{R_{in}} + \frac{1}{R_s}} = \frac{R_s}{R_s + R_{in}} \\ \frac{i_L}{i_i} &= A_{SI} \times \frac{\frac{1}{R_L}}{\frac{1}{R_L} + \frac{1}{R_o} + sC} \end{aligned} \right\} \Rightarrow \frac{i_L}{i_s} = \frac{i_i}{i_s} \times \frac{i_L}{i_i}$$

$$= \frac{R_s}{R_s + R_{in}} \times A_{SI} \times \frac{R_o}{R_L + R_o + sC R_L R_o}$$

$$\Rightarrow \frac{i_L}{i_s} = \frac{R_s}{R_s + R_{in}} A_{SI} \times \frac{R_o}{R_L + R_o} \times \frac{1}{1 + sC \frac{R_o R_L}{R_o + R_L}}$$


which is similar to the standard LP transfer function: $TF = K \frac{1}{1 + \frac{s}{\omega_0}}$

$$\omega_0 = \frac{1}{C \frac{R_o R_L}{R_o + R_L}} = \frac{1}{C(R_o || R_L)}$$


$$\Rightarrow f_0 = \frac{1}{2\pi C (R_o || R_L)} = 100 \text{ MHz}$$

$$\Rightarrow C = \frac{1}{2\pi \times 10^8 \times (100 || 10^6)} \approx 15.9 \times 10^{-12} \text{ F} = 15.9 \text{ pF}$$

$$f) \left. \frac{i_L}{i_s} \right|_{dc} = \frac{R_s}{R_s + R_{in}} \times A_{SI} \times \frac{R_o}{R_o + R_L} = 100 \stackrel{A/A}{=} 40 \text{ dB}$$

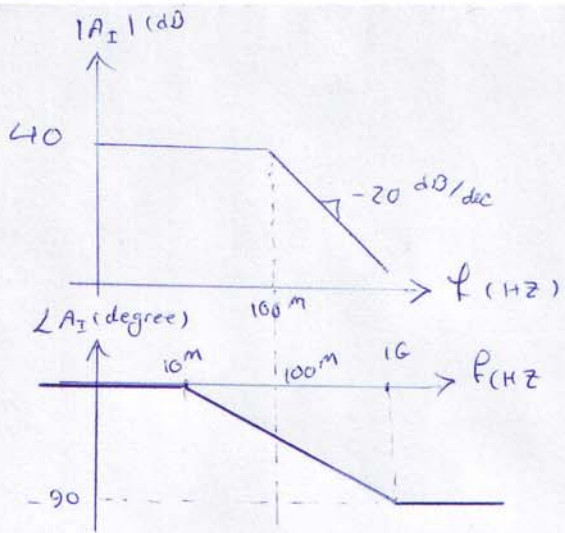

Question 2)

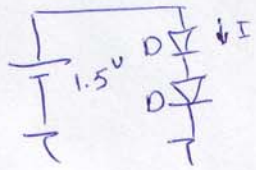

identical diodes $\Rightarrow V_{D_1} = V_{D_2}$
 $V_{D_1} + V_{D_2} = 1.5 \text{ V} \Rightarrow$

$$V_{D_1} = V_{D_2} = \frac{1.5 \text{ V}}{2} = 0.75 \text{ V}$$

$$I = I_S e^{\frac{V_D}{nV_T}} = 10^{-9} e^{\frac{0.75}{2 \cdot 0.025}} = 3.27 \text{ mA}$$