

$$\frac{7-0}{V_1-0} = 50 \Rightarrow V_1 = 0.14 \text{ V}$$

$$\frac{0+9}{0-V_2} = 50 \Rightarrow V_2 = -0.18 \text{ V}$$

\therefore DC op. pt. to obtain the largest output signal magnitude is given by,

$$V_{in(dc)} = \frac{V_1 + V_2}{2} = \frac{-0.04}{2} = -0.02 \text{ V}$$


$$V_{out(dc)} = \frac{7-9}{2} = -1 \text{ V}$$

\therefore Magnitude of maximum output signal,

$$V_{out(max)}(\text{pk-pk}) = 7 - (-9) = 16 \text{ V pk-pk}$$

$$V_{out(max)} = \frac{7 - (-9)}{2} = 8 \text{ V}$$

2.

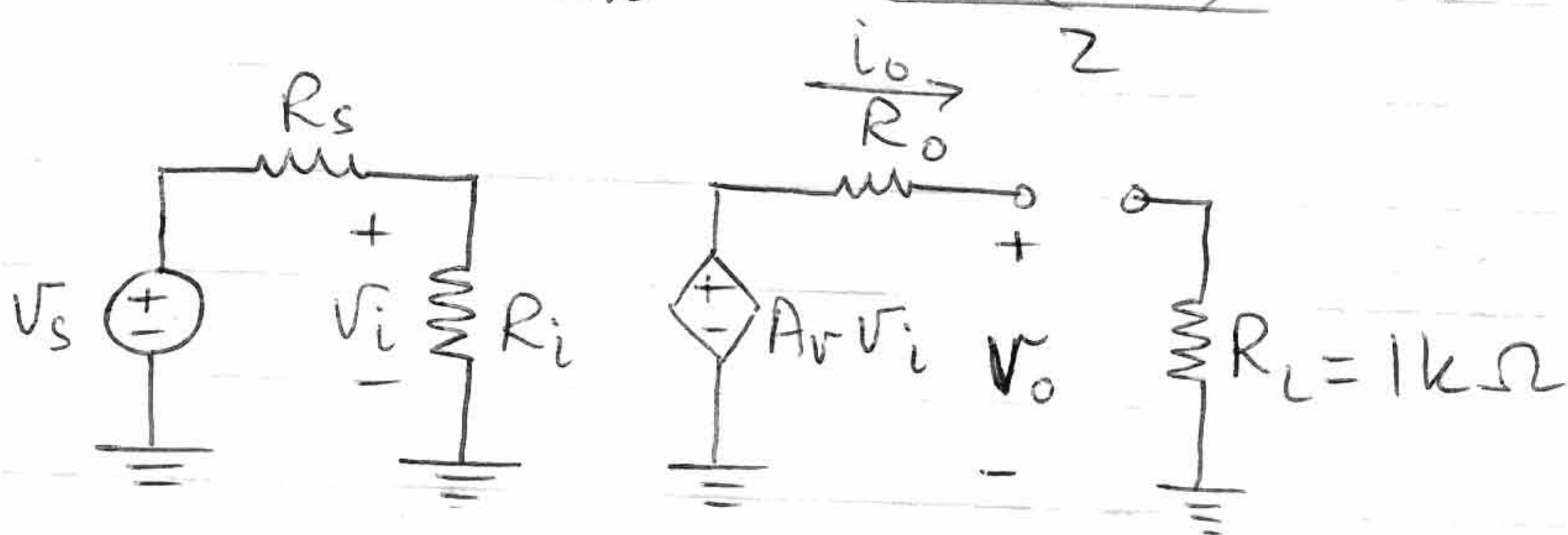

without load: $i_o = 0 \Rightarrow V_{R_o} = 0$

$$\therefore V_o = A_v V_i = A_v \left(V_s \times \frac{R_i}{R_i + R_s} \right)$$

$$\frac{V_o}{V_s} = A_v \times \frac{R_i}{R_i + R_s} = 100 \text{ V/V (given)}$$

$$\therefore V_o = A_v V_i = 100 V_s \quad \text{--- (1)}$$

with load: $V_o = \frac{1k}{R_o + 1k} \times A_v V_i$

∴ From ①,


$$V_o = \frac{1k}{R_o + 1k} \times (100 V_s)$$

$$\frac{V_o}{V_s} = \frac{1k}{R_o + 1k} \times 100 = 70 \text{ V/V} \quad (\text{given})$$

$$\therefore \frac{1k}{R_o + 1k} = 0.7$$

$$\Rightarrow R_o = 429 \Omega$$

3.

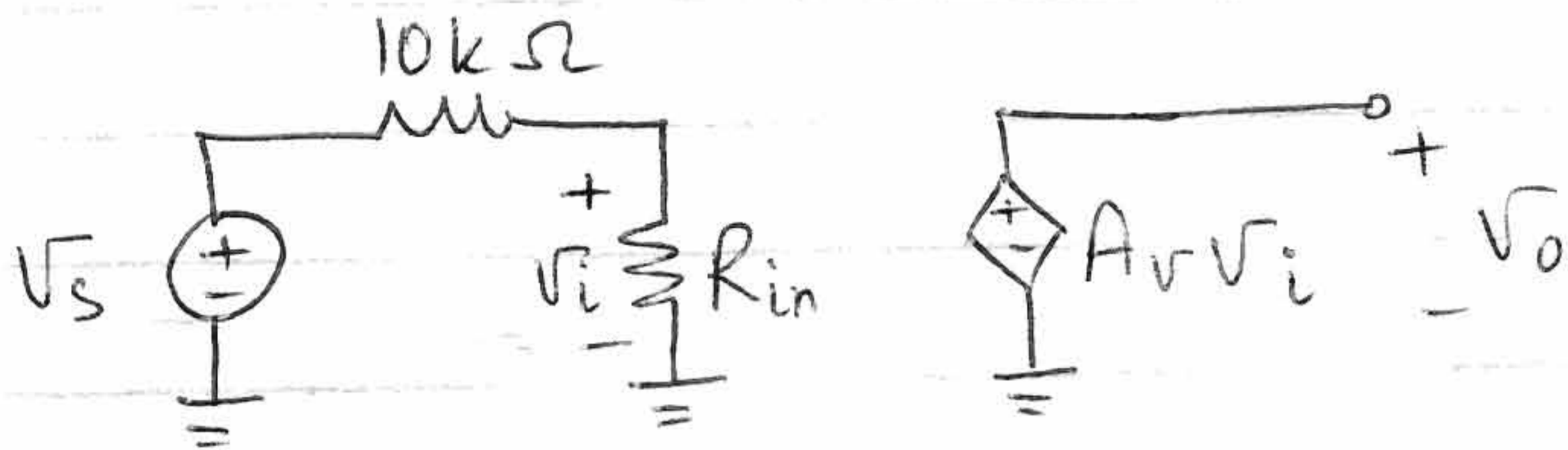


$$V_o = A_v V_i \Rightarrow \frac{V_o}{V_i} = A_v$$

$$V_i = \frac{R_{in}}{10k + R_{in}} \times V_s \Rightarrow \frac{V_i}{V_s} = \frac{R_{in}}{10k + R_{in}}$$

$$\therefore \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_v \cdot \frac{R_{in}}{10k + R_{in}} = 1667 \text{ V/V} \quad \text{--- ①}$$

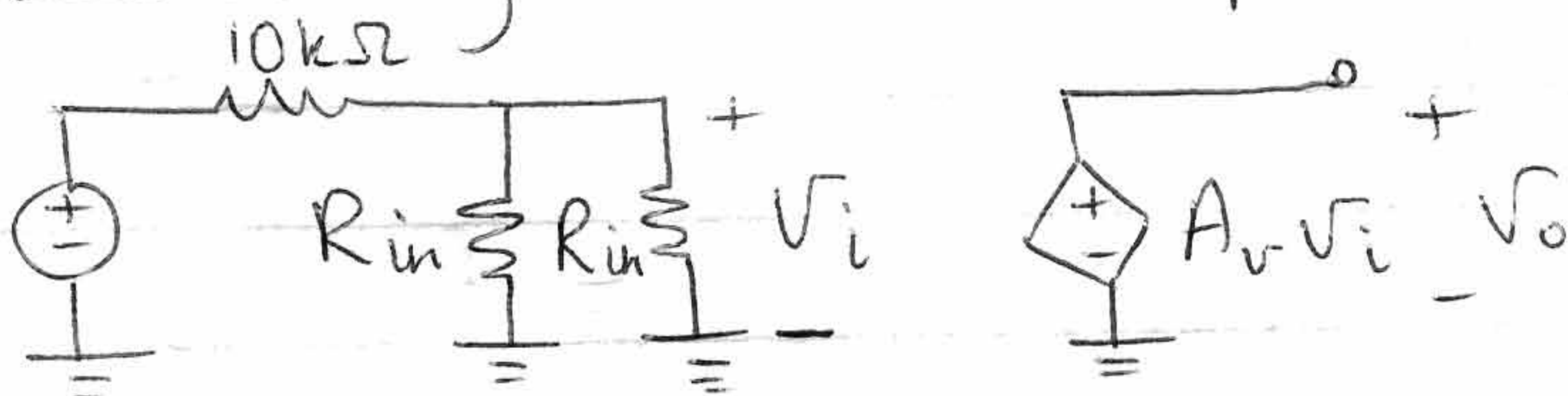Connecting the two amplifiers in parallel,



$$\text{Similarly, } \frac{V_o}{V_s} = A_v \cdot \frac{(R_{in} \parallel R_{in})}{10k\Omega + (R_{in} \parallel R_{in})}$$

$$= A_v \cdot \frac{(R_{in}/2)}{10k + (R_{in}/2)}$$


$$\frac{V_o}{V_s} = A_v \cdot \frac{R_{in}}{R_{in} + 20k} = 909 V/V \quad - (2)$$

$$\textcircled{1} \div \textcircled{2} \Rightarrow \frac{1667}{909} = \frac{R_{in} + 20k}{R_{in} + 10k}$$


$$\therefore R_{in} = 1.99 k\Omega$$

4.



Amplifier 1:

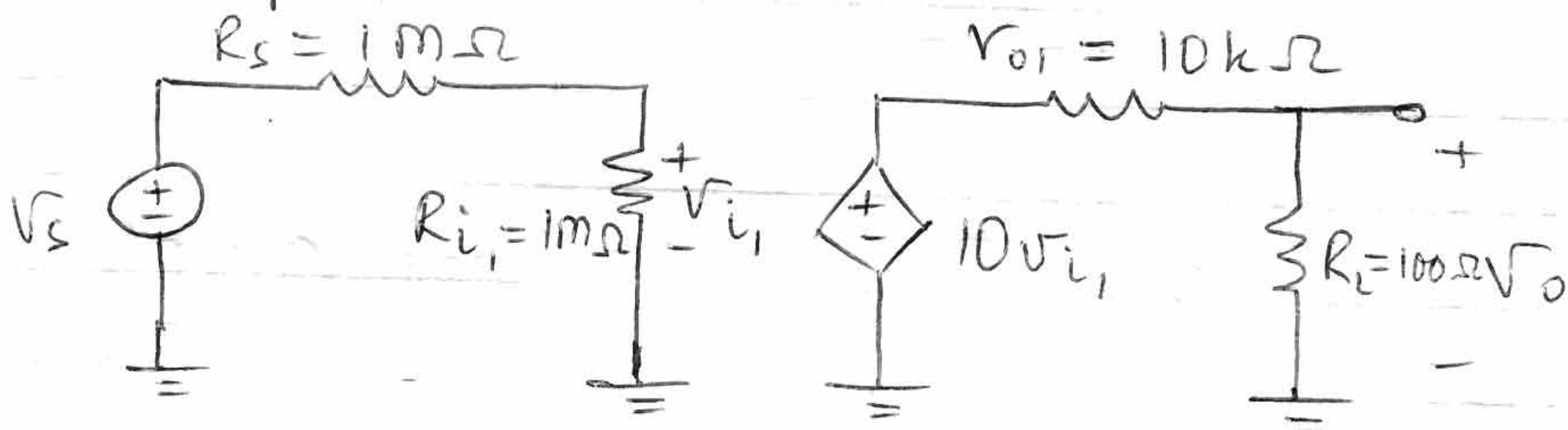

Amplifier 2:

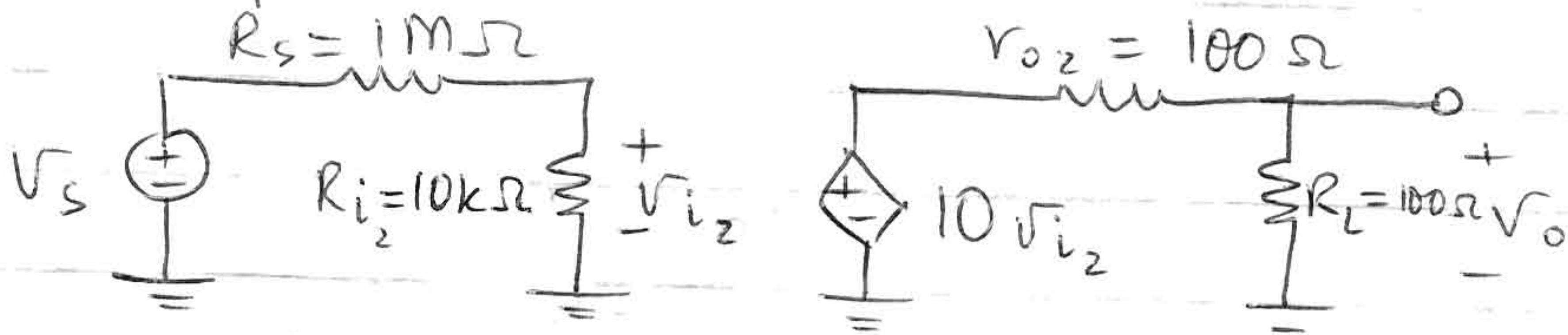

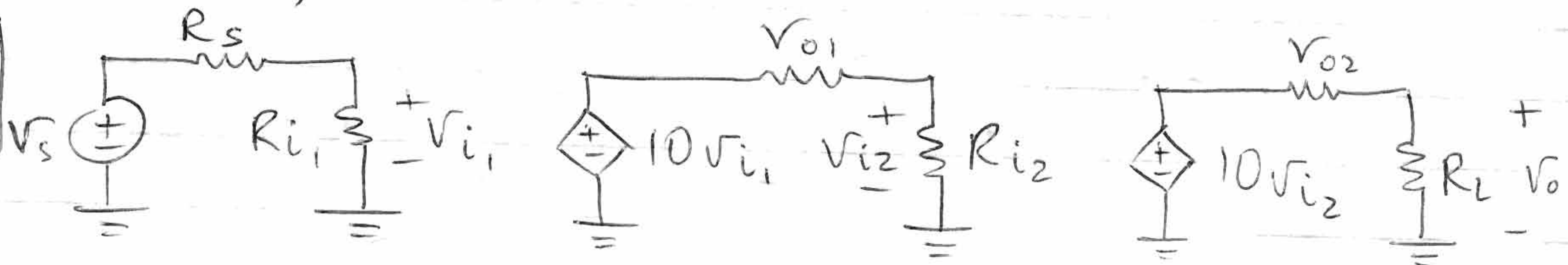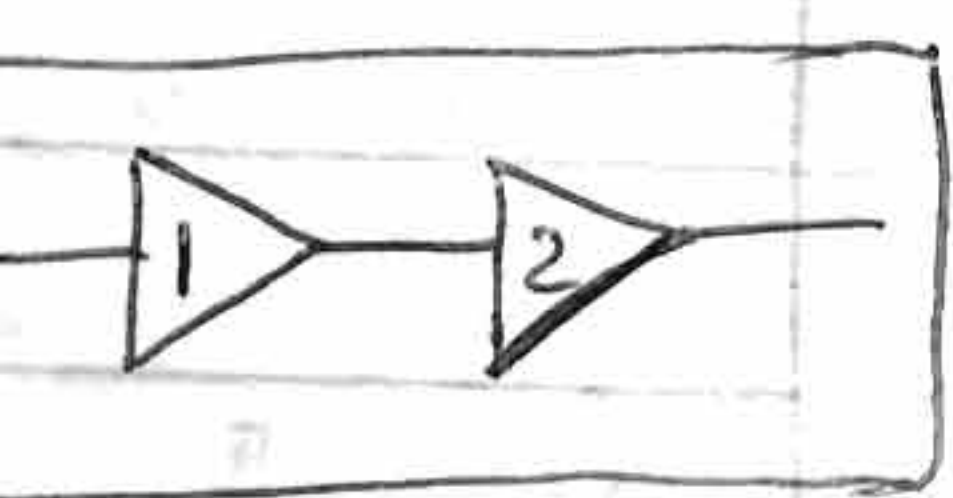Connecting amplifier 1 and amplifier 2 in series,



$$\frac{V_o}{V_{i2}} = 10 \cdot \frac{R_L}{V_{o2} + R_L}$$

$$\frac{V_{i2}}{V_{i1}} = 10 \cdot \frac{R_{i2}}{V_{o1} + R_{i2}}$$


$$\frac{V_{i1}}{V_s} = \frac{R_{i1}}{R_s + R_{i1}}$$

$$\therefore \frac{V_o}{V_s} = \frac{V_o}{V_{i2}} \times \frac{V_{i2}}{V_{i1}} \times \frac{V_{i1}}{V_s}$$

$$= \frac{R_{i1}}{R_s + R_{i1}} \times \frac{R_{i2}}{R_{i2} + r_{o1}} \times \frac{R_L}{R_L + r_{o2}} \times 100$$

$$\therefore \frac{V_o}{V_s} = \frac{1M}{1M + 1M} \times \frac{10k}{10k + 10k} \times \frac{100}{100 + 100} \times 100$$
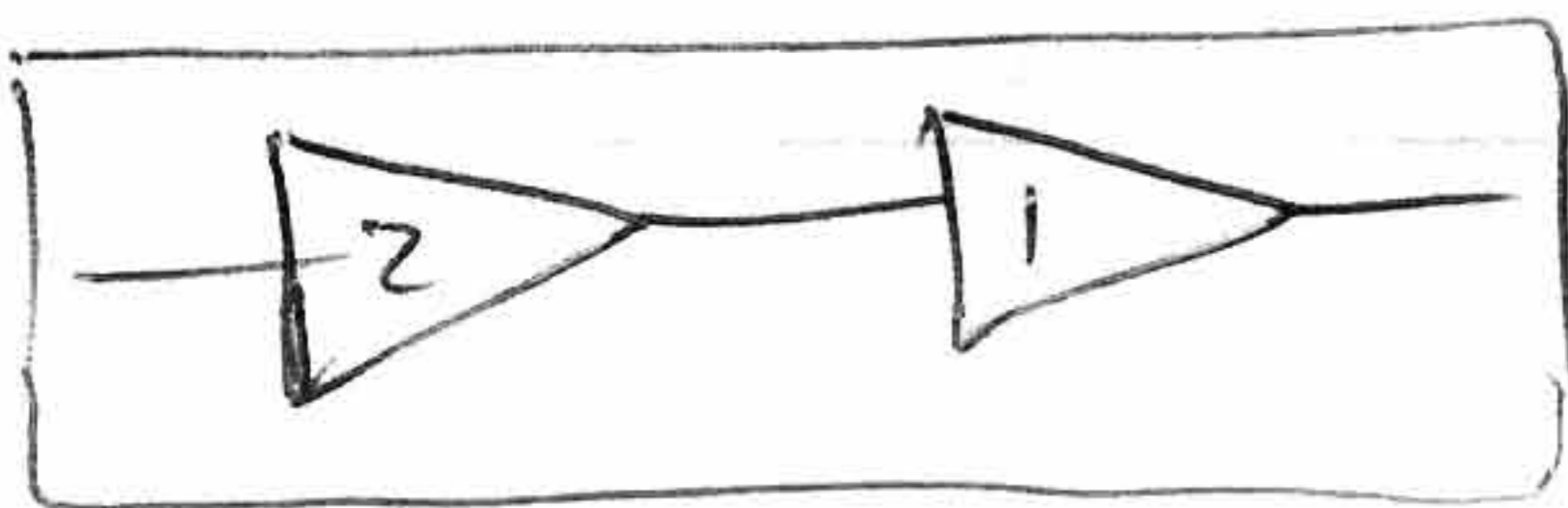
$$= 12.5 \text{ V/V} \quad \text{--- (1)}$$




Connecting amplifier 2 and amplifier 1 in series,

Similarly, $\frac{V_o}{V_s} = \frac{R_{i2}}{R_s + R_{i2}} \times \frac{R_{i1}}{R_{i1} + r_{o2}} \times \frac{R_L}{R_L + r_{o1}} \times 100$

$$= \frac{10k}{1M + 10k} \times \frac{1M}{1M + 100} \times \frac{100}{100 + 10k} \times 100$$

$$= 9.802 \text{ mV/V} \quad \text{--- (2)}$$

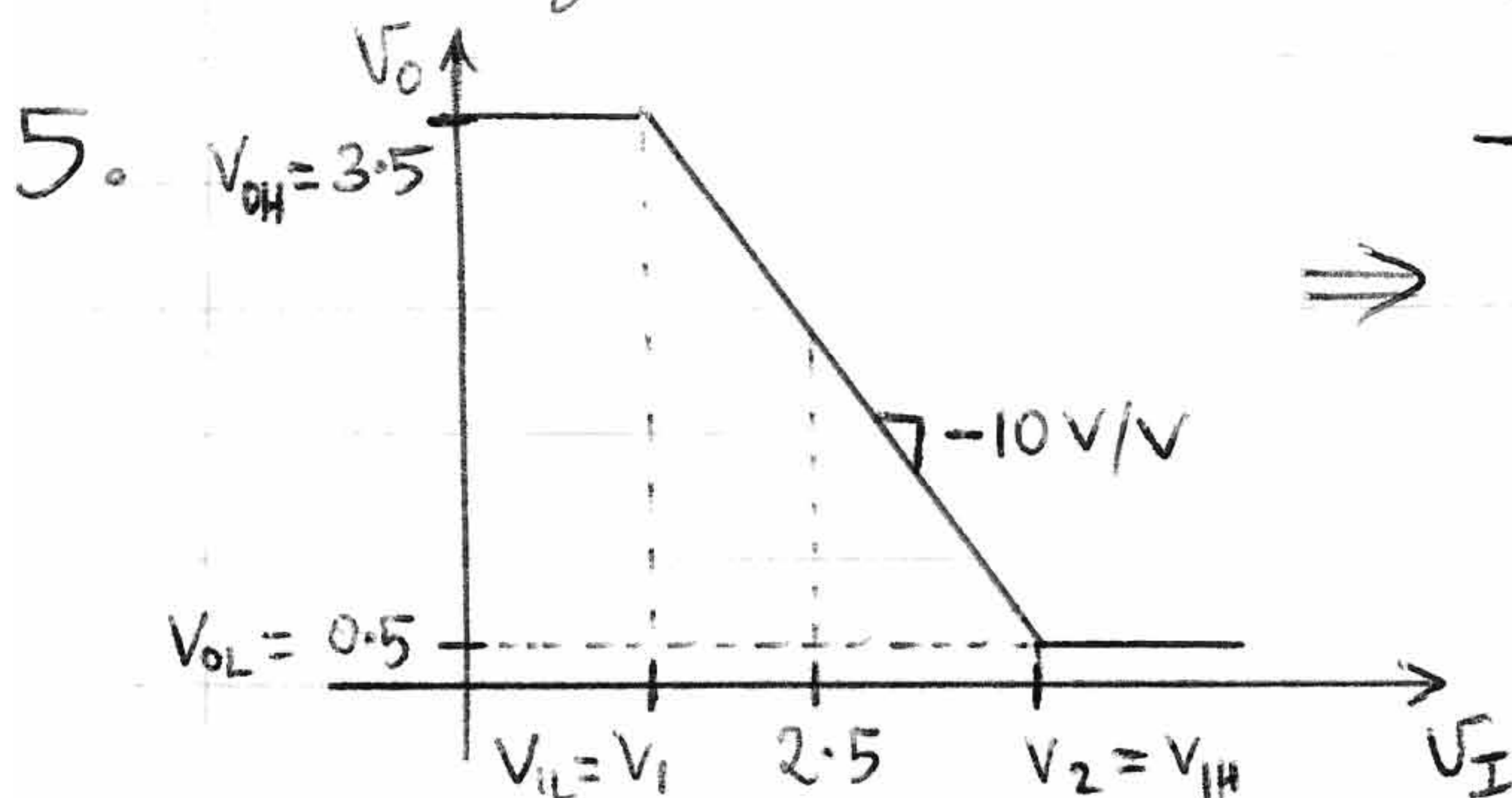\therefore Comparing (1) & (2), the configuration in which amplifier 1 and amplifier 2 are connected in series with amplifier 1 preceding amplifier 2 results in the highest overall gain of 12.5 V/V.



$$-10(V_2 - V_1) = 0.5 - 3.5$$

$$\Rightarrow V_2 - V_1 = 0.3$$

$$\frac{V_2 + V_1}{2} = 2.5 \quad (\text{given})$$

$$\therefore V_{iL} = V_1 = 2.35 \text{ V}$$

$$V_{iH} = V_2 = 2.65 \text{ V}$$

$$\therefore NM_H = V_{OH} - V_{IH} = 3.5 - 2.65 = 0.85V$$

$$NM_L = V_{IL} - V_{OL} = 2.35 - 0.5 = 1.85V$$

$$\text{Width of transition region} = V_{IH} - V_{IL}$$

$$= 2.65 - 2.35$$

$$= 0.3V$$

Doubling the width of the transition region

$$\Rightarrow V_{IH} - V_{IL} = 0.6V$$

$$\therefore \text{slope (constant gain)} = -5V/V$$

$$V_2 - V_1 = 0.6$$


$$\frac{V_2 + V_1}{2} = 2.5$$

$$\therefore V_{IL} = V_1 = 2.2V$$

$$V_{IH} = V_2 = 2.8V$$

$$NM_H = V_{OH} - V_{IH} = 3.5 - 2.8 = 0.7V$$

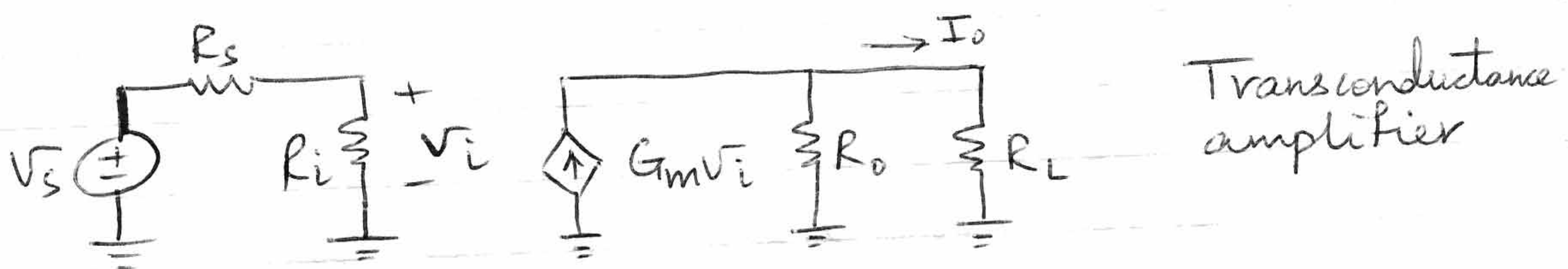
$$NM_L = V_{IL} - V_{OL} = 2.2 - 0.5 = 1.7V$$



$$\frac{v_i}{V_s} = \frac{R_i}{R_i + R_s} \quad I_o = \frac{R_o}{R_o + R_L} G_m v_i$$

$$\therefore G = \frac{I_o}{V_s} = \frac{R_i}{R_i + R_s} \times \frac{R_o}{R_o + R_L} \times G_m$$

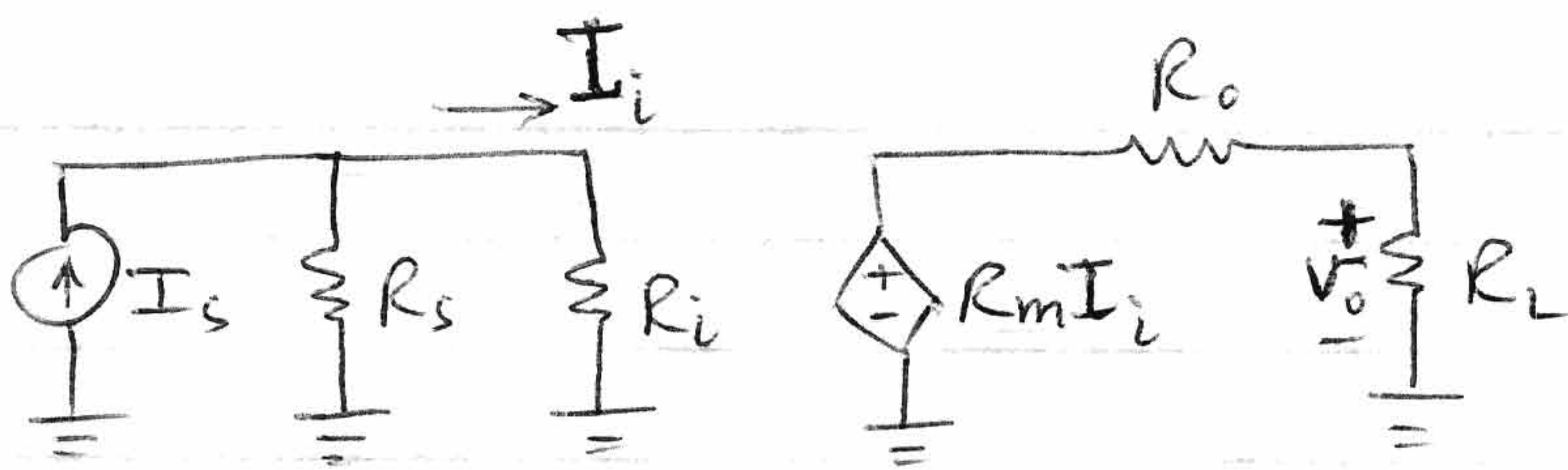$\Rightarrow R_i \rightarrow \text{large}$, ideal characteristics
 $R_o \rightarrow \text{large}$




$$I_i = \frac{R_s}{R_s + R_i} \cdot I_s \quad V_o = \frac{R_L}{R_L + R_o} \times R_m I_i$$

$$\therefore R = \frac{V_o}{I_s} = \frac{R_s}{R_s + R_i} \times \frac{R_L}{R_L + R_o} \times R_m$$

⇒ $R_i \rightarrow$ small, ideal characteristics
 $R_o \rightarrow$ small

⑦

Voltage amplifier :

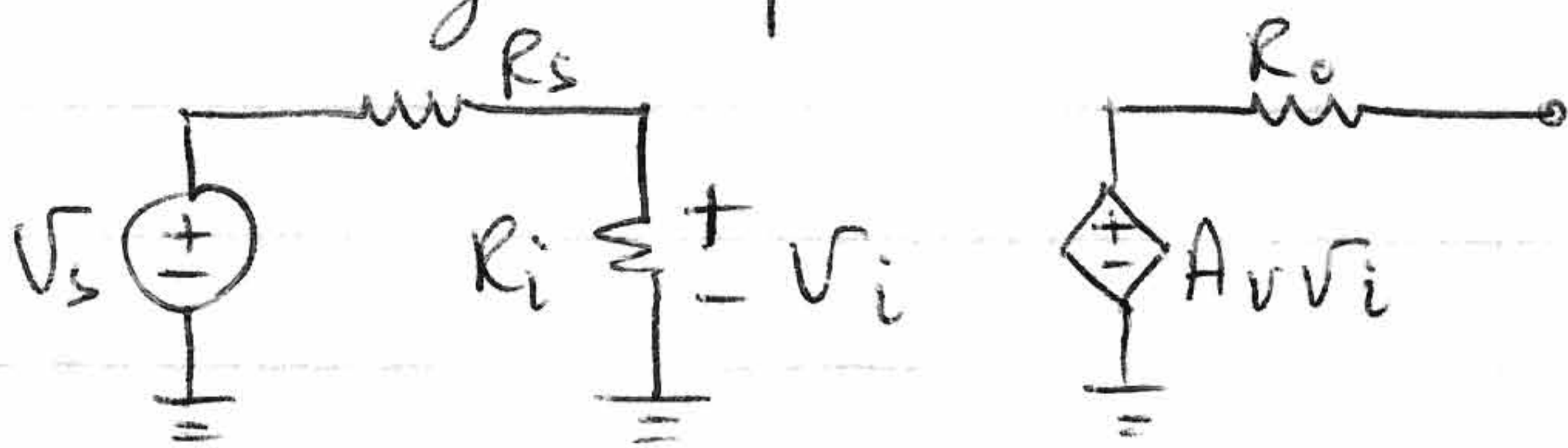


$$V_{oc} = A_v V_i = V_s \frac{R_i}{R_i + R_s} A_v$$

$$I_{sc} = \frac{A_v V_i}{R_o} = \frac{A_v R_i V_s}{R_o (R_i + R_s)}$$

$$\therefore \frac{V_{oc}}{I_{sc}} = R_o$$

Current amplifier :

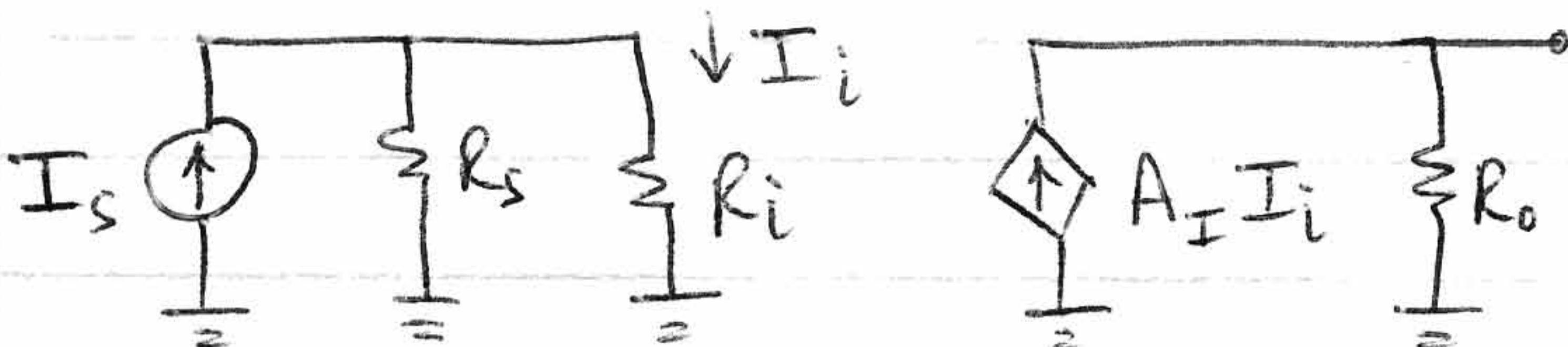


$$V_{oc} = A_i I_i R_o = A_i \frac{R_s}{R_s + R_i} I_s R_o$$

$$I_{sc} = A_i I_i$$

$$\therefore \frac{V_{oc}}{I_{sc}} = R_o$$

Transconductance amplifier :

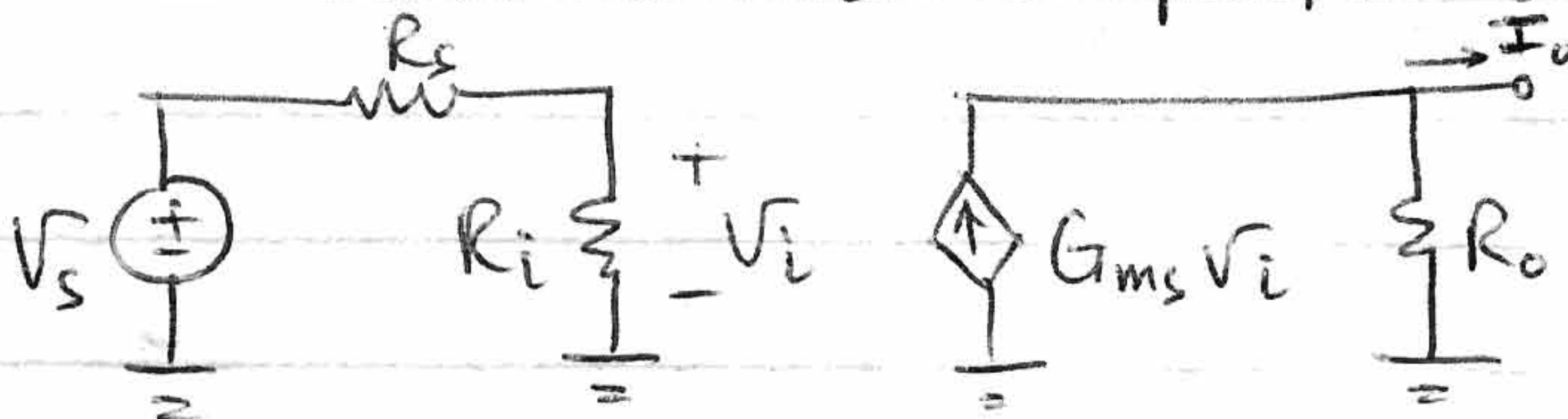


$$V_{oc} = G_m V_i R_o$$

$$I_{sc} = G_m V_i$$

$$\therefore \frac{V_{oc}}{I_{sc}} = R_o$$


Transresistance amplifier:

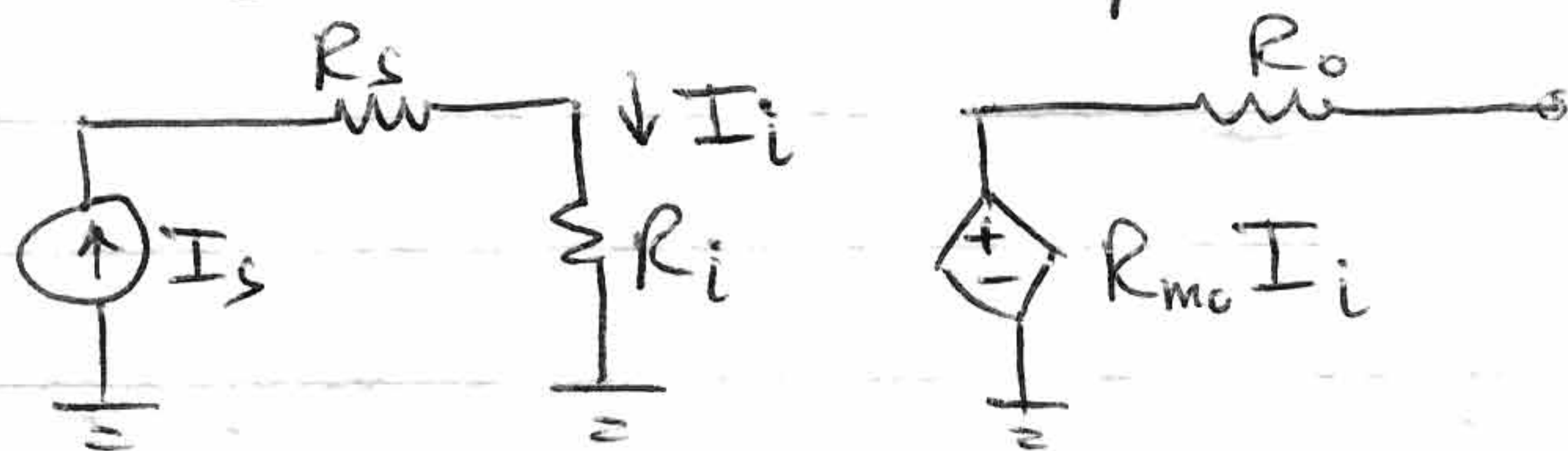

$$V_{oc} = R_{mo} I_i$$

$$I_{sc} = \frac{R_{mo} I_i}{R_o}$$
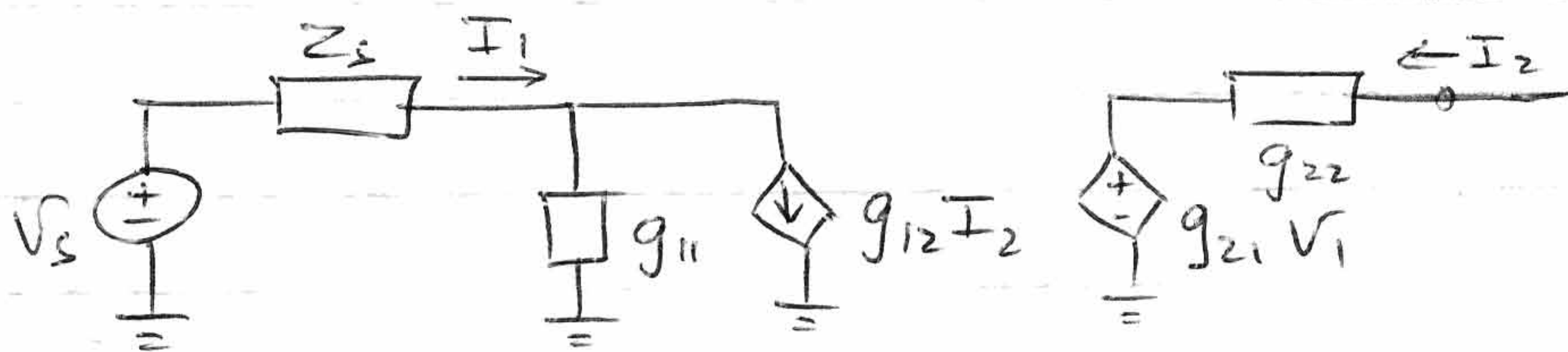
$$\therefore \frac{V_{oc}}{I_{sc}} = R_o$$



$$V_{oc} = g_{21} V_1 = g_{21} \frac{\frac{1}{g_{11}} V_s}{\frac{1}{g_{11}} + Z_s} = \frac{g_{21}}{g_{11} Z_s + 1} V_s$$

$$I_{sc} = g_{22} g_{21} V_1$$

$$\frac{V_s - V_1}{Z_s} = V_1 g_{11} + g_{12} I_2$$

$$I_2 = -I_{sc}$$

$$\therefore V_1 \left(g_{11} + \frac{1}{Z_s} \right) = \frac{V_s}{Z_s} + g_{12} I_{sc}$$

$$\therefore I_{sc} = \frac{g_{21} g_{22}}{g_{11} + \frac{1}{Z_s}} \left(\frac{V_s}{Z_s} + g_{12} I_{sc} \right)$$

$$I_{sc} \left(1 - \frac{g_{12} g_{21} g_{22}}{g_{11} + \frac{1}{Z_s}} \right) = \frac{g_{21} g_{22}}{g_{11} Z_s + 1} V_s$$


$$\therefore I_{sc} = \frac{1}{1 - \frac{g_{12} g_{21} g_{22}}{g_{11} + \frac{1}{Z_s}}} \cdot \frac{g_{21} g_{22}}{g_{11} Z_s + 1} V_s$$

Setting reverse current gain (g_{12}) to zero

$$\therefore I_{sc} = \frac{g_{21} g_{22}}{g_{11} Z_s + 1} V_s$$


$$\therefore \frac{V_{oc}}{I_{sc}} = \frac{1}{g_{22}} = \text{output impedance}$$

9.

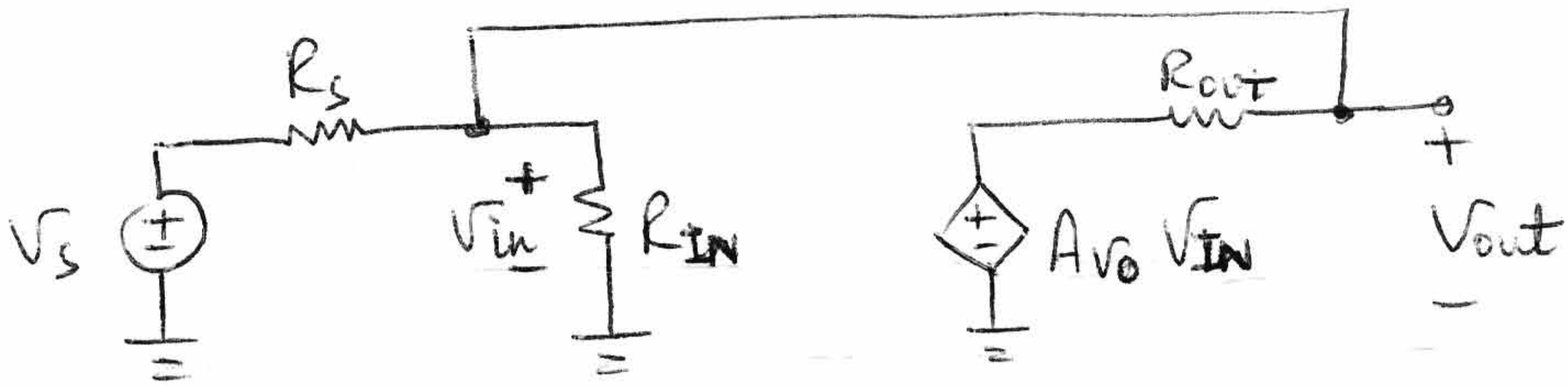

In order to determine R_{out}' set v_s to zero and apply a test voltage signal v_x to the output node. Determine the current i_x it supplies to the circuit.

$$R_{out}' = \frac{v_x}{i_x}$$

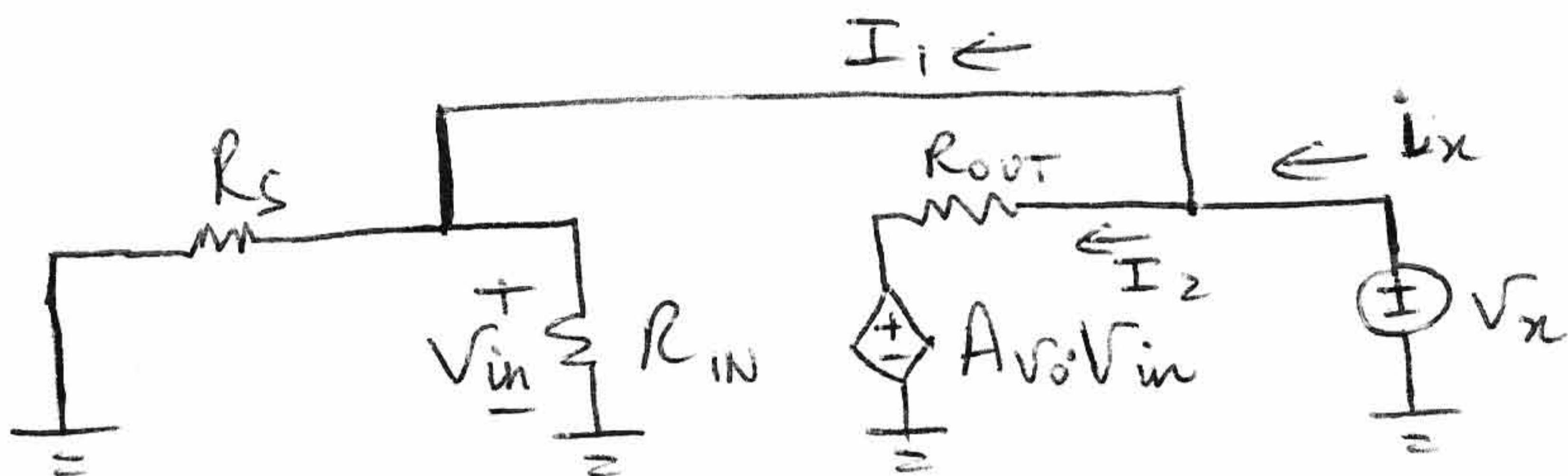

$$v_{in} = v_x$$

$$v_x = A_{v_0} \cdot v_{in} + I_2 R_{out}$$

$$I_2 = I_x - I_1 = i_x - \frac{v_x}{R_s \parallel R_{in}}$$

$$\therefore v_x = A_{v_0} \cdot v_x + i_x R_{out} - \frac{v_x R_{out}}{R_{out} \parallel R_{in}}$$

$$\frac{v_x}{i_x} = R_{out}' = \frac{R_{out}}{1 - A_{v_0} + \frac{R_{out}}{R_s \parallel R_{in}}} \quad \text{--- ①}$$

Since for a near-ideal amplifier,

$$\frac{R_{out}}{R_s \parallel R_{in}} \approx \frac{R_{out}}{R_s} < 1 \quad \text{and} \quad A_{v_0} \gg 1$$

①

be comes,

$$\frac{V_x}{V_0} = R_{out} \approx -\frac{R_{out}}{A_{v_0}}$$