

- From "chapter 3, no solutions"

i. Expressions:  $V_1 + V_2 = 1.657 \text{ V}$  (1)

$V_{D0} - I(1.67k) = 5 - (1.67k)I = 1.657 \text{ V}$  (2)

$I = I_s e^{\frac{V_1}{nV_T}}$  (3)

$\frac{I}{M} = I_s e^{\frac{V_2}{nV_T}}$  (4)

4 eqns

4 unknowns ( $I, V_1, V_2, M$ )


$\Rightarrow$  (2) yields  $I = 2 \text{ mA}$  directly

$\Rightarrow$  multiply (3)  $\times$  (4)  $\rightarrow \frac{I^2}{M} = I_s^2 e^{\frac{V_1 + V_2}{nV_T}} \rightarrow$  known from (1)

$\Rightarrow$  use (1)  $\rightarrow M = \frac{I^2}{I_s^2 e^{\frac{1.657}{1.25(25m)}}} = 37.56$  (pick a real integer: 37 or 38)

can we solve (3), (4) for  $V_1, V_2$  easily.

2.

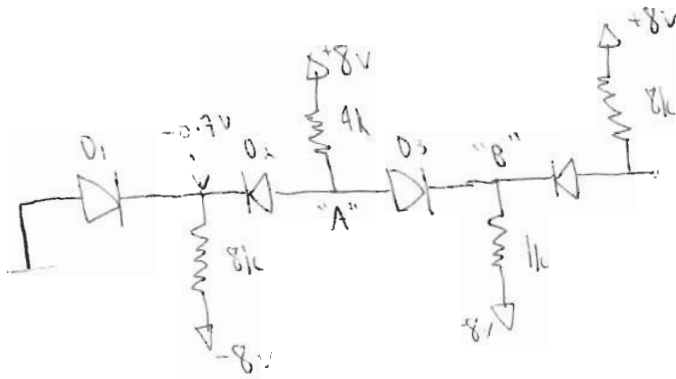

$\Rightarrow$  We must make assumptions & test them!

$\Rightarrow$  is  $D_3$  off? Try it!

$\Rightarrow$  get  $\frac{8 - V_{A,C}}{2k} = \frac{(V_{A,C} - 0.7) + 8}{1k}$

$V_{A,C} = -5.6 \text{ V}$ , so node B =  $-6.3 \text{ V}$

$\Rightarrow$   $D_2$  off would be obviously inconsistent!

$\Rightarrow$   $D_2$  on puts node "A" at ground  $\rightarrow$  no good for  $D_3$  off!

$\therefore D_3$  is ON


$\rightarrow$  so node "A" is at  $V_{A,C}$

$\rightarrow$  Try  $D_2$  off:  $\frac{(V_{A,C} - 0.7) + 8}{1k} = \frac{8 - V_{A,C}}{4k} + \frac{8 - V_{A,C}}{8k} = 3 \times \frac{8 - V_{A,C}}{8k}$   $V_{A,C} = -3.127 \text{ V}$


$\Rightarrow$  is  $D_2$  off? YES

- solution is consistent.

3.

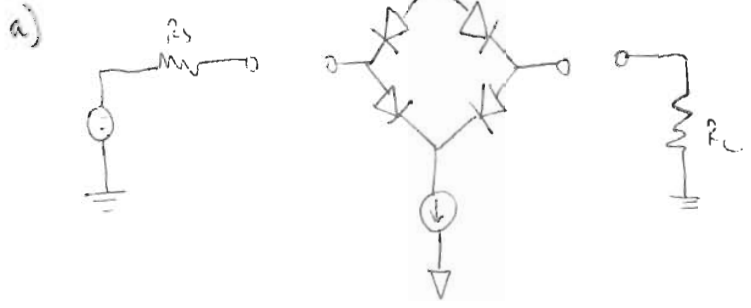

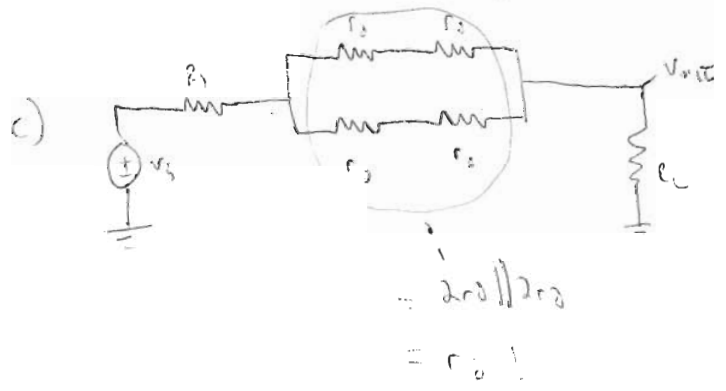b) by symmetry:  $I_{D1,2,3,4} = \frac{I_{ref}}{2}$  ;  $r_D = \frac{2nV_T}{I_{ref}}$



$$v_{out} = \frac{R_L}{R_L + r_s + R_L}$$

4.  $D_2, D_3$  off by inspection

$D_1, D_4$  cannot both be on

$D_5$  is most likely on  $\rightarrow v_D = 1.3 \rightarrow$  is  $D_1$  on?

yes  $\rightarrow$  (get by analysis)  $I_{back} = 11.3 \text{ mA}$  (no good...  $D_4$  is off by assumption?)  
 no  $\rightarrow$   $D_4$  must be on  $\rightarrow I_{back} = \frac{2V}{300 + 700} = 2 \text{ mA}$  ok


check  $D_1$ :  $\begin{matrix} 3.9V \\ \downarrow \\ \uparrow \\ 1.3V \end{matrix}$  off as assumed

b)  $I = \frac{1.3}{400} = 3.25 \text{ mA}$  (There must be 1.25 mA on  $D_5$ ...  $D_5$  is on as expected)

c)  $I_{back} = 2 \text{ mA}$

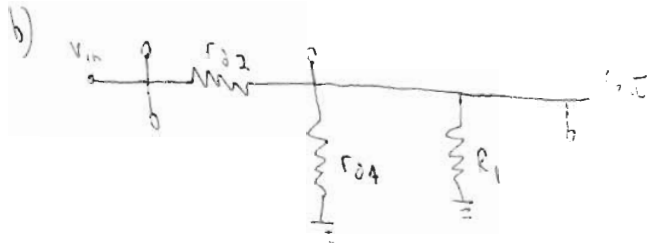5.a)  $D_1, D_5$  off by inspection

$I_{D2} = I_1, I_{D3} = I_2, I_{D4} = I_1 + I_2 \rightarrow$  these 3 diodes are ON




$$c) \frac{v_{out}}{v_{in}} = \frac{R_1 \parallel r_{D4}}{R_1 \parallel r_{D4} + r_{D2}} = 0.196 \text{ V/V}$$

$$r_{D2} = \frac{nV_T}{I_1}; \quad r_{D4} = \frac{nV_T}{I_1 + I_2}$$

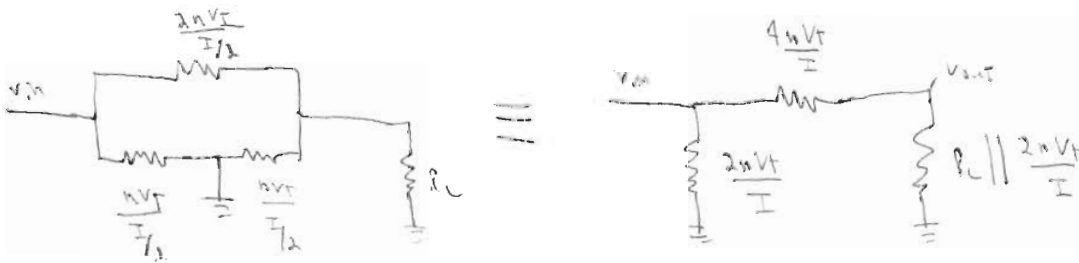6.  $I_{D3} = I$ ; if  $D_7$  is on then  $D_8$  is off (has 0.2 V reverse bias) ( $D_8$  on is impossible... Turns off  $D_7$ ... no current flow in  $D_8$ !)


$\rightarrow D_7$  on requires  $D_4, D_5, D_6$  on too  $\rightarrow I_{D4,5,6,7} = \frac{I}{2}$

$D_1, D_2$  are off (because  $v_{in}$  is not DC input)



$$\frac{v_{out}}{v_{in}} = 0.299 \text{ V/V by analysis}$$


7.

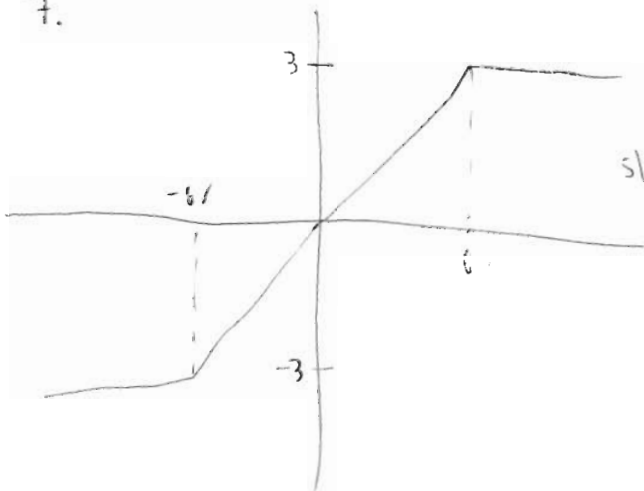

slope  $\cdot \frac{1}{2}$  by voltage divider

8-9 (skip)

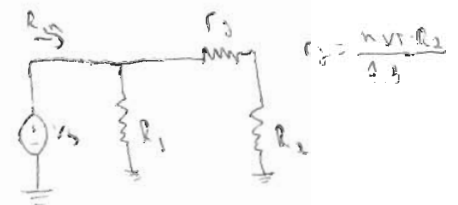
10. DC analysis:  $I_{R1} = \frac{5V}{R_1}; I_{R2} = \frac{4.3V}{R_2}$



$$R_{in} = R_1 \parallel \left( R_2 * \left( 1 + \frac{nV_T}{4.3} \right) \right)$$


7. (contd...)

1- When both diodes are off:

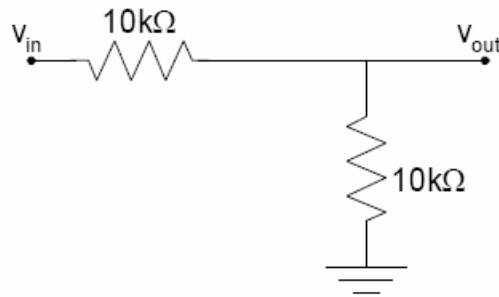

$$V_{out} = \frac{10k\Omega}{10k\Omega + 10k\Omega} V_{in} = V_{in} / 2$$

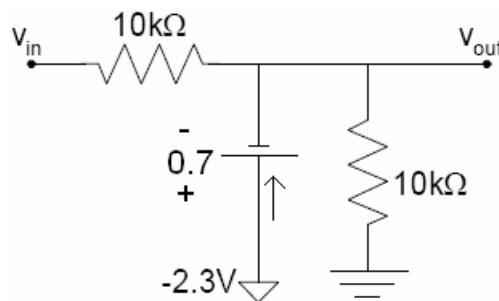2-The required input voltage to create the "ON" voltage at the cathode of  $D_2$  (let's call it  $V_A$ ):




When diode hasn't switched yet,

$$I_{D2} = 0A \Rightarrow V_A = \frac{10k\Omega}{10k\Omega + 10k\Omega} V_{in} = V_{in} / 2$$

We know  $V_A$  should be  $V_A < -2.3 - 0.7 = -3$  (note not -1.6) to switch  $D_2$  "ON"

Therefore  $v_{in} < -6$  for switching  $D_2$  "ON" and  $v_{out} = -3$

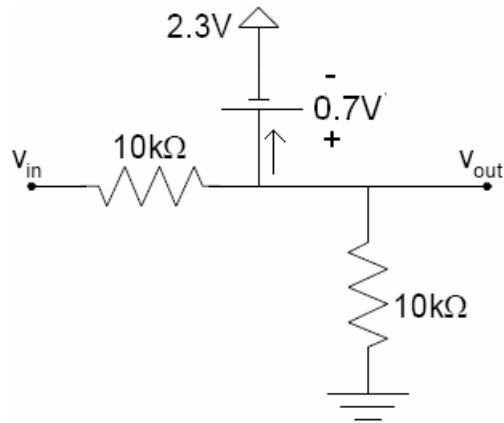3- Now, the required input voltage to create the "ON" voltage at the Anode of  $D_1$  (let's call it  $V_A$  again, it is the same node):



When the diodes are still off,

$$I_{D2} = 0A \Rightarrow V_A = \frac{10k\Omega}{10k\Omega + 10k\Omega} V_{in} = V_{in} / 2$$

We know  $V_A$  should be  $V_A > 2.3 + 0.7 = 3$  to switch  $D_1$  "ON"

Therefore  $v_{in} > 6$  for switching  $D_1$  "ON" and  $v_{out} = 3$

