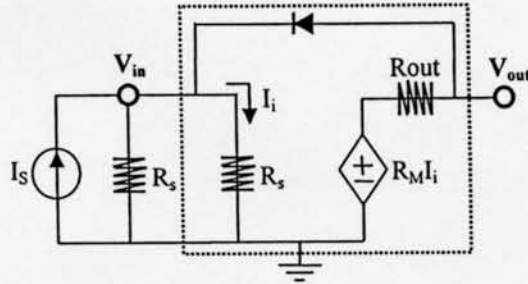


**Question#1 (9 pts.):**

(a) [2 pts.]

Correct Diagram:



*[-1 for incorrect source]  
[-0.5 for incorrect label]  
[0 for simply redrawing the given diagram]*

(b) [2 pts.]

The diode is OFF.

$$V_{in} = I_s \cdot R_s \parallel R_i$$

$$V_{out} = R_M \cdot I_i$$

$$I_i = \left[ \frac{R_s}{R_s + R_i} \right] \cdot I_s$$

*[-1 for incorrect  $V_{in}$ ,  $V_{out}$ , or  $I_i$ ]*

$$\begin{aligned} \therefore V_{out}/V_{in} &= R_M \cdot \left[ \frac{R_s}{R_s + R_i} \right] \cdot \left[ \frac{1}{R_s \parallel R_i} \right] \\ &= R_M \cdot \left[ \frac{R_s}{R_s + R_i} \right] \cdot \left[ \frac{(R_s + R_i)}{(R_s \cdot R_i)} \right] \\ &= R_M / R_i \\ &= 400 / 100 \\ &= 4 \end{aligned}$$

*[-1 for incorrect  $V_{out}/V_{in}$  expression]  
[-0.5 for mathematical error]*

(c) [2 pts.]

Clipping occurs when ( $V_{out} - V_{in} = 0.7V$ )

*[1 point for understanding this]*

$$V_{out} = R_M \cdot \left[ \frac{R_s}{R_s + R_i} \right] \cdot I_s$$

$$V_{in} = \left[ \frac{(R_s \cdot R_i)}{R_s + R_i} \right] \cdot I_s$$

$$\therefore I_s \cdot \left[ \frac{(R_M \cdot R_s) - (R_s \cdot R_i)}{R_s + R_i} \right] = 0.7$$

$$\begin{aligned} \therefore I_s &= 0.7(1.2k + 100) / 1.2K(400 - 100) \\ &= 2.53mA \end{aligned}$$

*[1 point for these calculations]*

(d) [1 pt.]

In the linear region, the diode is OFF.

$$\therefore R_{out} = R_o = 150\Omega.$$

*[No part marks]*

(e) [2 pts.]

$$I_L = (R_M \cdot I_i) / (R_o + R_L)$$

$$I_i = [R_s / (R_s + R_{in})] \cdot I_s$$

$$\therefore I_L / I_s = (R_M \cdot R_s) / [(R_o + R_L) \cdot (R_s + R_{in})]$$

$$= (400 \cdot 1.2K) / (200 + 1.3K)$$

$$= 1.846 \text{ A/A}$$

*[-1 for incorrect  $I_L$ ,  $I_i$ , or  $I_L/I_s$  expressions;*


*-1.5 for 2 out 3 incorrect]*

*[-1 for taking  $V_{out}$  from the previous parts and dividing by  $R_L$ . That is incorrect]*

*[-0.5 for mathematical errors]*

[Q2 Solution]:

a) [2 pts]

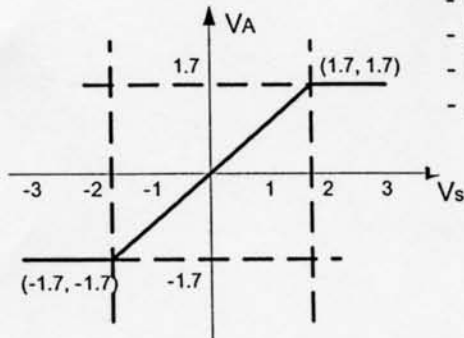

- Curve doesn't cross origin, -0.5 pts;
- Do not mark  $V_A$  axis correctly, -0.5 pts;
- Do not mark  $V_S$  axis correctly, -0.5 pts;
- Do not show voltage limiting on both sides, -0.5 pts;

b) [4pts] Since the DC component of  $V_s$  is 0, so both D1 and D2 are OFF by inspection, hence  $I_{D1} = I_{D2} = 0$ ;

By inspection, D4 and D5 cannot be both ON.

Assume D3, D4 and D6 ON, D5 OFF.

[Find out  $I_{D1} = I_{D2} = 0$  and made some assumptions, should get 0.5 pts;]

$$I_{D3} = \frac{3 - (V_B + 0.7)}{500} = \frac{2.3 - V_B}{500}$$

$$I_{D6} = \frac{3 - (V_C + 0.7)}{1k} = \frac{2.3 - V_C}{1k}$$

$$V_B = V_C + I_{D4} \times 100 + 0.7$$

By KCL:

$$I_{D3} = I_{D4} + I_1 = I_{D4} + 0.68m$$

$$I_{D4} + I_{D6} = I_2 = 10m$$

[Write these two sets equations right, got another 3 pts;]

Solve the above equations and got:


$$V_B = -0.84V \quad V_C = -2.1V \quad V_C - V_B = -1.26V \text{ so } D5 \text{ is OFF.}$$

$$I_{D3} = 6.8mA \quad I_{D4} = 5.6mA \quad I_{D5} = 0 \text{ and } I_{D6} = 4.4mA$$

[Find out the final answers correct, got another 0.5 pts, so total 4 pts;]

[Note: Failed to justify the assumption, -0.5 pts;

c) [2 pts]

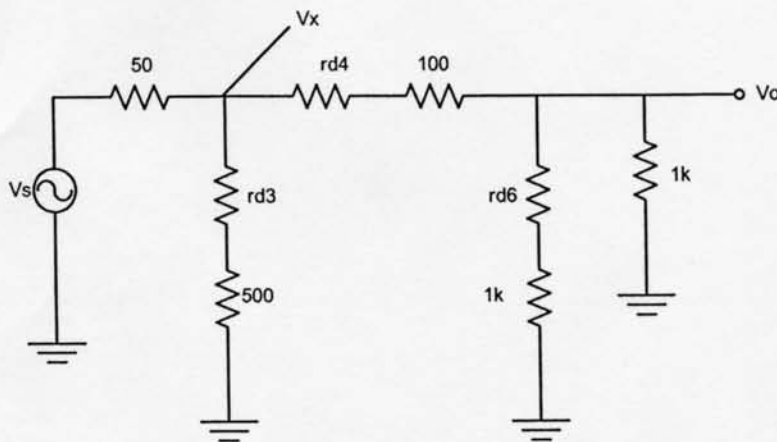

The small-signal must be consistent with the results in their part b). If due to the mistakes of part b that make part c any easier then expected, -1 pts;

For any single mistake in this part, -0.5 pts;

d)

[2 pts]

$$\frac{v_o}{v_s} = \frac{v_o}{v_x} \times \frac{v_x}{v_s}$$

$$\frac{v_o}{v_x} = \frac{1k \parallel (rd6 + 1k)}{rd4 + 100 + 1k \parallel (rd6 + 1k)} \quad 1 \text{ pts}$$

$$\frac{v_x}{v_s} = \frac{(rd3 + 500) \parallel (rd4 + 100 + 1k \parallel (rd6 + 1k))}{50 + (rd3 + 500) \parallel (rd4 + 100 + 1k \parallel (rd6 + 1k))} \quad 1 \text{ pts}$$

e) [3 pts] For D4 D5 both OFF,

$$|V_B - V_C| < 0.7V \quad (*) \quad 0.5 \text{ pts}$$

$$V_B = 3 - 500 * I_1 - 0.7 \quad (1) \quad 0.5 \text{ pts}$$

$$V_C = 3 - 1k * I_2 - 0.7 \quad (2) \quad 0.5 \text{ pts}$$

Substitute (1), (2) into (\*)

$$|10 - 500 * I_1| < 0.7$$


$$18.6mA < I_1 < 21.4mA \quad 1.5 \text{ pts}$$

If only got half of the answer, should get 1.5 pts in total; And if include 18.6mA and 21.4mA as the answer, -0.5 pts;

[Q3 Solution]:

a)

[5 pts]

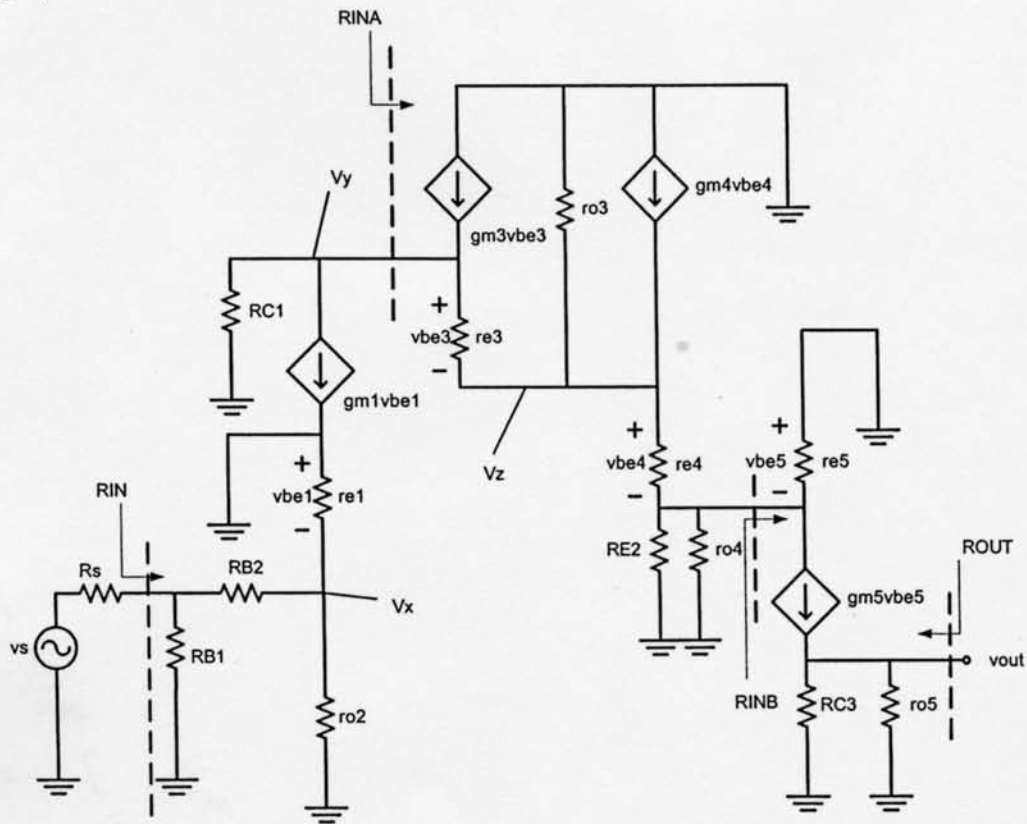

For any mistake, - 0.5 pts;

b)  $R_{IN} = R_{B1} \parallel (R_{B2} + r_{o2}/r_{e1})$  [1 pts]  
 $R_{INA} = (\beta+1) [r_{e3} + r_{o3} \parallel ((\beta+1) (r_{e4} + r_{o4} \parallel R_{E2} \parallel R_{INB}))]$  [1 pts]  
 $R_{INB} = (\beta+1) r_{e5}$  [1 pts]  
 $R_{out} = r_{o5} \parallel R_{C3}$  [1 pts]

For any mistake in part a) that makes part b) easier than expected, -0.5 pts.

c) [4 pts] 1 pts for each equation, -0.5 pts for partial answers;

$$\frac{v_x}{v_s} = \frac{r_o \parallel r_{e1}}{R_{B2} + r_o \parallel r_{e1}} \times \frac{R_{in}}{R_s + R_{in}}$$

$$\frac{v_y}{v_x} = gm_1 \cdot (R_{C1} \parallel R_{INA})$$

$$\frac{v_z}{v_y} = \frac{R_{E2} \parallel r_{o4} \parallel R_{INB}}{r_{e4} + R_{E2} \parallel r_{o4} \parallel R_{INB}} \times \frac{r_{o3} \parallel [(\beta+1)(r_{e4} + R_{E2} \parallel r_{o4} \parallel R_{INB})]}{r_{e3} + r_{o3} \parallel [(\beta+1)(r_{e4} + R_{E2} \parallel r_{o4} \parallel R_{INB})]}$$

$$\frac{v_{out}}{v_z} = -gm_5 \cdot (R_{C3} \parallel r_{o5})$$

Solution

Q4

$V_{DD} = 5V, \lambda = 0.02 V^{-1}, V_{t0} = 1V$

a)  $V_{t1} = 1V$  (no Body effect) 0.5

$V_{t2} = V_{t0} + \gamma (\sqrt{2\phi + V_{SB}} - \sqrt{2\phi}) = 1V + 0.75 (\sqrt{2.4 + 1} - \sqrt{2.4}) = 1.221 V$

b) both FETs are in saturation, so...

$I_3 = I_1 + I_2 = \frac{1}{2} k'_n \frac{W}{L} (V_{GS1} - V_{t1})^2 (1 + \lambda V_{DS1}) + \frac{1}{2} k'_n \frac{W}{L} (V_{GS2} - V_{t2})^2$  Eqn: 5 pt

$4mA = \frac{1}{2} k'_n \frac{W}{L} [(3-1)^2 (1 + 0.02(3)) + (3-1-1.221)^2]$  -1 if neglect CLM or Body  
 $k'_n \frac{W}{L} = 1.6505 mA/V^2$  ans: 0.5 pt (-0.5 for math error)


c)  $I_1 = \frac{1}{2} k'_n \frac{W}{L} (3-1)^2 (1 + 0.02(3)) = 3.5mA$

$I_2 = I_3 - I_1 = 0.5mA \Rightarrow R_{S2} = \frac{1-0}{0.5mA} = 2k\Omega$  1 pt

M2 sat mode requires  $V_D > V_G - V_{t2} > 1.779$

so  $R_{D2} < \frac{5-1.779}{0.5mA} = 6.44k\Omega$  1 pt (-0.5 if inequality sign is wrong)

d)

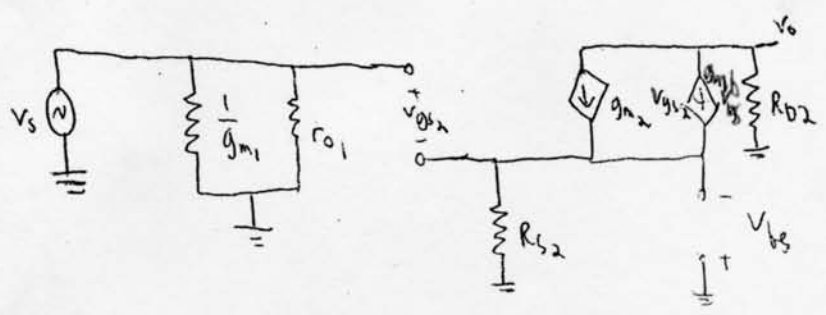


(-1. forgetting Body)

2 pts

(0.5 if "ro1" alone)

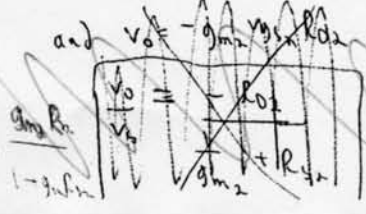e)  $v_{GS2} = v_s - g_{m1} v_{GS2} R_{S2} - g_{m1} v_{GS2} R_{S2}$   
 $\Rightarrow v_{GS2} = \frac{v_s}{1 + g_{m1} R_{S2}}$   
 $-V_{BS2} = v_s - v_{GS2}$



$R_{in} = \frac{1}{g_{m1}} \parallel r_{o1}$  1 pt

$v_o = \frac{-g_{m2} R_{D2}}{g_{m2} R_{D2} + 1 + g_{m2} R_{D2}} v_{GS2}$  2 pts / 4

see next page

$$e) \frac{-V_o}{R_o} = \frac{v_s - v_{gs2}}{R_{S2}} \quad (1)$$

$\Rightarrow$  need  $v_{gs}$  in terms of  $v_s$ !

$$v_{gs2} = v_s - [g_{m2} v_{gs2} + g_{m6} v_{bs}] R_s$$

$$= v_s - [g_{m2} v_{gs2} + g_{m6} (v_{gs2} - v_s)] R_s \quad (\text{using } -v_{bs} = v_s - v_{gs2})$$

$$v_{gs2} [1 + g_{m2} R_s + g_{m6} R_s] = v_s [1 + g_{m6} R_s]$$


$$v_{gs2} = v_s \frac{[1 + g_{m6} R_s]}{[1 + g_{m6} R_s + g_{m2} R_s]}$$

$$\Rightarrow (1) \therefore \frac{V_o}{v_s} = -\frac{R_o}{R_{S2}} \left( 1 - \frac{1 + g_{m6} R_s}{1 + g_{m6} R_s + g_{m2} R_s} \right)$$



Q5


a) by Thevenin, input looks like

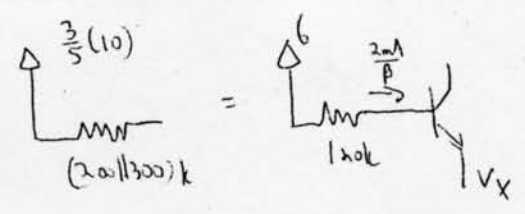

$$V_x = 6 - \frac{2mA}{99} (120k) - 0.7 = 2.875 V \quad \underline{2 \text{ pts}}$$

(-1 for incorrect Thevenin)

b)

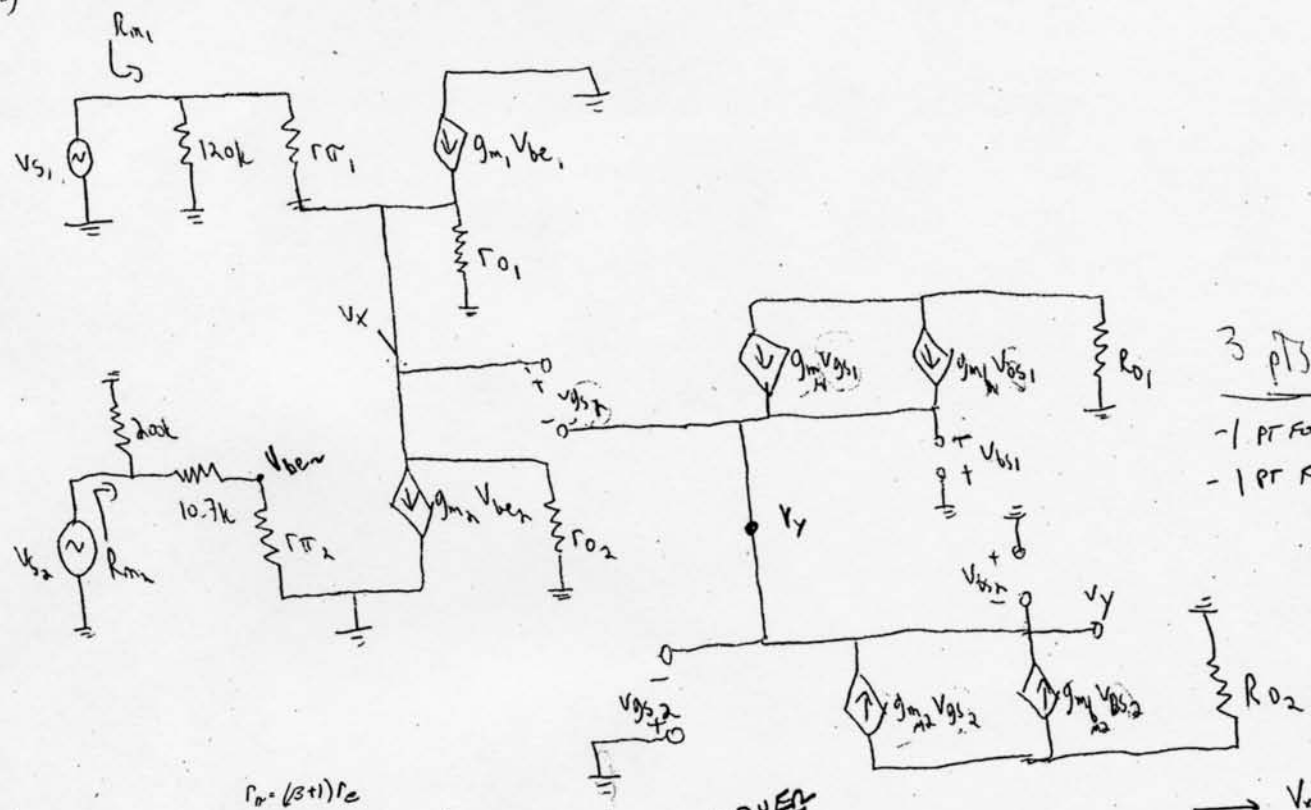

3 pts  
-1 pt for no ro1, ro2  
-1 pt for no Vbe2

$r_o = (\beta + 1)r_e$   
 $120k \parallel (\beta + 1)(r_e + r_{o1} \parallel r_{o2})$

c)  $R_{in1} = 120k \parallel [r_{\pi 1} + (\beta + 1)(r_{o1} \parallel r_{o2})]$  1 pt

$$\frac{V_x}{V_{S1}} = \frac{(\beta + 1)(r_{o1} \parallel r_{o2})}{(\beta + 1)(r_{o1} \parallel r_{o2}) + r_{\pi 1}} \quad \underline{2 \text{ pts}}$$

→ OVER

d)  $R_{in2} = 200k \parallel (10.7k + r_{\pi 2})$  1 pt

$$\Rightarrow V_{be2} = V_{S2} \frac{r_{\pi 2}}{r_{\pi 2} + 10.7k}; \quad g_{m2} V_{be2} = g_{m1} V_{be1} - \frac{V_x}{r_{\pi 1} \parallel r_{o1} \parallel r_{o2}}$$

$V_{S1} = V_x - V_y$

e)  $g_{m1}(V_{S1} + V_{S2}) + g_{m1}(V_{be1} + V_{be2}) = 0; \quad g_{m1}(V_x - V_y - V_y) + g_{m1}(-V_y - V_y)$

$$V_y (2g_{m1} + 2g_{m2}) = g_{m1} V_x$$

$$\frac{V_y}{V_x} = \frac{g_{m1}}{2g_{m1} + 2g_{m2}} \approx \frac{1}{2(1 + \frac{g_{m2}}{g_{m1}})} \quad \underline{2 \text{ pts}}$$

$$\Rightarrow g_{m2} V_{S2} \frac{r_{\pi 2}}{r_{\pi 2} + 10.7k} = -V_x \left[ g_{m1} - \frac{1}{r_{\pi 1} \parallel r_{o1} \parallel r_{o2}} \right]$$

$$\frac{V_x}{V_{S2}} = \frac{g_{m2} r_{\pi 2}}{r_{\pi 2} + 10.7k} \frac{1}{\frac{1}{r_{\pi 1} \parallel r_{o1} \parallel r_{o2}} + g_{m1}} \quad \underline{2 \text{ pts}}$$


$$-\beta \frac{(r_{o1} \parallel r_{o2})}{r_{\pi 2} + 10.7k}$$

... if they ignore Vbe1 Take off 1 mark



5d) From T-model
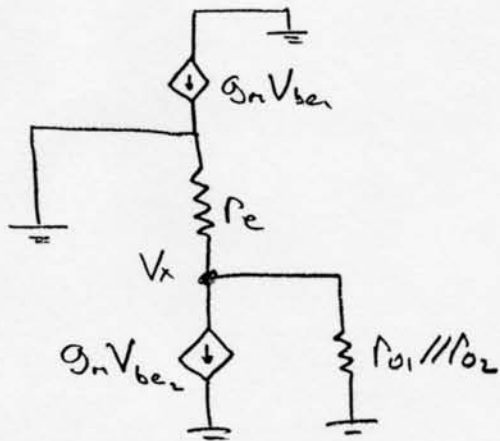
$$V_{be2} = V_{s2} \frac{r_{\pi 2}}{r_{\pi 2} + 10.7k}$$



$$0 - V_x = g_m V_{be2} + \frac{V_x}{r_{o1} // r_{o2}}$$

$$\frac{V_x}{V_{be2}} = -g_m (r_{o1} // r_{o2} // r_e)$$

$$\frac{V_x}{V_{s2}} = -g_m (r_{o1} // r_{o2} // r_e) \frac{r_{\pi 2}}{r_{\pi 2} + 10.7k}$$

**Question#6 (9 pts.):**

(a) [3 pts.]

$$I_{REF} = (1.8 - 1.2) / 12K = 50\mu A \quad [1 \text{ Point}]$$

$I_{oi}$  may be estimated as follows:

$$\therefore W_2/W_1 = 3\mu/1.2\mu = 2.5$$

$$\therefore I_{oi} = 2.5 \cdot 50\mu A = 125\mu A \quad [1 \text{ Point}]$$

$$R_{oi} = 1/(\lambda I_{oi}) = 1 / (0.02 \cdot 125\mu) = 400k\Omega \quad [1 \text{ Point}]$$

(b) [1 point]

The input resistance into a FET gate is  $R_{in} = \infty$  [No part marks]

(c) [3 Pts]

[Both  $R_{out1}$  and  $R_{out2}$  may be solved by symmetry/single-ended treatment. Each is worth 1.5 points. Partial marks are given for correct method but incorrect answer]

$$R_{out1} = 2 \cdot (R_L/2 \parallel R_D) \quad \Omega \quad [1.5 \text{ Pts.}]$$

$$R_{out2} = 2 \cdot (R_{oi} \parallel 1/g_m) \quad \Omega \quad [1.5 \text{ Pts.}]$$

(d) [3 Pts.]

[Both  $V_{o1}/V_{in}$  and  $V_{o2}/V_{in}$  may be solved by symmetry/single-ended treatment. Each is worth 1.5 points. Partial marks are given for correct method but incorrect answer]

$$V_{o1}/V_{in} = (V_{D1} - V_{D2})/V_{in} = -g_m \cdot [R_L/2 \parallel R_D] \quad V/V \quad [1.5 \text{ Pts.}]$$

$$V_{o2}/V_{in} = (V_{S1} - V_{S2})/V_{in} = 1/(1/g_m + R_{oi}) \quad V/V \quad [1.5 \text{ Pts.}]$$

Alternatively, one may use voltage divider to determine  $V_{o2}$ , using  $V_{o1}$  as the input voltage. This gives the following answer:

$$V_{o2}/V_{in} = (V_{S1} - V_{S2})/V_{in} = R_{oi} / (1/g_m + R_{oi}) \quad V/V \quad [Also acceptable for 1.5 Pts.]$$