

- Name: _____

Student Number: _____

McGill University


Faculty of Engineering

Department of Electrical and Computer Engineering

Final Examination: Electronic Circuits I - ECSE-330B

April 11th 2006, 2:00 PM – 5:00 PM

Examiner: Dr. Ramesh Abhari;

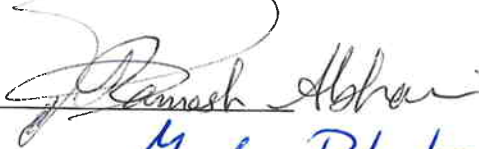

Associate Examiner: Dr. Gordon Roberts;



Instructions:

- 1) This is a closed-book examination, no notes permitted. There are 2 pages of equations provided at the end of the questions.
- 2) The examination consists of 7 problems with the total possible points of 50. Partial point distribution is indicated in brackets.
- 3) The examination consists of 10 pages, including this page and the equation pages; please ensure you have a COMPLETE exam book.
- 4) Only the Faculty Standard Calculator is permitted.
- 5) Write your answers in the provided Answer Booklets.
- 6) Show your work: Answers without justification will not receive marks. State any assumption you find necessary to complete your answer.

| | |
|----------------|--|
| Last Name | |
| First Name | |
| Student Number | |

| Question | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
|--------------|------------|----|----|----|-----|----|-----|
| Mark | /3 | /6 | /5 | /7 | /11 | /8 | /10 |
| TOTAL | /50 | | | | | | |


Question #1 (3 pts)

Two amplifier stages are connected in cascade to operate between a voltage source (v_s) with **1M Ω source resistance** and a **1k Ω load**. The first amplifier stage, which is a voltage amplifier, has an **input resistance of 500k Ω** , an **open circuit voltage gain of 200V/V**, and an **output resistance of 80k Ω** . The second stage, which is a transconductance amplifier, has an **input resistance of 100k Ω** , an **output resistance of 20k Ω** , and a **short circuit transconductance of 5mA/V**.

- a) Draw the entire circuit model from the voltage source to the 1k Ω load. (1 pt)
- b) What is the overall voltage gain, v_{out}/v_s . v_{out} is the voltage measured across the load.(1 pt)
- c) Consider the output current is i_o . What is the overall transconductance gain, i_o/v_s , if we replace the 1k Ω load resistor with a short circuit? (1 pt)

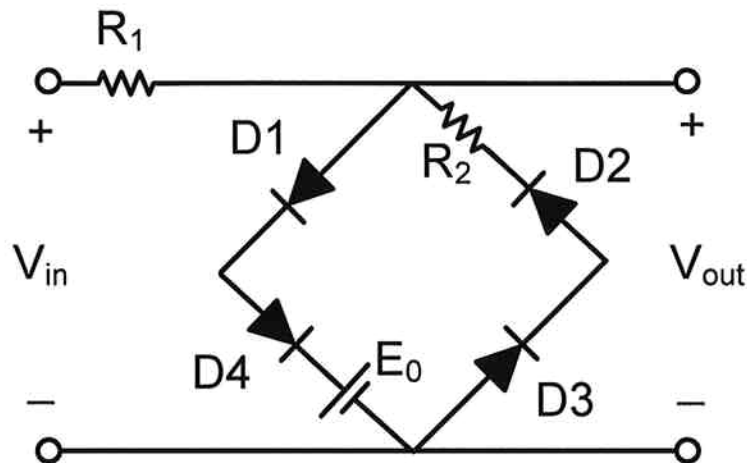Question #2 (6 pts)

In the following circuit, $R_1= 150\Omega$, $R_2= 100\Omega$, $E_0=1.6V$. All the diodes are the same with $V_{D(on)}= 0.7V$. The small signal resistance of each diode in forward bias is 25Ω .




- a) If the input voltage is $V_{in} = 5 + 0.001 \times \cos(2\pi t)$ V, find the DC and AC output voltages, i.e. $V_{out} = V_{out}(DC) + V_{out}(AC)$. (3 pts)

- b) If the DC level of the input voltage is changed to -5V as given in $V_{in} = -5 + 0.001 \times \cos(2\pi t)$ V, find the DC and AC output voltages, i.e. $V_{out} = V_{out}(DC) + V_{out}(AC)$. (3 pts)

Question #3 (5 pts)

Consider the following BJT current steering circuit. All npn transistors are identical with $\beta_N = 100$, and all pnp transistors are identical with $\beta_P = 80$. The operating mode for all transistors are assumed to be the active mode, and $|V_{BE}| = 0.7$.

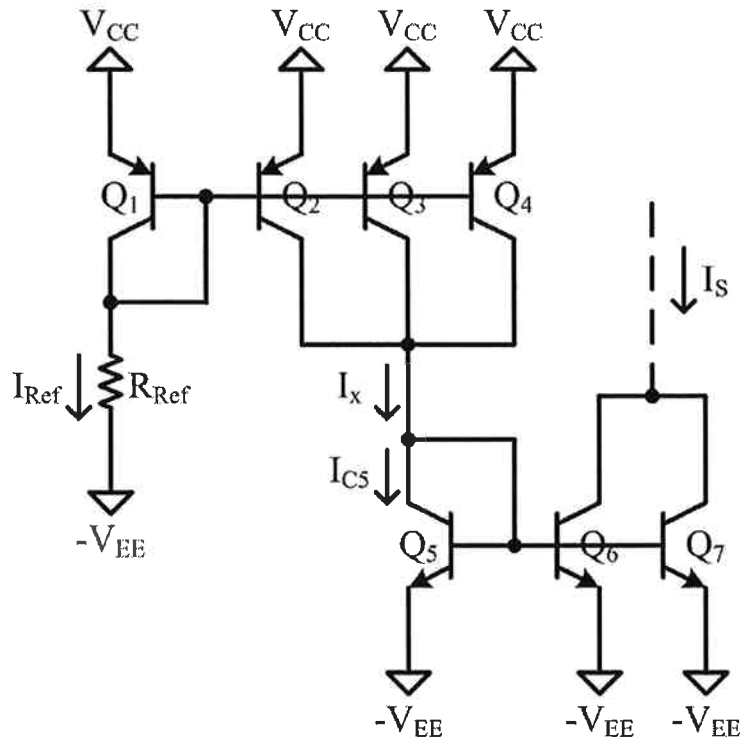


Considering $I_S = 8\text{mA}$, $V_{CC} = 5\text{V}$ and $V_{EE} = 5\text{V}$,

- Calculate I_{C5} and I_x . (2 pts)
- Calculate I_{Ref} and R_{Ref} . (3 pts)

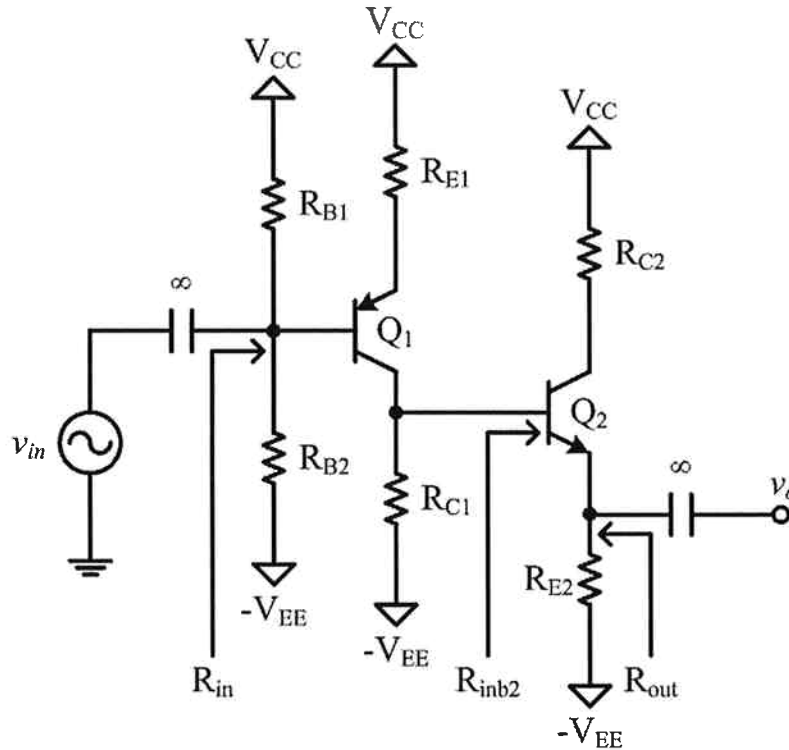Question 4 (7 pts)

Consider the following two-stage BJT amplifier. You can assume that all transistors are in active mode and that they have the same β . The early effect for both transistors can be ignored.



- Draw the small signal model of the above circuit. (2 pts)
- Find an expression for R_{in} . (1 pt)
- Find an expression for R_{inb2} . (1 pt)
- Find an expression for R_{out} . (1 pt)
- Derive an expression for v_o/v_{in} . (2 pts)


Question #5 (11 pts)

In the following circuit, all NMOS and PMOS transistors are operating in the saturation region. Assume $R_1 = 200\text{k}\Omega$, $R_2 = 400\text{k}\Omega$, $R_3 = 2\text{k}\Omega$, $R_4 = 1\text{k}\Omega$, $R_L = 3\text{k}\Omega$, $R_S = 1\text{k}\Omega$.

The transistor parameters are $\mu_n C_{OX} = 100\mu\text{A}/\text{V}^2$, $\mu_p C_{OX} = 50\mu\text{A}/\text{V}^2$, $V_{tn} = -V_{tp} = 0.5\text{V}$, $(W/L)_1 = (W/L)_3 = 10$, and $(W/L)_2 = 20$.

The supply voltage is $V_{DD} = 6\text{V}$. The DC voltage at the source of M1 is zero, i.e. $V_{in}(DC) = V_{S1}(M1) = 0$.

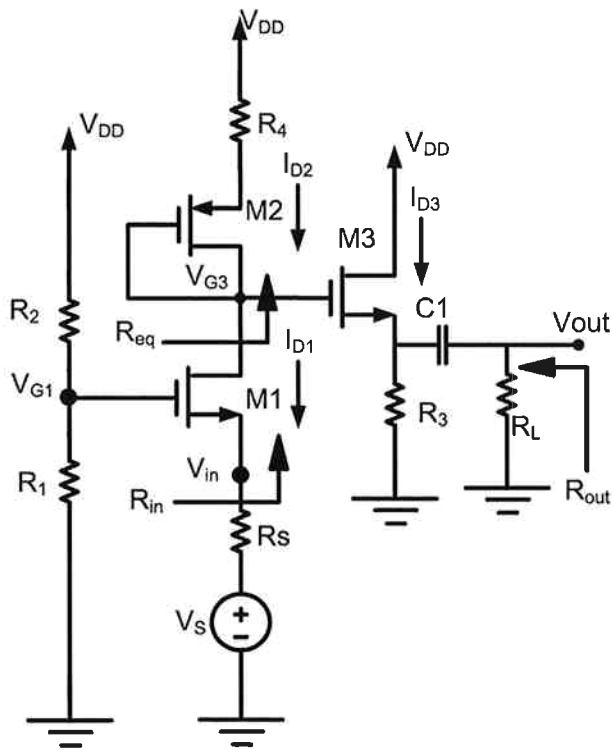Note that the body effect and channel length modulation can be ignored in DC and small signal analysis.




- Calculate V_{G1} , I_{D1} , I_{D2} , V_{G3} , and I_{D3} and verify that all transistors are operating in the saturation mode. (5 pts)
- Derive an expression for R_{eq} and draw the small signal model of the entire circuit. No need to calculate the numerical values. (2 pts)
- Derive expressions for R_{out} , R_{in} and V_{out}/V_S . No need to calculate the numerical values. (4 pts)

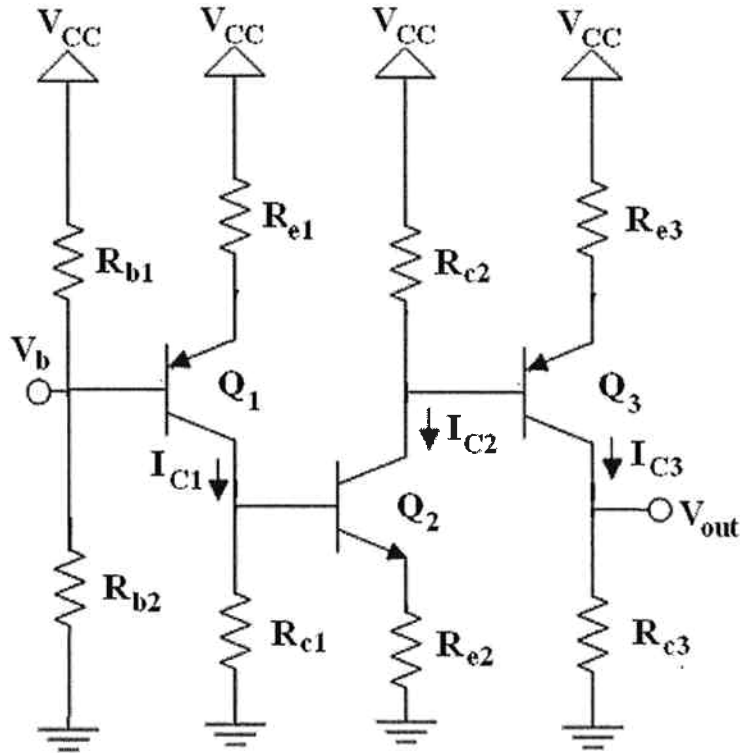Question 6 [8 pts]:

In the following circuit:

$R_{b1} = 3k\Omega$, $R_{b2} = 7k\Omega$, $R_{e1} = 2.25k\Omega$, $R_{c1} = 5k\Omega$, $R_{e2} = 2.25k\Omega$, $R_{c2} = 2k\Omega$, $R_{e3} = 3.3k\Omega$, $R_{c3} = 2k\Omega$, $V_{CC} = 10V$, and $\beta = 50$ for all transistors. The Early effect can be ignored for all transistors.



Find the values for V_b , I_{C1} , I_{C2} , I_{C3} , and V_{out} and verify your assumption about the mode of operation of all transistors. (8 pts)


Question 7 [10 pts]:

Consider the following differential amplifier circuit. Assume that all BJTs are identical and have $|V_{BE}| = 0.7\text{ V}$. The Early effect can be ignored for all transistors. The input terminals are v_{B1} and v_{B2} , the differential input is $v_d = v_{B1} - v_{B2}$ and the output terminals are v_{C1} and v_{C2} .

$R_{C1} = R_{C2} = 2\text{ k}\Omega$

$R_E = 5\text{ k}\Omega$

$\beta = 99$ for all BJTs

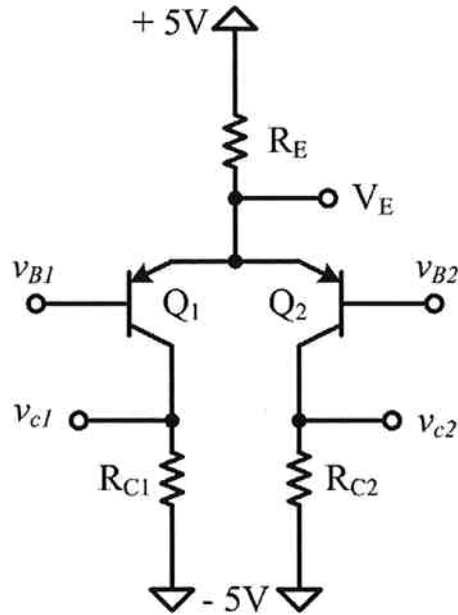

- a) If $V_{B1} = -0.8\text{ V}$ and $V_{B2} = 0.2\text{ V}$, find V_E , V_{C1} and V_{C2} . (2 pts)
- b) If $V_{B1} = 0.5\text{ V}$ and $V_{B2} = 0.5\text{ V}$, find V_E , V_{C1} and V_{C2} . (2 pts)
- c) Draw the small signal model for this circuit. (2 pts)
- d) Derive expressions for the *differential voltage gain*, *differential input resistance*, *differential output resistance* and the *Common mode gain*. Considering the base voltages indicated in part (b), calculate the numerical values for these four parameters. (3 pts)
- e) If the output is connected to a resistive load $R_L = 20\text{ k}\Omega$, i.e. R_L is connected between v_{c1} and v_{c2} terminals, calculate the new differential voltage gain. (1 pt)

Diodes:

$$i = I_s (\exp(v/nV_T) - 1)$$

FETs:

NMOS:

Cutoff: $V_{GS} < V_t$ $I_D = 0$ $k'_n = \mu_n C_{ox}$

Triode: $V_{GS} > V_t$ $I_D = k'_n \frac{W}{L} [(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2]$
 $V_{DS} < V_{GS} - V_t$

Saturation: $V_{GS} > V_t$ $I_D = \frac{1}{2}k'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$
 $V_{DS} > V_{GS} - V_t$

Body effect: $V_t = V_{t0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$

PMOS:

Cutoff: $V_{GS} > V_t$ $I_D = 0$ $k'_p = \mu_p C_{ox}$

Triode: $V_{GS} < V_t$ $I_D = k'_p \frac{W}{L} [(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2]$
 $V_{DS} > V_{GS} - V_t$

Saturation: $V_{GS} < V_t$ $I_D = \frac{1}{2}k'_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$
 $V_{DS} < V_{GS} - V_t$

Body effect: $|V_t| = |V_{t0}| + \gamma (\sqrt{2\phi_f + |V_{SB}|} - \sqrt{2\phi_f})$

SMALL SIGNAL

$$g_m = \frac{2 \cdot I_D}{V_{GS} - V_t}$$

$$g_m = k'_n \frac{W}{L} (V_{GS} - V_t) (1 + \lambda \cdot V_{DS})$$

$$g_m = \sqrt{2k'_n} \sqrt{\frac{W}{L}} \sqrt{1 + \lambda \cdot V_{DS}} \sqrt{I_D}$$

$$r_o = \frac{1}{\lambda \cdot I_D}$$

$$g_{mb} = \chi \cdot g_m$$

$$\chi = \frac{\gamma}{2} \cdot \frac{1}{\sqrt{2\phi_f + V_{SB}}}$$

Two-Page

Formula Sheet

Page 1 of 2

BJTs:

$$i_C = I_S \exp(v_{BE}/V_T)$$

$$i_B = \frac{i_C}{\beta}$$

$$i_E = \frac{i_C}{\alpha}$$

$$i_B = (1-\alpha)i_E = \frac{i_E}{\beta+1}$$

$$i_E = (\beta+1)i_B$$

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C} = \frac{\alpha}{g_m}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{\beta}{g_m} \quad r_o = \frac{V_A}{I_C}$$

$$r_\pi = (\beta+1)r_e$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \alpha = \frac{\beta}{\beta+1} \quad \beta+1 = \frac{1}{1-\alpha}$$