



Introduction to Electronics ECSE330 - Sec.001

April 25th 2007, 2:00pm - 5:00pm

Examiner: Prof. Ramesh Abhari

Assoc Examiner: Prof. Roni Khazaka

Signature:

Signature:


Student Name:		McGill ID:												
---------------	--	------------	--	--	--	--	--	--	--	--	--	--	--	--

INSTRUCTIONS:


- This is a **CLOSED BOOK** examination. No notes are permitted.
- There are 2 pages of equations provided at the end of the questions.
- The examination consists of **8 problems** with the **total possible points of 50**. Partial point distribution is indicated in brackets.
- The examination consists of **11 pages**, including this page and the equation pages; make sure you have a **COMPLETE** exam book.
- Faculty of Engineering **STANDARD CALCULATOR** permitted **ONLY**.
- **Show your work:** Answers without justification will not receive marks. State any assumption you find necessary to complete your answer.

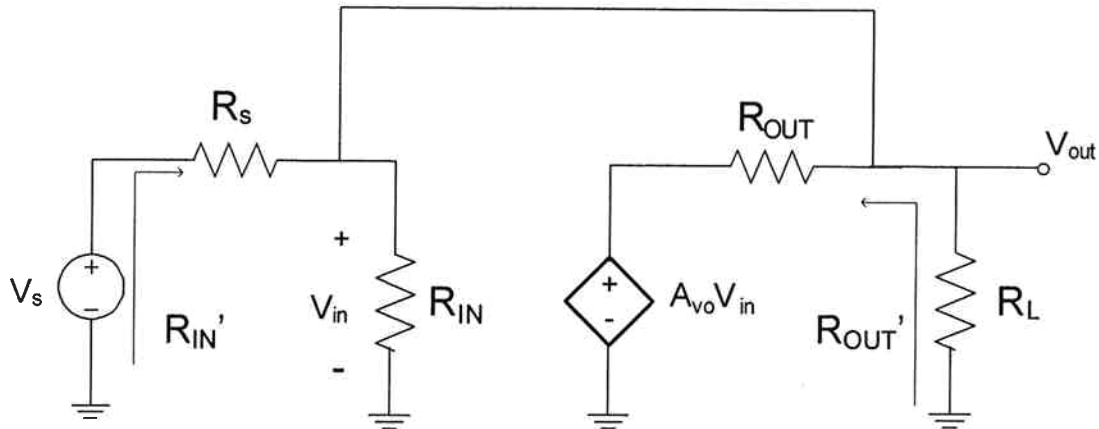Question 1 (4 pts)

A voltage amplifier has its output connected back to its input as indicated in the figure below.




- Derive expressions for the output resistance (R_{OUT}') and input resistance (R_{IN}') of the amplifier. (1 pt)
- Derive the expression for the overall voltage transfer function (V_{out}/V_s) of the amplifier. (0.5 pt)
- The circuit in part c) is now modified such that a coupling capacitor (C_C) is used to connect the output terminal (V_{out}) of the amplifier to the load resistor (R_L) as shown below. Find the cutoff frequency and derive the expression for the modified transfer function $T(s)=V_{out}/V_s$ of the amplifier. (1.5 pt)

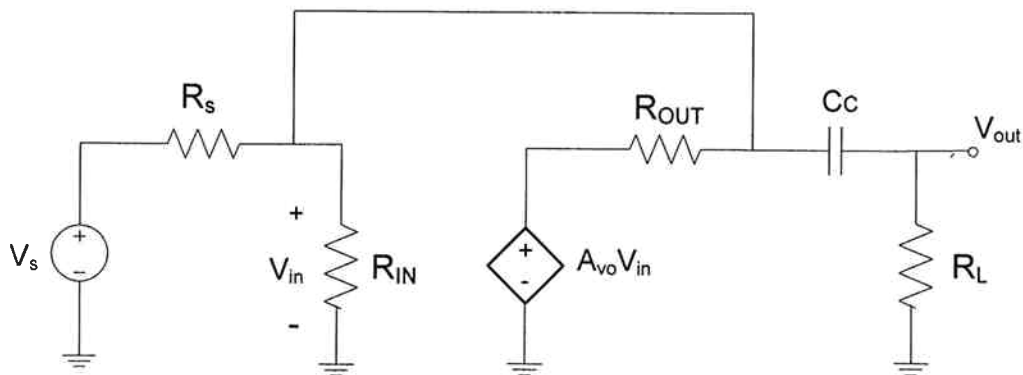

- Provide a Bode magnitude plot for $T(s)$ derived in part (c) clearly showing all the relevant details. (1pt)

Question 2 (5 pts)

In the following circuit:

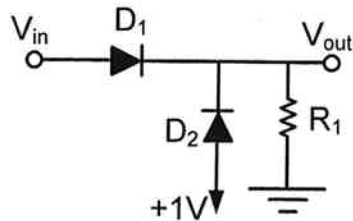

D_1 and D_2 are identical diodes with $n=2$, $V_T = 25 \text{ mV}$ and $R_1=1\text{K}\Omega$.


- a) Use constant voltage drop model (CVD) for the diodes to find the voltage transfer characteristic of the above circuit (plot V_{out} vs V_{in} for $-5V < V_{in} < 5V$). (2 pts)
- b) Assume that $V_{in}=1.5V+1^{mV}\sin(20t)$ and (3 pts)
 - I. Determine the state of each diode.
 - II. Find the DC current going through the diodes that are “on”.
 - III. Find the small-signal resistance of the diodes that are “on”.
 - IV. Find the DC and AC components of the output voltage.

Question 3 (6 pts)

Assume $V_t = 1\text{V}$, $k_n' (W/L) = 2\text{ A/V}^2$, $\lambda = 0$ and both transistors are operating in the saturation mode. The current source as shown in the diagram supplies 0.25 A and all capacitors are large. Ignore CLM and body effect.


Solve the circuit below for the DC values of :

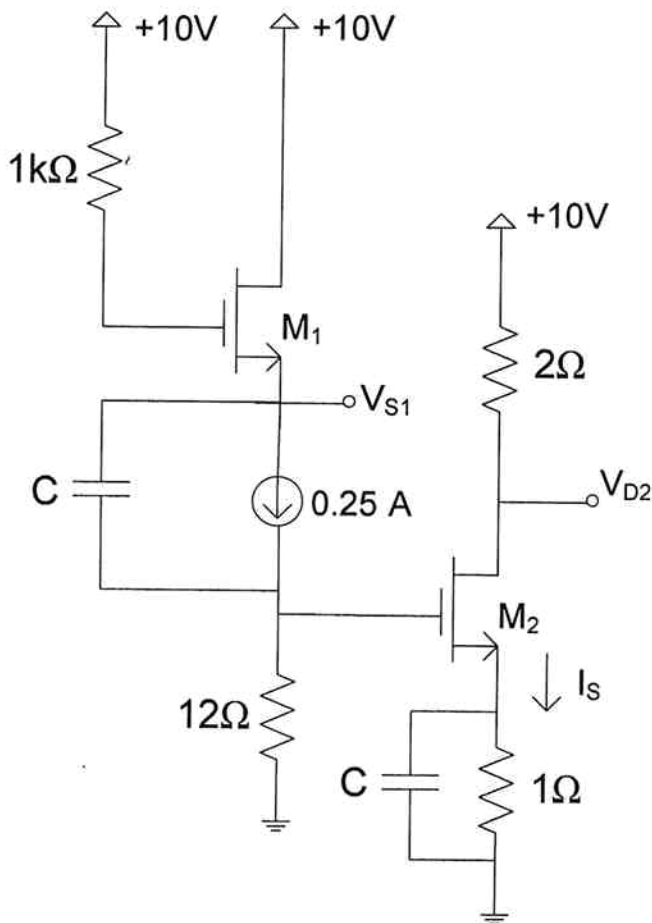- a) V_{D2} (2 pts)
- b) V_{S1} (2 pts)
- c) I_S (2 pts)



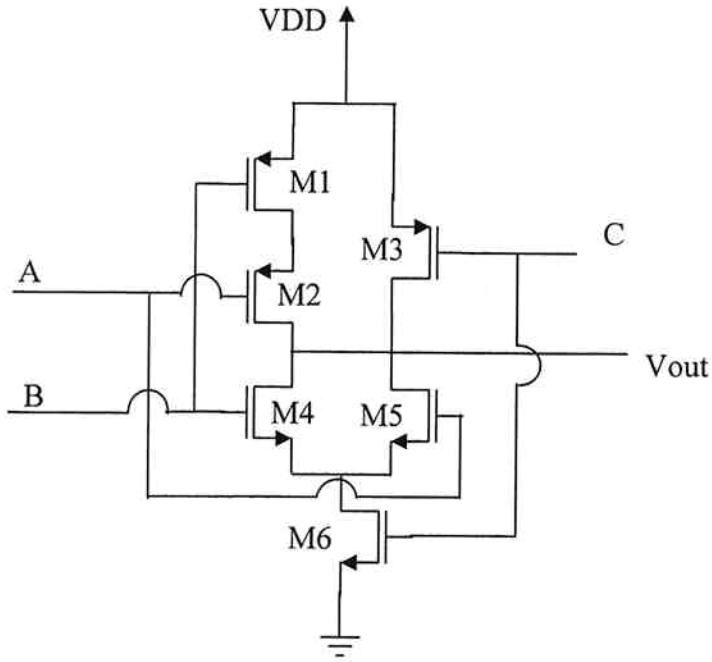Question 4 (3 points)

Consider the following digital CMOS circuit with three logic inputs labeled as A, B, and C. Note: VDD is logic 1 and GND is logic 0.




Find Vout for each of the following input combinations. Explain in each case which transistors are ON and which ones are OFF.

- a) A=0 B=0 C=0. (1 pt)
- b) A=1 B=1 C=1. (1 pt)
- c) A=0 B=1 C=1. (1 pt)

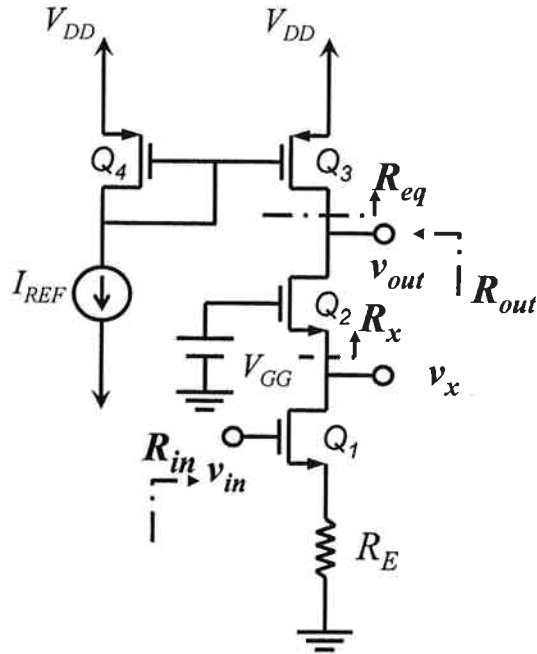Question 5 (9 Points)

Consider the following circuit. All FETs are operating in saturation.




- Specify the type of amplifiers configured by Q1 and Q2 (1 pt)
- Draw the small signal equivalent circuit for the section of circuit containing Q3 and Q4. Also, find an expression for R_{eq} . (1.5 pts)

For the following parts replace the loading effect of Q3 with R_{eq} . Ignore the channel length modulation but you must include the Body effect if needed.


- Draw the small signal equivalent circuit of the entire amplifier circuit. (2 pts)
- Find expressions for R_{in} , R_x and R_{out} . (2.5 pts)
- Find expressions for V_{out}/V_x and V_{out}/V_{in} . (2 pts)

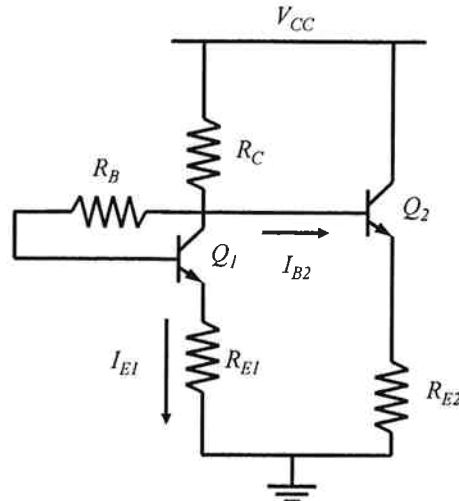Question 6 (8 pts):

Consider the multistage BJT amplifier shown below. In this circuit, $V_{CC} = 2.5V$, $I_{E1} = 2mA$, $R_B = 2 k\Omega$, $R_C = 0.6 k\Omega$, $R_{E2} = 0.2 k\Omega$, $\beta = 99$, and V_A is infinite.




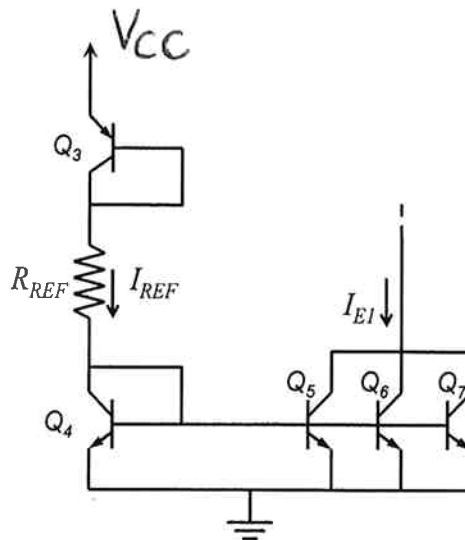- If $I_{E1} = 2 \text{ mA}$, determine the value of R_{E1} . (4 pts)
- If I_{B2} is fixed to value you found in part (a) and $I_{E1} = 2 \text{ mA}$, determine the minimum value for R_C to keep Q_1 in the active mode. (1pt)
- In order to generate the $I_{E1} = 2 \text{ mA}$, the following current steering circuit is used, if all BJTs are identical with $\beta = 99$, find R_{REF} . (3 pts)



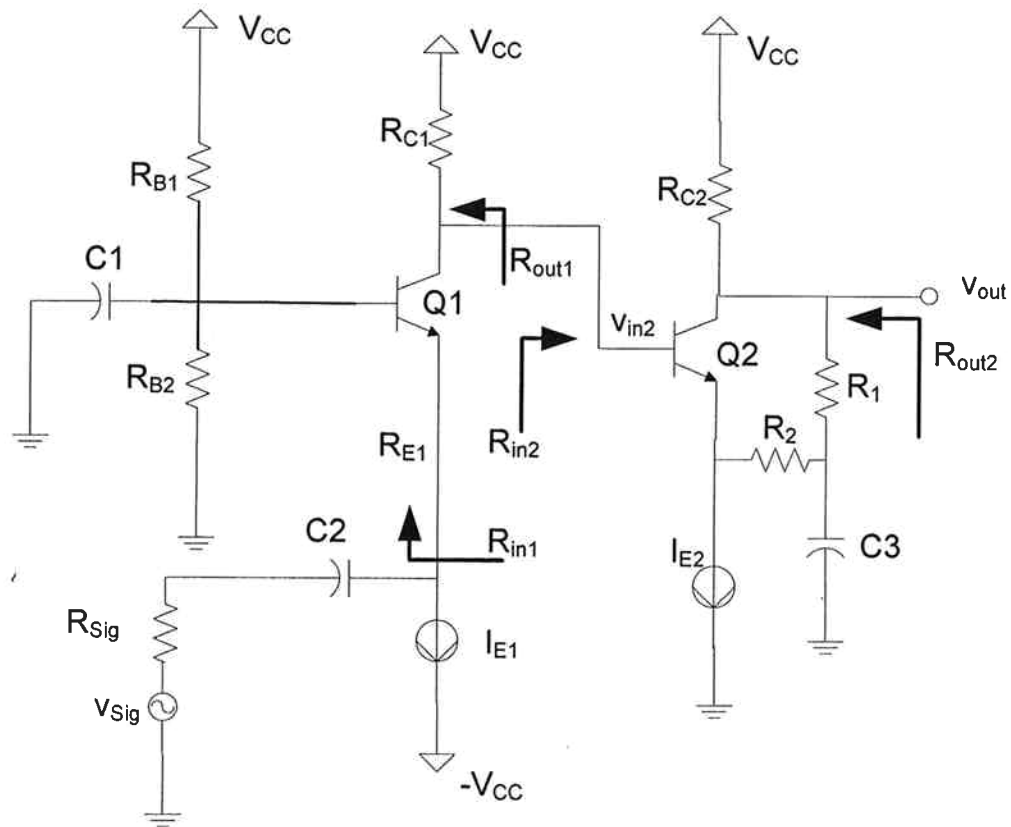Question 7 (10 pts):

Consider the following amplifier circuit. All capacitors are infinite valued.



- This is a two stage amplifier. Specify the type of the amplifiers used at each stage. (1 pt)
- Draw the small-signal model of the entire circuit and include the early effect. (2 pts)
- Derive an expression for R_{out1} including the early effect. (2 pts)

For the following parts ignore the early effect.

- Find expressions for R_{in1} , R_{in2} , R_{out1} , R_{out2} . (3 pts)
- Find expressions for the voltage gains, v_{out}/v_{in2} and v_{out}/v_{sig} . (2 pts)

Question 8 (5 pts):

Draw the high-frequency hybrid- π model of the BJT. (2 pts)

- a) Derive an expression for the short circuit current gain, $h_{fc}=I_c/I_b$. (2 pts)
- b) Derive an expression for the unity-gain bandwidth, f_T . (1 pts)

Diodes:

$$i = I_s (\exp(v/nV_T) - 1)$$

FETs:

NMOS:

Cutoff: $V_{GS} < V_t$ $I_D = 0$ $k'_n = \mu_n C_{ox}$

Triode: $V_{GS} > V_t$ $I_D = k'_n \frac{W}{L} [(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2]$
 $V_{DS} < V_{GS} - V_t$

Saturation: $V_{GS} > V_t$ $I_D = \frac{1}{2}k'_n \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$
 $V_{DS} > V_{GS} - V_t$

Body effect: $V_t = V_{t0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$

PMOS:

Cutoff: $V_{GS} > V_t$ $I_D = 0$ $k'_p = \mu_p C_{ox}$

Triode: $V_{GS} < V_t$ $I_D = k'_p \frac{W}{L} [(V_{GS} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2]$
 $V_{DS} > V_{GS} - V_t$

Saturation: $V_{GS} < V_t$ $I_D = \frac{1}{2}k'_p \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$
 $V_{DS} < V_{GS} - V_t$

Body effect: $|V_t| = |V_{t0}| + \gamma (\sqrt{2\phi_f + |V_{SB}|} - \sqrt{2\phi_f})$

SMALL SIGNAL

$$g_m = \frac{2 \cdot I_D}{V_{GS} - V_t}$$

$$g_m = k'_n \frac{W}{L} (V_{GS} - V_t) (1 + \lambda \cdot V_{DS})$$

$$g_m = \sqrt{2k'_n} \sqrt{\frac{W}{L}} \sqrt{1 + \lambda \cdot V_{DS}} \sqrt{I_D}$$

$$r_o = \frac{1}{\lambda \cdot I_D}$$

$$g_{mb} = \chi \cdot g_m$$

$$\chi = \frac{\gamma}{2} \cdot \frac{1}{\sqrt{2\phi_f + V_{SB}}}$$

Two - Page

Formula Sheet

Page 1 of 2

BJTs:

$$i_C = I_S \exp(v_{BE}/V_T)$$

$$i_B = \frac{i_C}{\beta}$$

$$i_E = \frac{i_C}{\alpha}$$

$$i_B = (1-\alpha)i_E = \frac{i_E}{\beta+1}$$

$$i_E = (\beta+1)i_B$$

$$g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \frac{V_T}{I_C} = \frac{\alpha}{g_m}$$

$$r_\pi = \frac{V_T}{I_B} = \frac{\beta}{g_m} \quad r_o = \frac{V_A}{I_C}$$

$$r_\pi = (\beta+1)r_e$$

$$\beta = \frac{\alpha}{1-\alpha} \quad \alpha = \frac{\beta}{\beta+1} \quad \beta+1 = \frac{1}{1-\alpha}$$