

Midterm Examination

Electronic Circuits I - 304-330A

October 18th 2001, 10:05 AM – 11:25 AM


Professor David Plant

Pertinent Information:


- 1) This is a closed-book examination, no notes permitted.
- 2) The examination consists of 4 problems; 37 total possible points.
- 3) Only the Faculty Standard Calculator is permitted.

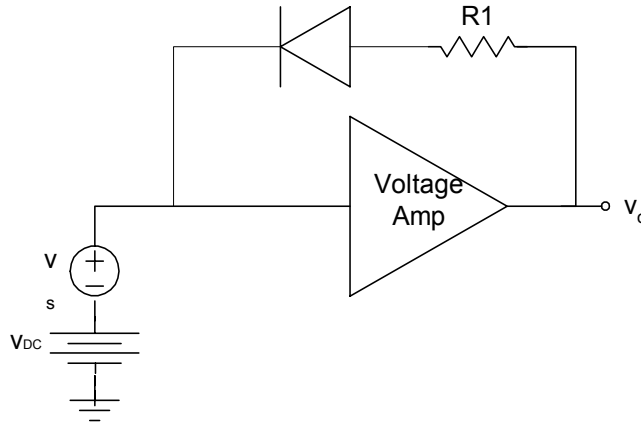Question #1 [10 pts]:

Consider the following circuit. Ignore the output resistances of the amplifier and voltage sources. Assume $n=1$ for the diode.



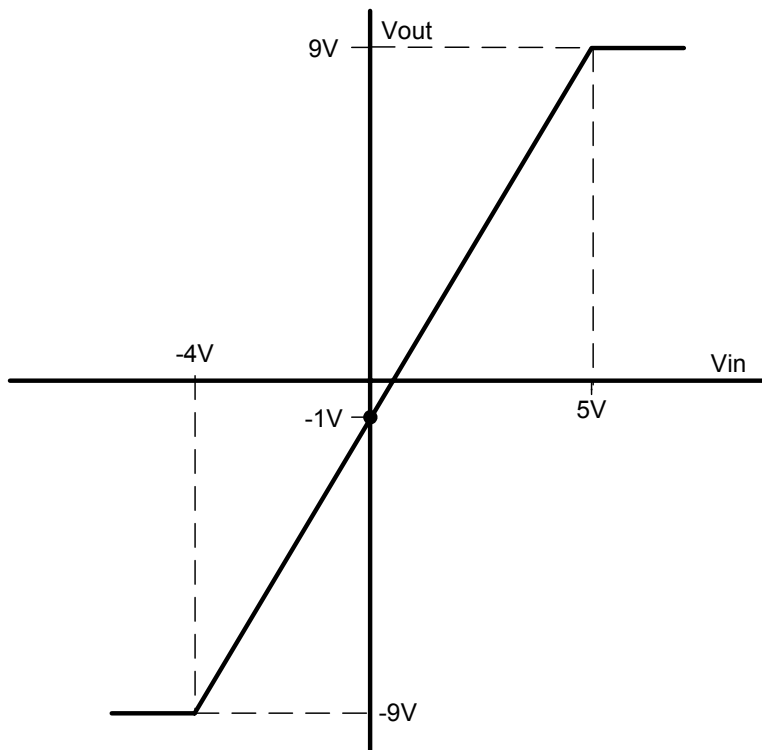The Voltage Amplifier in the above circuit has the following voltage transfer characteristic:



For parts (a) and (b) V_s is off and use the Constant Voltage Drop Model (CVDM) for the diode.


- [2 pts] Find the values of V_{DC} for which the diode is *off*.
- [2 pts] For $V_{DC} = 2.5$, find the value of $R1$ for which the current through the diode is 2mA.

For parts (c),(d) and (e), assume that the $V_{DC} = 3.5V$, V_S is a small signal source of the form $V_S = V_1 \sin \omega t$, $R_1 = 2k\Omega$ and the DC current through the diode is $0.9mA$.

- c) [2 pts] Draw the small signal equivalent circuit.
- d) [2 pts] Write down the expression for the *total* current through the diode in terms of V_S .
- e) [2 pts] Find the maximum value for V_1 for which the circuit operates with no clipping.

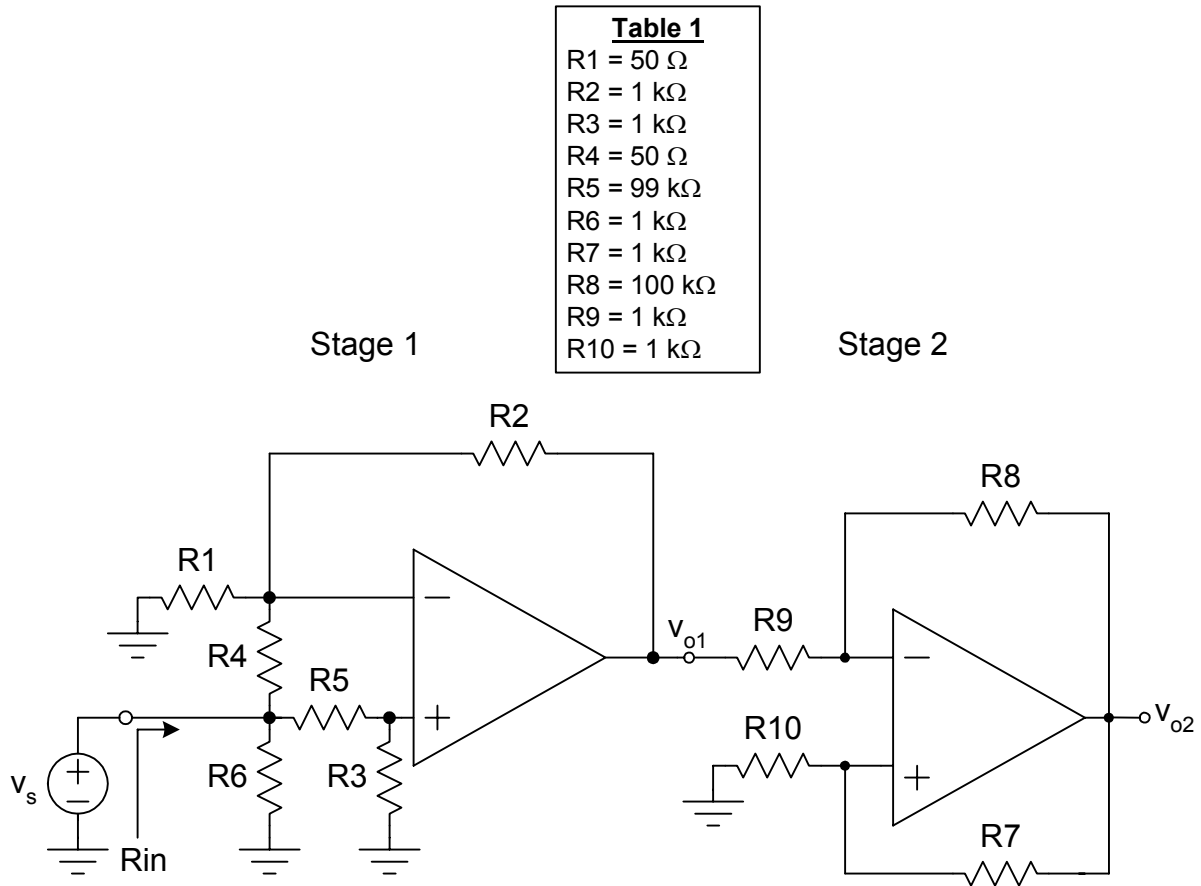Question #2 [12 pts]:


Consider the following circuit. Assume that both op-amps have infinite gain.



- [3 pts] Calculate the voltage gain (v_{o1}/v_s) of the first stage using the resistor values of Table 1.
- [1 pts] Find the expression (i.e. do not plug in resistor values) for the input resistance (R_{in}) of the first stage. Assume that R_4 is ∞ for this part of the problem only.
- [3 pts] Calculate the voltage gain (v_{o2}/v_{o1}) of the second stage using the resistor values of Table 1.
- [2 pts] Calculate the overall voltage gain: v_{o2}/v_s .
- [3 pts] Replace R_7 by an open-circuit and calculate the gain of the second stage v_{o2}/v_{o1} , assuming that $A = 100$.

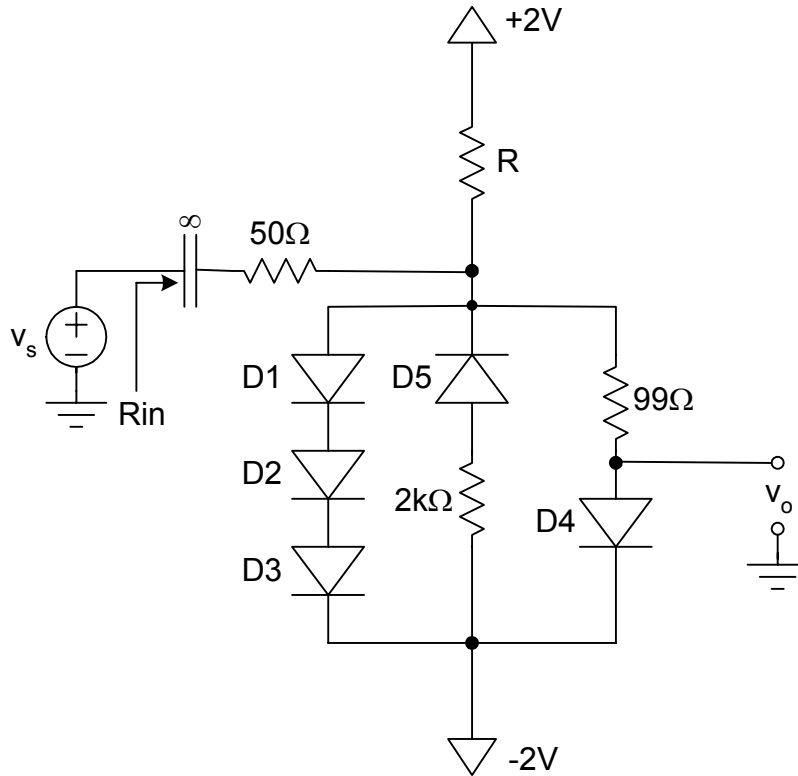Question #3 [10 pts]:


Consider the following circuit. Assume that all diodes are identical with $n=2$, and conduct 5 mA when forward biased at 0.7V.



- [3 pts] Calculate R such that the DC output voltage, V_o , is $-1.25V$. Do NOT assume the Constant Voltage Drop model. Hint: all diodes but one are on.
- [3 pts] Draw the small-signal equivalent circuit diagram, and calculate the values of the small signal diode resistances.
- [2 pts] Calculate the small-signal voltage gain v_o/v_s .
- [2 pts] Calculate the small-signal input resistance seen by the source, V_s .

Question #4 [5 pts]:

Consider the following circuit.

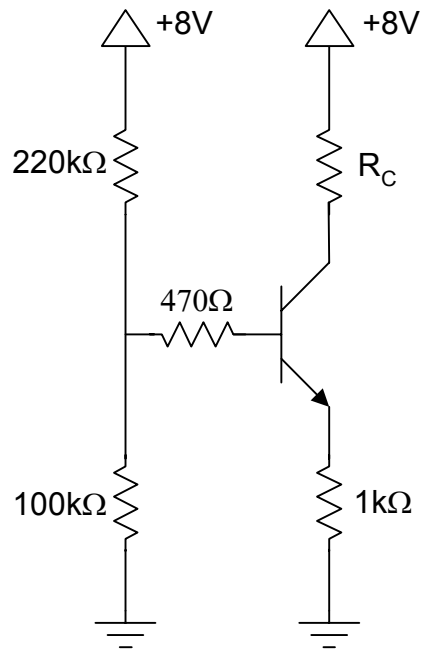

- a) [2 pts] Assume $\beta = \infty$, $V_A = \infty$, and $R_C = 4\text{k}\Omega$. Determine whether or not the BJT is in the active mode.
- b) [3 pts] Assume $\beta = 100$, $V_A = \infty$, and $R_C = 3\text{k}\Omega$. Find the DC voltages and currents: V_C , V_B , V_E , I_C , I_E and I_B . Verify the BJT is in the active mode.