

① a) Diode is off $\Rightarrow V_{\text{diode}} < 0.7\text{V}$, $I_{\text{diode}} = 0$

$$\therefore V_o < V_{\text{in}} + 0.7$$

from graph: $V_o = 2V_{\text{in}} - 1$

$$2V_{\text{in}} - 1 < V_{\text{in}} + 0.7$$

$$\Rightarrow V_{\text{in}} < 1.7\text{V} \quad \text{or} \quad V_{\text{DC}} < 1.7\text{V}$$


b) $V_{\text{DC}} = 2.5\text{V} \Rightarrow V_{\text{out}} = 4\text{V}$

$$V_R = V_o - V_{\text{DC}} - V_{\text{diode}}$$

$$= 4 - 2.5 - 0.7 = 0.8\text{V}$$

$$R = \frac{V_R}{I_R} = \frac{0.8}{2\text{m}} = 400\Omega$$

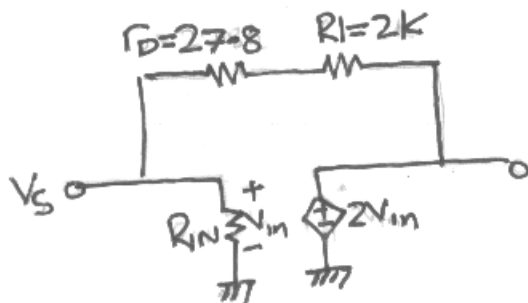c) $r_D = \frac{nV_T}{I_D} = \frac{25\text{m}}{0.9\text{m}} = 27.8\Omega$



$$d) i_D = \frac{V_{OUT} - V_{in}}{2k + 27.8} = \frac{2V_s - V_s}{2.0278k} = 0.493 \text{ mA}$$

$$I = (0.9 + 0.493 V_s) \text{ mA}$$

DC AC

e) For amplifier clipping:

$$V_{in} = 3.5 \text{ V}$$

$$(V_i)_{\max} = 5 - 3.5 = 1.5 \text{ V}$$

For linear operation of diode:

$$V_d < 10 \text{ mV}$$

$$i_d < \frac{10 \text{ m}}{r_D} = \frac{10 \text{ m}}{27.8} = 0.3597 \text{ mA}$$

from (d):

$$0.493 V_i \sin \omega t < 0.3597$$

$$\Rightarrow (V_i)_{\max} = 0.729 \text{ V}$$

\therefore limiting condition is diode linear operation limit

$$\Rightarrow (V_i)_{\max} = 0.729 \text{ V}$$

#2

$$(a) \quad v_- = \frac{R_3}{R_3 + R_5} v_s$$

$$i_{R_2} = \left(\frac{v_-}{R_1} + \frac{v_- - v_s}{R_4} \right)$$

$$v_{o1} = \left(\frac{v_-}{R_1} + \frac{v_- - v_s}{R_4} \right) R_2 + v_-$$

$$= \frac{R_3 R_2 v_s}{R_1 (R_3 + R_5)} + \frac{R_3 R_2 v_s}{R_4 (R_3 + R_5)} - \frac{R_2 v_s}{R_4} + \frac{R_3 v_s}{R_3 + R_5}$$

$$\Rightarrow \frac{v_{o1}}{v_s} = -19.59 \text{ V/V}$$

(b) By inspection: $R_{in} = R_6 \parallel (R_5 + R_3)$

3/7

#2

$$(c) \quad v_+ = \frac{R_{10}}{R_{10} + R_7} v_{o2}$$

$$v_{o2} = \frac{\frac{R_{10}}{R_{10} + R_7} v_{o2} - v_{o1}}{R_9} R_8 + \frac{R_{10}}{R_{10} + R_7} v_{o2}$$

$$v_{o2} \left[1 - \frac{R_{10}}{R_{10} + R_7} \left(\frac{R_8}{R_9} + 1 \right) \right] = v_{o1} \left[-\frac{R_8}{R_9} \right]$$

$$\Rightarrow \frac{v_{o2}}{v_{o1}} = 2.02 \frac{V}{V}$$

$$(d) \quad \frac{v_{o2}}{v_{o1}} = \frac{v_{o2}}{v_{o1}} \times \frac{v_{o1}}{v_{o1}} = -39.57 \frac{V}{V}$$

$$(e) \quad v_{o2} = \frac{-v_{o2}}{A} + \frac{-v_{o2}/A - v_{o1}}{R_9} R_8$$

$$\Rightarrow v_{o2} \left[1 + \frac{1}{A} + \frac{R_8}{A R_9} \right] = -v_{o1} \frac{R_8}{R_9}$$

$$\Rightarrow \frac{v_{o2}}{v_{o1}} = \frac{-R_8/R_9}{1 + \frac{1}{A} + \frac{R_8/R_9}{A}} = -49.75 \frac{V}{V}$$

$$\textcircled{3a) } V_0 = -1.25V$$

$$V_{D4} = -0.75V$$

$$I_{D4} = 5m e^{\frac{0.05}{2 \times 25m}} = 13.6mA$$

$$V_2 = V_1 + nV_T \ln\left(\frac{I_2}{I_1}\right)$$

$$I_2 = I_1 e^{\frac{V_2 - V_1}{nV_T}}$$

$$\therefore \text{at node above } 99\Omega \text{ resistance, } V = V_0 + 99(13.6m) = 0.0955V$$

$$V_{D1} = V_{D2} = V_{D3} = \frac{0.0955 - (-2)}{3} = 0.6985V$$


$$I_{D1} = I_{D2} = I_{D3} = 5m e^{\frac{-1.48 \times 10^{-3}}{50m}} = 4.854mA$$

$$I_R = 4.854m + 13.6mA = 18.45mA$$

$$R = \frac{V}{I_R} = \frac{2 - 0.0955}{18.45m} = \underline{\underline{103.2\Omega}}$$

$$D) r_{D1} = r_{D2} = r_{D3} = \frac{nV_T}{I_D} = \frac{2 \times 25m}{4.85m} = 10.3\Omega$$

$$r_{D4} = 3.676\Omega$$

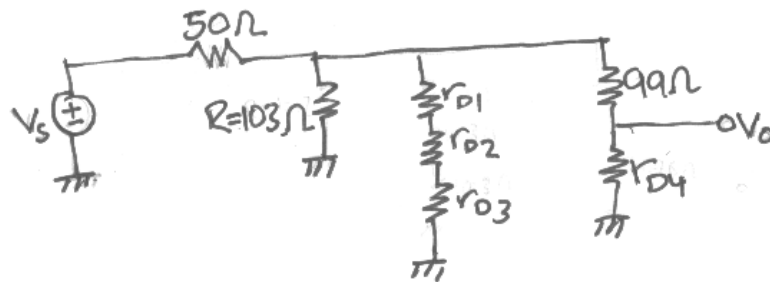

$$c) \frac{V_o}{V_s} = \frac{R_{eq}}{R_{eq} + 50} \times \frac{3.676}{99 + 3.676}$$

$$R_{eq} = (103.2) \parallel (3 \times 10^3) \parallel (99 + 3.676) = 19.3 \Omega$$

$$\frac{V_o}{V_s} = 9.974 \text{ mV/V}$$

$$d) R_{in} = 50 + R_{eq} = 69.3 \Omega$$

④ a) $\beta = \infty \Rightarrow I_B = 0; I_C = I_E$

$$V_B = \frac{100}{100+220} \times 8 = 2.5V$$



If $V_{BE} = 0.7V; V_E = 1.8V$

$$I_E = \frac{V_E}{1K} = 1.8mA = I_C$$

$$V_C = 8 - I_C R_C = 8 - 7.2 = 0.8V$$

$\therefore V_C < V_B \Rightarrow$ NOT in active mode

b) $\beta = 100$

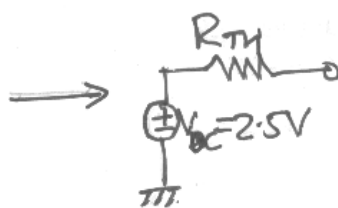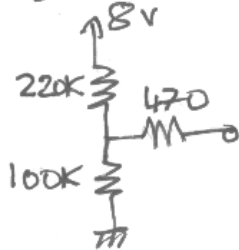

$V_{ac} = 2.5V$ (from a))

$$R_{TH} = 470 + 220K \parallel 100K = 69.22K\Omega$$

by KVL: $2.5 - I_B R_B - 0.7 - I_E R_E = 0; I_E = (\beta + 1) I_B$

$$1.8 - I_B (69.22K) - (101) I_B 1K = 0$$

$$I_B = 10.6\mu A$$

$$I_C = \beta I_B = 1.06mA$$

$$I_E = (\beta + 1) I_B = 1.07mA$$

$$V_B = 2.5 - I_B R_B = 1.768V$$

$$V_E = V_B - 0.7 = 1.068V$$

$$V_C = 8 - I_C R_C = 4.827V$$

Also:

$$V_C > V_B \Rightarrow \text{active mode}$$

7/7