

Midterm Examination # 1

Electronic Circuits I - ECSE-330B

February 17th 2004, 8:35 AM – 9:55 AM

Professor Ramesh Abhari

Pertinent Information:

- 1) This is a closed-book examination, no notes permitted.
- 2) Answers should be written in pen.
- 3) This examination consists of 4 questions with total possible points of 36. Partial point distribution is indicated in brackets.
- 4) Only the Faculty Standard Calculator is permitted.
- 5) Show your work: answers without justification will not receive marks. State any assumption you find necessary to complete your answer.

Last Name	
First Name	
Student Number	


Question	Mark
1	/9
2	/9
3	/9
4	/9
Total	/36

Question #1 (9 pts)

In the circuit shown below, D1, D2, D3 and D4 are identical and are represented by constant voltage drop model (CVDM) $V_{D0} = 0.7$ Volt. Z is a Zener diode with the specified Zener voltage of 8V at 10mA and $r_z = 20 \Omega$ and can be represented by a piecewise-linear model.


a) Find V_{Z0} in the piecewise-linear model for the Zener diode. (2 pts)

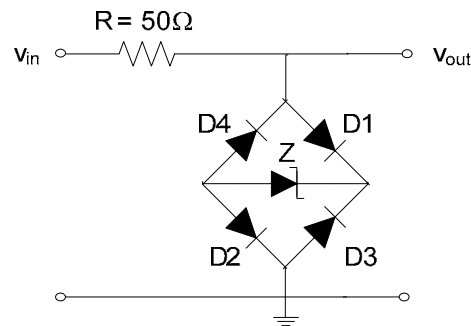b) Sketch and clearly label the voltage transfer characteristic (VTC) of this circuit for $-20 \text{ V} < v_{in} < +20 \text{ V}$. (7 pts)



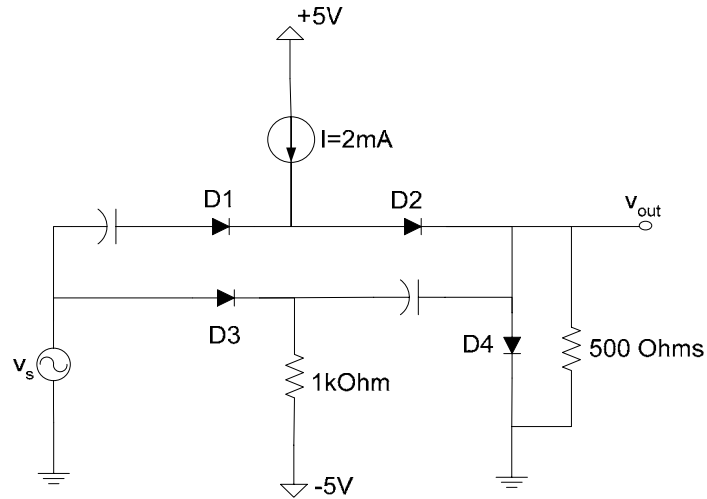Question #2 (9 Points)

Consider the circuit below. All capacitors are “infinite”. The source v_s is a signal source with no DC voltage (0V DC) and $v_s \ll nV_T$. Diodes are all identical ($n=2$).



- Assume the constant voltage drop model. Determine the DC current flowing in each diode. (4 pts)
- Determine the small signal gain v_{out}/v_s . (5 pts)


Question #3 (9 Points)

The NMOS and PMOS transistors in the circuit below are matched with $(k_n'W/L = k_p'W/L = 1\text{mA/V}^2)$ and $V_{tn} = -V_{tp} = 1\text{ V}$, assuming $\lambda = 0\text{ V}^{-1}$ for both devices find the drain currents i_{DN} and i_{DP} and the voltage v_O for:

a) $v_I = 0$ (4 pts)

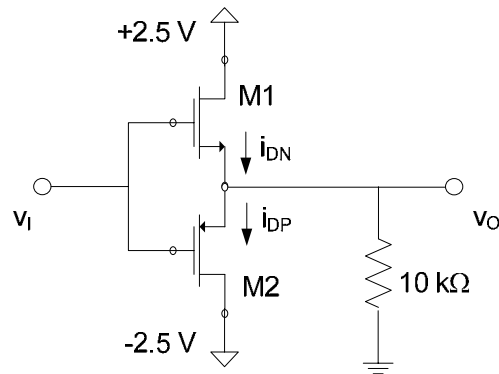
b) $v_I = 2.5\text{ V}$ (5 pts)

For each case, explain the assumption you make for the mode of operation of M1 and M2.



Question #4 (9 Points)

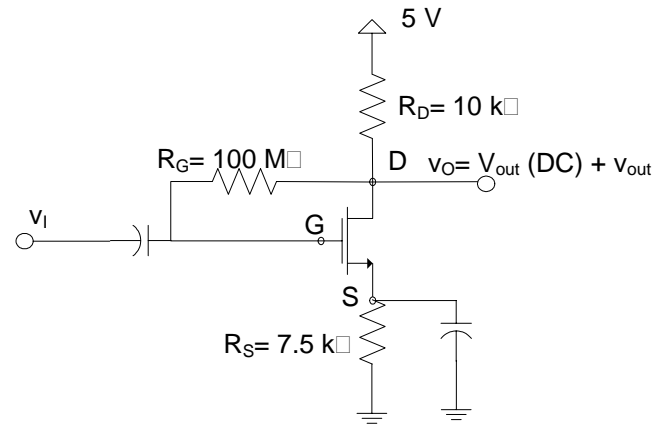- a) In the following MOSFET circuit, $\lambda=0.05\text{V}^{-1}$ and $V_{tn}=1\text{ V}$ and all the capacitors are infinite. Draw the small-signal model. (3 pts)



- b) Assume $V_S = 1.5\text{ V}$ and $V_{\text{out}}(\text{DC}) = 3\text{ V}$. What is the voltage gain of the circuit in part (a)? (2 pts)
- c) In the following circuit $|\lambda|=0.05\text{V}^{-1}$, $V_{\text{ref}} = 3\text{ V}$ and $V_{tp} = -1\text{ V}$. I_{ref} is equal to the I_{D_S} found for the circuit shown in part (a). Draw the small-signal model of the circuit below and calculate the drain-source resistance. (4 pts)

