

# **Midterm Examination**

Electronic Circuits I - 304-330A

November 15<sup>th</sup> 2001, 10:05 AM – 11:25 AM


Professor David Plant

## **Pertinent Information:**

- 1) This is a closed-book examination, no notes permitted.
- 2) The examination consists of 3 problems; 36 total possible points.
- 3) Only the Faculty Standard Calculator is permitted.

**Question #1 [10 pts]:**

Consider the following circuit.

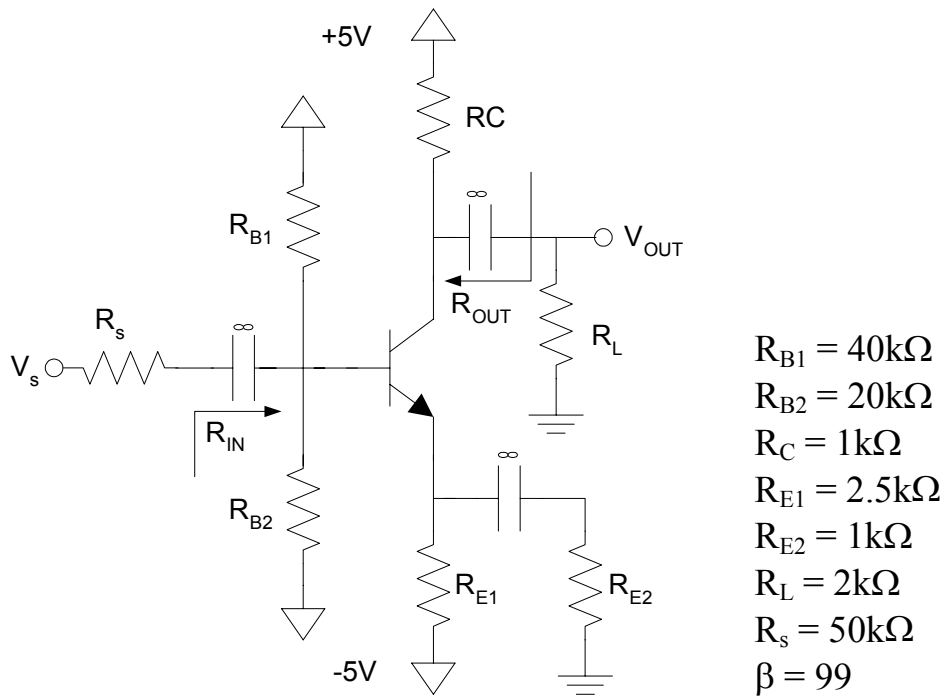

a) [2 pts] Calculate the DC emitter current,  $I_E$ , and the DC collector voltage,  $V_C$ . You can neglect the Early Voltage effect ( $V_A = \infty$ )

For parts (b) through (e), assume  $I_E = 1\text{ mA}$  (you can neglect the Early Voltage effect:  $V_A = \infty$ ).

b) [2 pts] Calculate the input resistance,  $R_{IN}$ .

c) [2 pts] Calculate the output resistance,  $R_{OUT}$ .


d) [2 pts] Calculate the gain,  $V_{OUT}/V_S$ .

e) [2 pts] Calculate the largest allowable input signal magnitude,  $|V_S|$ , for which the small signal model holds.

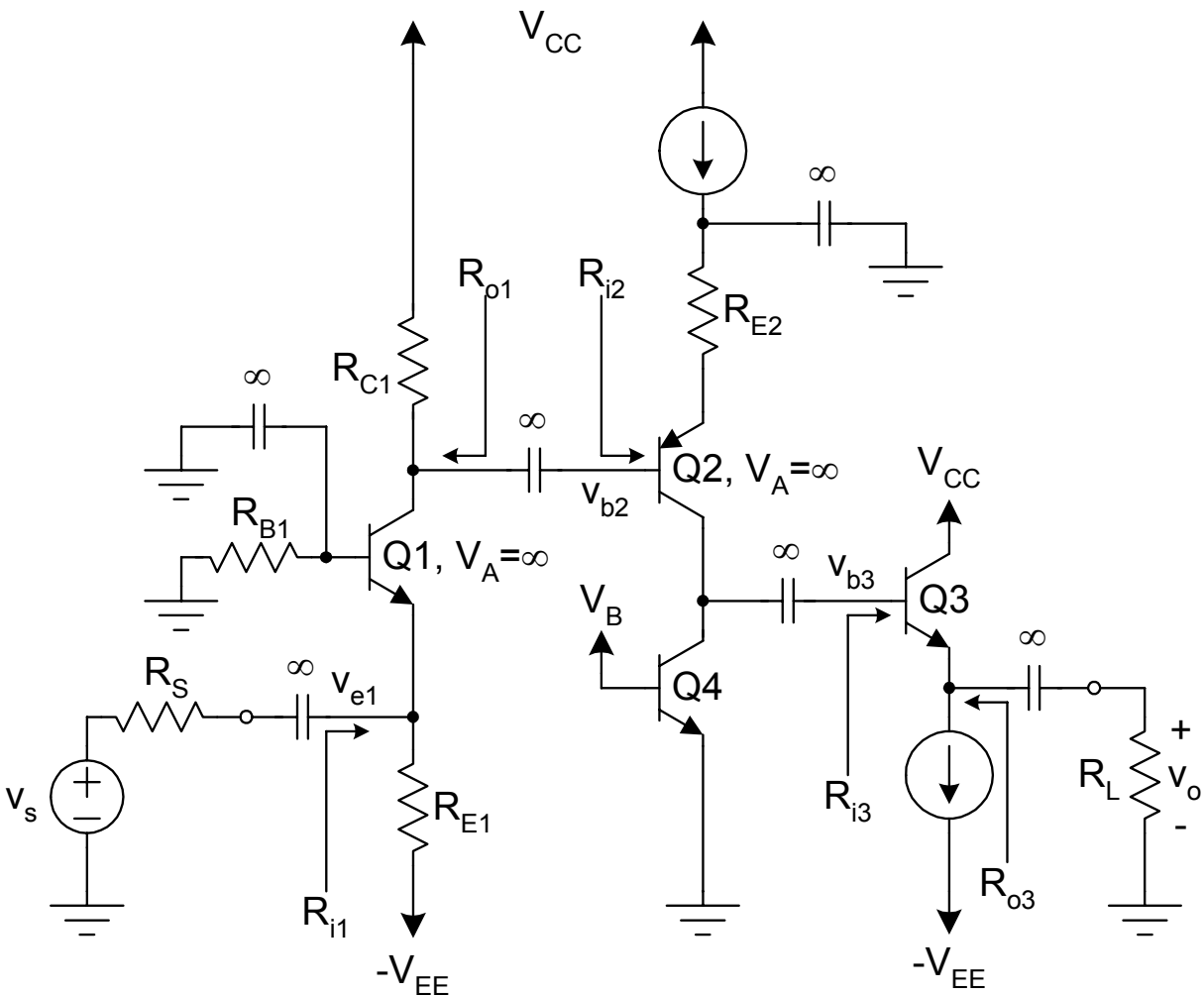**Question #2 [21 pts]:**

Consider the following circuit. You can assume that all transistors are in active mode and that they have the same  $\beta$ . For Q3 and Q4, DO NOT assume that  $V_A = \infty$ . You can assume that  $V_A = \infty$  for the Q1 and Q2.

Give your answers in terms of  $\beta$ ,  $R_s$ ,  $R_{E1}$ ,  $R_{B1}$ ,  $R_{C1}$ ,  $R_{E2}$ ,  $R_L$  and the small signal parameters (for example, use  $g_{m1}$ ,  $r_{e1}$  and  $r_{o1}$  for the small signal parameters of Q1). You can leave your answers for parts 3), 5), 6) and 9) in terms of the input and output resistances (e.g.  $R_{i1}$ ,  $R_{o1}$ , etc.). If two transistors appear in parallel (say  $R_1$  and  $R_2$ ), use the notation  $R_1//R_2$  in your answers instead of expanding  $R_{eq}$  to  $(R_1 \times R_2)/(R_1 + R_2)$ . Please circle the final expression that you find for each question.



- [2 pts] Find  $R_{i3}$  with the load  $R_L$  connected.
- [3 pts] Find  $R_{o3}$ .
- [2 pts] Find  $v_o/v_{b3}$ .
- [2 pts] Find  $R_{i2}$ .

**Question #2 continued:**

e) [3 pts] Find  $v_{b3}/v_{b2}$ .

f) [3 pts] Find  $v_{b2}/v_{e1}$ .

g) [2 pts] Find  $R_{i1}$ .


h) [1 pts] Find  $R_{o1}$ .

i) [1 pts] Find  $v_{e1}/v_s$ .

j) [2 pts] Can you say why Q4 was preferred over a resistor at the collector of Q2? (You answer should have no more than two lines. Answers longer than two lines will NOT be corrected).

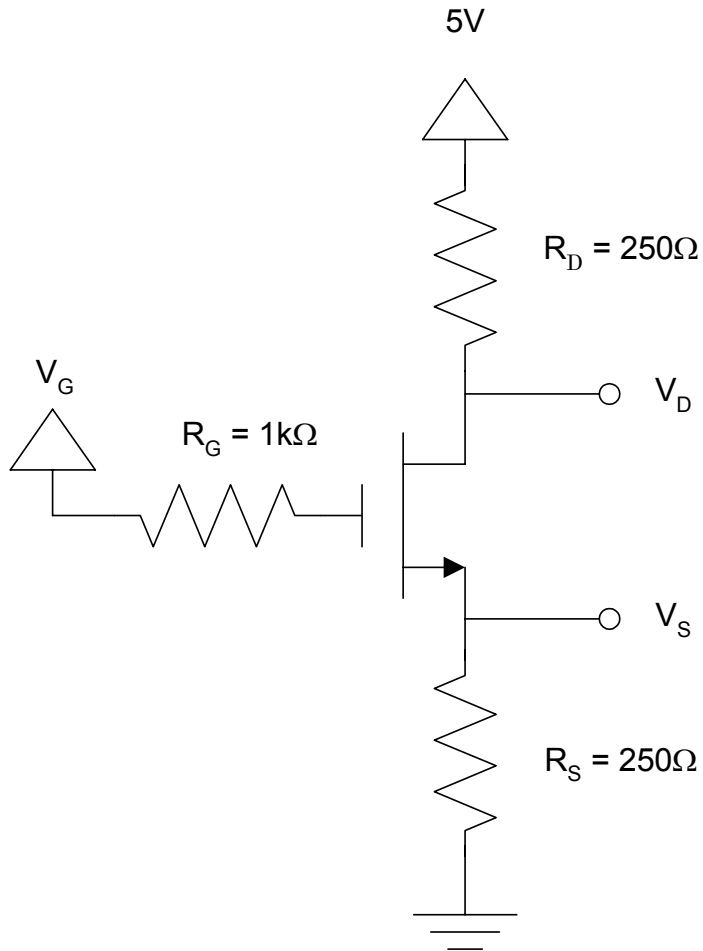**Question #3 [5 pts]:**

Consider the following circuit. The NMOS transistor has the following characteristics:  $k_n' = 100 \mu\text{A}/\text{V}^2$ ;  $W/L = 20$ ,  $V_t = 1.0\text{V}$  and  $V_A = \infty$ . You can neglect the Body Effect for this problem.



a) [3 pts] Assuming  $V_S = 1.0\text{V}$ , calculate  $V_D$ ,  $V_G$  and  $I_D$ . What mode of operation is the transistor in?

b) [2 pts] For  $V_G = 3\text{V}$  and  $I_D = 2\text{mA}$ , find the new value of  $R_D$  which puts the NMOS FET at the saturation/triode boundary assuming  $R_S$  and  $R_G$  remain unchanged.