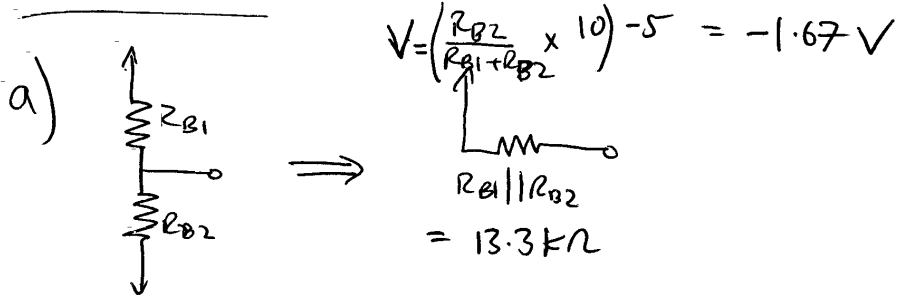


SOLUTIONS

Midterm Examination II
304-330A
November 15th 2001

Question 1



Using KVL:

$$-1.67 - I_B (13.3 \text{ k}) = 0.7 - \underbrace{100 I_B R_{E1}}_{\substack{V_{BE} = 0.7 \\ I_E = (B+1) I_B}} = -5$$

$$\Rightarrow I_B = 0.01 \text{ mA}$$

$$I_E = 1 \text{ mA}$$

$$V_C = 5 - R_C I_C = 5 - 0.99 \quad 4.01 \text{ V}$$

$$b) R_{in} \approx R_{B1} || R_{B2} || (B+1) [r_e + R_E || R_{E2}]$$

$$= 11.29 \text{ k}\Omega$$

$$c) R_{out} = R_C = 1 \text{ k}\Omega$$

$$d) \frac{V_{out}}{V_s} = \frac{R_{in}}{R_{in} + R_s} \times \frac{-\alpha R_C || R_L}{r_e + R_E || R_{E2}}$$

$$= -0.1645 \text{ V/V}$$

e) Condition required

$$|v_{be}| < 10 \text{ mV}$$

$$\begin{aligned} \frac{v_{be}}{v_s} &= \frac{R_{in}}{R_{in} + R_s} \times \frac{-r_c}{r_c + R_{E1} \parallel R_{E2}} \\ &= 6.232 \text{ mV/V} \end{aligned}$$

$$|v_{be}| < 10 \text{ mV} \Rightarrow |v_s| < 1.6 \text{ V}$$

Answers
for
Test #2.

$$1 \rightarrow R_{i3} = (\beta + 1)(r_{o3} \parallel R_L + r_{e3})$$

(a)

$$2 \rightarrow R_{o3} = r_{o3} \parallel \left(\frac{r_{o4}}{\beta + 1} + r_{e3} \right)$$

(b)

$$3 \rightarrow \frac{v_o}{v_{b3}} = \frac{(R_L \parallel r_{o3})}{(R_L \parallel r_{o3}) + r_{e3}}$$

(c)

$$4 \rightarrow R_{in2} = (\beta + 1)(r_{e2} + R_{E2})$$

(d)

$$v_{b3} = g_{m2} v_{eb} (r_{o4} \parallel R_{i3})$$

where $v_{eb} = -\frac{r_{e2}}{r_{e2} + R_{E2}} v_{b2}$ & $R_{i3} =$

$$\Rightarrow \frac{v_{b3}}{v_{b2}} = \overset{+ \text{ sign}}{-} g_{m2} \frac{r_{e2}}{r_{e2} + R_{E2}} (r_{o4} \parallel R_{i3})$$

(e)

where $r_{e2} = \frac{\alpha_2}{g_{m2}} \Rightarrow g_{m2} = \frac{\alpha_2}{r_{e2}}$

$$= \frac{\alpha}{r_{e2} + R_{E2}} (r_{o4} \parallel R_{i3}) = -\frac{\beta}{R_{in2}} (r_{o4} \parallel R_{i3})$$

$$v_{b2} = -g_m v_{be} (R_{c1} \parallel R_{in2})$$

$$\text{where } v_{be} = (-) v_{e1}$$

$$\textcircled{f} \Rightarrow \frac{v_{b2}}{v_{e1}} = g_m (R_{c1} \parallel R_{in2}) = \frac{\alpha}{r_{e1}} (R_{c1} \parallel R_{in2})$$

$$\textcircled{g} \Rightarrow R_{i1} = r_{e1} \parallel R_{E1}$$

$$\textcircled{i} \Rightarrow \frac{v_{e1}}{v_s} = \frac{R_{i1}}{R_{i1} + R_s}$$

$$\textcircled{h} \Rightarrow R_{o1} = R_{c1}$$

#3 a)

$$\textcircled{1} \quad \frac{V_s}{250} = \frac{5 V_D}{250}$$

② Assume saturation

$$\frac{1}{2} k_n \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 (1 + \lambda v_{DS})$$

$$50 \mu (20) (V_G - 1)^2 = \frac{V_s}{250}$$

$$\frac{1}{0.25} V_G^2 = 1$$

$$\Rightarrow V_G = \pm 2 \quad V_G = 2 \pm 2$$

$$V_G = 0 \quad V_G = 4$$

③ Need

$$V_G - V \geq V_t$$

$$V_G - \geq$$

$$V_G \geq 2 \Rightarrow \boxed{V_G = 4}$$

④

$$I_D = \frac{V_s}{250} = \frac{4}{250} \Rightarrow \boxed{I_D = 4 \text{ mA}}$$

⑤

$$V_D = 5 - 4 \text{ mA} \cdot 250 \Omega \Rightarrow \boxed{V_D = 4 \text{ V}}$$

⑥ Verify saturation

$$V_D \geq V_G - V_t$$

$$4 \geq 4$$

yes \Rightarrow saturation ^{assumption} OK

↳ 3 b.)

① $V_s = 250 \cdot 2\text{mA} = 0.5\text{V}$

② For saturation or triode, need

$$-V_s \geq V_t$$

$$3 - 0.5 \geq 1 \quad \text{OK}$$

③ Saturation $\Rightarrow V_D \geq V_G - V_t$

Triode $\Rightarrow V_D \leq V_G - V_t$

Edge $\Rightarrow V_D = V_G - V_t$

$$= 3 - 1$$

$$\Rightarrow V_D = 2\text{V}$$

④ $R_D = ?$

$$R_D = \frac{5\text{V} - 2\text{V}}{2\text{mA}}$$

$$\Rightarrow R_D = 1.5\text{k}\Omega$$