

## Midterm Examination # 2

Electronic Circuits I - ECSE-330B

March 25<sup>th</sup> 2004, 8:35 AM – 9:55 AM

Professor Ramesh Abhari

### Pertinent Information:

- 1) This is a closed-book examination, no notes permitted.
- 2) Answers should be written in pen.
- 3) This examination consists of 4 questions with total possible points of 36. Partial point distribution is indicated in brackets.
- 4) Only the Faculty Standard Calculator is permitted.
- 5) Show your work: answers without justification will not receive marks. State any assumption you find necessary to complete your answer.

Last Name	
First Name	
Student Number	


Question	Mark
1	/7
2	/10
3	/7
4	/12
Total	/36

**Question #1 (7 pts)**

In the following circuit, in all transistors  $V_{tn} = -V_{tp} = 1V$ .

$k_p' W_2/L_2 = k_n' W_1/L_1 = 200\mu A/V^2$ , and  $W_3/L_3 = W_4/L_4 = 10W_2/L_2$ .  $k_p'$  is the same in all PMOS transistors.

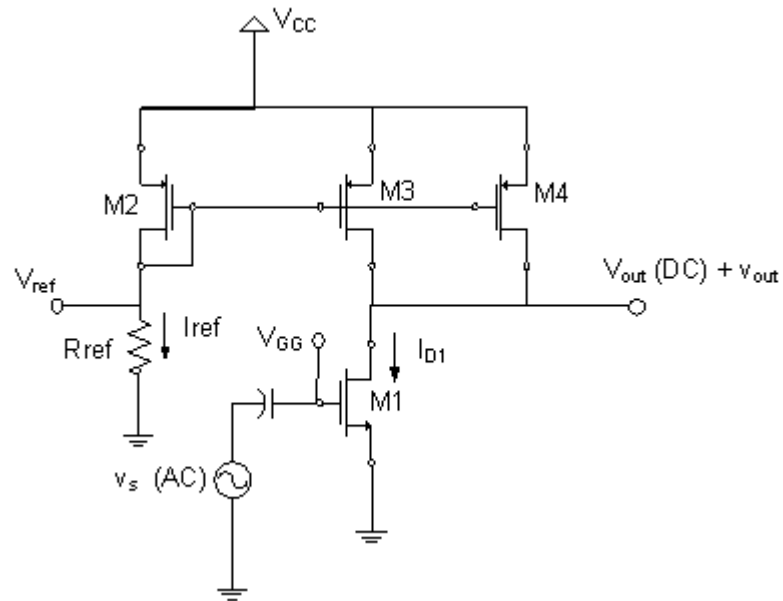$V_{cc} = 5V$  and  $V_{ref} = V_{out} (DC) = 3V$ .




- Ignore the channel length-modulation and find  $I_{ref}$ ,  $R_{ref}$ , and  $I_{D1}$ ? (3 pts)
- Assume  $|\lambda| = 0.05V^{-1}$  for all of the transistors. Replace the current mirror with an appropriate output resistance and draw the small-signal model for the amplifier circuit. Be sure to calculate the small-signal parameters. (3 pts)
- Calculate the gain  $v_{out}/v_{s.}$  (1 pts)

**Question #2 (10 Points)**

In the following circuit, neglect the channel length modulation for both M1 and M2 and consider the DC

current source ideal.

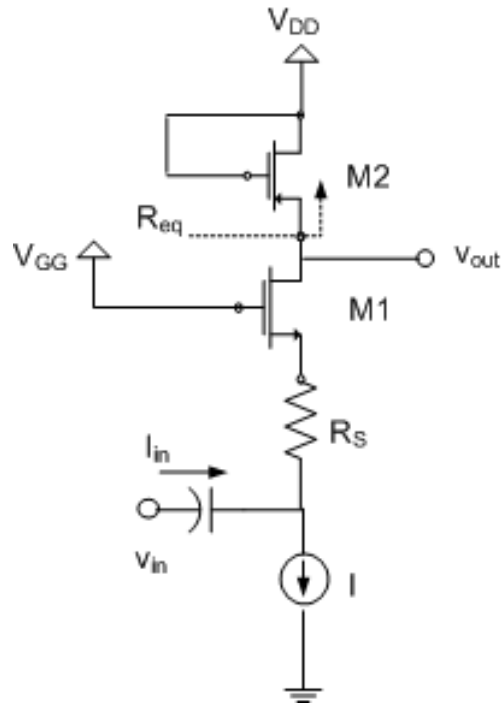


- Find the  $R_{eq}$  as indicated in the above diagram. (2 pts)
- Replace M2 with the equivalent resistance found in part (a). Draw the small signal model for this circuit and include the Body Effect for M1 in your model. (3 pts)
- Based on the model found in part (b), find an expression for the voltage gain ( $V_{out}/V_{in}$ ). (5 pts)
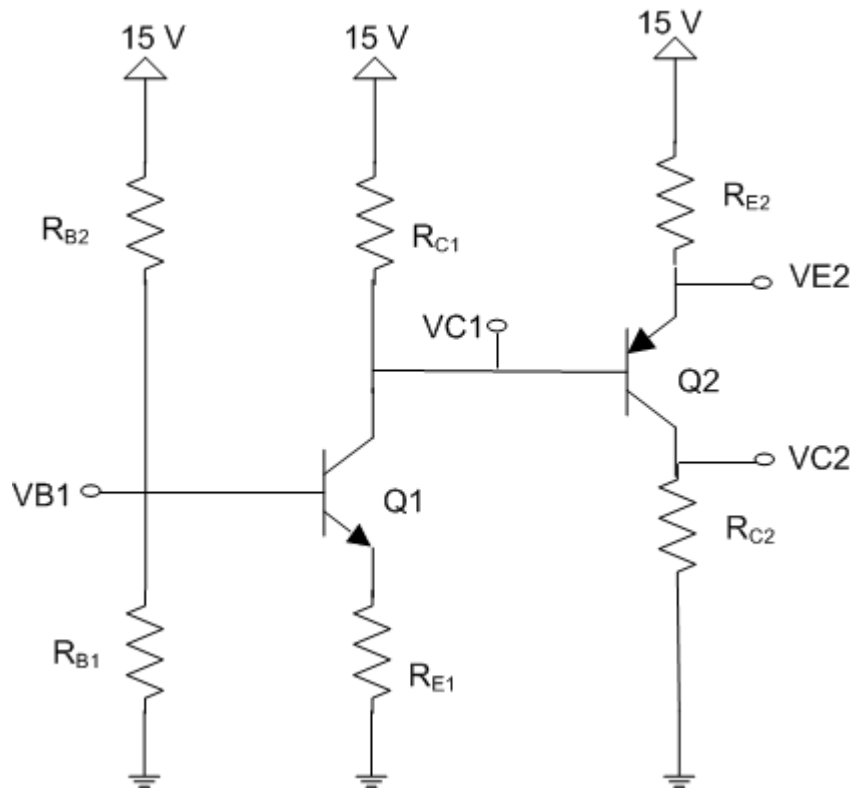
### **Question #3 (7 Points)**

Consider the following circuit. Both NPN and PNP transistors have  $\beta = 100$  and  $V_{BE} = V_{EB} = 0.7V$ .

$R_{B2} = 200 \text{ K}\Omega$ ,  $R_{B1} = 100 \text{ K}\Omega$ ,  $R_{C1} = 10 \text{ K}\Omega$ ,  $R_{E1} = 10 \text{ K}\Omega$  and  $R_{E2} = 1 \text{ K}\Omega$ .




- a) Assume the active mode operation for both transistors. If  $R_{C2}$  is  $1 \text{ K}\Omega$ , find  $V_{B1}$ ,  $V_{C1}$ ,  $V_{E2}$  and  $V_{C2}$ . (6 pts)
- b) If  $V_{ECsat} = 0.3 \text{ V}$  and  $V_{EB} = 0.7 \text{ V}$ , what is the maximum value for  $R_{C2}$  in order to keep Q2 operating in the active mode. (1 pt)

#### **Question #4 (12 Points)**

Consider the following common-emitter amplifier circuit. The signal source has a resistance of  $10 \text{ k}\Omega$  as shown in the figure, and a  $1 \text{ k}\Omega$  load  $R_L$  is attached at the output. Capacitors are infinite-valued, and

transistor  $\beta=100$ .

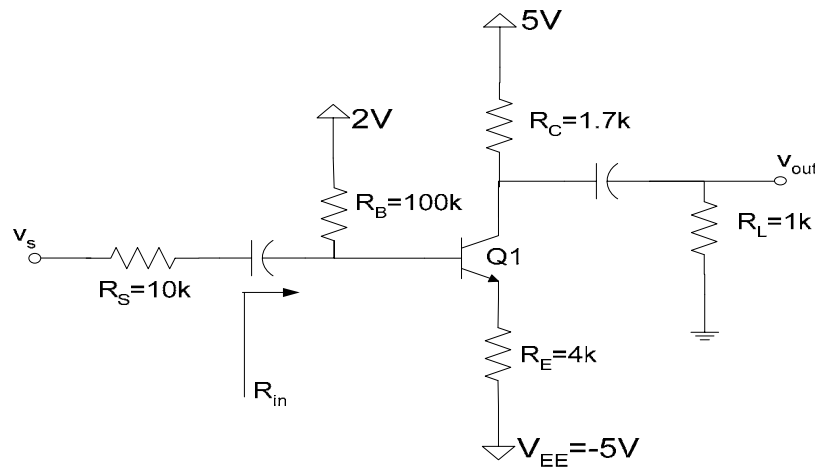

Figure

- Solve for the DC value of the emitter current  $I_E$  and the collector voltage  $V_C$ . (3 pts)
- Draw the small-signal model and find an expression for the input resistance  $R_{in}$  seen by the signal source and calculate it based on your answers from part (a). Ignore the Early Effect. (4 pts)
- Find an expression for the overall voltage gain  $A_V = v_{out}/v_s$  and calculate it using answers from parts (a) and (b). (2 pts)
- Consider what happens if the negative power supply has a voltage ripple noise which is not uncommon. You may treat such a ripple as a small-signal source  $v_{ee}$  at the negative power supply. This signal has no source resistance. Find an expression for the voltage gain  $v_{out}/v_{ee}$  (do not calculate it). Ignore the Early Effect. (3 pts)