

Midterm # 2

Question 1

a) For M_2 : PMOS

$$\begin{cases} V_{DS2} = V_{GS2} = V_{ref} - V_{oc} = 3 - 5 = -2 < +V_{tp} = -1 \rightarrow \text{Triode} \\ V_{DS2} < V_{GS2} - V_{tp} \rightarrow 0 < -(-1) = 1 \checkmark \rightarrow \text{saturation mode} \end{cases}$$

$$I_{ref} = \frac{1}{2} k'_p \frac{W_2}{L_2} (V_{GS2} - V_{tp})^2 = 100 \mu A \cdot 10^{-6} (-2 + 1)^2 = 0.1 \text{ mA}$$


$$R_{ref} = \frac{V_{ref}}{I_{ref}} = \frac{3}{0.1} = 30 \text{ k}\Omega$$

$$\frac{W_3}{L_3} = 10 \frac{W_2}{L_2}, \quad V_{GS3} = V_{GS2}$$

$$V_{DS3} = 3 - 5 = -2 < V_{GS3} - V_{tp} = 3 - (-1) = 4 \Rightarrow I_{D3} = \frac{1}{2} k'_p \frac{W_3}{L_3} (V_{GS2} - V_{tp})^2 = 10 I_{ref} = 1 \text{ mA}$$

$$V_{GS3} = 3 - 5 = -2 < V_{tp} = -1 \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{saturation mode} \quad I_{D4} = 10 I_{ref} = 1 \text{ mA}$$
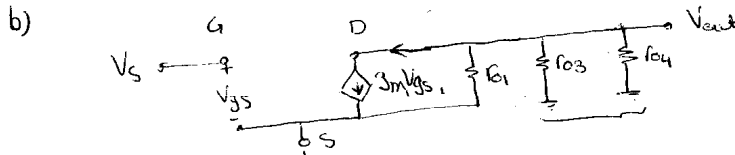
$$I_{D1} = I_{D3} + I_{D4} = 2 \text{ mA}$$





$$g_{m1} = \sqrt{2k'_n} \sqrt{\frac{W_1}{L_1}} \sqrt{1 + \lambda V_{DS1}} \sqrt{I_{D1}} = \sqrt{2 \times 100 \mu A \times 10^{-6} (1 + 0.05 \times 3) 2 \times 10^{-3}} = 0.95$$

$$r_{o1} = \frac{1}{\lambda I_{D1}} = \frac{1}{0.05 \times 2 \times 10^{-3}} = 10 \text{ k}\Omega$$


$$r_{o3} = r_{o4} = \frac{1}{\lambda I_{D3}} = \frac{1}{\lambda \frac{I_{D1}}{2}} = 2r_{o1} = 20 \text{ k}\Omega$$

c) $V_{out} = -g_{m1} \frac{V_{gs1}}{V_s} (r_{o1} \parallel (2r_{o3} \parallel r_{o4}))$, $A_v = -g_{m1} \frac{r_{o1}}{2} = -4.795 \text{ V/V}$


Question #2

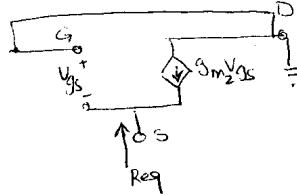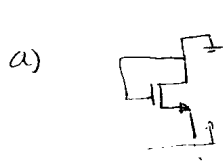

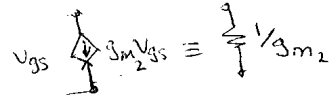
$V_{DS} = V_{GS}$
 \downarrow
 source absorption




$$R_{eq} = \frac{1}{g_{m2}}$$

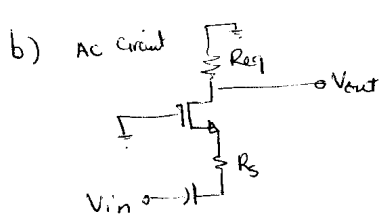

\Rightarrow CGA

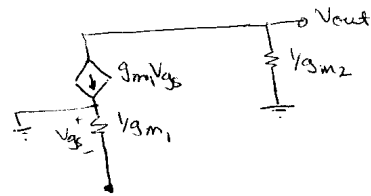

including body effect · hybrid- π model

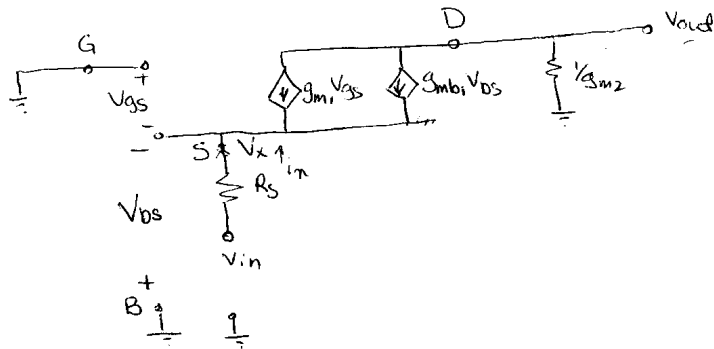

$$c) \quad v_{out} = - (g_{m1} v_{gs1} + g_{mb1} v_{bs1}) \frac{1}{g_{m2}} \quad v_{gs1} = v_{bs1}$$

$$v_x = -v_{bs1} = -v_{gs1}$$

$$A_v = \frac{v_{out}}{v_x} = + (g_{m1} + g_{mb1}) \frac{1}{g_{m2}}$$

$$A_{vout} = \frac{v_{out}}{v_{in}} = \frac{v_{out}}{v_x} \cdot \frac{v_x}{v_{in}}$$

To find $\frac{v_x}{v_{in}}$, we need to know R_{in}


$$R_{in} = \frac{v_x}{i_x} = \frac{v_x}{-(g_{m1} v_{gs1} + g_{mb1} v_{bs1})} = \frac{1}{g_{m1} + g_{mb1}}$$

$$\frac{v_x}{v_{in}} = \frac{R_{in}}{R_s + R_{in}} = \frac{\frac{1}{g_{m1} + g_{mb1}}}{R_s + \frac{1}{g_{m1} + g_{mb1}}} = \frac{1}{R_s (g_{m1} + g_{mb1}) + 1}$$

$$A_{vout} = + (g_{m1} + g_{mb1}) \frac{1}{g_{m2}} \cdot \frac{1}{R_s (g_{m1} + g_{mb1}) + 1}$$

Question 3

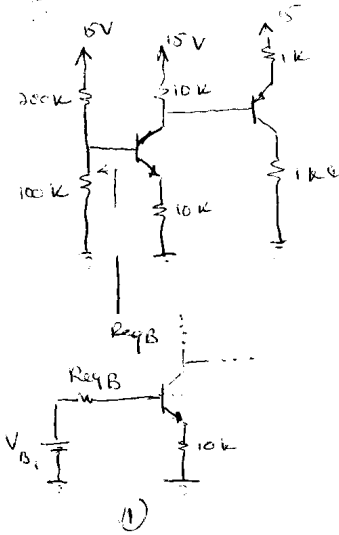a) Assume active mode operation for both transistor and verify this later



$$V_{DB} = \frac{15}{100+200} = 5V$$

$$R_{eqB} = 200 || 100 = 66.7 k\Omega$$

$$\textcircled{1} \quad 5 - R_{eqB} \bar{I}_{B1} - 0.7 - 10(\beta+1)\bar{I}_{B1} = 0$$


$$4.3 - \bar{I}_{B1}(66.7 + 10 \times 101) = 0$$

$$\Rightarrow \bar{I}_{B1} = \frac{4.3}{66.7 + 10 \times 101} = \frac{4.3 \mu A}{1076.7} = 0.4 \mu A$$

$$I_{E1} = 101 \bar{I}_{B1} = 0.4034 \text{ mA}$$

$$V_{E1} = 10 I_{E1} = 4.034 \text{ V}$$
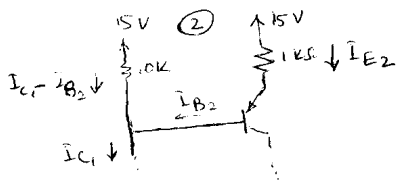
$$V_{B1} = V_{E1} + 0.7 = 4.734 \text{ V}$$



$$\textcircled{2} \quad 15 - 10(I_{C1} - I_{B2}) = 15 - 10 I_{E2} = 0.7$$

$$\Rightarrow 10(\alpha I_{E1} - I_{B2}) = -10 I_{E2} = 0.7$$


$$10 \left(\frac{100}{101} 0.4034 - I_{B2} \right) = +101 I_{B2} = 0.7$$

$$10 \times \frac{100}{101} 0.4034 - 0.7 = 111 I_{B2}$$

$$\Rightarrow V_{E2} = 15 - I_{E2} = 12.003 \text{ V}$$

$$\Rightarrow V_{C2} = \alpha I_{E2} \cdot 1k = 2.96 \mu A \cdot 1k = 2.96 \text{ V}$$

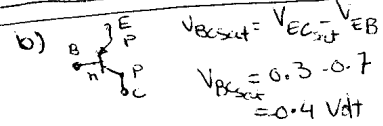Active mode operation for both is verified $\Rightarrow V_{BC2} = 9.34 > 0$ Reverse bias



$$V_{BC_{out}} = V_{EC_{out}} - V_{EB}$$

$$V_{BC_{out}} = 0.3 - 0.7 = -0.4 \text{ V}$$

for active mode operation:

$$\frac{V_{B2} - V_{C2}}{V_{C1} R_C} > -0.4$$

$$11.3 - R_C 2.96 > -0.4$$

$$R_C < \frac{11.7}{2.96} = 3.953 \text{ k}\Omega$$

$$\Rightarrow I_{B2} = 0.0297 \text{ mA}$$

$$\Rightarrow I_{E2} = 2.99 \text{ mA}$$

$$\Rightarrow V_{C1} = 11.3 \text{ V} \Rightarrow \left. \begin{matrix} V_{CB1} = 5.57 \text{ V} \\ V_{EB1} > 0 \end{matrix} \right\} \text{Reverse bias}$$

Question 4

a) $-2 - R_B I_B - 0.7 - R_E (\beta + 1) I_B - 5 = 0$

$$7.7 = (100\text{k} + 101.4\text{k}) I_B \Rightarrow I_B = \frac{7.7}{504\text{k}} =$$

$$I_E = (\beta + 1) I_B = 1.26 \text{ mA}$$


$$I_C = \alpha I_E = 1.25 \text{ mA}$$

$$V_E = -5 + I_E R_E = 0.05 \text{ V}$$

$$V_B = 0.7 + V_E = 0.75 \text{ V}$$

$$V_C = 5 - I_C R_C = 2.88 \text{ V}$$

b)

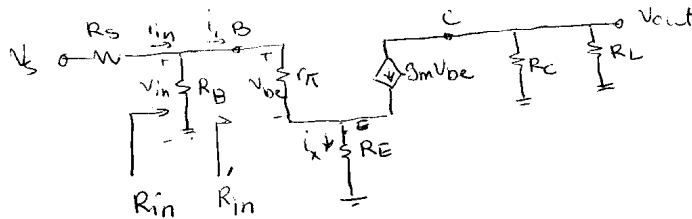

$$V_{in} = V_{be} + i_x R_E$$

$$i_x = \frac{V_{be}}{r_{\pi}} + g_m V_{be} R_E = V_{be} \left(\frac{1}{r_{\pi}} + g_m \right) = \frac{V_{be}}{r_{\pi}} (\beta + 1) R_E$$

$$V_{in} = V_{be} + \frac{V_{be}}{r_{\pi}} R_E (\beta + 1) = \frac{V_{be}}{r_{\pi}} [r_{\pi} + R_E (\beta + 1)]$$

$$R'_{in} = \frac{V_{in}}{i_x} = [r_{\pi} + R_E (\beta + 1)]$$

$$r_{\pi} = \frac{V_T}{I_B} = 19.84 \Omega$$

$$R_{in} = R_B \parallel R'_{in} = R_B \parallel [r_{\pi} + R_E (\beta + 1)] = 80.2 \text{ k}\Omega$$

$$c) A_v = ? = \frac{V_{out}}{V_s} = \frac{V_{out}}{V_{in}} \cdot \frac{V_{in}}{V_s} = \frac{V_{out}}{V_{in}} \cdot \frac{R_{in}}{R_s + R_{in}}$$


$$\begin{cases} V_{out} = -g_m V_{be} (R_C \parallel R_L) \\ V_{in} = V_{be} [r_{\pi} + R_E (1 + \beta)] \end{cases}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{-g_m r_{\pi} (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E} = -0.155$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E}$$

$$A_v = \frac{-\beta (R_C \parallel R_L)}{r_{\pi} + (\beta + 1) R_E} \cdot \frac{R_{in}}{R_s + R_{in}} = -0.138 \text{ V/V}$$

d) source at the emitter \Rightarrow CBA

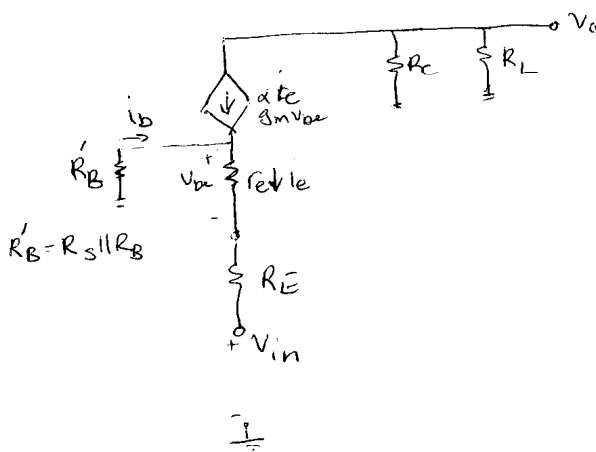

$$V_{out} = -g_m V_{be} (R_C \parallel R_L)$$

$$V_{in} = -(r_{\pi} + R_E) i_e - i_b R'_B = -\left[(r_{\pi} + R_E) - \frac{R'_B}{\beta + 1} \right] i_e$$

$$A_v = \frac{-\alpha i_e (R_C \parallel R_L)}{-i_e \left[r_{\pi} + R_E + \frac{R'_B}{\beta + 1} \right]}$$

$$A_v = \frac{\beta}{\beta + 1} \cdot \frac{R_C \parallel R_L}{(r_{\pi} + R_E) + \frac{R'_B}{\beta + 1}}$$