

## Midterm Examination # 2

Electronic Circuits I - ECSE-330B  
March 31st 2005, 8:35 AM – 9:55 AM  
Professor Ramesh Abhari

### Pertinent Information:

- 1) This is a closed-book examination, no notes permitted.
- 2) This examination consists of 4 questions with total possible points of 32. Partial point distribution is indicated in brackets.
- 3) Only the Faculty Standard Calculator is permitted.
- 4) Show your work: answers without justification will not receive marks. State any assumption you find necessary to complete your answer.

Last Name	
First Name	
Student Number	

Question	Mark
1	/7
2	/8
3	/9
4	/8
Total	/32

**Question #1 (8 Points)**

In the following circuit:


$$k_p = k_n,$$

$$V_{t0n} = |V_{t0p}|,$$

$$\left(\frac{W}{L}\right)_2 = 2\left(\frac{W}{L}\right)_1,$$

$$\left(\frac{W}{L}\right)_4 = \left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_6 = \left(\frac{W}{L}\right)_7 = \left(\frac{W}{L}\right)_8 = \left(\frac{W}{L}\right)_1,$$

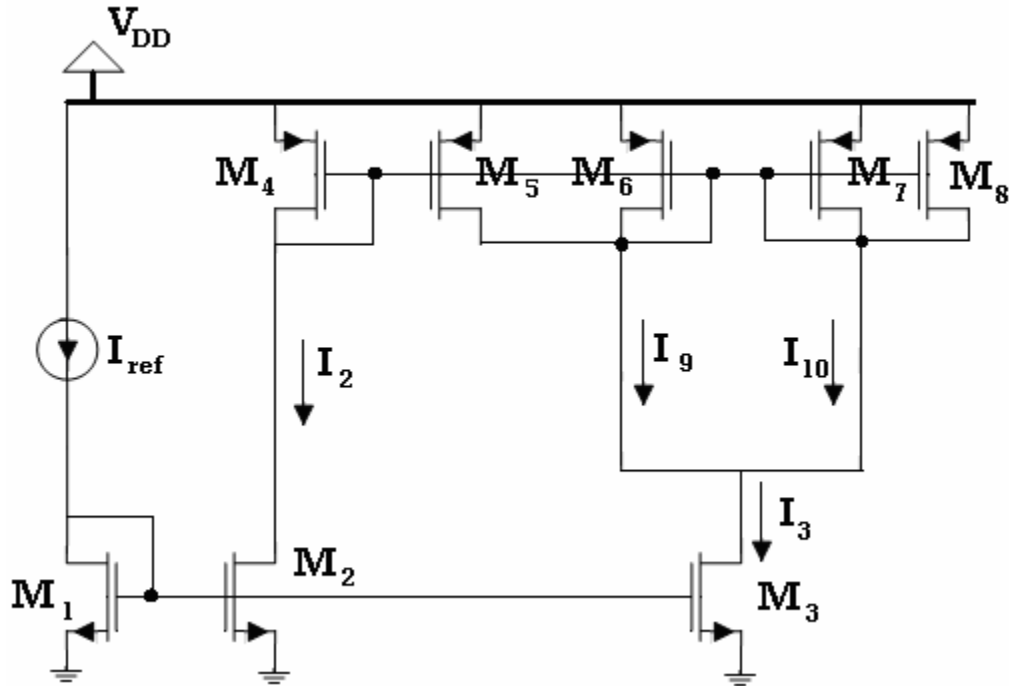Channel length modulation can be ignored ( $\lambda = 0$ ). (Assume that all the transistors are operating in the saturation mode)




(a) Calculate  $I_2$ ,  $I_9$ , and  $I_{10}$  in terms of  $I_{ref}$ . (5 pts)

(b) Find  $I_3$  and determine  $\left(\frac{W}{L}\right)_3$  in terms of  $\left(\frac{W}{L}\right)_1$ . (2 pts)

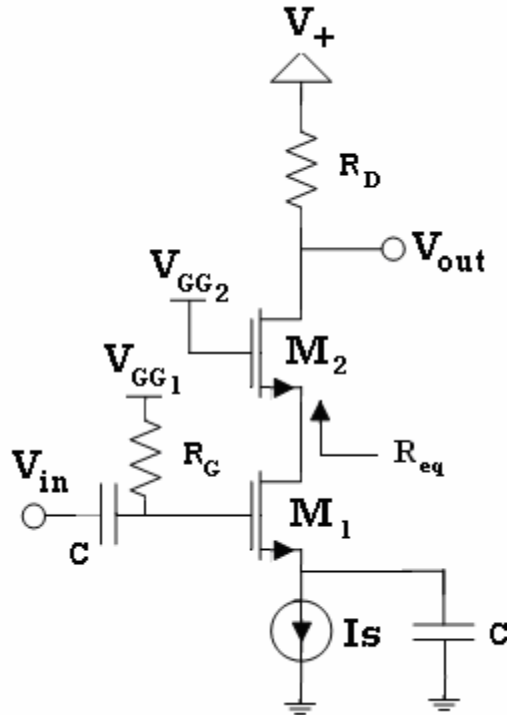**Question #2 (8 Points)**

In the following amplifier ignore the body effect and the channel length modulation.  $V_{GG1}$  and  $V_{GG2}$  are the DC voltage supplies used for biasing the gates of  $M_1$  and  $M_2$ .




- (a) Draw the small signal equivalent circuit. (2 pts)
- (b) Derive an expression for the small signal equivalent resistance ( $R_{eq}$ ) when looking into the source of  $M_2$  (as shown above). (3 pts)
- (c) Derive an expression for the small signal voltage gain  $A_v = \frac{V_{out}}{V_{in}}$ . (3 pts)

**Question #3 (9 Points)**

In the following circuit:

$\beta_1 = \beta_2 = 100$ ,  $V_{CC} = 10V$ ,  $C$  is very large,  $R_{b1} = 70K \Omega$ ,  $R_{b2} = 30K \Omega$ ,  $R_{e1} = 2K \Omega$ ,  $R_{c1} = 4K \Omega$ ,  $R_{c2} = 4K \Omega$ , and  $R_{e2} = 3K \Omega$ .

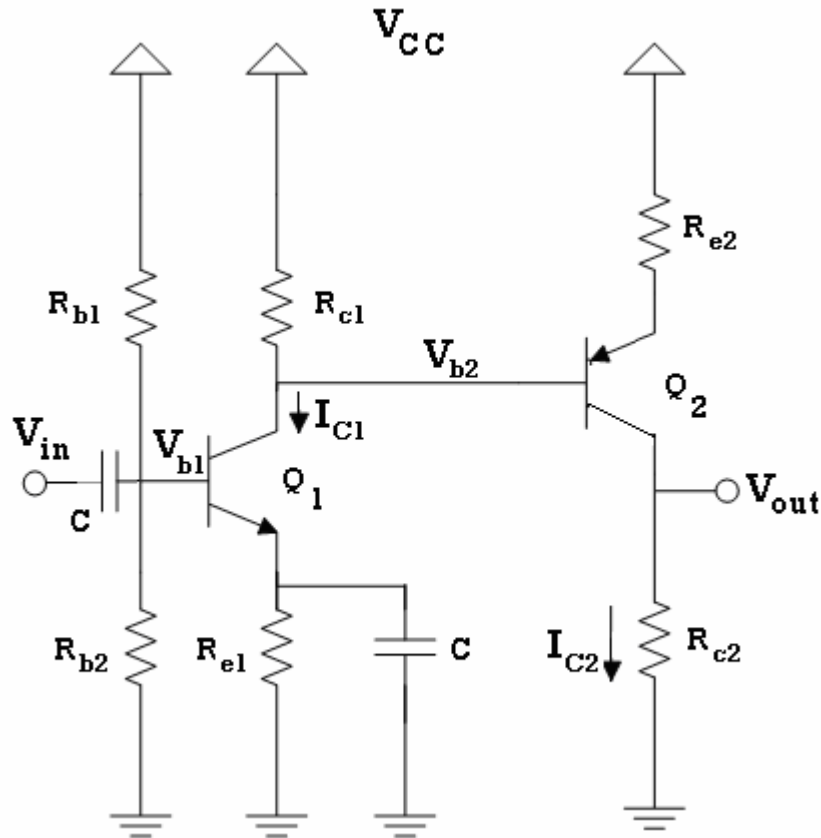
The Early effect can be ignored for all transistors.



- Calculate  $I_{C1}$ ,  $I_{C2}$ ,  $V_{b1}$ , and  $V_{b2}$  and verify the assumed mode of operation for the transistors. (8 pts)
- Determine the maximum value for  $R_{c2}$  so that  $Q_2$  operates in the active mode. (1 pt)

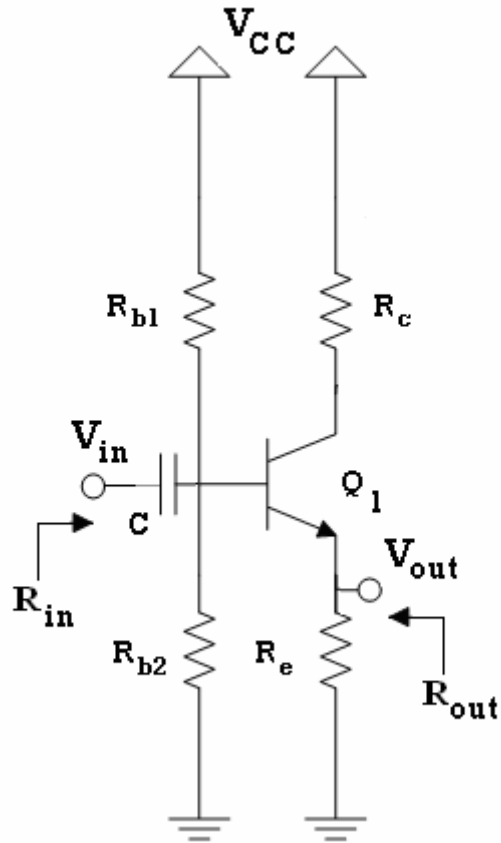**Question #4 (8 Points)**

In the following amplifier the Early effect can be neglected.



- (a) Draw the small signal equivalent circuit. (2 pts)
- (b) Derive an expression for the small signal voltage gain  $A_v$ . (2 pts)
- (c) Derive an expression for the small signal current gain  $A_{IS}$ . (2 pts)
- (d) Derive expressions for  $R_{in}$  and  $R_{out}$ . (2 pts)