

Midterm Examination # 2

Electronic Circuits I - ECSE-330B
March 27th 2007, 8:35 AM – 9:55 AM
Professor Ramesh Abhari

Pertinent Information:

- 1) This is a closed-book examination, no notes permitted.
- 2) This examination consists of 4 questions with total possible points of 50. Partial point distribution is indicated in brackets.
- 3) Only the Faculty Standard Calculator is permitted.
- 4) Show your work: answers without justification will not receive marks. State any assumption you find necessary to complete your answer.


| | |
|----------------|--|
| Last Name | |
| First Name | |
| Student Number | |

| Question | Mark |
|----------|------|
| 1 | /8 |
| 2 | /22 |
| 3 | /9 |
| 4 | /11 |
| Total | /50 |

QUESTION 1 (8 marks)

In the following circuit:

$V_{DD} = 5V$, $R_2 = 10K\Omega$, $R_3 = 4K\Omega$, $\mu_n C_{OX} = \mu_p C_{OX} = 100 \mu A/V^2$, $|V_t| = V_{tn} = -V_{tp} = 1V$, $(W/L)_1 = (W/L)_3 = (W/L)_4 = 20$, $(W/L)_5 = (W/L)_6 = 40$. The channel length modulation and body effect can be ignored. Assume that all transistors are in saturation mode.

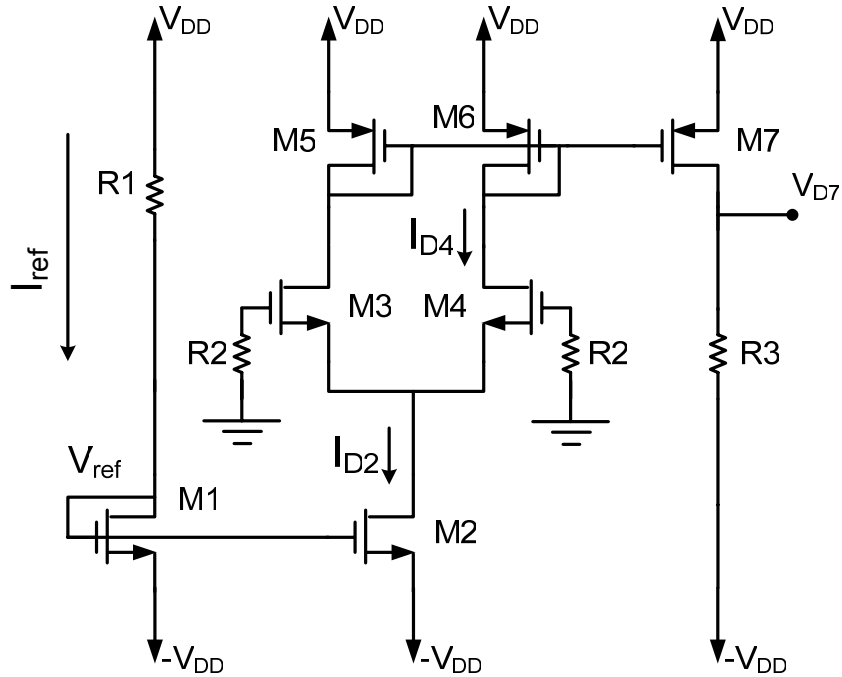


- Find V_{ref} such that $I_{ref} = 250 \mu A$. (2 marks)
- Find R_1 . (0.5 mark)
- Find $(W/L)_2$ such that $I_{D2} = 1 \text{ mA}$. (2 marks)
- Find I_{D4} . (0.5 mark)
- Find $(W/L)_7$ if V_{D7} is to be $1V$. (3 marks)

- Name: _____ **Student Number:** _____ -

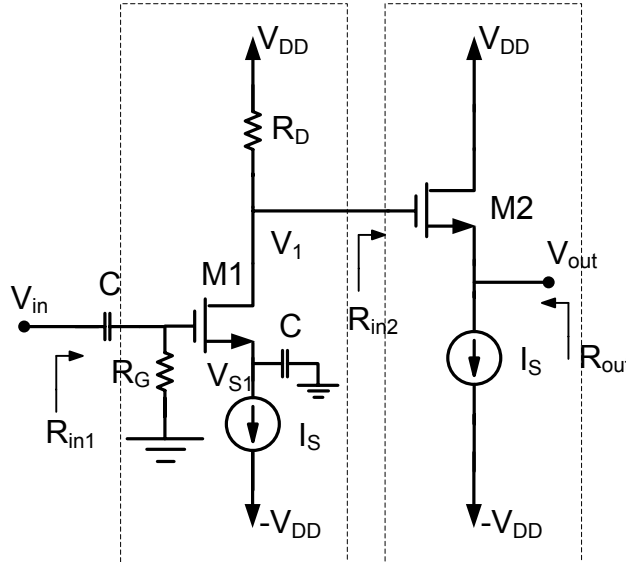QUESTION 2 (22 marks)

Consider the two-stage amplifier in Fig.2. Assume $V_{DD} = 5\text{ V}$, $R_G = 4\text{ K}\Omega$, $R_D = 4\text{ K}\Omega$, $\mu_n C_{OX} = \mu_p C_{OX} = 100\ \mu\text{A}/\text{V}^2$, $V_{tn} = 1\text{ V}$, $\chi=0.2$, $\lambda = 0.025\ \text{V}^{-1}$ and $(W/L)_1 = (W/L)_2 = 40$. Also assume that $I_S = 500\ \mu\text{A}$ and that for the small-signal analysis the current sources can be replaced by 100 K Ω resistors. The capacitors are ideal AC short circuits.

For DC analysis you may ignore CLM and body effect. Consider body effect and CLM for AC analysis.




- Specify the type of the amplifiers in each stage? (i.e. CS, CG, or CD) (1 mark)
- Assume that all transistors are in saturation. From the DC analysis find V_{S1} , V_1 and V_{out} . (6 marks)
- Draw the small-signal equivalent circuit of the entire amplifier. (4 marks)
- Calculate g_{m1} , r_{o1} , g_{m2} , and r_{o2} . (2 marks)
- Find R_{in1} and R_{in2} . (1 mark)
- Derive expressions for the small-signal gains V_1/V_{in} and V_{out}/V_{in} and calculate their values. (6 marks)
- Calculate the output resistance (R_{out}) of the above amplifier. (2 marks)

- Name: _____ **Student Number:** _____ -

- Name: _____ **Student Number:** _____ -

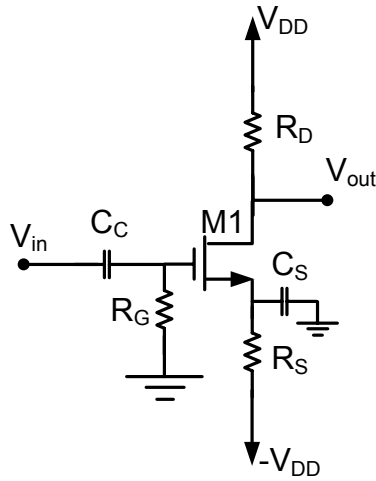QUESTION 3 (9 marks)

In the following amplifier ignore body effect but consider CLM.




- a) Draw the high frequency small-signal equivalent circuit of the amplifier. (3marks)
- b) Derive an expression for the mid-band gain. (2 marks)
- c) Find the frequency of the pole associated with C_S . (2 marks)
- d) Find the frequency of the pole associated with C_C . (2 marks)

- Name: _____ **Student Number:** _____ -

QUESTION 4 (11 marks)


Part I)

- Draw a table naming the different modes of operation of an npn BJT. Specify the state of the BE and BC junctions for each mode. (4 marks)
- Which mode is used in designing amplifiers? Explain the physics of the BJT operation at this mode. (3 marks)

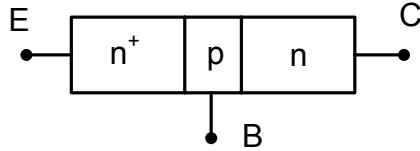

Part II)

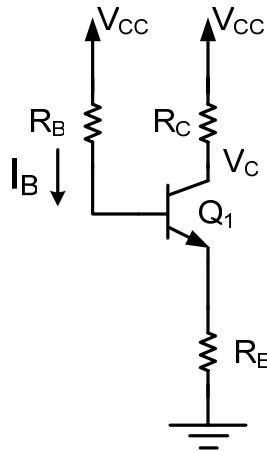In the following BJT circuit $V_{CC}=5\text{ V}$, $R_B=200\text{ K}\Omega$, $R_E=2.3\text{ K}\Omega$, $R_C=1\text{ K}\Omega$, $\beta=100$, and $V_{BE(on)}=0.7\text{ V}$.



- Find the DC values of I_B and V_C . (3 marks)
- Verify the mode of operation of Q_1 . (1 mark)

- Name: _____ **Student Number:** _____ -

- Name: _____ **Student Number:** _____ -